
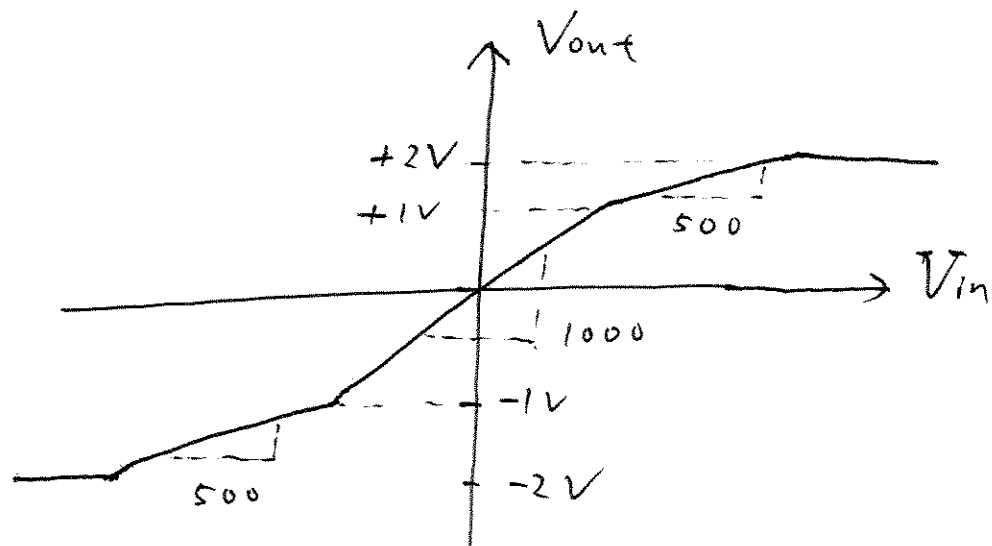


① a)

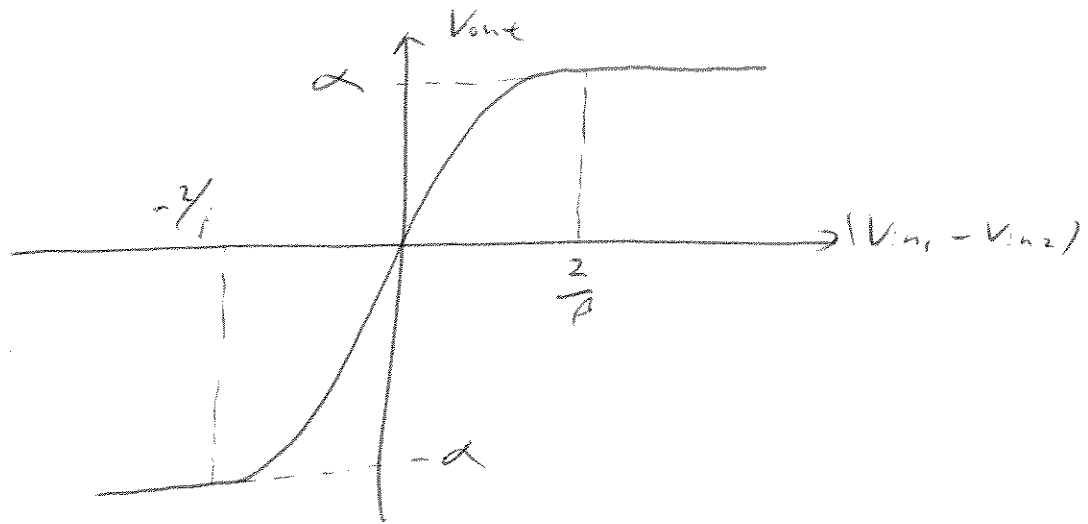

b/ The largest input swing is $\pm 1mV$, because gain is constant at 1000 over this range of input.

$$(2) \quad V_{out} = \alpha \tanh [\beta (V_{in1} - V_{in2})]$$



To find small-signal gain,

$$\therefore \tanh z = z - \frac{1}{3} z^3 + \frac{2}{15} z^5 + \dots$$

\therefore for $\beta(V_{in1} - V_{in2}) \approx 0$,

$$\frac{d V_{out}}{d (V_{in1} - V_{in2})} \approx \frac{d}{d (V_{in1} - V_{in2})} \alpha \beta (V_{in1} - V_{in2})$$

$$= \underline{\underline{\alpha \beta}}$$

$$\textcircled{3} \quad \text{closed-loop gain} = \left(1 + \frac{R_1}{R_2}\right)$$

$$= 8$$

$$\text{Gain error} = \left(1 + \frac{R_1}{R_2}\right) (A_0)^{-1}$$

$$= \frac{8}{2000}$$

$$= \underline{\underline{0.4\%}}$$

$$\textcircled{4} \quad \text{closed loop gain} = \left(1 + \frac{R_1}{R_2}\right) \\ = 4$$

$$\text{Gain error} = \left(1 + \frac{R_1}{R_2}\right) \left(\frac{1}{A_o}\right) \\ = 0.1\%$$

$$\therefore 4/A_o = 0.1\%$$

$$A_o = \underline{\underline{4000}}$$

⑤ Let $G_o = (1 + \frac{R_1}{R_2})$

Desired gain = α_1

$$= \frac{A_o}{1 + \frac{R_2}{R_1 + R_2} A_o}$$

$$\therefore \alpha_1 = \frac{A_o}{1 + \frac{A_o}{G_o}}$$

$$1 + \frac{A_o}{G_o} = \frac{A_o}{\alpha_1}$$

$$\frac{1}{G_o} = \frac{1}{\alpha_1} - \frac{1}{A_o}$$

$$G_o = \frac{A_o \alpha_1}{A_o - \alpha_1}$$

$$\therefore \frac{R_2}{R_1 + R_2} = \frac{1}{G_o} = \frac{1}{\alpha_1} - \frac{1}{A_o} //$$

b) if A_o drops to $0.6 A_o$,

$$\text{Actual gain} = \frac{0.6 A_o}{1 + (\frac{1}{\alpha_1} - \frac{1}{A_o}) 0.6 A_o}$$

$$= \frac{0.6 A_o}{0.4 + \frac{0.6 A_o}{\alpha_1}}$$

⑤ b) (cont'd)


$$\text{Actual gain} = \frac{\alpha_1}{1 + \frac{0.4}{0.6} \frac{\alpha_1}{A_0}}$$

$$\approx \alpha_1 \left(1 - \frac{0.4}{0.6} \frac{\alpha_1}{A_0} \right)$$

$$\therefore \text{the gain error} = \frac{0.4}{0.6} \frac{\alpha_1^2}{A_0}$$

$$= \underline{\underline{\frac{2}{3} \frac{\alpha_1^2}{A_0}}}$$

⑥ Using the model in Fig. 8.44,

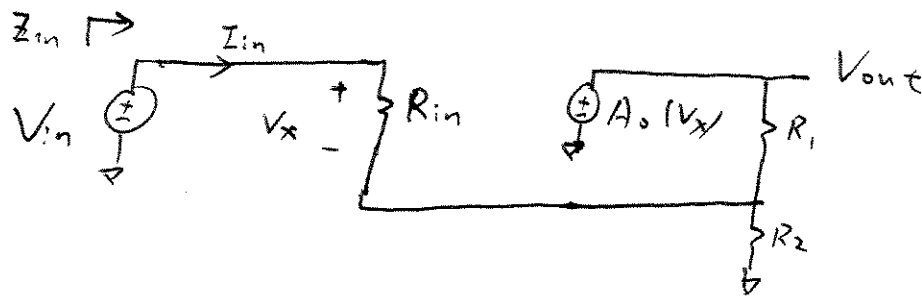

$$V_x = V_{in} - V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = A_0 V_x$$

$$= A_0 \left(V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right)$$

$$A_0 V_{in} = V_{out} \left(1 + A_0 \frac{R_1}{R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + A_0 \frac{R_1}{R_1 + R_2}} \quad \text{--- (1)}$$

To find input impedance (Z_{in}),

$$I_{in} = \frac{V_x}{R_{in}}$$

$$= \frac{1}{R_{in}} \left(V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right)$$

$$= \frac{V_{in}}{R_{in}} \left(1 - \frac{V_{out}}{V_{in}} \frac{R_1}{R_1 + R_2} \right)$$

⑥ (cont. d)

$$I_{in} = \frac{V_{in}}{R_{in}} \left(1 - \frac{A_o}{1 + A_o \frac{R_1}{R_1 + R_2}} \frac{R_1}{R_1 + R_2} \right)$$

$$= \frac{V_{in}}{R_{in}} \left(1 - \frac{1}{\frac{R_1 + R_2}{A_o R_1} + 1} \right)$$

$$= \frac{V_{in}}{R_{in}} \left(\frac{\frac{R_1 + R_2}{A_o R_1}}{\frac{R_1 + R_2}{A_o R_1} + 1} \right)$$

$$\therefore Z_{in} = \frac{V_{in}}{I_{in}} = R_{in} \left[\frac{1 + \frac{R_1 + R_2}{A_o R_1}}{\frac{R_1 + R_2}{A_o R_1}} \right] \quad \text{--- (2)}$$

As $A_o \rightarrow \infty$,


$$Gain = \frac{V_{out}}{V_{in}} \Big|_{A_o \rightarrow \infty} \quad [From (1)]$$

$$= 1 + \frac{R_2}{R_1} //$$

$$Z_{in} = \frac{V_{in}}{I_{in}} \Big|_{A_o \rightarrow \infty} \quad [From (2)]$$

$$= \infty //$$

7

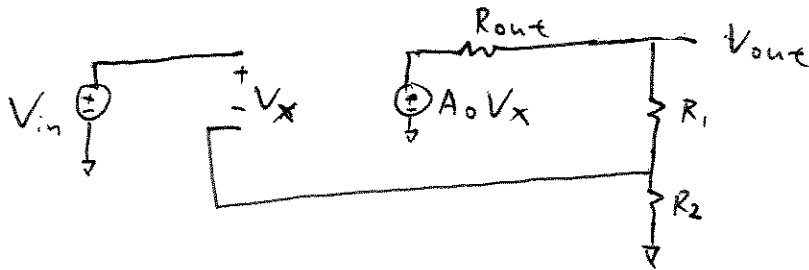

Similar to Prob. (6),

$$\text{gain} = \frac{V_{out}}{V_{in}}$$

$$V_x = V_{in} - V_{out} \frac{R_2}{R_1 + R_2}$$


$$V_{out} = A_0 V_x \frac{R_1 + R_2}{R_{out} + R_1 + R_2}$$

$$= A_0 \left(V_{in} - V_{out} \frac{R_2}{R_1 + R_2} \right) \frac{R_1 + R_2}{R_{out} + R_1 + R_2}$$

$$V_{in} A_0 \frac{R_1 + R_2}{R_{out} + R_1 + R_2} = V_{out} \left(1 + \frac{A_0 R_2}{R_{out} + R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0 \frac{R_1 + R_2}{R_{out} + R_1 + R_2}}{1 + \frac{A_0 R_2}{R_{out} + R_1 + R_2}}$$

To find output impedance (Z_{out})

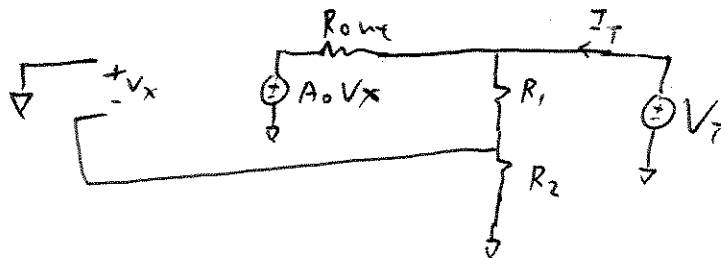

$$(7) \text{ (cont'd)} \quad V_x = \frac{R_2}{R_1 + R_2} V_T$$

$$\begin{aligned} I_T &= \frac{V_T}{R_1 + R_2} + \frac{V_T - A_o V_x}{R_{out}} \\ &= V_T \left[\frac{R_{out} + R_1 + R_2 - A_o R_2}{(R_{out})(R_1 + R_2)} \right] \end{aligned}$$


$$Z_{out} = \frac{V_T}{I_T} = \frac{(R_{out})(R_1 + R_2)}{R_{out} + R_1 + R_2 - A_o R_2}$$

As $A_o \rightarrow \infty$,

$$\text{gain} = 1 + \frac{R_1}{R_2} //$$

$$Z_{out} = 0 //$$

⑧

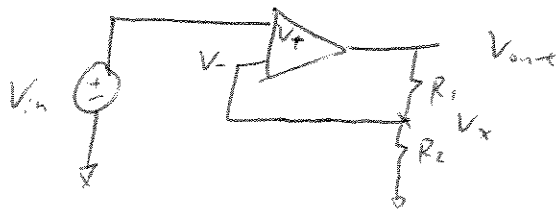

ΔR for now.

$$V_{out} = A_o (V_x)$$

$$V_x = V_{in} - \frac{R_2}{R_1 + R_2} V_{out}$$

$$\therefore \frac{-V_{out}}{A_o} = V_{in} - \frac{R_1}{R_1 + R_2} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_o (R_1 + R_2)}{A_o R_1 - 1} = \text{nominal gain}$$

$$\text{if } R_2' = \Delta R + R_2$$

$$\left(\frac{V_{out}}{V_{in}} \right)' = \frac{A_o (R_1 + \Delta R + R_2)}{A_o R_1 - 1}$$

$$\therefore \text{gain error} = \frac{\left(\frac{V_{out}}{V_{in}} \right)' - \left(\frac{V_{out}}{V_{in}} \right)}{\frac{V_{out}}{V_{in}}}$$

$$= \frac{\Delta R}{A_o R_1 - 1} \times \frac{A_o R_1 - 1}{A_o (R_1 + R_2)}$$

$$= \frac{\Delta R}{A_o (R_1 + R_2)} //$$

$$(9) \text{ Closed-loop gain } \approx \left(1 + \frac{R_1}{R_2}\right) \left[1 - \left(1 + \frac{R_1}{R_2}\right) \frac{1}{A_0}\right]$$

$$= 5 \left[1 - \frac{5}{A_0}\right]$$

\therefore As A_0 decreases to $0.8A_0$, closed-loop gain decreases along. (deviating more from the nominal)

A_0 drops to $0.8A_0$ when $|V_{in1} - V_{in2}| = 2\text{mV}$.

$$\therefore V_{in2} = V_{out} \left(\frac{R_2}{R_1 + R_2} \right)$$


$$\text{and } V_{out} = 5 \left(1 - \frac{5}{A_0}\right) V_{in1}$$

$$\therefore V_{in2} = 5 \left(1 - \frac{5}{A_0}\right) \left(\frac{1}{5}\right) V_{in1}$$

$$V_{in1} - V_{in2} = \frac{5}{A_0} V_{in1}$$

$$\text{At } V_{in1} - V_{in2} = 2\text{mV},$$

$$V_{in1} = \frac{A_0}{5} (2\text{mV})$$

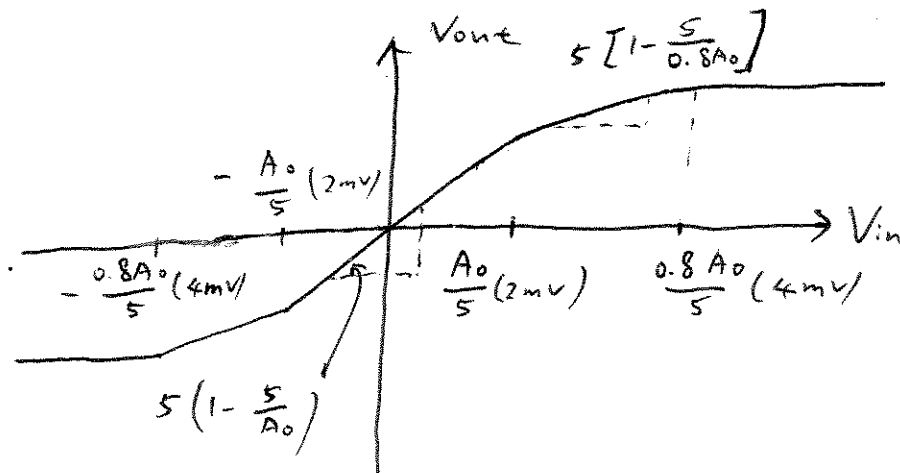

(10)

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

$$\therefore V_{in} = 1V, \quad V_{out} = 1 + \frac{R_1}{R_0 + \alpha W}$$

$$\frac{dV_{out}}{dW} = -R_1 \alpha (R_0 + \alpha W)^{-2}$$

$$= \frac{-R_1 \alpha}{(R_0 + \alpha W)^2}$$

⑪ if $A_o = \infty$,

$$V_+ = V_- = V_{in}$$

$$V_- = \left(\frac{R_2}{R_2 + R_3} \right) \left[\frac{R_4 \parallel (R_2 + R_3)}{R_1 + R_4 \parallel (R_2 + R_3)} \right] V_{out}$$

\therefore closed-loop gain $\frac{V_{out}}{V_{in}}$

$$= \frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]}$$

if $R_1 = 0$,

$$G|_{R_1=0} = 1 + \frac{R_3}{R_2} //$$

if $R_3 = 0$,

$$G|_{R_3=0} = \frac{R_2 [R_1 + R_4 \parallel R_2]}{R_2 [R_4 \parallel R_2]}$$

$$= 1 + \frac{R_1}{R_4 \parallel R_2} //$$

$$\textcircled{12} \quad \text{Gain Error} = \frac{1}{A_o} \left(1 + \frac{R_1}{R_2} \right)$$


$$= \frac{1}{A_o} (1 + 8)$$

$$= 0.2 \%$$

$$\therefore \frac{1}{A_o} (9) = 0.2 \%$$

$$A_o = 4500 //$$

(13)

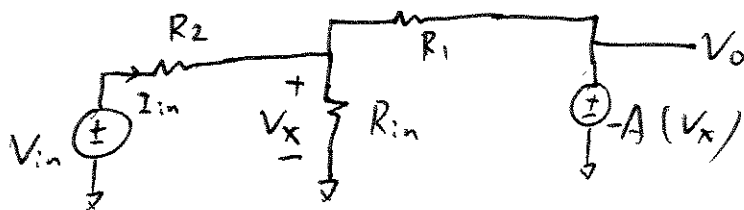

$$V_o = -A V_x \quad \text{--- (1)}$$

$$\frac{V_{in} - V_x}{R_2} + \frac{V_o - V_x}{R_1} = \frac{V_x}{R_{in}} \quad \text{--- (2)}$$

Combining (1) and (2),

$$\frac{V_{in}}{R_2} = -\frac{V_o}{R_1} + \frac{V_o}{(-A)} \left(\frac{1}{R_{in}} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{V_{in}}{R_2} = V_o \left[\frac{A R_{in} R_2 + R_1 R_2 + R_{in} R_2 + R_{in} R_1}{(-A) R_{in} R_1 R_2} \right]$$

$$\frac{V_o}{V_{in}} = - \frac{A R_{in} R_1}{R_1 R_2 + R_{in} R_2 + R_{in} R_1 + A R_{in} R_2}$$

Input impedance $(Z_{in}) = \frac{V_{in}}{I_{in}}$

$$I_{in} - \frac{V_x}{R_{in}} + \frac{(-A)V_x - V_x}{R_1} = 0$$

$$I_{in} = V_x \left[\frac{1}{R_{in}} + \frac{A+1}{R_1} \right]$$


$$\therefore V_x = V_{in} - I_{in} R_2$$

$$I_{in} = [V_{in} - I_{in} R_2] \left[\frac{1}{R_{in}} + \frac{A+1}{R_1} \right]$$

$$I_{in} \left[1 + \frac{R_2}{R_{in}} + \frac{R_2}{R_1} (A+1) \right] = V_{in} \left(\frac{1}{R_{in}} + \frac{A+1}{R_1} \right)$$

$$I_{in} = \frac{V_{in}}{I_{in}} = \frac{1 + \frac{R_2}{R_{in}} + \frac{R_2}{R_1} (A+1)}{\frac{1}{R_{in}} + \frac{A+1}{R_1}} //$$

14

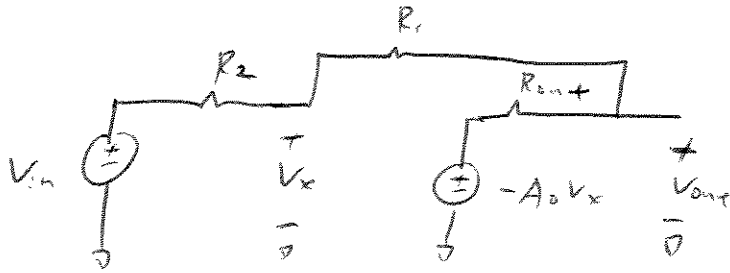

By KCL,

$$\frac{V_{in} - V_x}{R_2} = - \frac{-A_0 V_x - V_x}{R_1 + R_{out}}$$

$$\therefore V_x = - \frac{V_{out}}{A_0}$$

$$\frac{V_{in}}{R_2} = - \frac{V_{out}}{A_0 R_2} - \frac{A_0 + 1}{A_0} \frac{V_{out}}{R_1 + R_{out}}$$

$$\therefore \frac{A_0 + 1}{A_0} \approx 1$$


$$\therefore \frac{V_{in}}{R_2} \approx - \frac{V_{out}}{A_0 R_2} - \frac{V_{out}}{R_1 + R_{out}}$$

$$\frac{V_{in}}{R_2} \approx -V_{out} \left(\frac{R_1 + R_{out} + A_0 R_2}{A_0 R_2 (R_1 + R_{out})} \right)$$

$$\therefore \frac{V_{out}}{V_{in}} \approx - \frac{A_0 (R_1 + R_{out})}{R_1 + R_{out} + A_0 R_2}$$

⑭ cont'd:

To find output impedance (Z_{out})

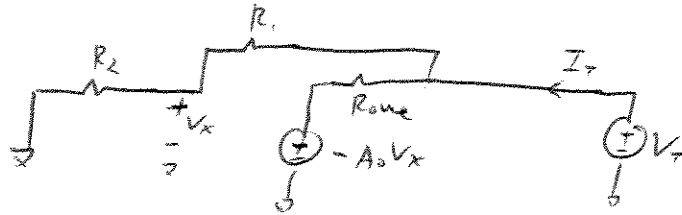

$$Z_{out} = \frac{V_T}{I_T}$$


$$V_X = \frac{R_2}{R_1 + R_2} V_T \quad \text{--- (1)}$$

$$I_T = \frac{V_T}{R_1 + R_2} + \frac{V_T + A_o V_X}{R_{out}} \quad \text{--- (2)}$$

$$I_T = V_T \left[\frac{1}{R_1 + R_2} + \frac{1 + \frac{A_o R_2}{R_1 + R_2}}{R_{out}} \right]$$

$$\frac{V_T}{I_T} = \frac{R_{out} (R_1 + R_2)}{R_{out} + R_1 + (A_o + 1) R_2} //$$

15

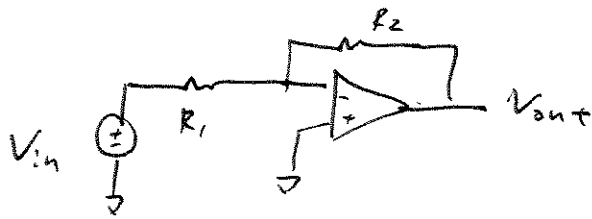

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{R_2}{R_1} = 4 \quad \text{--- (1)}$$

$$\therefore R_2 = 4R_1$$


$$Z_{in} \approx R_1 = 10 \text{ k}\Omega \quad \text{--- (2)}$$

$$\therefore R_2 = 40 \text{ k}\Omega$$

$$A_o = 1000 \quad \text{--- (3)}$$

$$\begin{aligned} \text{gain error} &= \frac{1}{A_o} \left(1 + \frac{R_2}{R_1} \right) \\ &= \frac{1}{1000} (1 + 4) \\ &= 0.5\% \end{aligned}$$

(16)

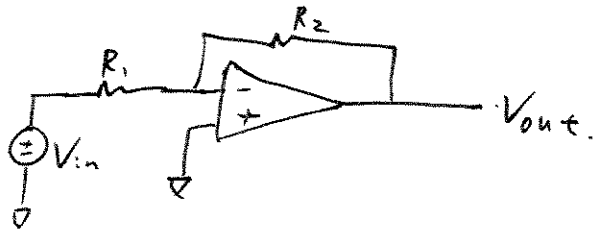

$$\text{Nominal gain} = \frac{R_2}{R_1} = 8 \quad \text{--- (1)}$$

$$R_2 = 8R_1$$

$$\text{Input impedance} \approx R_1 = 1000 \, \Omega \quad \text{--- (2)}$$

$$\therefore R_2 = 8000 \, \Omega.$$


$$\text{Gain error} = 0.1\% \quad \text{--- (3)}$$

$$\therefore \frac{1}{A_0} \left(1 + \frac{R_2}{R_1} \right) = 0.1\%$$

$$\frac{1}{A_0} (9) = \frac{0.1}{100}$$

$$\therefore A_0 = 9000 //$$

(17)

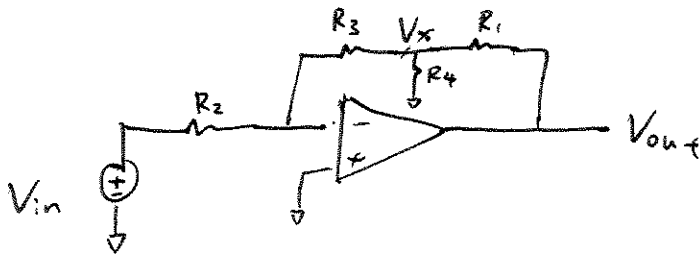

$$V_- = V_+ = 0 \quad (\because A = \infty)$$

$$\frac{V_{in}}{R_2} = - \frac{V_x}{R_3} \quad \text{--- (1)}$$

$$V_x = \frac{R_3 // R_4}{R_1 + R_3 // R_4} V_{out} \quad \text{--- (2)}$$

Combining (1) and (2),

$$\frac{V_{in}}{R_2} = - \frac{R_3 // R_4}{R_3 (R_1 + R_3 // R_4)} V_{out}$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_3}{R_2} \frac{(R_1 + R_3 // R_4)}{R_3 // R_4} //$$


if $R_1 \rightarrow 0$,

$$\frac{V_{out}}{V_{in}} = - \frac{R_3}{R_2} \quad (\text{typical inverting amplifier}) //$$

if $R_3 \rightarrow 0$,

$$\frac{V_{out}}{V_{in}} = - \frac{R_1}{R_2} \quad (\text{typical inverting amplifier}) //$$

(18)

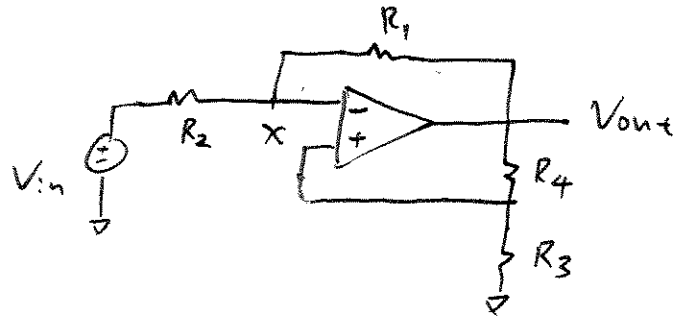

$$\therefore A = \infty$$

$$V_- = V_+$$

$$\therefore V_x = \frac{R_3}{R_3 + R_4} V_{out}$$

$$\frac{V_{in} - V_x}{R_2} = - \frac{V_{out} - V_x}{R_1}$$

$$\frac{V_{in}}{R_2} = V_x \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_{out}}{R_1}$$

$$= \left[\left(\frac{R_3}{R_3 + R_4} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_1} \right] V_{out}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{\frac{1}{R_2}}{\left(\frac{R_3}{R_3 + R_4} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_1}} //$$

(19)

From eq (8.31),

$$V_{out} = - \frac{1}{R_1 C_1} \int V_{in} dt$$

$$= - \frac{1}{R_1 C_1} \int V_0 \sin \omega t dt$$

$$= \frac{V_0}{R_1 C_1 \omega} \cos \omega t$$

$$\therefore \text{Amplitude of output} = \frac{V_0}{R_1 C_1 \omega} //$$

(20) From prob. (19)

Amplification of the integrator $= \frac{1}{R_1 C_1 \omega}$

$$\therefore \frac{1}{R_1 C_1 \omega} = 10$$

$$\frac{1}{\omega} = 10 \times 10^{-6}$$

$$\therefore \omega = 10 \text{ MHz}$$

\therefore The frequency of the sinusoid is 10 MHz.

(21)


From Eq. (8.37)

$$S_p = \frac{-1}{2\pi (A_0 + 1) R_1 C_1} \quad \angle -180^\circ$$

$$\therefore 2\pi (A_0 + 1) (10 \text{ k}\Omega) (1 \text{ nF}) \geq 1$$

$$A_0 \geq 15915 //$$

(22)

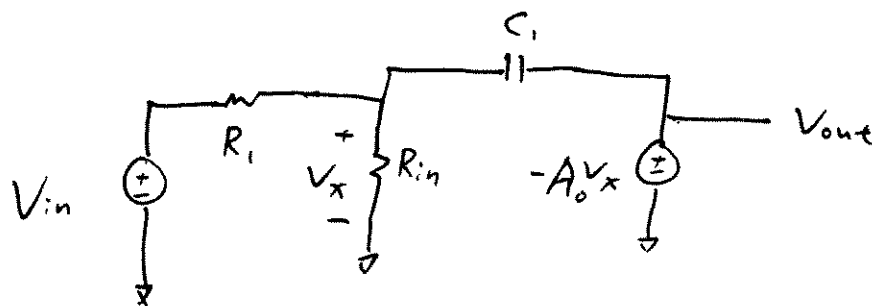

$$\frac{V_{in} - V_x}{R_i} + \frac{V_{out} - V_x}{\frac{1}{sC_1}} = \frac{V_x}{R_{in}}$$

Where $s = j\omega$

$$\therefore V_{out} = -A_o V_x$$

$$\begin{aligned} \therefore \frac{V_{in}}{R_i} &= (sC_1) \left[-\frac{V_{out}}{A_o} - V_{out} \right] - \frac{V_{out}}{A_o} \left(\frac{1}{R_{in}} + \frac{1}{R_i} \right) \\ &= -V_{out} \left[\frac{sC_1}{A_o} + sC_1 + \frac{1}{A_o R_{in}} + \frac{1}{A_o R_i} \right] \end{aligned}$$


$$\frac{V_{out}}{V_{in}} = \frac{-1}{\left(\frac{1}{A_o} + \frac{R_i}{A_o R_{in}} \right) + \left(1 + \frac{1}{A_o} \right) s R_i C_1}$$

To find the pole, equate denominator to zero,

$$s_p = \frac{-1}{(A_o + 1) R_i C_1} \left(1 + \frac{R_i}{R_{in}} \right)$$

$$[\therefore \text{pole shifted out by } \left(1 + \frac{R_i}{R_{in}} \right)]$$

(23)

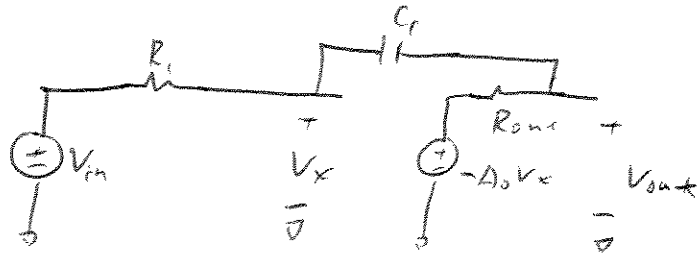

By KCL,

$$\frac{V_{in} - V_x}{R_1} = - \frac{-A_0 V_x - V_x}{R_{out} + \frac{1}{sC_f}}$$

$$\therefore V_x = - \frac{V_{out}}{A_0}$$

$$\frac{V_{in}}{R_1} = - \frac{V_{out}}{A_0 R_1} - \frac{(A_0 + 1)}{A_0} \frac{V_{out}}{R_{out} + \frac{1}{sC_f}}$$

$$\approx - V_{out} \left[\frac{1}{A_0 R_1} + \frac{1}{R_{out} + \frac{1}{sC_f}} \right]$$

$$\left(\because \frac{A_0 + 1}{A_0} \approx 1 \right)$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{A_0 \times (R_{out} + \frac{1}{sC_f})}{(A_0 R_1 + R_{out} + \frac{1}{sC_f})}$$

$$\text{pole} = - \frac{1}{C_f (R_{out} + A_0 R_1)}$$

$$(24) \because A_o = \infty$$

$$|A_v| = \frac{R_i}{\frac{1}{\omega C_i}}$$

$$= \omega R_i C_i$$

$$= 5$$

$$\therefore R_i C_i = \frac{5}{\omega}$$

$$= \frac{5}{2\pi \times 10^6}$$

$$= 7.958 \times 10^{-7}$$

(25)

From eqn (8.55)


$$S_p = - \frac{A_0 + 1}{R_1 C_1}$$

$$2\pi \times 100 \times 10^6 = \frac{A_0 + 1}{1000 \times 10^{-9}}$$

(ie. R_1 and C_1 are chosen at minimum)

$$A_0 \approx 627$$

26

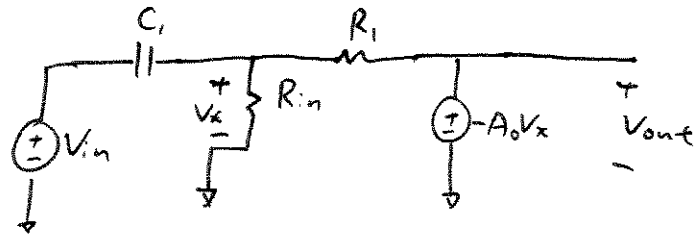

By KCL,

$$(V_{in} - V_x) s C_1 = \frac{V_x}{R_{in}} + \frac{(V_x + A_0 V_x)}{R_1}$$

$$(V_{in}) s C_1 = V_x \left[s C_1 + \frac{1}{R_{in}} + (A_0 + 1) \frac{1}{R_1} \right]$$


$$\frac{s C_1}{s C_1 + \frac{1}{R_{in}} + (A_0 + 1) \frac{1}{R_1}} = \frac{V_x}{V_{in}}$$

$$\therefore V_{out} = -A_0 V_x,$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{A_0 s C_1}{s C_1 + \frac{1}{R_{in}} + (A_0 + 1) \frac{1}{R_1}} //$$

$$\text{As } A_0 \rightarrow \infty, \quad \frac{V_{out}}{V_{in}} \rightarrow - R_1 C_1 s. \quad [8.42]$$

(27)

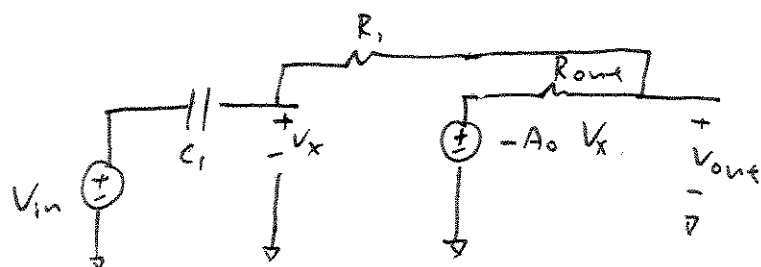

By KCL,

$$(V_{in} - V_x) / sC_1 = (V_x + A_0 V_x) \frac{1}{R_1 + R_{out}}$$

$$(V_{in}) / sC_1 = V_x \left[sC_1 + (A_0 + 1) \frac{1}{R_1 + R_{out}} \right]$$

$$\frac{V_x}{V_{in}} = \frac{sC_1}{sC_1 + (A_0 + 1) \frac{1}{R_1 + R_{out}}}$$

$$V_{out} = (-A_0 V_x - V_x) \frac{R_1}{R_1 + R_{out}}$$

(resistive divider)

$$= -V_x \frac{(A_0 + 1) R_1}{R_1 + R_{out}}$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{(A_0 + 1) R_1 sC_1}{R_1 + R_{out} \left[sC_1 + (A_0 + 1) \frac{1}{R_1 + R_{out}} \right]}$$

$$\frac{V_{out}}{V_{in}} = -R_1 sC_1 \quad (\text{as } A_0 \rightarrow \infty)$$

[8.42]

(28)

$$\therefore A_o = \infty,$$

$$V_+ = V_- = 0$$

$$\text{By KCL,}$$

$$\frac{V_{in}}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out}}{R_2 \parallel \frac{1}{sC_2}}$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 \parallel \frac{1}{sC_1}}$$

$$= - \frac{R_2}{R_1} \times \frac{1 + R_1 C_1 s}{1 + R_2 C_2 s} //$$

$$\text{For } \left| \frac{V_{out}}{V_{in}} \right| = 1,$$

$$R_2 \parallel \frac{1}{sC_2} = R_1 \parallel \frac{1}{sC_1}$$

That is, choose the components such that the impedance of $R_2 \parallel \frac{1}{sC_2}$ is equal to $R_1 \parallel \frac{1}{sC_1}$ at the specific frequency.

(29) if $A_0 < \infty$,

Let V_- be the voltage at the negative input terminal of the opamp.

By KCL,

$$\frac{V_{in} - V_-}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out} - V_-}{R_2 \parallel \frac{1}{sC_2}}$$

$$V_{out} = -A_0 V_-$$

$$\frac{V_{in} + \frac{V_{out}}{A_0}}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out} + \frac{V_{out}}{A_0}}{R_2 \parallel \frac{1}{sC_2}}$$

$$V_{in} = - \left[R_1 \parallel \frac{1}{sC_1} \right] \left[\frac{\left(R_2 \parallel \frac{1}{sC_2} \right) \frac{V_{out}}{A_0} + V_{out} + \frac{V_{out}}{A_0}}{R_2 \parallel \frac{1}{sC_2}} \right]$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 \parallel \frac{1}{sC_1}} \left[\frac{A_0}{(A_0 + 1) + \left(R_2 \parallel \frac{1}{sC_2} \right)} \right]$$

$$\text{To see } \left| \frac{V_{out}}{V_{in}} \right| = 1,$$

$$\text{Let } x = R_1 \parallel \frac{1}{sC_1} \quad \text{and } y = R_2 \parallel \frac{1}{sC_2},$$

$$\therefore \text{For } \left| \frac{V_{out}}{V_{in}} \right| = 1, \quad y A_0 = x [(A_0 + 1) + y]$$

$$y (A_0 - 1) = x (A_0 + 1)$$

(29) Cont'd

$$\therefore \frac{x}{y} = \frac{A_0 + 1}{A_0 - 1},$$

ie. we need to set $\frac{R_1 // \frac{1}{sC_1}}{R_2 // \frac{1}{sC_2}} = \frac{A_0 + 1}{A_0 - 1}.$

Since A_0 is generally rather large,

$\frac{A_0 + 1}{A_0 - 1}$ is a rational fraction,
in which the numerator and the
denominator are large, and differ
by a small amount.

(e.g. if $A_0 = 1000$, $\frac{A_0 + 1}{A_0 - 1} = \frac{1001}{999}$)

Hence, setting $\left| \frac{V_{out}}{V_{in}} \right|$ to unity is possible
in principle, although it would be rather
difficult to precisely control A_0 .


30

From eqn = 18.63%

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$\therefore R_1 = R_2,$$
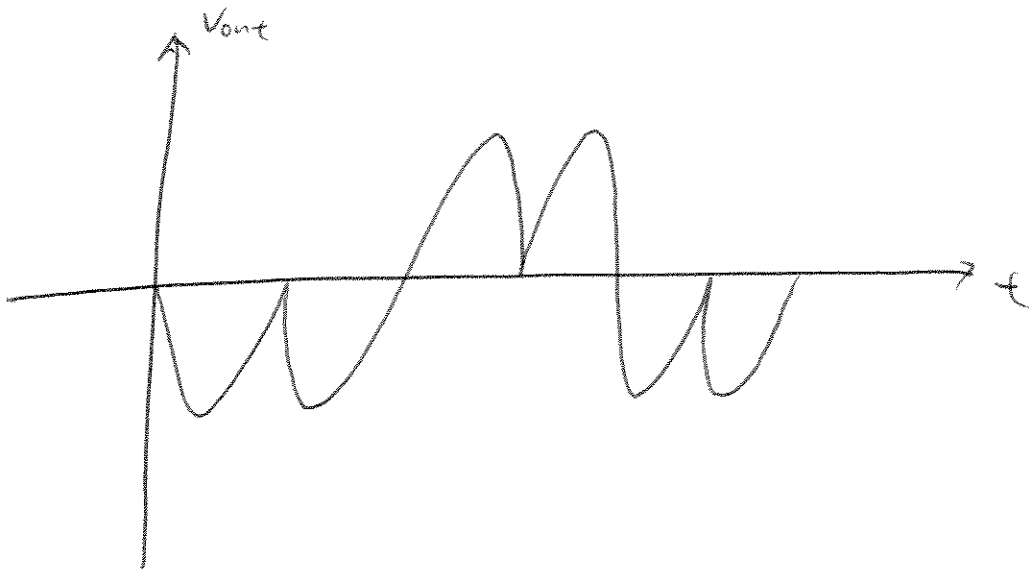
$$V_{out} = - \frac{R_2}{R_1} (V_1 + V_2)$$



31) By KCL,

$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} = - \frac{V_{out} - V_x}{R_F}$$

$$\therefore V_{out} = -A_o V_x$$

$$V_x = - \frac{V_{out}}{A_o}$$

$$\left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) + \frac{V_{out}}{A_o} \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_F} \right) = - \frac{V_{out}}{R_F}$$

$$- \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = V_{out} \left[\frac{1}{R_F} + \frac{1}{A_o} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) \right]$$

$$\therefore V_{out} = - \left(\frac{1}{R_F} + \frac{1}{A_o} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) \right)^{-1} \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

(32) For $A_o = \infty$,

$$V_+ = V_- = 0,$$

\therefore No current flows through R_P ,

\therefore No effect due to R_P

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) //$$

For $A_o \neq \infty$,

By KCL


$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} - \frac{V_x}{R_P} = - \frac{V_{out} - V_x}{R_F}$$

$$\therefore V_x = \frac{-V_{out}}{A_o},$$

$$\left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) + \frac{V_{out}}{A_o} \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_P} + \frac{1}{R_F} \right] = - \frac{V_{out}}{R_F}$$

$$V_{out} = - \left[\frac{1}{R_F} + \frac{1}{A_o} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_P} + \frac{1}{R_F} \right) \right]^{-1} \\ \times \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) //$$

33

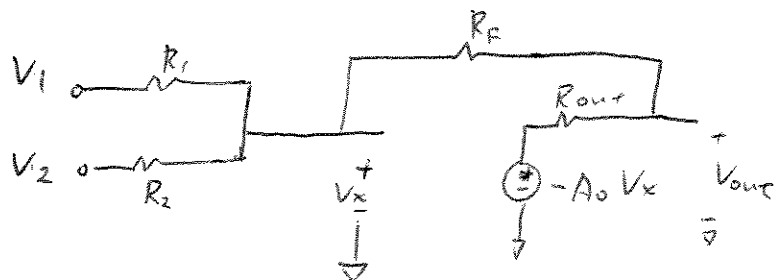

By KCL,

$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} = \frac{V_x (A_0 + 1)}{R_F + R_{out}}$$

$$\left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = V_x \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{A_0 + 1}{R_F + R_{out}} \right]$$


$$\begin{aligned} \therefore V_{out} &= (-A_0 V_x - V_x) \frac{R_F}{R_F + R_{out}} \\ &= -V_x (1 + A_0) \frac{R_F}{R_F + R_{out}} \end{aligned}$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} = - \frac{R_F + R_{out}}{R_F (A_0 + 1)} \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{A_0 + 1}{R_F + R_{out}} \right] V_{out}$$

$$V_{out} = - \frac{R_F (A_0 + 1)}{R_F + R_{out}} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{A_0 + 1}{R_F + R_{out}} \right)^{-1}$$

$$\times \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) //$$

34

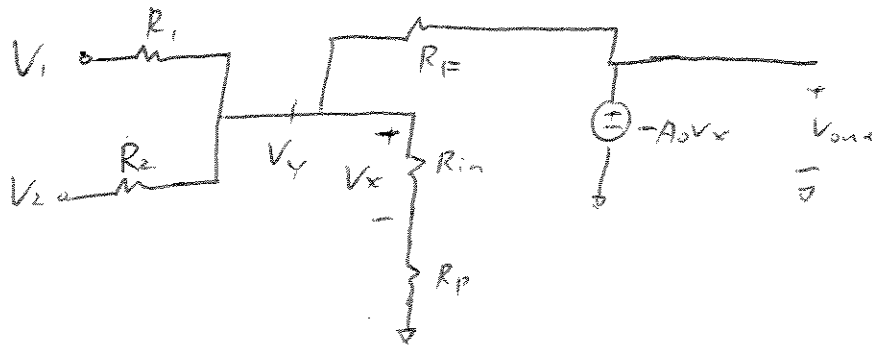

By KCL,

$$\frac{V_1 - V_Y}{R_1} + \frac{V_2 - V_Y}{R_2} = \frac{V_Y + A_0 V_X}{R_F} + \frac{V_Y}{R_{in} + R_P}$$

Using voltage divider,

$$V_X = V_Y \frac{R_{in}}{R_{in} + R_P}$$

$$V_Y = \frac{R_{in} + R_P}{R_P} V_X$$

$$\therefore \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = V_Y \left(\frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0 V_X}{R_F}$$

$$= \left[\left(\frac{R_{in} + R_P}{R_P} \right) \left(\frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0}{R_F} \right] V_X$$

$$\therefore V_{out} = -A_0 V_X$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} = - \left(\frac{V_{out}}{A_0} \right) \left[\left(\frac{R_{in} + R_P}{R_P} \right) \left(\frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0}{R_F} \right]$$


$$V_{out} = -A_0 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \times \left[\left(\frac{R_{in} + R_P}{R_P} \right) \left(\frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in} + R_P} \right) + \frac{A_0}{R_F} \right]^{-1}$$

(35) When D_1 is on, (i.e. when $V_{in} > 0$)

$$V_{out} = V_{in} = I_{D1} R_1,$$

$$\therefore I_{D1} = \frac{V_{in}}{R_1}$$

When D_1 is off, $I_{D1} = 0$.

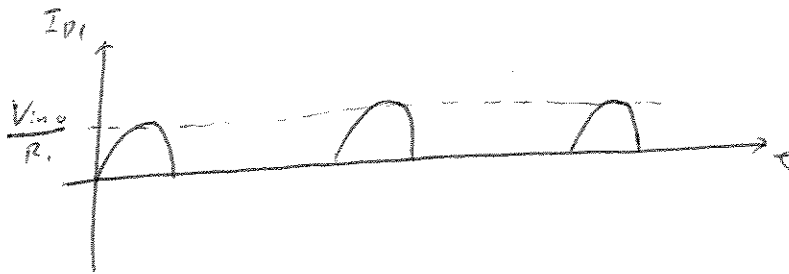


(36) D_1 is on when $V_{in} > 0$,





$$V_K = 0$$

By KCL ;

$$I_{D1} = \frac{V_{in}}{R_1}$$

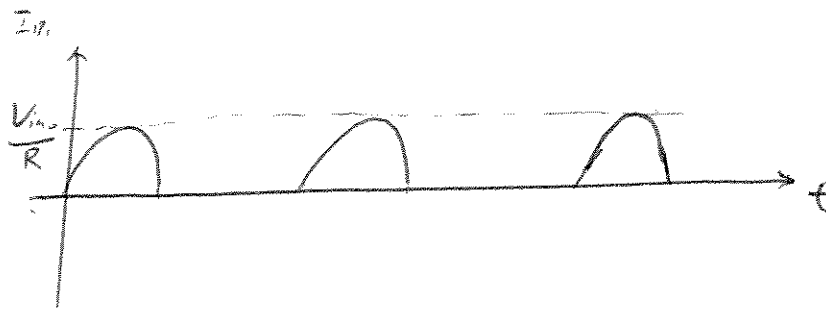

37

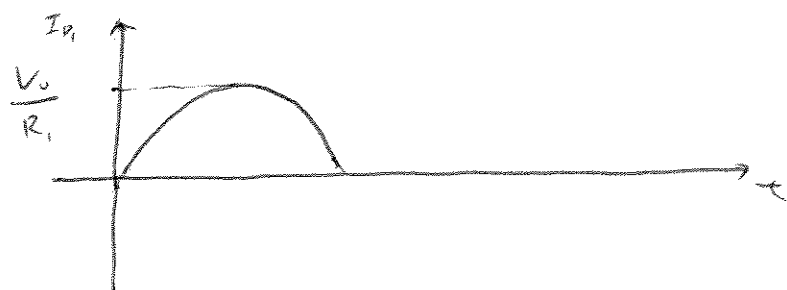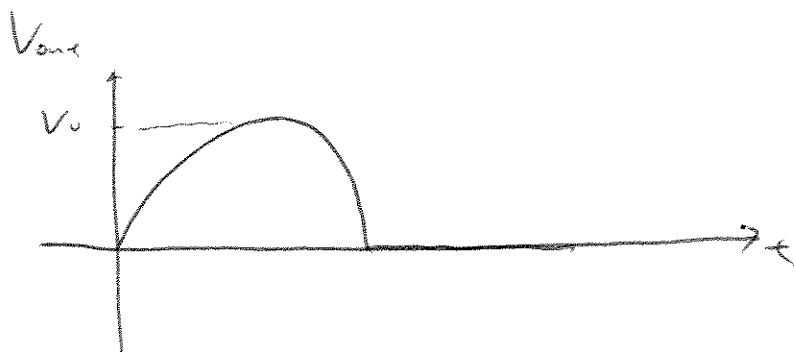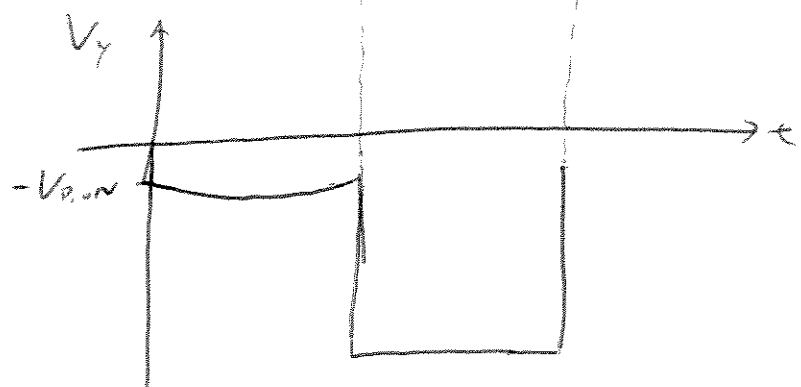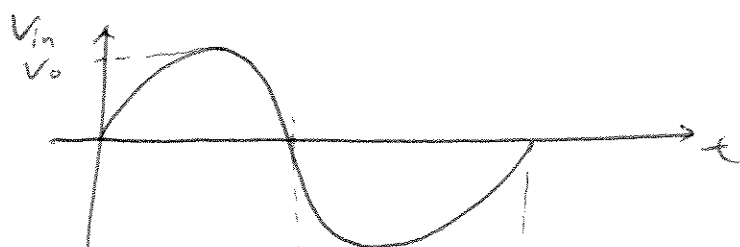

38

$$\therefore R_{D, on} \ll R_p$$

\therefore when diode is on, R_p has no effect.


(diode "shorts" nodes x and y)

when diode is off, R_p functions as a feedback resistor,

$$\therefore \frac{V_y}{V_{in}} = 1 + \frac{R_1}{R_p}$$


$$\text{and } V_{in} = V_{out}$$

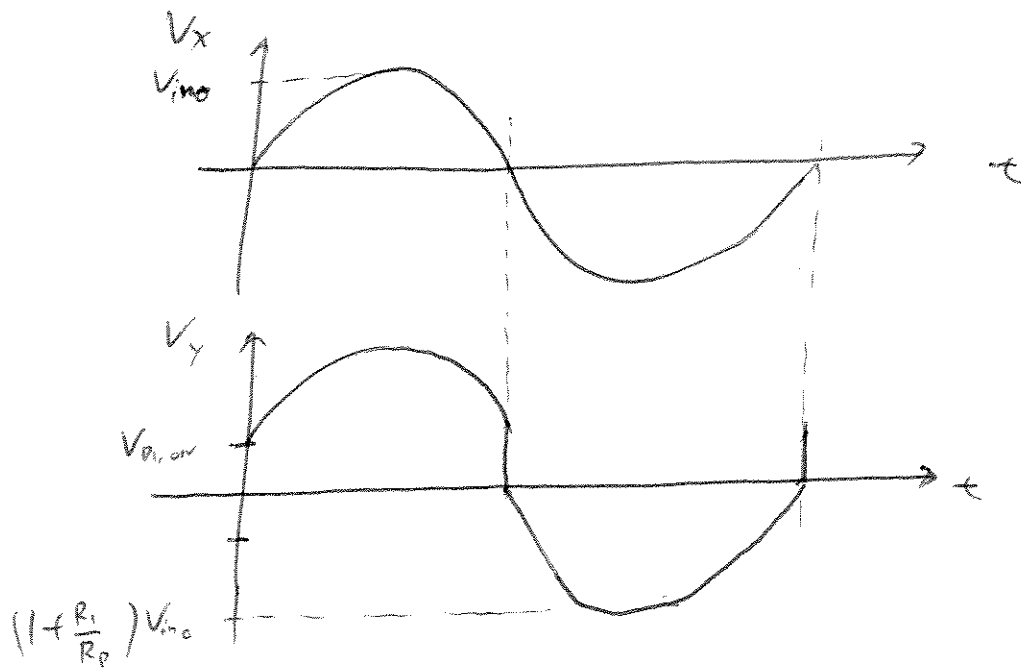$\therefore V_x = V_{in}$ for both D_1 is on and off.




39

Connecting a diode as below:

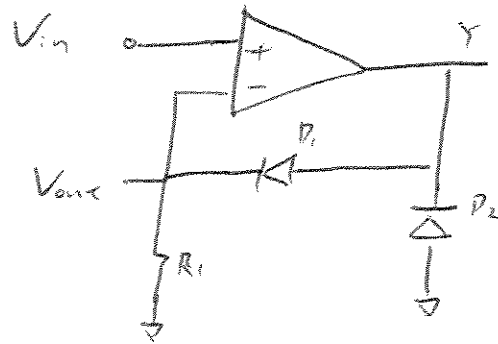


D_2 allows the parasitic capacitance to charge up faster, right before D_1 conducts.

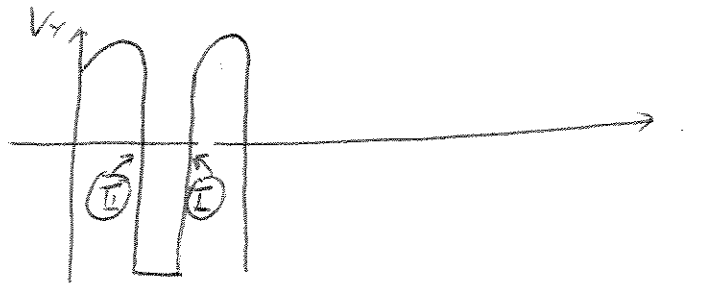This corresponds to sharpening the transition (I) of V_y , as shown below



But it will not speed up transition (II).
(which is not critical)

40

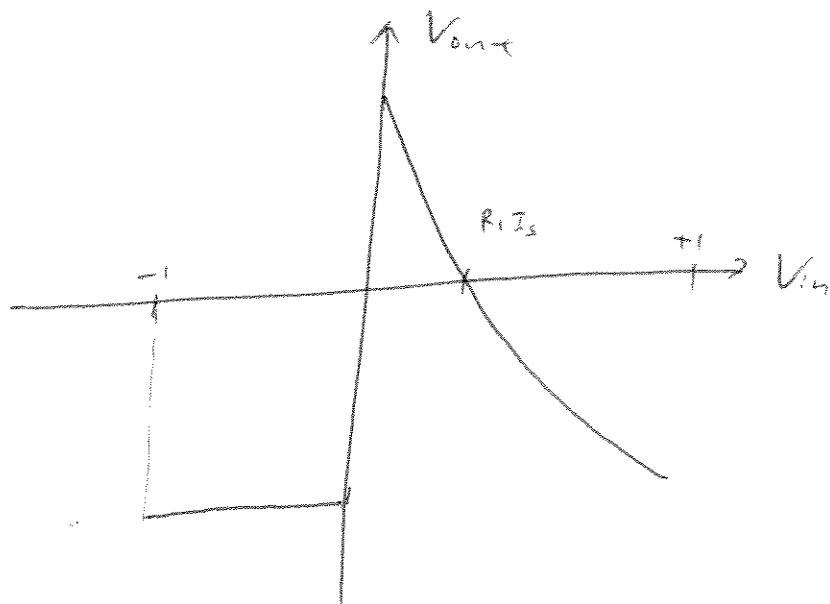

④ By KCL,

$$\frac{V_{in} - V_x}{R_1} = I_{R_1}$$

$$\therefore V_{BE} = V_T \ln \frac{\frac{V_{in} - V_x}{R_1}}{I_s}$$

$$= -V_{out}$$

$$\therefore -A_o V_x = V_{out}$$

$$V_x = -\frac{V_{out}}{A_o}$$

$$\therefore V_{out} = -V_T \ln \frac{V_{in} + \frac{V_{out}}{A_o}}{R_1 I_s}$$



(42). This circuit will not function as a noninverting opamp:

assuming $A_o = \infty$,


$$V_+ \approx V_- = V_{in}$$

$$\therefore V_{BE} = V_T \ln \frac{\frac{-V_{in}}{R_1}}{I_S}$$

$$\therefore V_{out} = -V_{BE}$$

$$V_{out} = -V_T \ln \frac{-V_{in}}{R_1 I_S}$$

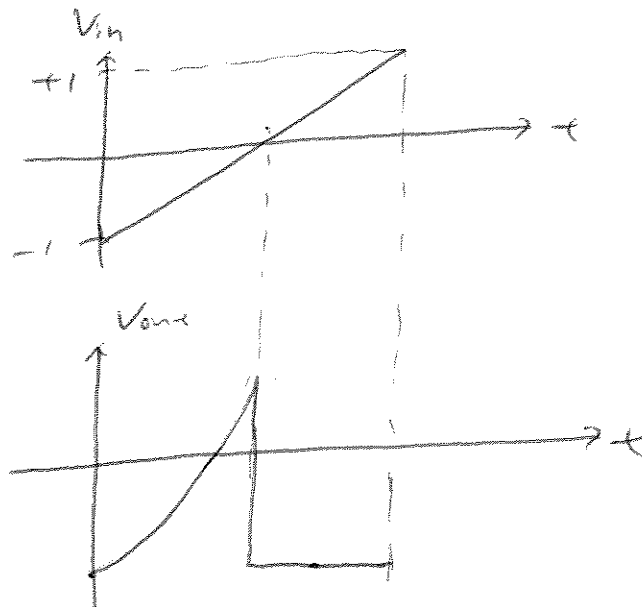
For example, as V_{in} varies from $-1V$ to $+1V$:



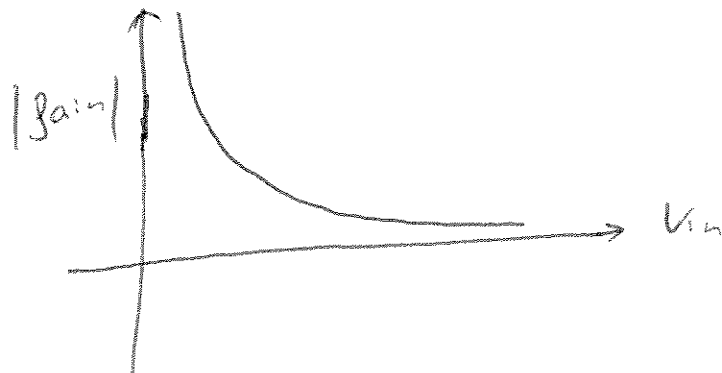(43)

$$V_{out} = -V_T \ln \frac{V_{in}}{R_i I_s}$$

$$\frac{dV_{out}}{dV_{in}} = -\frac{V_T}{V_{in}}$$



The gain is compressive, because as V_{in} increases, the magnitude of the gain decreases.

(44) Set $V_{out} = -0.5V$ when $V_{in} = 1V$

$$-0.5 = -V_T \ln \frac{1}{R_1 I_S}$$

$$\therefore R_1 I_S = 2.0612 \times 10^{-9}$$

When $V_{in} = 10V$,

$$V_{out} = -V_T \ln \frac{10}{2.0612 \times 10^{-9}}$$

$$= -0.558V > -1V.$$

\therefore setting $R_1 I_S = 2.0612 \times 10^{-9}$ meets the specification.

$$\text{choose } I_S = 1 \times 10^{-16} A.$$

$$R_1 = 20.61 \text{ M}\Omega //$$

45

Assume $A_o = \infty$,

$$I_{R_1} = \frac{V_{in} - V_{TH}}{R_1}$$

$$= \frac{1}{2} k' (V_{GS} - V_{TH})^2$$

$$\text{where } k' = \frac{W}{L} C_{ox} \mu_n$$

$$\therefore V_{GS} = -V_{out}$$

$$\therefore \frac{1}{2} k' (-V_{out} - V_{TH})^2 = \frac{V_{in} - V_{TH}}{R_1}$$

$$(-V_{out} - V_{TH})^2 = \frac{2(V_{in} - V_{TH})}{k' R_1}$$

$$(-V_{out} - V_{TH}) = \sqrt{\frac{2(V_{in} - V_{TH})}{k' R_1}}$$

$$V_{out} = -\sqrt{\frac{2(V_{in} - V_{TH})}{k' R_1}} - V_{TH}$$

$$\text{small signal gain} = -\frac{d}{dV_{in}} \sqrt{\frac{2(V_{in} - V_{TH})}{k' R_1}}$$

$$= -\frac{1}{k' R_1} \sqrt{\frac{k' R_1}{2(V_{in} - V_{TH})}}$$

$$= -\frac{1}{\sqrt{2k' R_1 (V_{in} - V_{TH})}}$$

(46)

By KCL,

$$\frac{V_x - V_{in}}{R_i} = I_{sp, m,}$$

Assume $A_o = \infty$, $\therefore V_x = V_+ = 0V$.

$$\therefore -\frac{V_{in}}{R_i} = \frac{1}{2} k' (V_{GS} - |V_{TH}|)^2,$$

where $k' = \mu_p \frac{W}{L} C_{ox}$.

$$\therefore V_{GS} = -V_{out}$$

$$\therefore -\frac{V_{in}}{R_i} = \frac{1}{2} k' (-V_{out} - |V_{TH}|)^2$$

$$-\frac{2V_{in}}{R_i k'} = (V_{out} + |V_{TH}|)^2$$

$$\therefore V_{out} = \sqrt{-\frac{2V_{in}}{R_i k'}} - |V_{TH}|$$

(47)

Assume $A_o = \infty$,

$$\therefore V_+ = V_- = V_{in}$$

Using voltage divider:

$$V_{in} + V_{os} = V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = \left(1 + \frac{R_2}{R_1} \right) (V_{in} + V_{os}) //$$

(48)

In Fig. (8.25),


Assuming input is zero,

$$\begin{aligned} V_x &= 10 \times V_{os, A_1} \\ &= 30 \text{ mV} \end{aligned}$$

$$\begin{aligned} \therefore V_{out} &= 10 \times (V_{os, A_2} + V_x) \\ &= 330 \text{ mV} \end{aligned}$$

Thus, the maximum offset error is 330 mV.

(49)

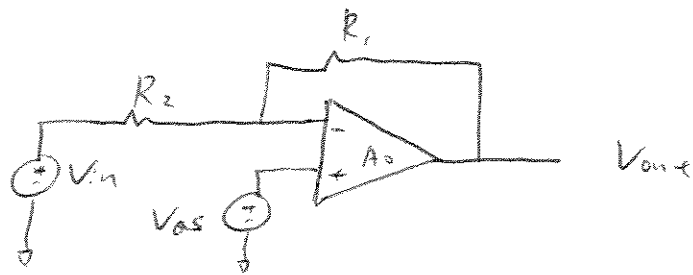

By KCL,

$$\frac{V_{in} - V_{os}}{R_2} = - \frac{V_{out} - V_{os}}{R_1}$$

$$V_{out} = - \frac{R_1}{R_2} (V_{in} - V_{os}) + V_{os}$$

⑤ By eqn (8.72)

$$V_{out} = V_{os} \left(1 + \frac{R_2}{R_1} \right)$$

$$\therefore 20 \text{ mV} = 3 \text{ mV} \left(1 + \frac{R_2}{R_1} \right)$$

$$\frac{17}{3} = \frac{R_2}{R_1} \quad \text{————— ①}$$

$$\therefore \frac{1}{R_2 C_1} \ll 2\pi (1000)$$

and setting $C_1 = 100 \text{ pF}$,

$$\frac{1}{R_2 \times 100 \times 10^{-12}} \ll 2\pi (1000)$$

$$\frac{1}{R_2} \ll 6.283 \times 10^{-7}$$

$$\therefore R_2 \gg 1.59 \text{ M}\Omega$$

$$\text{choose } R_2 = 17 \text{ M}\Omega //$$

$$R_1 = 3 \text{ M}\Omega // \quad (\text{From ①})$$

(51) From eqn (8.44),

$$V_{out} \propto \frac{dV_{in}}{dt}$$

(proportional)

Since offset is static (invariant with time)

$$\text{i.e. } \frac{dV_{os}}{dt} = 0.$$

\therefore offset has no effect to V_{out} .

(52) From eqn (8.60),

with the presence of offset (V_{os}),

$$V_{out} = -V_T \ln \frac{V_{in} + V_{os}}{R \cdot I_s}$$

The effect of offset to V_{out} is

very small, because V_{out} is
proportional to the log. of $(V_{in} + V_{os})$.

Thus, V_{out} is very insensitive to
the magnitude of the offset.

(53). From eqⁿ (8.76),

$$V_{out} = R_1 I_{B2}$$


• V_{out} is independent of I_{B1}

Also I_{B1} will not affect $\frac{V_{out}}{V_{in}}$.

Thus, the small offset (ΔI) in the input bias currents has no effect on V_{out} .


54 Using superposition:

(I) turn off I_{B1} :

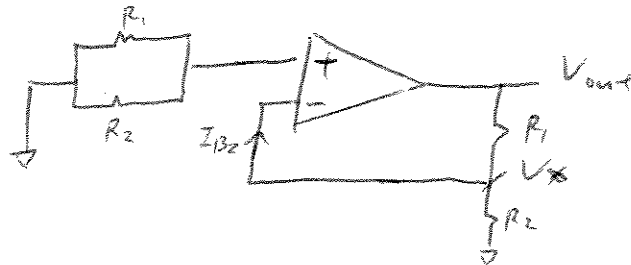


$$\therefore V_+ = V_- = 0, \quad \therefore V_x = 0,$$

The circuit becomes:

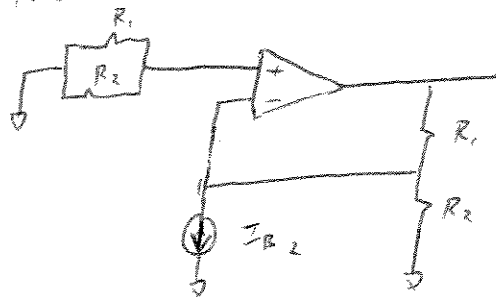

$$\therefore \text{From eqn (8.76), } V_{out, 2} = -R_1 I_{B2}$$

(II) turn off I_{B2} :

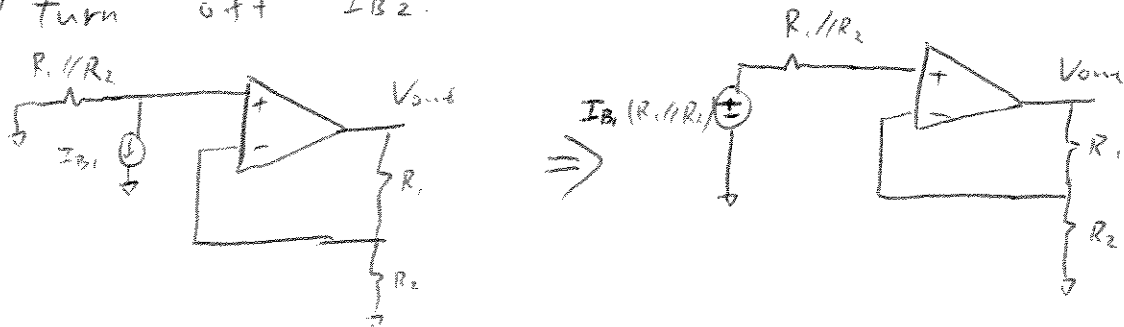

$$\begin{aligned} \therefore V_{out, IB1} &= I_{B1} \left(\frac{R_1 R_2}{R_1 + R_2} \right) \times \left(1 + \frac{R_1}{R_2} \right) \\ &= I_{B1} R_1 \end{aligned}$$

(54) cont'd

\therefore given $I_{B1} - I_{B2} = \Delta I$, and $V_{out} = I_{B1} + I_{B2}$,

$$I_{B1} R_1 - I_{B2} R_1 < \Delta V$$

$$\Delta I R_1 < \Delta V$$

$$\therefore R_1 < \frac{\Delta V}{\Delta I}$$

There is no dependence of output error on R_2 .

(55) Using eqn. (8.84)

$$\text{Gain} = \frac{A_0}{1 + \frac{s}{\omega_1}}$$

For opamp (a); At 100 MHz:

$$\text{Gain}_{(a)} = \frac{1000}{1 + \frac{2\pi \times 100 \times 10^6}{2\pi \times 50}}$$

$$\approx 5 \times 10^{-4}$$


For opamp (b) at 100 MHz,

$$\text{Gain}_{(b)} = \frac{500}{1 + \frac{2\pi \times 100 \times 10^6}{2\pi \times 10}}$$

$$\approx 4.95 > 4$$

\therefore opamp (b) is a possible candidate

56

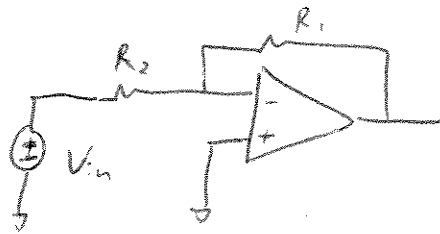

Using eqⁿ (8.20),

$$\frac{V_{out}}{V_{in}} = - \frac{1}{\frac{R_2}{R_1} + \frac{1}{A_0} \left(1 + \frac{R_2}{R_1}\right)}$$

Here, A_0 becomes $\frac{A_0}{1 + \frac{s}{\omega_1}}$,

$$\begin{aligned} \therefore \frac{V_{out}}{V_{in}} &= \frac{-1}{\frac{R_2}{R_1} + \frac{A_0}{1 + \frac{s}{\omega_1}} \left(1 + \frac{R_2}{R_1}\right)} \\ &= \frac{-1}{\left(1 + \frac{s}{\omega_1}\right) \frac{R_2}{R_1} + A_0 \left(1 + \frac{R_2}{R_1}\right)} \end{aligned}$$


To find the pole, equate denominator to 0.

$$\text{i.e. } \left(1 + \frac{s}{\omega_1}\right) \frac{R_2}{R_1} + A_0 \left(1 + \frac{R_2}{R_1}\right) = 0$$

$$\left(1 + \frac{s}{\omega_1}\right) = - \frac{R_1}{R_2} A_0 \left(1 + \frac{R_2}{R_1}\right)$$

$$\therefore | \omega_{p, \text{closed}} | = \left(1 + \frac{R_1}{R_2} A_0 \left(1 + \frac{R_2}{R_1}\right)\right) \omega_1$$

57.

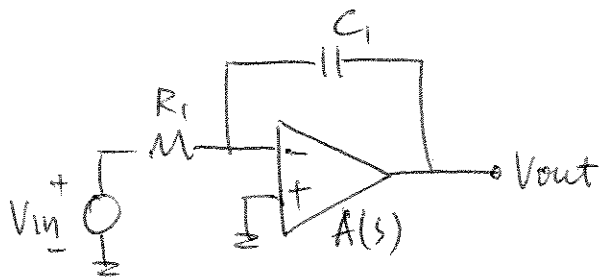

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

$$\omega_0 \gg \frac{1}{RC_i}$$


$$\frac{V_{in} - V_{(-)}}{R_i} = (V_{(-)} - V_{out}) s C_i$$

$$-V_{(-)} \times A(s) = V_{out}$$

Substitute ② into ①:

$$\begin{aligned} \frac{V_{out}}{V_{in}}(s) &= - \left[\frac{s C_i R_i + 1}{A(s)} + s C_i R_i \right]^{-1} \\ &= - \left[\frac{(s C_i R_i + 1)(1 + \frac{s}{\omega_0})}{A_0} + s C_i R_i \right]^{-1} \\ &\approx \left(\frac{1}{A_0 \omega_0} \left[s \omega_0 C_i R_i + s^2 C_i R_i + s \right] + s C_i R_i \right)^{-1} \\ &\approx - \left[s \left(C_i R_i + \frac{1}{A_0 \omega_0} \right) + s^2 \left(\frac{C_i R_i}{A_0 \omega_0} \right) \right]^{-1} \\ &\approx - \left[s C_i R_i + s^2 \frac{C_i R_i}{A_0 \omega_0} \right]^{-1} \\ &= \frac{-1}{\left(1 + \frac{s}{A_0 \omega_0} \right) \frac{s}{\left(\frac{1}{R_i C_i} \right)}} \end{aligned}$$

58.

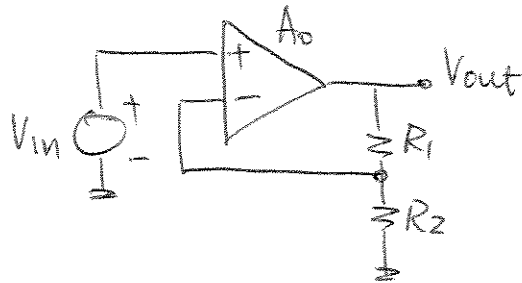

Nominal gain = 4
Slew Rate = 1V/ns

$$V_p = 0.5 \text{ V}$$

$$V_{in}(t) = 0.5 \sin \omega t \Rightarrow V_{out} = 0.5 \times \overbrace{\left(1 + \frac{R_1}{R_2}\right)}^{=4} \sin \omega t.$$

$$\frac{dV_{out}}{dt} = 0.5 \left(1 + \frac{R_1}{R_2}\right) \omega \cdot \cos \omega t.$$


= Maximum when $\cos \omega t = 1$

$$\Rightarrow \left. \frac{dV_{out}}{dt} \right|_{\max} = 0.5 \omega \left(1 + \frac{R_1}{R_2}\right) = 2 \omega$$

\therefore Highest frequency $\Rightarrow 2 \omega = 1 \text{ V/ns}$

$$\Rightarrow \omega = 0.5 \text{ rad/ns} \Rightarrow f_{\max} \approx 79.6 \text{ MHz}$$


59.

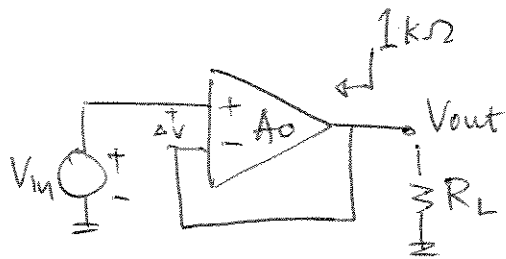

$$R_L = 100 \Omega$$

$$\text{Gain Error} = 0.5\%$$
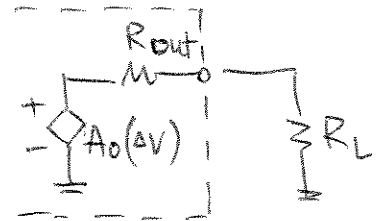
$$(V_{in} - V_{out}) A_o \times \frac{R_L}{R_{out} + R_L} = V_{out}$$




$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{R_{out} + R_L}{A_o R_L}} \approx 1 - \underbrace{\frac{R_{out} + R_L}{A_o R_L}}_{= \epsilon}$$

$$\therefore \epsilon = \frac{R_{out} + R_L}{A_o R_L} \Rightarrow A_o = \frac{R_{out} + R_L}{\epsilon R_L} = \frac{1000 + 100}{0.5\% \times 100}$$

$$\approx 2200$$

60.

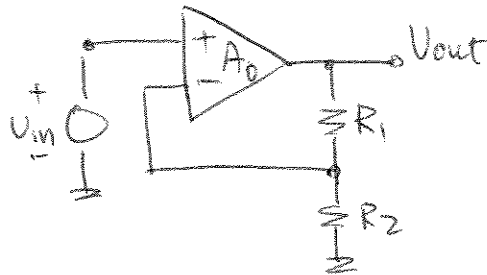

Nominal Gain = 4

Gain Error = 0.2%

$R_1 + R_2 = 20 \text{ k}\Omega$

$$\left[V_{in} - \frac{R_2}{R_1 + R_2} \times V_{out} \right] A_0 = V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0} \approx \left(1 + \frac{R_1}{R_2} \right) \left[1 - \left(1 + \frac{R_1}{R_2} \right) \frac{1}{A_0} \right]$$


$$\left(1 + R_1/R_2 \right) = 4 \quad \& \quad (R_1 + R_2) = 20 \text{ k}\Omega$$

$$\Rightarrow R_1 = 15 \text{ k}\Omega, \quad R_2 = 5 \text{ k}\Omega.$$

$$0.2\% = \left(1 + \frac{R_1}{R_2} \right) \frac{1}{A_0} \Rightarrow A_0 = \left(1 + \frac{R_1}{R_2} \right) \times \frac{1}{0.2\%}$$

$$= 2000$$

b1.

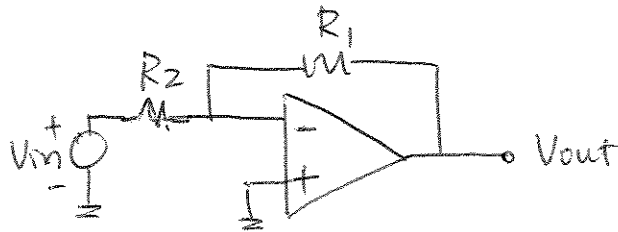

Nominal gain = 8
Gain Error = 0.1%
 $R_{out} = 0.1\%$

$$V_x = V_{in} + (V_{out} - V_{in}) \frac{R_2}{R_1 + R_2} \quad \text{--- (1)}$$

$$\frac{V_{out} - V_{in}}{R_1 + R_2} = \frac{-A_0 V_x - V_{out}}{R_{out}} \quad \text{--- (2)}$$

Substitute (2) into (1) gives:

$$\frac{V_{out}}{V_{in}} = \left(-\frac{R_1}{R_2} \right) \frac{A_0 - R_{out}/R_1}{\underbrace{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}}_{(1-\epsilon)}}$$


$$\Rightarrow 8 = R_1/R_2$$

$$0.1\% = 1 - \frac{A_0 - 100/R_1}{1 + \frac{100}{R_2} + A_0 + (8)}$$

$$\Rightarrow \text{Choose } R_1 = 8\text{ k}\Omega, R_2 = 1\text{ k}\Omega$$

$$\Rightarrow A_0 \approx 9100$$

62.

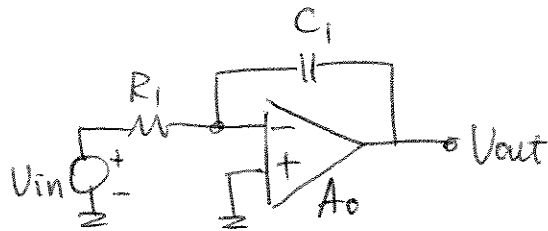

$$\begin{aligned} &= 100 \text{ kHz} \\ \text{pole} &= 100 \text{ Hz} \\ C_{\text{MAX}} &= 50 \text{ pF}. \end{aligned}$$

$$\frac{V_{in} - V_{(-)}}{R_1} = (V_{(-)} - V_{out}) \leq C_1 \quad \text{--- (1)}$$

$$V_{(-)} \cdot (-A_0) = V_{out} \quad \text{--- (2)}$$

Substitute (2) into (1):

$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{A_0} + (1 + \frac{1}{A_0}) R_1 C_1 s}$$

$$\Rightarrow s_p = \frac{-1}{(A_0 + 1) R_1 C_1} = -100 \text{ Hz} \quad \text{--- (1)}$$


$$\text{Attenuation above } 100 \text{ kHz} \Rightarrow \left| \frac{V_{out}}{V_{in}} \right|_{100 \text{ kHz}} = 1$$

$$\Rightarrow \left| \frac{A_0}{\sqrt{1 + [(A_0 + 1) R_1 C_1 \omega]^2}} \right|_{100 \text{ kHz}} = 1 \quad \text{--- (2)}$$

Substitute (1) into (2):

$$\Rightarrow A_0 \approx 1000. \quad \text{Choose } C = 50 \text{ pF} \Rightarrow R \approx 200 \text{ k}\Omega.$$

63.

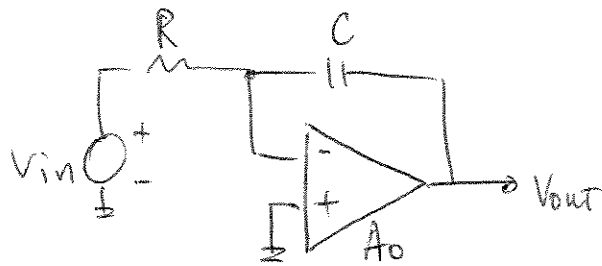

$$V(t) = \alpha t$$


$$0 < V(t) < V_0$$

$$\text{where } \alpha = 10 \text{ V}/\mu\text{s}$$

$$V_0 = 1 \text{ V}$$

$$C_{\text{max}} = 20 \text{ pF}$$

$$\text{Error} < 0.1\%$$

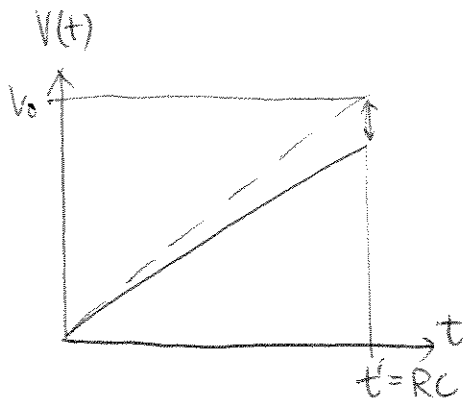

$$V_{\text{out}}(t) = -\frac{V_0}{RC} t, \quad t \in [0, RC]$$

$$V(t) = -\alpha t$$

$$\text{At } t = RC, \quad \frac{\Delta V}{V_0} = \frac{V_{\text{out}}(t) - V(t)}{V_0} \bigg|_{t=RC} < 0.1\%$$


$$\Rightarrow \Delta V = V_0 \times 0.1\% = 0.001 \text{ V}$$

$$\Rightarrow -\frac{V_0}{RC} \times t + \alpha t \bigg|_{t=RC} = 0.001 \text{ V } (= \Delta V)$$

$$\text{Choose } C = 20 \text{ pF}$$

$$\therefore R = \frac{V_0 - \Delta V}{\alpha C} = \frac{1 \text{ V} - 0.001 \text{ V}}{10 \text{ V}/\mu\text{s} \times 20 \text{ pF}} = 4995 \Omega$$

64.

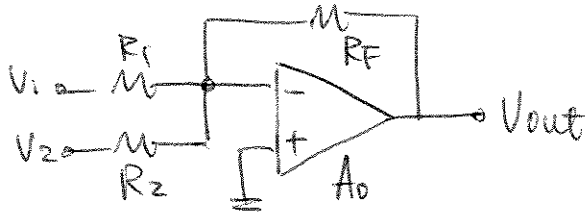

$$V_{out} = \alpha_1 V_1 + \alpha_2 V_2$$

\uparrow \uparrow
 0.5 1.5

Error of $\alpha \leq 0.5\%$
 $R_{in} \geq 10 \text{ k}\Omega$.

$$\frac{V_1 - V(-)}{R_1} + \frac{V_2 - V(-)}{R_2} = \frac{V(-) - V_{out}}{R_F} \quad \text{--- ①}$$

$$V(-) = V_{out} \quad \text{--- ②}$$

Substitute ② into ① & solve for V_{out} :

$$V_{out} = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right) \cdot \left[\frac{1}{A_0} \left(\frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right) + 1 \right]^{-1}$$


$$\approx - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right) \cdot \left[1 - \frac{1}{A_0} \left(\frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right) \right]$$

Choose $R_{in, V_2} (\approx R_2) = 10 \text{ k}\Omega \Rightarrow R_F = \alpha_2 \times R_2 = 15 \text{ k}\Omega$
 $\Rightarrow R_1 = R_F / \alpha_1 = 30 \text{ k}\Omega$
 $\approx R_{in, V_1}$

$$\Rightarrow \epsilon = 0.5\% = \frac{1}{A_0} \left(\frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right)$$

$$\Rightarrow A_0 = \frac{1}{0.5\%} (0.5 + 1.5 + 1) = 600 \quad (\text{or larger})$$

65.

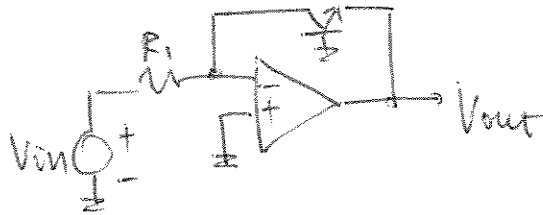

$$[0.1, 2]V \mapsto [-0.5, -1]V$$

$$V_{out} = -V_T \ln \frac{V_{in}}{I_s R_i}$$

$$-0.5V = -V_T \ln \left[\frac{(0.1)}{I_s R_i} \right] \Rightarrow I_s R_i = 4.45 \cdot 10^{-10} V \quad \text{--- ①}$$

$$\Rightarrow -V_T \ln \left(\frac{2}{I_s R_i} \right) = -0.026V \ln \left(\frac{2}{4.45 \cdot 10^{-10}} \right) \approx -0.58V$$

∴ input range of $0.1 \leftrightarrow 2V$ corresponds to output range of $-0.5 \leftrightarrow -0.58V$

$$\text{Choose } I_s = 1 \times 10^{-16} A \Rightarrow R_i = 4.45 M\Omega.$$

(6b.) No, this is not possible to meet requirements.

$$\frac{\Delta V_{out}}{\Delta V_{in}} = \frac{V_T}{V_{in}}$$

Assuming temperature is fixed, V_T is a fixed quantity that is both process and design independent.

At 25°C , $V_T \approx 25\text{mV}$.

$$\therefore \left. \frac{\Delta V_{out}}{\Delta V_{in}} \right|_{V_{in}=1\text{V}} = 25\text{mV/V}$$

$$\left. \frac{\Delta V_{out}}{\Delta V_{in}} \right|_{V_{in}=2\text{V}} = 12.5\text{mV/V}$$