

① For M_1 to stay in saturation,

$$V_{DS} > V_{GS} - V_{TH},$$

i.e. $V_{DS} > V_{DD} - V_{TH}$

$$V_{DS} > 1.4$$

$$\therefore V_{DS} = V_{DD} - I_{DS} (R_L)$$

where $R_L = 1 \text{ k}\Omega$.

and
$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.4)^2$$

$$\therefore V_{DS} = V_{DD} - 10^{-4} \left(\frac{W}{L}\right)_1 (1.96 \times 1000)$$

i.e. $1.8 - 1.96 \times 10^{-4} \left(\frac{W}{L}\right)_1 > 1.4$

$$\frac{0.4}{1.96 \times 10^{-4}} > \left(\frac{W}{L}\right)_1$$

Maximum allowable $\left(\frac{W}{L}\right)_1$ is 204.

② To get $I_{DS} = 1 \text{ mA}$,

$$\frac{1}{2} \mu C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2 = 1 \times 10^{-3} \text{ A.}$$

$$\frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18} \right)_1 (V_{GS} - V_{TH})^2 = 10^{-3}$$

$$(V_{GS} - V_{TH})^2 = 0.09$$

$$V_{GS} - V_{TH} = 0.3,$$

$$\text{ie. } V_{GS} = 0.7.,$$

$$\text{Since } V_{GS} = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$0.7 = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$0.7 R_1 = R_2,$$

$$\therefore \frac{R_1}{R_2} = \frac{11}{7} \quad \text{————— ①}$$

To get input impedance $\geq 20 \text{ k}$.

$$R_1 \parallel R_2 \geq 20 \text{ k}\Omega. \quad \text{————— ②}$$

By inspection, setting $R_1 = 55 \text{ k}\Omega$ and $R_2 = 35 \text{ k}\Omega$ will satisfy both ① and ②.

$$(3) \quad V_G = 1.8 \text{ V}$$

$$V_S = I_{DS} (100)$$

$$V_D = 1.8 - 1000 I_{DS}$$

For M_1 to be in saturation,

$$V_{DS} \geq V_{GS} - V_{TH}$$

$$\therefore V_D - V_S \geq V_G - V_S - V_{TH}$$

$$V_D \geq V_G - V_{TH}$$

$$V_D \geq 1.4 \text{ V}$$

$$\therefore I_{DS, \max} = \frac{1.8 - 1.4}{1000} = 0.4 \text{ mA}$$

$$\text{and } \therefore V_S = (0.4 \times 10^{-3}) / (100)$$

$$= 0.004 \text{ V}$$

$$V_{GS} = 1.76 \text{ V}$$

$$g_{m, \max} = \frac{2 I_{DS, \max}}{(1.76 - 0.4)}$$

$$= 0.588 \text{ mS} //$$

④ a) $\therefore V_{RS} = 200 \text{ mV},$

$\therefore I_{DS} R_S = 200 \text{ mV}$

$$I_{DS} = \frac{0.2}{100}$$

$$I_{DS} = 2 \text{ mA}.$$

For M_1 to stay in saturation,

$$V_{DS} \geq V_{GS} - V_{TH}.$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ &= [1.8 - (2 \times 10^{-3}) \times 500] - 0.2 \\ &= 0.6, \end{aligned}$$

$$\therefore V_{GS} - V_{TH} \leq 0.6,$$

Since $I_{DS} = \frac{1}{2} (M_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2,$

$\left(\frac{W}{L}\right)$ is min. when $(V_{GS} - V_{TH})$ is max,

$\therefore \text{Min. } \left(\frac{W}{L}\right)_1 \text{ is when } (V_{GS} - V_{TH}) = 0.6 \text{ V},$

$$2 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right)_1 (0.6)^2$$

$$\therefore \text{min. } \left(\frac{W}{L}\right)_1 \approx 56$$

b) With $(V_{GS} - V_{TH}) = 0.6$,

$$V_{GS} = 1,$$

$$\therefore V_G = 1 + V_S$$

$$V_G = 1.2V,$$

$$\text{i.e. } 1.8 \times \frac{R_2}{R_1 + R_2} = 1.2V,$$

$$\frac{R_2}{R_1} = 2 \quad \text{--- (1)}$$

$$\text{Input impedance} = R_2 // R_1,$$

$$\text{i.e. } R_2 // R_1 \geq 30k\Omega \quad \text{--- (2)}$$

Set $R_1 = 50k\Omega$ and $R_2 = 100k\Omega$

will satisfy both (1) & (2).

⑤.

$$\begin{aligned} V_S &= V_{R_S} \\ &= I_{D_1} (200) = 0.1 \text{ V} \end{aligned}$$

$$I_{D_S} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{G_S} - V_{TH})^2$$

$$0.5 \text{ mA} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18} \right) (V_{G_S} - V_{TH})^2$$

$$\therefore V_{G_S} = 0.612 \text{ V}$$

$$\begin{aligned} \therefore V_G &= 0.612 + 0.1 \\ &= 0.712. \end{aligned}$$

$$\therefore V_G = V_{DD} - I_{R_1} \times R_1$$

$$R_1 = \underline{\underline{21.76 \text{ k}\Omega}}$$

$$\text{and } V_{G_S} = I_{R_2} \times R_2$$

$$\therefore R_2 = \frac{0.712}{0.05 \times 10^{-3}}$$

$$= \underline{\underline{14.24 \text{ k}\Omega}}$$

⑥.

$$f_m = \sqrt{2 \beta I_{DS}} = \frac{1}{100},$$

$$\therefore I_{DS} = 1 \text{ mA}, \quad \beta = 0.05,$$

$$\text{and } I_{DS} = \frac{1}{2} \beta (V_{GS} - V_{TH})^2,$$

$$\text{where } \beta = \mu_n C_{ox} \left(\frac{W}{L} \right),$$

$$\therefore 1 \text{ mA} = \frac{1}{2} (0.05) (V_{GS} - V_{TH})^2.$$

$$V_{GS} = 0.6.$$

$$\therefore V_{GS} = V_{DS} = V_{DD} - I_{DS} R_D,$$

$$0.6 = 1.8 - (0.5 \times 10^{-3}) R_D,$$

$$R_D = \underline{\underline{2.4 \text{ k}\Omega}}$$

⑦.

$$I_{DS} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2$$

$$0.5 \times 10^{-3} = (100 \times 10^{-6}) \left(\frac{50}{0.18} \right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.534 \text{ V}$$

$$\therefore R_2 = \frac{0.534}{0.05 \times 10^{-3}}$$

$$R_2 = \underline{\underline{10.68 \text{ k}\Omega}}$$

$$\therefore V_{D1} = 1.8 - (1.1 \times I_{DS} \times 2 \text{ k}\Omega) = 0.1 I_{DS} (R_1 + R_2),$$

$$\therefore 14 \text{ k}\Omega = R_1 + 10.68 \text{ k}\Omega.$$

$$\therefore R_1 = \underline{\underline{3320 \Omega}}$$

⑧ Without defect,

$$V_{GS} = V_{DS}, \quad (\text{i.e. } V_G = V_D)$$

$$\therefore \frac{20k}{10k+20k} \times 1.8 = 1.8 - I_{DS} (1k\Omega)$$

$$I_{DS} = 0.6 \text{ mA}$$

$$\begin{aligned} \therefore V_{GS} &= V_G - V_S \\ &= 1.2 - (0.6 \times 10^{-3})(200) \\ &= 1.08 \end{aligned}$$

$$\text{and, } 0.6 \text{ mA} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L} \right) (V_{GS} - 0.4)^2$$

$$\frac{W}{L} \approx 13 //$$

With R_P

$$V_{GS} = V_{DS} + V_{TH}$$

$$1.2 = V_{DS} + 0.4$$


$$\therefore V_{DS} = 0.8 \text{ V}$$

$$\therefore V_{DS} = V_{DD} - V_{1k\Omega} - V_{200\Omega}$$

$$\begin{aligned} \therefore I_{D1} + I_{RP} &= \frac{1 \text{ V}}{1k\Omega + 200\Omega} \\ &= 0.833 \text{ mA} \end{aligned}$$

$$\therefore I_{RP} = \frac{V_{DS}}{R_P} = \frac{0.8}{R_P}$$
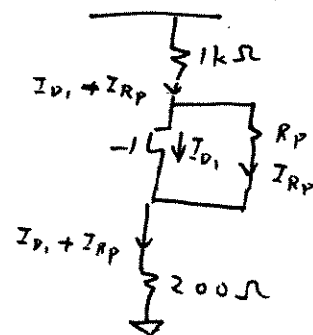
$$\text{and } I_{D1} = 0.6 \text{ mA (from above)}$$



$$\therefore \frac{0.8V}{R_p} + 0.6 \text{ mA} = 0.833 \text{ mA}$$

$$R_p \approx 3430 \Omega //$$

⑨ With out defects,

$$V_{GS} = 1.8V,$$

$$\text{i.e. } V_{DS} = (1.8 - 0.1)V$$

$$= 1.7V$$

$$I_{DS} = \frac{(1.8 - 1.7)V}{2000\Omega} = 0.05mA.$$

$$\therefore 0.05mA = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1.8 - 0.4)^2$$

$$\therefore \left(\frac{W}{L}\right) = 0.255 //$$

b) With defects,

$$V_{GS} = V_{DS} + 50mV$$

$$\therefore V_{RP} = 50mV$$

$$I_{RP} = \frac{50mV}{R_P}$$

$$V_{GS} = 1.8V - \frac{0.05V}{R_P} \times 30k\Omega \quad \text{--- (1)}$$

$$\therefore V_{DD} - \left(I_{DS} - \frac{50mV}{R_P}\right) 2k\Omega = V_{DS}$$

$$V_{DD} - \left(I_{DS} - \frac{50mV}{R_P}\right) 2k\Omega = V_{GS} - 50mV \quad \text{--- (2)}$$

$$\begin{aligned}
 \therefore I_{DS} &= \frac{1}{2} \left(\frac{W}{L} \right) (\mu_n C_{ox}) (V_{GS} - V_{TH})^2 \\
 &= \frac{1}{2} (0.255) (200 \times 10^{-6}) (V_{GS} - 0.4)^2 \\
 &= 2.55 \times 10^{-5} (V_{GS} - 0.4)^2
 \end{aligned}$$

\therefore From ②,

$$\begin{aligned}
 1.8 - \left[2.55 \times 10^{-5} (V_{GS} - 0.4)^2 - \frac{0.2}{R_P} \right] 2000 \\
 = V_{GS} - 0.05.
 \end{aligned}$$

From ①,

$$\frac{0.05}{R_P} = \frac{1.8 - V_{GS}}{30000}$$

$$\therefore 1.8 - \left[0.051 (V_{GS} - 0.4)^2 - \frac{1.8 - V_{GS}}{15} \right] = V_{GS} - 0.3$$

$$1.85 - 0.051 V_{GS}^2 + 0.0408 V_{GS} - 0.00816 + \frac{1.8 - V_{GS}}{15} = V_{GS}$$

$$29.4276 - 15.388 V_{GS} - 0.765 V_{GS}^2 = 0$$

$$\therefore V_{GS} = 1.76 \text{ V} //$$

$$R_P = \frac{0.05 \times 30000}{1.8 - 1.76}$$

$$\approx 36.3 \text{ k}\Omega$$

(10) For M_1 ,

$$I_x = \frac{1}{2} (200 \times 100^{-6}) \left(\frac{W_1}{0.25} \right) (0.8 - 0.4)^2 \times (1 + 0.1(0.8))$$

$$10^{-3} = 0.16 \times 10^{-4} \left(\frac{W_1}{0.25} \right) (1.08)$$

$$\therefore W_1 = 14.5 \mu //$$

For M_2 ,

$$0.5 \times 10^{-3} = 0.16 \times 10^{-4} \left(\frac{W_2}{0.25} \right) (1.08)$$

$$\therefore W_2 = 7.25 \mu //$$

Output resistance $= r_o$
 $= \frac{1}{\lambda} \times \frac{1}{I_D}$

$$\therefore r_{o1} = \left(\frac{1}{0.1} \right) \left(\frac{1}{10^{-3}} \right)$$

$$= 10 \text{ k}\Omega //$$

$$r_{o2} = \left(\frac{1}{0.1} \right) \left(\frac{1}{0.5 \times 10^{-3}} \right)$$

$$= 20 \text{ k}\Omega //$$

(11)

$$R_{out} = \frac{1}{\eta} \left(\frac{1}{I_D} \right)$$
$$= \frac{1}{0.5 \times 10^{-3} \eta} = 20 k\Omega$$

$$\therefore \eta = 0.1 V^{-1}$$

(12) For M_1 , $\mu = 0.1$

$$0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W_1}{0.25} \right) (1 - 0.4)^2$$

$$W_1 \approx 3.47 \text{ mm.}$$

For M_2 ,

$$0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W_2}{0.25} \right) (1.2 - 0.4)^2$$

$$W_2 \approx 1.95 \text{ mm.}$$

$$\frac{r_{o1}}{r_{o2}} = \frac{\frac{1}{\lambda I_x}}{\frac{1}{\lambda I_y}}$$

$$= 1 \quad (\because I_x = I_y)$$

$$\therefore r_{o1} = r_{o2}$$

⑬ Impedance at source of M_1 , $Z_s = \frac{1}{f_{mp}}$

$$\begin{aligned} f_{mp} &= \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L} \right) I_D (1 + \lambda) V_{DS}} \\ &= \sqrt{2 \times 100 \times 10^{-6} \left(\frac{10}{0.25} \right) (1 + 0.1 \times 1.2) I_D} \\ &= \sqrt{0.0896 I_D} \end{aligned}$$

$$\begin{aligned} I_D &= \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{10}{0.25} \right) (V_{B1} - V_{th} + 0.4)^2 \\ &\quad \times (1 + 0.1 \times 1.2) \\ &\approx 0.806 \text{ mA} \end{aligned}$$

$$\begin{aligned} \therefore f_{mp} &= \sqrt{0.0896 \times 0.806 \times 10^{-3}} \\ &\approx 8.50 \text{ mS} \end{aligned}$$

$$\therefore Z_s \approx 118 \Omega //$$

(14)

$$I_x = \frac{1}{2} (100 \times 10^{-6}) \left(\frac{20}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 0.64 \text{ mA} //$$

$$I_y = \frac{1}{2} (100 \times 10^{-6}) \left(2 \times \frac{20}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 1.28 \text{ mA} //$$

$$\therefore r_o \propto \frac{1}{I}$$

$$\text{and } I_y = 2 I_x$$

$$\therefore r_{out, m_1} = 2 r_{out, m_2} //$$

$$(15) \quad |I_{D S 1}| = |I_{D S 2}|,$$

$$\begin{aligned} \frac{1}{2} (200 \times 10^{-6}) \left(\frac{10}{0.18} \right) (V_B - 0.4)^2 (1 + 0.1 \times 0.9) \\ = \frac{1}{2} (100 \times 10^{-6}) (1.8 - V_B - 0.4)^2 (1 + 0.1 \times 0.9) \\ \times \left(\frac{30}{0.18} \right) \end{aligned}$$

$$2 (V_B - 0.4)^2 = 3 (1.4 - V_B)^2$$

$$\sqrt{\frac{2}{3}} (V_B - 0.4) = (1.4 - V_B)$$

$$1.816 V_B = 1.7264$$

$$V_B = 0.95 //$$

①6 a) For M_1 ,

$$I_{D1} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{5}{0.18} \right) (V_B - 0.4)^2 (1 + 0.1 \times 0.9)$$

$$\therefore V_B \approx 0.806 \text{ V}$$

b) There are 3 regions of operation:


For $V_x < V_B - V_{TH1}$, M_1 is in triode.
and $|I_{DS2}| > |I_{DS1}|$

For $|V_x - V_{DD}| > |V_B - V_{DD} - V_{TH2}|$, M_2 is in triode
and $I_{DS1} > |I_{DS2}|$

For $V_B - V_{TH1} < V_x$ and $|V_x - V_{DD}| < |V_B - V_{DD} - V_{TH2}|$,
 M_1 and M_2 are in saturation.

and $I_{DS1} = |I_{DS2}| = 0.5 \text{ mA}$ at $V_x = 0.9 \text{ V}$

In all cases, $I_x = I_{DS1} - |I_{DS2}|$

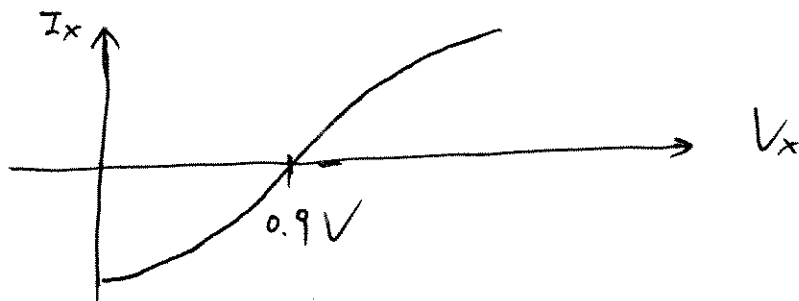

$$(17) \quad a) \quad 0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{30}{0.18} \right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.573 \text{ V} //$$

$$V_{DS} = 1.8 - 0.5 \times 10^{-3} \times 2000$$

$$= 0.8.$$

$$\therefore V_{DS} > V_{GS} - V_{TH},$$

M_1 is in saturation.

$$b) \quad \therefore \lambda = 0, \quad r_o = \infty.$$

$$\therefore A_v = g_m R_D$$

$$= \sqrt{2 \times (200 \times 10^{-6}) \times \frac{30}{0.18} \times 0.5 \text{ mA}} \times 2000$$

$$= 11.55 //$$

18

$$a/ \quad 0.25 \times 10^{-3} = \frac{1}{2} \times (200 \times 10^{-6}) \left(\frac{20}{0.18} \right) (V_{GS} - 0.4)^2$$

$$\therefore V_{GS} = 0.55 //$$

$$b/ \quad V_{DS, \min} = V_{GS} - V_{TH} \\ = 0.15 V.$$

$$\text{with } V_{DS} = 0.15 V,$$

$$I_{DS, \max} = \frac{1.8 - 0.15}{2000} \\ = 0.825 \text{ mA}.$$

$$\therefore \frac{0.825 \times 10^{-3}}{0.25 \times 10^{-3}} = \frac{\left(\frac{W}{L} \right)'}{\left(\frac{W}{L} \right)},$$

where $\left(\frac{W}{L} \right)'$ is the new $\left(\frac{W}{L} \right)$.

$\therefore \left(\frac{W}{L} \right)$ can be increased by 3.3 times.

$$\therefore A_v \propto \frac{f_m}{\sqrt{\beta I}}$$

$\therefore A_v$ is also increased by 3.3 times.

(since both β & I increase by 3.3 times)

(19) Voltage gain (A_v) = 5,

i.e. $f_m R_D = 5.$

Power (P) = $I_{DS} \times V_{DD},$

$\therefore P \leq 1 \text{ mW},$

$I_{DS} \times 1.8 \leq 1 \text{ mW}.$

$I_{DS} \leq 0.556 \text{ mA}.$

$f_m = \sqrt{2 \beta I_{DS}}$

$\therefore f_{m, \max} = \sqrt{2 \times 200 \times 10^{-6} \times \left(\frac{20}{0.18}\right) \times 0.556 \text{ mA}}$

$= 0.00497 \text{ s}^{-1}$

$\therefore R_D = \frac{5}{0.00497}$

$\approx 1006 \Omega$

\therefore This is minimum value required for $R_D.$

(20)

$$|A_v| = f_{m,} (r_{o1} // r_{o2}) = 10,$$

$$r_{o1} = \frac{1}{\lambda_1 I_1} = \frac{1}{0.1 \times 0.5 \times 10^{-3}}$$

$$= 20 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_1} = \frac{1}{0.15 \times 0.5 \times 10^{-3}}$$

$$= 13.3 \text{ k}\Omega$$

$$\therefore f_{m,} = \frac{10}{20 \text{ k} // 13.3 \text{ k}}$$

$$= 0.00138 \Omega^{-1}$$

$$\therefore f_{m,} = \sqrt{2 \beta_1 I_{D5}}$$

$$\beta_1 = 0.00192$$

$$200 \times 10^{-6} \left(\frac{W}{L}\right)_1 = 0.00192$$

$$\therefore \left(\frac{W}{L}\right)_1 \approx 9.6 //$$

$$b) \quad 0.5 \times 10^{-3} = \frac{1}{2} (100 \times 10^{-6}) (1.8 - V_B - 0.4)^2 \left(\frac{20}{0.18}\right)$$

$$\therefore V_B \approx 1.1 \text{ V} //$$

(21)

$$|A_v| = g_{m1} (r_{o1} \parallel r_{o2})$$

$$g_{m1} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{20}{0.18} \right) \times (0.001)}$$

(Since V_{ds1} is not given, assume
(if $\lambda_1 V_{ds1}$) has minimal effect on g_{m1})

$$= 6.67 \text{ mS.} \quad (S = \Omega^{-1})$$

$$\begin{aligned} r_{o1} &= \frac{1}{\lambda_1 \times I_{D1}} \\ &= \frac{1}{0.1 \times 1 \text{ mA}} \\ &= 10 \text{ k}\Omega. \end{aligned}$$

$$r_{o2} = \infty$$

$$(\because \lambda_2 \ll \lambda_1)$$

$$\therefore |A_v| = 6.67 \times 10^{-3} \times 10^3 \times 10$$

$$= 66.7 //$$

(22) a) $A_v = g_{m1} (r_{o1} \parallel r_{o2})$

When length of M_1 and M_2 double,
 r_o doubles ($\because r_o \propto L$)

$$r_{o1} \parallel r_{o2} = \frac{r_{o1} r_{o2}}{r_{o1} + r_{o2}}$$

$$\therefore (r_{o1} \parallel r_{o2}) \propto \frac{L^2}{L},$$

$$\text{i.e. } (r_{o1} \parallel r_{o2}) \propto L.$$

g_{m1} is constant because both
 $(\frac{W}{L})_{1,2}$ and I_{D3} are constant.

\therefore Voltage gain is doubled.

b) When both length and bias current double,
 r_o remains the same.

$$\therefore g_{m1} \propto \sqrt{I_{D3}}$$

\therefore Voltage gain increased by $\sqrt{2}$.

(23). To get higher voltage gain,

(a) is preferred.

For the same dimensions of transistors
and same bias current,

(a) has a high " g_m " than (b).

$$\therefore g_{m1} > g_{m2}$$

(since $\mu_n C_{ox} > \mu_p C_{ox}$)

while $(R_{o1} \parallel R_{o2})$ is the same
for both cases.

(24)

$$A_v = f_{m2} (r_{o1} // r_{o2})$$

$$r_{o1} = \frac{1}{0.15 \times 0.5 \text{ mA}}$$

$$= 13.3 \text{ k}\Omega.$$

$$r_{o2} = \frac{1}{0.05 \times 0.5 \text{ mA}}$$

$$= 40 \text{ k}\Omega.$$

$$\therefore r_{o1} // r_{o2} = 10 \text{ k}\Omega.$$

$$\therefore 15 = \left[\sqrt{2 \times (100 \times 10^{-6}) \left(\frac{W}{L} \right)_2 0.5 \text{ mA}} \right] \cdot (10 \text{ k}\Omega)$$

$$\left(\frac{W}{L} \right)_2 = 22.5 //$$

(25) From Eq (7.57),

$$3 = \sqrt{\frac{20/0.18}{(w/L)_2}}$$

$$\therefore (w/L)_2 \approx 12.3//.$$

(26)

a) For M_1 ,

$$0.5 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{10}{0.18} \right) (V_{GS1} - 0.4)^2$$

$$\therefore V_{GS1} = 0.7 \text{ V}$$

$$\begin{aligned} \therefore V_{DS1, \min} &= V_{GS1} - V_{TH} \\ &= 0.3 \text{ V} \end{aligned}$$

For M_2 ,

$$\begin{aligned} V_{S, \min} &= V_{DS1, \min} \\ &= 0.3 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{GS, \max} &= 1.8 - 0.3 \\ &= 1.5 \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore I_{OS2} &= \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L} \right)_2 (1.5 - 0.4)^2 \\ &= 0.5 \text{ mA} \end{aligned}$$

$$\left(\frac{W}{L} \right)_2 = 4.13 //$$

$$\begin{aligned} \text{b) volt. gain} &= - \sqrt{\frac{(W/L)_1}{(W/L)_2}} \\ &\approx \underline{\underline{3.67}} \end{aligned}$$

c) Because with M_1 at the edge of saturation, V_{GS} of M_2 is at maximum (V_S of M_2 is at minimum). Thus, a minimum (W/L) is required to set up the same bias current. With minimum (W/L), g_{m2} is at minimum. Since $A_v \propto \frac{1}{g_{m2}}$, A_v is at maximum.

$$(27) \quad a) \quad A_v = \sqrt{\frac{(w/L)_1}{(w/L)_2}}$$

$$1.5 = \sqrt{\frac{(w/L)_1}{(2/0.18)}}$$

$$\therefore (w/L)_1 \approx 277.8 //$$

b) For M_2 ,

$$I_{DS2} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{2}{0.18} \right) (1.8 - V_{S2} - 0.4)^2$$

$$I_{DS2} = (0.00111) (1.4 - V_{S2})^2$$

$$\therefore V_{S2} = \quad I_{DS2} = (0.00111) (1.4 - V_{DS1})^2$$

For M_1 ,

$$I_{DS1} = \frac{1}{2} (200 \times 10^{-6}) (277.8) (V_{GS1} - 0.4)^2$$

$$= 0.02778 (V_{GS1} - 0.4)^2$$

$$\therefore I_{DS1} = I_{DS2}$$

$$\therefore (0.02778) (V_{GS1} - 0.4)^2 = (0.00111) (1.4 - V_{DS1})^2$$

$$5 (V_{GS1} - 0.4) = (1.4 - V_{DS1})$$

At edge of saturation,

$$V_{DS1} = V_{GS1} - 0.4,$$

$$\text{Let } m = V_{DS1} = V_{GS1} - 0.4.$$

$$\therefore 5m = 1.4 - m$$

$$m = 0.233,$$


$$\begin{aligned}\therefore I_{DS1} &= 0.02778 (V_{GS1} - 0.4)^2 \\ &= I_{Bias}.\end{aligned}$$

$$\begin{aligned}\therefore I_{Bias} &= 0.02778 (0.233)^2 \\ &= 6.48 \text{ mA} //\end{aligned}$$

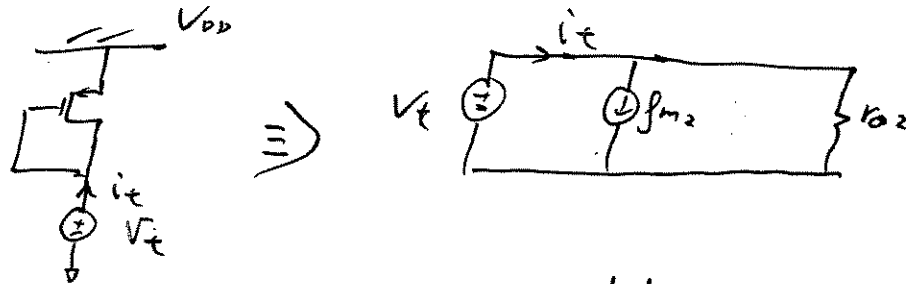(28) a/ $A_v = -g_{m1} r_{o1} \parallel Z_2$,

where Z_2 is the impedance presented by M_2 .

To find Z_2 , apply a test voltage (V_t) at the drain of M_2 :



From the small-signal model,

$$i_t = g_{m2} V_t + \frac{V_t}{r_{o2}}$$

$$Z_2 = \frac{V_t}{i_t} = r_{o2} \parallel \frac{1}{g_{m2}}$$

$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}})$$

b/ $A_v = -g_{m1} (r_{o1} \parallel Z_2 \parallel Z_3)$

where Z_2 and Z_3 are impedances presented by M_2 and M_3 respectively.

From (a) $Z_3 = r_{o3} \parallel \frac{1}{g_{m3}}$

By inspection, $Z_2 = r_{o2}$

$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

$$c) \quad A_v = -g_{m1} r_{o1} \parallel Z_2 \parallel Z_3$$

Similar to (b),

$$Z_2 = r_{o2},$$

$$\text{and } Z_3 = r_{o3} \parallel \frac{1}{g_{m3}}$$

(the small signal model of M_3 in this case is equivalent to that of M_2 in (a))

$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

d). M_2 is in CS arrangement. (similar to (c))

$$A_v = g_{m2} r_{o2} \parallel Z_1 \parallel Z_3$$

$$Z_3 = \frac{1}{g_{m3}} \parallel r_{o3}$$

$$Z_1 = r_{o1}$$

$$\therefore A_v = g_{m2} (r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{m3}} \parallel r_{o3})$$

$$e). \quad A_v = g_{m2} (r_{o2} \parallel Z_1 \parallel Z_3)$$

$$Z_1 = r_{o1}$$


$$Z_3 = \frac{1}{g_{m3}} \parallel r_{o3}$$

(recall: impedance looking into source = $\frac{1}{g_m}$)


$$\therefore A_v = g_{m2} (r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{m3}} \parallel r_{o3})$$

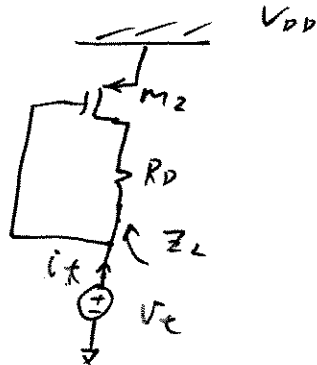(28) f) $A_v = -g_{m_1} (r_{o1} \parallel Z_L)$

Where Z_L is the impedance depicted as follows:



The equivalent small-signal model is:

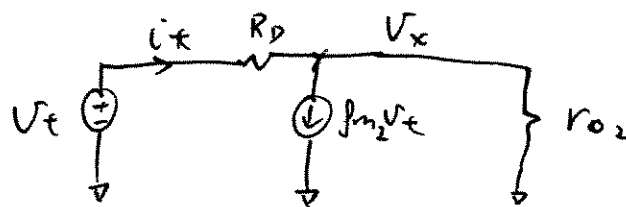

$$i_t = g_{m_2} V_t + \frac{V_x}{r_{o2}}$$

$$V_x = V_t - R_D i_t$$

$$\therefore i_t = g_{m_2} V_t + \frac{V_t}{r_{o2}} - \frac{R_D i_t}{r_{o2}}$$

$$i_t \left(1 + \frac{R_D}{r_{o2}}\right) = V_t \left(g_{m_2} + \frac{1}{r_{o2}}\right)$$

$$\frac{V_t}{i_t} = \frac{r_{o2} + R_D}{g_{m_2} r_{o2} + 1}$$

$$\therefore A_v = -g_{m_1} \left(r_{o1} \parallel \frac{r_{o2} + R_D}{1 + g_{m_2} r_{o2}} \right)$$

30 a) From Eq. (7.67)

$$|A_v| = \frac{R_D}{\frac{1}{g_m} + R_S},$$

$$4 = \frac{1000}{\frac{1}{g_m} + \frac{0.2V}{1mA}}$$

$$\frac{4}{g_m} + 800 = 1000$$

$$\therefore g_m = 20 \text{ mS.}$$

$$\therefore 20 \times 10^{-3} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1 \times 10^{-3})}$$

$$\therefore \frac{W}{L} = 1000 //$$

To check if M_1 is in saturation:

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= [1.8 - (10^{-3} \times 1k)] - 0.2 \\ &= 0.6 \text{ V} \end{aligned}$$

$$\text{and } 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) (1000) (V_{GS} - 0.4)^2$$

$$V_{GS} = 0.5$$

$$\therefore V_{DS} > V_{GS} - V_t,$$

ie. transistor is in operation.

$$b) \quad f_m = \sqrt{2 \times (200 \times 10^{-6}) \times \left(\frac{50}{0.18}\right) \times 10^{-3}}$$

$$\approx 10.5 \text{ mS}$$

$$|A_v| = \frac{R_D}{\frac{1}{f_m} + R_S}$$

$$4 = \frac{R_D}{\frac{1}{10.5 \times 10^{-3}} + 200}$$

$$\therefore R_D \approx 1179 \Omega$$

To check if M_1 is in saturation:

$$V_{DS} = [1.8 - (1179 \times 10^{-3})] - 0.2$$

$$= 0.421$$

$$\text{and } 10^{-3} = \frac{1}{2} (V_{GS} - 0.4)^2 (200 \times 10^{-6}) \left(\frac{50}{0.18}\right)$$


$$V_{GS} \approx 0.590$$

$$\therefore V_{DS} > V_{GS} - V_{th}$$

Transistor is in saturation.

(31)

The small signal model is:

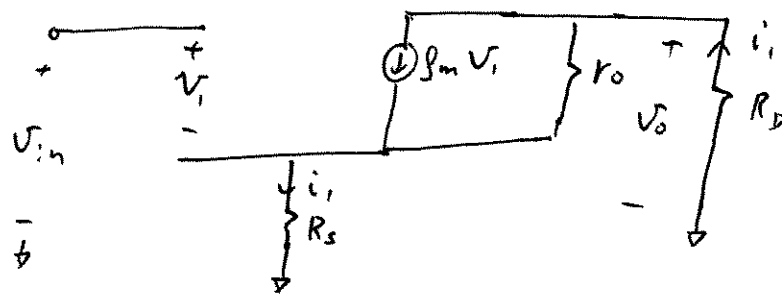

$$v_o = -i_c R_D \quad \text{--- (1)}$$

$$i_c = \beta_m v_i + \frac{v_o - v_i}{r_o}$$

$$= \frac{(\beta_m r_o - 1) v_i + v_o}{r_o}$$

$$i_c \approx \beta_m v_i + \frac{v_o}{r_o}$$

$$-\frac{v_o}{R_D} = \beta_m v_i + \frac{v_o}{r_o} \quad \text{--- (2)}$$

$$v_{in} = v_i + i_c R_s$$

$$\therefore v_i = v_{in} + \frac{v_o}{R_D} R_s \quad \text{--- (3)}$$

(2) combined with (3):


$$-\frac{v_o}{R_D} = \beta_m v_{in} + \beta_m v_o \frac{R_s}{R_D} + \frac{v_o}{r_o}$$

$$-v_o \left[\frac{1}{R_D} + \beta_m \frac{R_s}{R_D} + \frac{1}{r_o} \right] = \beta_m v_{in}$$

$$\therefore \text{Volt. gain} = \frac{v_o}{v_{in}} = - \left[\frac{\beta_m}{r_o + \beta_m R_s R_D + R_D} \right] (r_o R_D) //$$

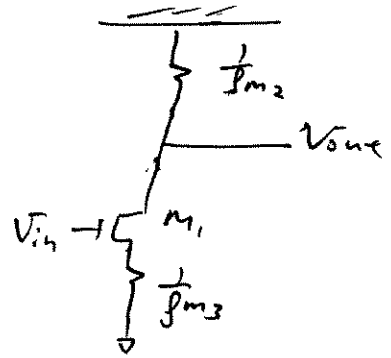32. a) Equivalent circuit is:

$$\therefore A_v = - \frac{\frac{1}{\beta_{m2}}}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m3}}}$$




b) Similar to Prob. 28(f),

Equivalent circuit is:

From Prob. 28(f),


$$Z_L = \frac{1}{\beta_{m2}} \quad (\text{as } r_{o2} \rightarrow \infty)$$
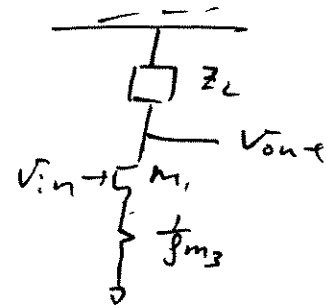
$$\therefore A_v = - \frac{\frac{1}{\beta_{m2}}}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m3}}}$$



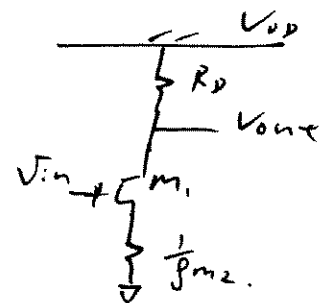
c) Equivalent circuit is:

$$\therefore A_v = - \frac{R_D}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m2}}}$$




(d). Equivalent circuit is
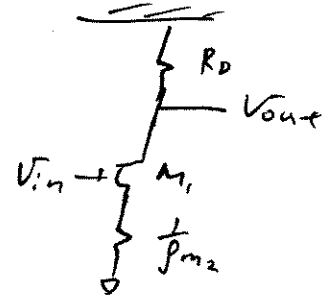
$$A_V = - \frac{R_D}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m2}}}$$



(e). Equivalent circuit is
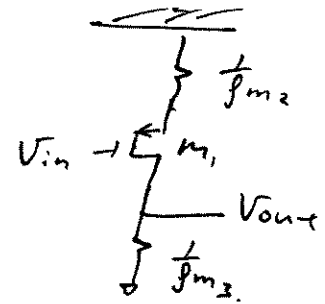
$$A_V = \frac{\frac{1}{\beta_{m3}}}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m2}}}$$



33

a) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left(\frac{1}{\beta_{m2}} + r_{o1} \right) //$$

b) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left(\frac{1}{\beta_{m2}} + r_{o1} \right) //$$

c) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m2} r_{o2}) (r_{o1} // \frac{1}{\beta_{m3}}) + r_{o2} //$$

d) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) (r_{o2} // \frac{1}{\beta_{m3}}) + r_{o1} //$$

34 To find $\left(\frac{W}{L}\right)$

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1 - 0.4)^2 \times (1 + 0.1 V_{DS})$$

$$\text{Where } V_{DS} = 1.8 - 1 \text{ k}\Omega \times 1 \text{ mA} \\ = 0.8 \text{ V}$$

$$\therefore \left(\frac{W}{L}\right) \approx 25.7 //$$

$$\text{Voltage gain, } (A_v) = -g_{m1} (r_{o1} // R_D)$$

$$g_{m1} = \sqrt{2(200 \times 10^{-6}) / (25.7 / \times 10^{-3} \times (1 + 0.1 \times 0.8))} \\ = 3.33 \text{ mS}$$

$$r_{o1} = \frac{1}{0.1 \times 10^{-3}} \\ = 10 \text{ k}\Omega$$

$$\therefore A_v = (-3.33 \times 10^{-3}) / (10 \text{ k}\Omega // 1 \text{ k}\Omega) \\ = -3.03 //$$

(35) With $\lambda = 0$,

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{w}{L} \right) (1 - 0.4)^2$$

$$\therefore \left(\frac{w}{L} \right) \approx 27.8 //$$


$$A_v = -g_m R_D$$

$$= -\sqrt{2(200 \times 10^{-6})(27.8) \times 10^{-3}} \times 1000$$

$$= -3.33 //$$

Without r_o , gain increases due mainly to increase in load resistance.

36 The small-signal circuit is:

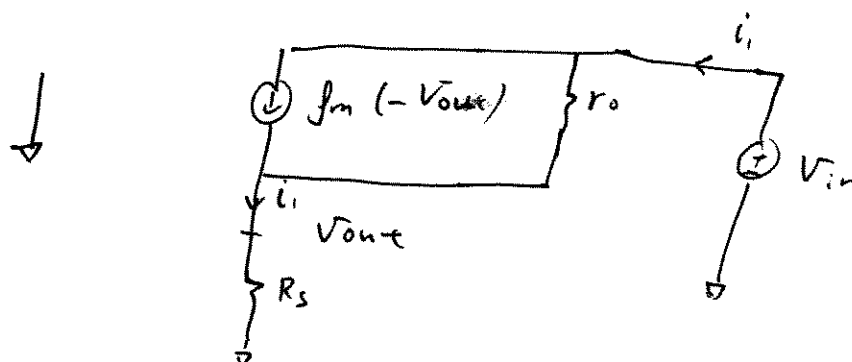

$$i_1 = \frac{V_{out}}{R_s} \quad \text{--- (1)}$$

$$i_1 = g_m(-V_{out}) + \frac{V_{in} - V_{out}}{r_o} \quad \text{--- (2)}$$

$$\therefore \frac{V_{out}}{R_s} = -g_m V_{out} + \frac{V_{in}}{r_o} - \frac{V_{out}}{r_o}$$

$$V_{out} \left(\frac{1}{R_s} + g_m + \frac{1}{r_o} \right) = \frac{V_{in}}{r_o}$$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{1}{r_o} \left(\frac{R_s r_o}{r_o + g_m r_o R_s + R_s} \right) \\ &= \frac{R_s}{g_m r_o R_s + r_o + R_s} \end{aligned}$$

Since $(g_m r_o R_s + r_o) > 0$, the voltage gain < 1 .

This is expected: Any variation in V_{in} causes minimal change in the bias current.

$\therefore V_{out}$ is determined largely by the amount of bias current ($\therefore V_{out}$ is set by V_{BS1})

\therefore There is almost no variation in V_{out} . (ie. $\frac{V_{out}}{V_{in}} \ll 1$)

37 a) $|Voltage\ gain| = g_m R_D$

$$= 5$$

$$\therefore g_m = \frac{5}{500}$$

$$= 10\text{ mS}$$

$$= \sqrt{2(200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \frac{W}{L} = 250 //$$

b) $V_D = 1.8 - 500 \times 10^{-3}$

$$= 1.3\text{ V}$$

To obtain $V_{DS} \geq V_{GS} - V_{TH} + 0.2$,

$$V_D \geq V_G - 0.2$$

$$\therefore V_G \leq 1.5$$

Also, $I_{R_1+R_2} = 0.1 \times 10^{-3}\text{ A}$

$$\therefore R_1 + R_2 = \frac{1.8}{0.1 \times 10^{-3}}$$

$$= 18\text{ k}\Omega$$

choose $R_2 = 15\text{ k}\Omega$ & $R_1 = 3\text{ k}\Omega$

c) With twice of (W/L) , M_1 will go further away from triode. As (W/L) doubles, & I_{bias} is fixed by the current source, V_{GS} is forced to decrease (so M_1 will have same I_{DS}). Thus, $(V_{GS} - V_{TH})$ decreases, and V_{DS} can be allowed to drop more before M_1 goes into triode.

Gain will be increased by $\sqrt{2}$, because $g_{m1} \propto \sqrt{I_{DS}}$, and $f_m \propto \sqrt{W/L}$.

38) a/ $V_G = 1.8V$.

$$\therefore V_{D, \min} = 1.8 - 0.4 \quad (\text{for } M_1 \text{ stays in saturation})$$

$$= 1.4V$$

$$\therefore R_{D, \max} = \frac{1.4V}{1mA}$$

$$= 1.4k\Omega //$$

b/ $|Voltage\ gain| = g_m R_D$

$$= 5.$$

$$\therefore g_m = \frac{5}{R_D}$$

$$= 3.57mS.$$

$$= \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) = 31.9 //$$

③ To get $R_{in} = 50\Omega$,

$$\frac{1}{f_m} = 50\Omega$$

$$\therefore f_m = 20\text{ms}$$

$$\text{voltage gain (A}_v\text{)} = f_m R_D$$

$$= 4,$$

$$\therefore R_D = \frac{4}{0.02}$$

$$R_D = 200\Omega //$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 0.5 \times 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) = 2000 //$$

④ To get $R_{in} = 50 \Omega$,

$$f_m = \frac{1}{50}$$
$$= 20 \text{ ms}$$

Voltage gain $(A_v) = f_m R_D$

$$f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L} \right) \times 0.5 \times 10^{-3}}$$

$$\therefore \frac{W}{L} = 2000$$

$$\therefore V_G = V_E = 1 \text{ V},$$

$$V_{D, \min} = V_G - V_{TH}$$
$$= 0.6 \text{ V}$$

$$\therefore R_{D, \max} = \frac{1.8 - 0.6}{0.5 \times 10^{-3}}$$


$$= 2400$$

$$\therefore \text{max. Voltage gain} = 0.02 \times 2400$$

$$= 48 //$$


④ Voltage gain (A_v) = $G_m R_{out}$,
 where G_m and R_{out} are the transconductance
 and output resistance of the circuit respectively.

To find G_m :

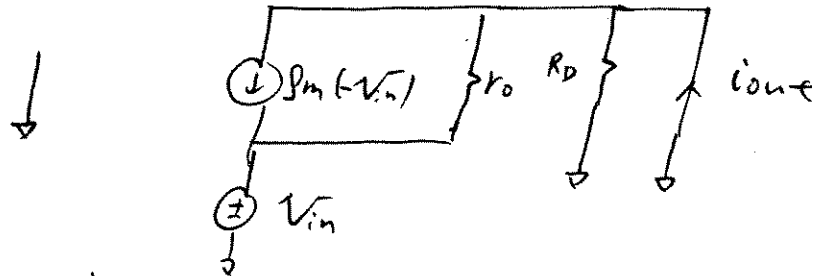

$$G_m = \frac{i_{out}}{V_{in}} = g_m + \frac{1}{r_o} \\ \approx g_m \quad (\because g_m r_o \gg 1)$$

To find R_{out} :

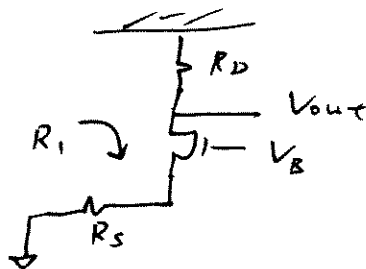

$$R_{out} = R_D \parallel R_1 \\ = R_D \parallel [(1 + g_m r_o) R_S + r_o] \\ \text{(from Eq. (7.110))} \\ \approx R_D \parallel (g_m r_o R_S + r_o) \quad (\because g_m r_o \gg 1) \\ = \frac{g_m r_o R_S R_D + r_o R_D}{R_D + g_m r_o R_S + r_o}$$

$$\therefore \text{Voltage gain} = \beta_m \left[\frac{\beta_m r_o R_D R_S + r_o R_D}{R_D + \beta_m r_o R_S + r_o} \right]$$

(42) a) To get $R_{in} = 50 \Omega$,

$$f_m = \frac{1}{50} \\ = 20 \text{ mS.}$$

To get $R_{out} = 500 \Omega$,

$$R_D = 500 \Omega \quad (\because R_o = \infty)$$

$$\therefore V_{D, \min} = 1.8 - 0.4 = 1.4 \text{ V}$$

$$\therefore I_{D, \max} = \frac{1.8 - 1.4}{500}$$

$$= 0.8 \text{ mA} //$$

$$b) \quad f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L} \right) \times 0.8 \times 10^{-3}}$$

$$\therefore \left(\frac{W}{L} \right) = 1250 //$$

$$c) \quad \text{Voltage gain} = 0.02 \times 500$$

$$= 10 //$$

43 a) To place M_1 100mV away from triode,

$$V_{D,min} = V_G - V_{TH} + 0.1V$$
$$= 1.5V.$$

$$\therefore R_D = \frac{(1.8 - 1.5)V}{1mA}$$
$$= 300\Omega //$$

b/ Voltage gain $= g_m R_D$

$$\therefore g_m = \frac{5}{300}$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) \approx 694 //$$

44 a/ Voltage gain (A_v) = $\left[\frac{\frac{1}{\beta_{m1}}}{R_s + \frac{1}{\beta_{m1}}} \right] \frac{\beta_{m1}}{\beta_{m2}}$
 $= \frac{\beta_{m1} \cancel{\beta_{m2}}}{1 + \beta_{m1} R_s}$

b/ Voltage gain (A_v) = $\beta_{m1} Z_L$
 (similar to prob. 32(b))
 $= \frac{\beta_{m1}}{\beta_{m2}}$

c/ Voltage gain = $\left[\frac{\frac{1}{\beta_{m1}} \parallel R_i}{R_s + \frac{1}{\beta_{m1}} \parallel R_i} \right] \frac{\beta_{m1}}{\beta_{m2}}$

d/ Voltage gain = $\beta_{m1} [R_D + r_{o3} \parallel \frac{1}{\beta_{m2}}]$

$\therefore r_{o3} = \infty$

gain = $\beta_{m1} [R_D + \frac{1}{\beta_{m2}}]$

e/ Voltage gain = $\beta_{m1} [R_D + \frac{1}{\beta_{m2}}]$

$$(45) \quad a) \quad \frac{V_x}{V_{in}} = -\beta_{m1} \left[R_{D1} \parallel \frac{1}{\beta_{m2}} \right]$$

$$\frac{V_{out}}{V_x} = \beta_{m2} R_{D2}$$

$$\therefore \frac{V_{out}}{V_{in}} = -(\beta_{m2} R_{D2}) \left[\beta_{m1} (R_{D1} \parallel \frac{1}{\beta_{m2}}) \right] //$$

b) if $R_{D1} \rightarrow \infty$,

$$\frac{V_{out}}{V_{in}} = (-\beta_{m2} R_{D2}) \left(\frac{\beta_{m1}}{\beta_{m2}} \right)$$

$$= -\beta_{m1} R_{D2} //$$

This is expected, because the circuit reduces to a cascode stage.

(\therefore gain is the same as that of a cascode stage.)

$$(46) \quad \frac{V_x}{V_{in}} = (R_{D1} \parallel \frac{1}{g_{m2}}) g_{m1}$$


$$\frac{V_{out}}{V_x} = g_{m2} R_{D2}$$

$$\therefore \frac{V_{out}}{V_{in}} = g_{m1} g_{m2} R_{D2} (R_{D1} \parallel \frac{1}{g_{m2}})$$

Similar to prob. (45), voltage gain approaches that of cascode stage as R_{D1} approaches infinity. The gain is $g_{m1} R_{D2}$.

(47) With $\lambda = 0$, M_1 appears as a diode-connected device.

\therefore the circuit becomes :

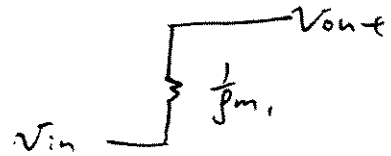


ie. $\frac{v_{out}}{v_{in}} = 1 //$

This is not a common-gate amplifier, (CG)
because the gate is not fixed. (ie. gate is not at an "a.c. ground").

(48)

The small-signal model is :

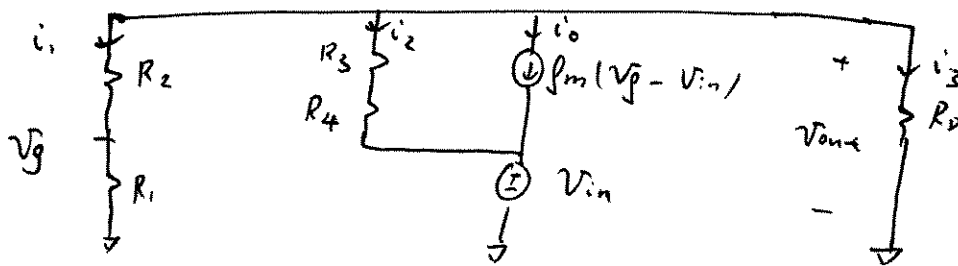

$$\therefore -i_0 = i_1 + i_2 + i_3$$

$$-g_m (V_g - V_{in}) = \frac{V_{out}}{R_2 + R_1} + \frac{V_{out} - V_{in}}{R_3 + R_4} + \frac{V_{out}}{R_D}$$

$$g_m (V_{in} - \frac{R_1}{R_1 + R_2} V_{out}) = V_{out} \left(\frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4} + \frac{1}{R_D} \right) - \frac{V_{in}}{R_3 + R_4}$$

$$V_{in} \left(g_m + \frac{1}{R_3 + R_4} \right) = V_{out} \left(\frac{g_m R_1 + 1}{R_1 + R_2} + \frac{1}{R_3 + R_4} + \frac{1}{R_D} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{\left(g_m + \frac{1}{R_3 + R_4} \right)}{\frac{1}{R_D} + \frac{1}{R_3 + R_4} + \frac{g_m R_1 + 1}{R_1 + R_2}}$$

(49)

$$\text{Voltage gain } (A_v) = \frac{r_o // R_s}{\frac{1}{g_m} + r_o // R_s}$$

To find I_{DS} ,

$$\begin{aligned} I_{DS} &= \frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18} \right) (1.8 - V_s - 0.4)^2 \\ &= 0.0111 (1.4 - I_{DS} \times 1000)^2 \end{aligned}$$

$$11100 I_{DS}^2 - 32.08 I_{DS} + 0.021756 = 0$$

$$\therefore I_{DS} = 1.80 \text{ mA or } 1.08 \text{ mA.}$$

Reject $I_{DS} = 1.80 \text{ mA.}$

$$(\because V_s = 1.80 \text{ V} > V_{DD})$$

$$\begin{aligned} \therefore g_m &= \sqrt{2 \times (200 \times 10^{-6}) \times 1.08 \times 10^{-3}} \\ & \text{(ignore channel-length modulation)} \end{aligned}$$

$$g_m = 0.659 \text{ ms}$$

$$r_o = \frac{1}{0.1 \times 1.08 \times 10^{-3}} \approx 9260 \Omega$$

$$\therefore A_v = \frac{9260 \Omega // 1000 \Omega}{\frac{1}{0.659 \text{ ms}} + 9260 \Omega // 1000 \Omega}$$

$$\approx 0.372 //$$

(50)

$$A_v = \frac{R}{\frac{1}{g_m} + R}$$

$$\approx 0.8$$

$$\therefore 0.8 = \frac{500}{\frac{1}{g_m} + 500}$$

$$\frac{0.8}{g_m} + 400 = 500$$

$$\therefore g_m = 8 \text{ mS}$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \times \left(\frac{30}{0.18}\right) I_{DS}}$$

$$\therefore I_{DS} = 0.86 \text{ mA}$$

$$\therefore V_S = 0.86 \times 10^{-3} \times 500$$
$$= 480 \text{ mV}$$

To find V_G :

$$0.86 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) / \left(\frac{30}{0.18}\right) (V_G - 0.48 - 0.4)^2$$

$$\therefore V_G = 1.12 \text{ V}$$

(51)

$$A_v = \frac{R_s}{\frac{1}{g_m} + R_s}$$
$$= 0.8$$

$$0.8 = \frac{500}{\frac{1}{g_m} + 500}$$

$$\therefore g_m = 8 \text{ mS.}$$

$$\therefore I_{ds} = \frac{1}{2} \beta (V_{gs} - V_t)^2,$$

$$\text{where } \beta = \left(\frac{w}{L}\right) \mu_n C_{ox}$$

$$\text{and } g_m = \beta (V_{gs} - V_t).$$

$$\therefore I_{ds} = \frac{1}{2} g_m (V_{gs} - V_t)$$

$$= \frac{1}{2} g_m (1.8 - I_{ds}(500) - 0.4)$$

$$I_{ds} = 4 \times 10^{-3} (1.4 - 500 I_{ds})$$

$$\therefore I_{ds} = 1.87 \text{ mA.}$$

$$\therefore g_m = \sqrt{2(200 \times 10^{-6}) \frac{w}{L} \times 1.87 \times 10^{-3}}$$

$$\therefore \frac{w}{L} \approx 85.7 //$$

52. To get $R_{out} = 100 \Omega$,

$$\frac{1}{g_m} = 100$$

$$\therefore g_m = 10 \text{ mS.}$$

$$\therefore I_{ds} = \frac{1}{2} \beta (V_{gs} - V_{th})^2$$

$$\text{where } \beta = \mu_n C_{ox} \frac{W}{L}$$

$$\text{and } g_m = \beta (V_{gs} - V_{th})$$

$$\begin{aligned} \therefore I_{ds} &= \frac{1}{2} g_m (V_{gs} - V_{th}) \\ &= \frac{1}{2} (10 \times 10^{-3}) (0.8 - 0.4) \end{aligned}$$

$$\therefore I_{ds} = 2.5 \text{ mA.}$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) (2.5 \times 10^{-3})}$$

$$\therefore \left(\frac{W}{L}\right) = 100 //$$

(53) To get $R_{out} = 50 \Omega$,

$$\frac{1}{g_m} = 50 \Omega$$

$$\therefore g_m = 20 \text{ mS},$$

$$\begin{aligned} \text{Power (P)} &= 1.8 \times I_{Ds} \\ &= 2 \times 10^{-3} \text{ W.} \end{aligned}$$

$$\therefore I_{Ds} = 1.11 \text{ mA}.$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L} \right) (1.11 \text{ mA})}$$

$$\therefore \frac{W}{L} = 900 //$$

(54)

$$A_v = \frac{R_L}{\frac{1}{\beta_m} + R_L}$$

$$\therefore 0.8 = \frac{50}{\frac{1}{\beta_m} + 50}$$

$$\beta_m = 80 \text{ mS}$$

$$\begin{aligned} \text{Power (P)} &= 1.8 \times I_{DS} \\ &= 3 \text{ mW} \end{aligned}$$

$$\therefore I_{DS} = 1.67 \text{ mA}$$

$$\beta_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{\text{W}}{\text{cm}^2}\right) (1.67 \times 10^{-3})}$$


$$\therefore \left(\frac{\text{W}}{\text{cm}^2}\right) = 9600 //$$

(55)

$$a) A_v = \frac{r_{o1} \parallel (R_s + r_{o2})}{\frac{1}{g_{m1}} + r_{o1} \parallel (R_s + r_{o2})}$$

$$b) A_v = \frac{r_{o1} \parallel R_L}{\frac{1}{g_{m1}} + (r_{o1} \parallel R_L)}$$

where R_L is :

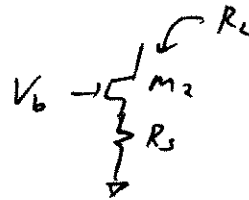


$$R_L = (1 + g_{m2} r_{o2}) R_s + r_{o2} \quad \text{Eq. (7.110)}$$

$$\therefore A_v = \frac{r_{o1} \parallel [(1 + g_{m2} r_{o2}) R_s + r_{o2}]}{\frac{1}{g_{m1}} + r_{o1} \parallel [(1 + g_{m2} r_{o2}) R_s + r_{o2}]}$$


$$c) A_v = \frac{r_{o1} \parallel \frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + (r_{o1} \parallel \frac{1}{g_{m2}})}$$

$$d) A_v = \frac{r_{o1} \parallel R_L}{\frac{1}{g_{m1}} + (r_{o1} \parallel R_L)}$$

where R_L is :

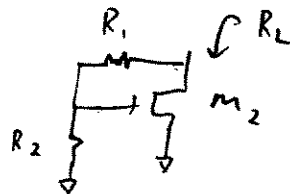

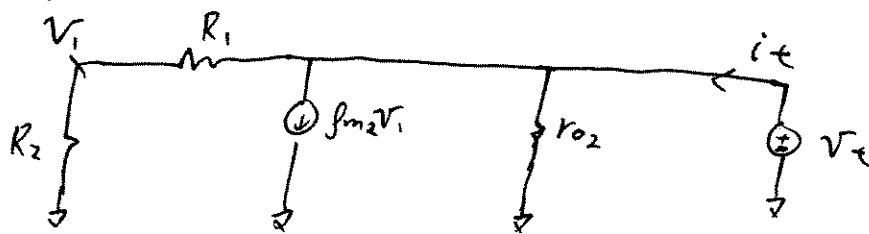(c) Finding R_L with small-signal model:
(cont'd)



$$R_L = \frac{V_x}{i_x}$$

$$\text{where } i_x = \frac{V_x}{r_{o2}} + g_{m2} V_i + \frac{V_x}{R_1 + R_2}$$

$$= \frac{V_x}{r_{o2}} + \frac{g_{m2} R_2 V_x}{R_1 + R_2} + \frac{V_x}{R_1 + R_2}$$

$$\therefore R_L = \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + g_{m2} r_{o2} R_2}$$

$$\therefore A_v = \frac{r_{o1} \parallel \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + g_{m2} r_{o2} R_2}}{\frac{1}{g_{m1}} + r_{o1} \parallel \frac{r_{o2} (R_2 + R_1)}{R_2 + R_1 + r_{o2} + g_{m2} r_{o2} R_2}}$$

$$e) \quad A_v = \frac{r_{o2} \parallel (\frac{1}{g_{m1}} \parallel r_{o3})}{\frac{1}{g_{m2}} + r_{o2} (\frac{1}{g_{m1}} \parallel r_{o3})}$$

$$f) \quad A_v = \frac{r_{o1} \parallel [(1 + g_{m2} r_{o2}) r_{o3} + r_{o2}]}{\frac{1}{g_{m1}} + \{r_{o1} \parallel [(1 + g_{m2} r_{o2}) r_{o3} + r_{o2}]\}}$$

$$(56) \quad \frac{V_x}{V_{in}} = \frac{g_{m2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\frac{V_{out}}{V_x} = g_{m2} R_D$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

b) if $g_{m1} = g_{m2}$,

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} R_D}{2}$$

(57)

$$\therefore R_{out} = 1k\Omega$$

$$\therefore R_D = 1k\Omega$$

$$\begin{aligned}\therefore A_v &= 5 \\ &= g_{m1} R_D\end{aligned}$$

$$\therefore g_{m1} (1000) = 5$$

$$g_{m1} = 5mS$$

$\therefore M_1$ is 00 mV away from triode,

$$V_D = (V_G - V_{TH}) + 0.1$$

$$V_D = (1.8 - 0.4) + 0.1$$

$$V_D = 1.5V$$

$$\therefore I_{DS} = \frac{1.8 - 1.5}{R_D} = \frac{0.3}{R_D}$$

$$= 0.3mA$$

$$\therefore g_{m1} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) I_{DS}}$$

$$\therefore \left(\frac{W}{L}\right) \approx 208$$

$$\therefore R_D = 1k\Omega, R_G = 10k\Omega, \left(\frac{W}{L}\right) = 208$$

$$(58) \therefore \text{Power (P)} = 2 \text{ mW},$$

$$\therefore I_{DS} = \frac{2 \times 10^{-3}}{1.8}$$

$$= 1.11 \text{ mA}.$$

$$\therefore R_D I = 1$$

$$\therefore R_D = 900 \Omega.$$

$$\therefore | \text{gain (Av)} | = 5,$$

$$f_m R_D = 5$$

$$f_m = 5.56 \text{ ms}.$$

$$\therefore f_m = \sqrt{2(200 \times 10^{-6}) \left(\frac{\omega}{L} \right) (1.11 \times 10^{-3})}$$

$$\frac{\omega}{L} \approx 69.4 //$$

(59) $|A_v| = g_m R_L$.

∴ To achieve maximum gain, use maximum R_L

i.e. set $R_D = 500 \Omega$.

For maximum g_m , use maximum I_{D_S} .

(... while keeping M_1 in saturation),

i.e. $V_D \geq V_G - V_{TH}$

$$1.8 - (I_{D_S})(500) \geq 1.8 - 0.4$$

$$\therefore I_{D_S} \leq \frac{0.4}{500}$$

$$I_{D_S, \max} = 0.8 \text{ mA}$$

Note: Setting a large R_D in this case would force $I_{D_S, \max}$ to be lower (in order to keep M_1 in saturation).

But since $A_v \propto R_D$, while $A_v \propto \sqrt{I_{D_S}}$, sacrificing I_{D_S} to get higher R_D would yield a higher gain.

60 \therefore Power (P) = 2 mW,

$$\therefore I_{DS} = (0.95) \left(\frac{2 \times 10^{-3}}{1.8} \right)$$

(assuming $(R_1 + R_2)$ consumes 5% of total power)

$$I_{DS} = 1.06 \text{ mA}$$

$$\therefore R_S = \frac{0.2 \text{ V}}{1.06 \text{ mA}}$$

$$\approx 189 \Omega$$

$$\therefore g_m = \beta V_{eff}$$

(where $\beta = \mu_n C_{ox} \left(\frac{W}{L} \right)$, $V_{eff} = V_{GS} - V_{TH}$)

and $I_{DS} = \frac{1}{2} \beta V_{eff}^2$

$$\therefore I_{DS} = \frac{1}{2} g_m V_{eff}$$

Set $V_{eff} = 0.1 \text{ V}$ (< maximum allowable overdrive)

$$1.06 \times 10^{-3} = \frac{1}{2} g_m (0.1)$$

$$g_m = 21.2 \text{ mS}$$

$$\therefore |A_v| = \frac{g_m R_D}{1 + g_m R_S} = 4$$

$$\therefore \frac{21.2 \times 10^{-3} \times R_D}{1 + (21.2 \times 10^{-3}) \times 189} = 4$$

$$R_D \approx 147 \Omega$$

With $V_{GS} - V_{TH} = 0.1V$,

$$V_{GS} = 0.1 + 0.4V$$

$$= 0.5V$$

$$= V_G - V_S$$

$$\therefore V_G - 0.2V = 0.5V$$

$$\therefore V_G = 0.7V$$

To find R_1 & R_2 ,

$$\therefore I_{R_1+R_2} = (0.05) \left(\frac{2 \times 10^{-3}}{1.8} \right)$$

$$= 5.56 \times 10^{-5} A$$

$$\therefore R_1 + R_2 = \frac{1.8V}{5.56 \times 10^{-5} A}$$

$$= 32.4 k\Omega$$

$$V_G = \frac{R_2}{R_1 + R_2} \times 1.8 = 0.7V$$

$$\therefore R_2 = 12.6 k\Omega$$

$$R_1 = (32.4 - 12.6) k\Omega = 19.8 k\Omega$$

To find $(\frac{W}{L})_1$,

$$f_m = \sqrt{2 \times 200 \times 10^{-6} \times (\frac{W}{L})_1 \times 1.06 \times 10^{-3}} = 21.2 ms$$

$$\therefore (\frac{W}{L})_1 = 1060$$

$$\therefore R_1 = 19.8 k, R_2 = 12.6 k, R_S = 189 \Omega, R_D = 947 \Omega$$

$$(\frac{W}{L})_1 = 1060, I_{DS} = 1.06 mA$$

(61)

$$\text{Power (P)} = 6 \text{ mW}$$

$$\therefore I_{DS} = (0.95) \left(\frac{6 \times 10^{-3}}{1.8} \right) = 3.17 \text{ mA}$$

$$A_{v1} = 5,$$

$$\therefore \frac{g_m R_D}{1 + g_m R_S} = 5$$

$$5 = (R_D - 5 R_S) g_m$$

for g_m to be positive,

$$R_D > 5 R_S, \text{ i.e. } R_S < 50 \Omega$$

$$\text{choose } R_S = 30 \Omega$$

$$\therefore V_{ov} \text{ (over drive voltage)} = V_{R_S}$$

$$\therefore V_{ov} = 3.17 \times 10^{-3} \times 30$$
$$= 95.1 \text{ mV}$$

$$\text{From } A_v = \frac{g_m R_D}{1 + g_m R_S} = 5,$$

$$g_m = 100 \text{ mS}$$

$$\therefore g_m = \mu_n C_{ox} / \left(\frac{W}{L} \right) V_{ov}$$

$$\therefore \left(\frac{W}{L} \right) \approx 5260$$

To find R_1 and R_2 ,

$$I_{R_1 + R_2} = (0.05) \left(\frac{6 \times 10^{-3}}{1.8} \right) = 0.167 \text{ mA}$$

$$\therefore R_1 + R_2 = \frac{1.8}{0.167 \times 10^{-3}} = 10.8 \text{ k}\Omega$$

$$\therefore V_{GS} - V_{TH1} = V_{OV} = 85.1 \text{ mV},$$

$$\text{and } V_S = 85.1 \text{ mV},$$

$$\therefore (V_G - 85.1 \text{ mV}) - 0.4 = 85.1 \text{ mV}$$

$$V_G = 0.5902$$

$$\therefore V_G = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$\therefore R_2 = 3.54 \text{ k}\Omega$$

$$\begin{aligned} \text{and } R_1 &= 10.8 \text{ k}\Omega - 3.54 \text{ k}\Omega \\ &= 7.26 \text{ k}\Omega \end{aligned}$$

$$\therefore R_1 = 7.26 \text{ k}\Omega, \quad R_2 = 3.54 \text{ k}\Omega, \quad R_S = 30 \Omega$$

$$\left(\frac{W}{L}\right) = 5260 \quad I_{DS} = 3.17 \text{ mA}.$$

(62) Power $(P) = 2 \text{ mW}$,

$$\therefore I_{DS} = \frac{2 \text{ mW}}{1.8 \text{ V}}$$

$$= 1.11 \text{ mA}$$

$\therefore M_1$ operates 200 mV away from Triode

$$V_{DS} = (V_{GS} - V_{TH}) + 0.2$$

$$\therefore V_D = 1.6 \text{ V}$$

$$R_D = \frac{V_{RD}}{I_{DS}} = \frac{(1.8 - 1.6) \text{ V}}{1.11 \times 10^{-3} \text{ A}}$$

$$= 180 \Omega$$

$$\therefore \text{Gain (Av)} = \frac{g_m R_D}{1 + g_m R_S} = 6$$

$$\therefore 6 = (R_D - 6 R_S) g_m$$

for $g_m > 0$, $R_D - R_S > 0$, i.e. $R_S < 30 \Omega$.

Set $R_S = 20 \Omega$,

$$g_m = \frac{6}{180 - 6 \times 20} = 100 \text{ mS}$$

$$\therefore g_m = (\mu_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - V_{TH})$$

$$0.1 = 200 \times 10^{-6} \left(\frac{W}{L} \right) (1.8 - 1.11 \times 10^{-3} \times 20 - 0.4)$$

$$\therefore \frac{W}{L} \approx 363$$

$$R_{in} = \frac{1}{sC_1} + R_1$$

$\therefore \frac{1}{sC_1}$ is negligible,

$$R_{in} = R_1 = 20 \text{ k}\Omega$$

To make $\frac{1}{sC_1}$ negligible,

$$\frac{1}{sC_1} \ll R_1$$

$$\frac{1}{2\pi(10^6)C_1} \ll$$

$$\therefore C_1 \ll 7.96 \text{ pF}$$

$$\text{Set } C_1 = 0.796 \text{ pF}$$

To make $\frac{1}{sC_s}$ negligible,

$$\frac{1}{sC_s} \ll R_s \parallel \frac{1}{g_m}$$

$$\frac{1}{2\pi(10^6)C_s} \ll 20 \parallel \frac{1}{100 \text{ ms}}$$

$$C_s \ll 23.9 \text{ nF}$$

$$\text{Set } C_s = 2.39 \text{ nF}$$

$$\therefore R_D = 180 \Omega, R_s = 20 \Omega, R_1 = 20 \text{ k}\Omega, \frac{W}{L} = 363$$

$$C_1 = 0.796 \text{ pF}, C_s = 2.39 \text{ nF}$$

63. Power $(P) = 2 \text{ mW}$,

$$\therefore I_{DS1} = |I_{DS2}| = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA}.$$

$$\begin{aligned} r_{o1} = r_{o2} &= \frac{1}{\lambda I_{DS}} \\ &= \frac{1}{0.1 \times 1.11 \times 10^{-3}} \\ &= 9000 \, \Omega. \end{aligned}$$

$$f_{\text{ain}} (A_v) = g_{m1} (r_{o1} \parallel r_{o2}) = 20,$$

$$g_{m1} \left(\frac{9000}{2} \right) = 20.$$

$$\therefore g_{m1} = 4.44 \text{ mS}.$$

$$\text{Set } V_{DS1} \text{ (ie. } V_{out}) = 1.2 \text{ V}$$

$$(\text{which is } < 1.5 \text{ V})$$

$$\therefore V_{IN} = V_{GS1} \leq 1.2 + V_{TH1}$$

$$(\text{for } M_1 \text{ to stay in saturation})$$

$$\text{Set } V_{GS1} = 1.2 \text{ V}$$

$$\therefore g_{m1} = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TH1})$$

$$\left(\frac{W}{L} \right)_1 = 27.75$$

$$\text{For } M_2, \therefore M_2 \text{ must be in saturation}$$

$$\text{for } V_{out} \leq 1.5 \text{ V}.$$

$$\therefore V_{DD} - V_B \leq V_{DD} - 1.5 \text{ V} + V_{TH1}$$

$$\therefore V_B \geq 1.1 \text{ V}$$

Set $V_B = 1.2V$

$$|I_{DS2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (|V_{GS2}| - V_{TH})^2 (1 + \lambda |V_{DS2}|)$$

$$1.11 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L} \right)_2 (0.6 - 0.2)^2 (1 + 0.1 \times (1.8 - 1.5))$$

(assuming $V_{out} = 1.5V$)

$$\therefore \left(\frac{W}{L} \right)_2 \approx 135$$


$$\therefore \left(\frac{W}{L} \right)_1 = 27.75 \quad \left(\frac{W}{L} \right)_2 = 135$$

$$V_{IN} = 1.2 \quad V_b = 1.1$$


$$I_{DS1} = I_{DS2} = 1.11 \text{ mA}$$

64 a) gain $(A_v) = -g_{m1} r_{o1} \parallel R_L$,

Where R_L is:

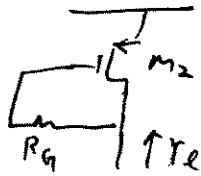

The small-signal model is:

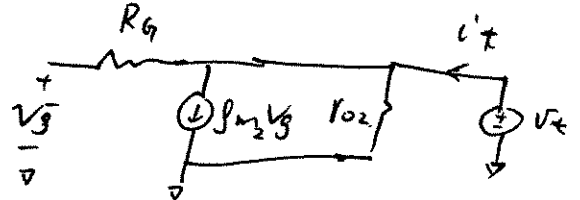

$$R_L = \frac{V_e}{i_e} = r_{o2} \parallel \frac{1}{g_{m2}}$$

$$\therefore A_v = -g_{m1} r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

b) Power = 3mW

$$\therefore I_{D1} = |I_{D2}| = \frac{3\text{mW}}{1.8\text{V}}$$

$$= 1.67\text{mA}$$

$$V_{OUT} = V_{G2} = \frac{V_{DD}}{2}$$

$$\therefore V_{GS2} = -0.9\text{V}$$

$$I_{D2} = \frac{1}{2} (100 \times 10^{-6}) \left(\frac{W}{L}\right)_2 \times (1 - 0.9 - V_{TH})^2$$

$$\times (1 + 0.1 \times \frac{V_{DD}}{2})$$

$$\therefore \left(\frac{W}{L}\right)_2 \approx 122$$

$$f_{m2} = \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TH})$$

$$= 6.1 \text{ ms.}$$

$$\text{From (a), } |A_v| = \frac{1}{f_{m1}} \times (r_{o1} // r_{o2} // \frac{1}{f_{m2}})$$

$$\therefore r_{o1} = \frac{1}{0.1 \times 1.67 \times 10^{-3}} = 6000 \Omega$$

$$r_{o2} = \frac{1}{0.2 \times 1.67 \times 10^{-3}} = 3000 \Omega$$

$$\therefore 15 = f_{m1} \left(6000 // 3000 // \frac{1}{6.1 \text{ ms}} \right)$$

$$f_{m1} = 99 \text{ ms}$$

$$f_{m1} = \sqrt{2 \left(\frac{W}{L} \right)_1 \mu_n C_{ox} I_{DS1}}$$

$$\therefore \left(\frac{W}{L} \right)_1 = 14672$$

$$\therefore \left(\frac{W}{L} \right)_1 = 14672, \left(\frac{W}{L} \right)_2 = 122, I_{DS1} = |I_{DS2}| = 1.67 \text{ mA}$$

$$\begin{aligned}
 \textcircled{65} \text{ a) Impedance looking into drain of } M_2 \\
 &= (1 + g_{m2} r_{o2}) R_s + r_{o2} \\
 &\approx 10 r_{o1}
 \end{aligned}$$

$$\text{Assume } g_{m2} r_{o2} \gg 1,$$

$$\therefore g_{m2} r_{o2} R_s + r_{o2} \approx 10 r_{o1}$$

$$\therefore r_{o1} = r_{o2} \quad (\lambda_1 = \lambda_2 \text{ and } |I_{D1}| = |I_{D2}|)$$

$$\begin{aligned}
 \therefore g_{m2} R_s + 1 &= 10 \\
 g_{m2} R_s &= 9 \quad \text{--- (1)}
 \end{aligned}$$

$$\text{Given } V_B = 1V,$$

$$\text{Set } |V_{GS2}| = 0.6V, \quad (\text{ie. } V_{GS2} - V_{TH} = 0.2V)$$

$$\therefore V_{S2} = 1.6V,$$

$$\therefore V_{RS} = 1.8V - 1.6V = 0.2V$$

$$\therefore \text{Power} = 2mW$$

$$I_{D1} = |I_{D2}| = \frac{2mW}{1.8V} = 1.11mA$$

$$\therefore R_s = \frac{V_{RS}}{1.11 \times 10^{-3}} \approx 180\Omega //$$

$$\text{From (1), } g_{m2} = \frac{9}{180} = 50 \text{ mS.}$$

$$\therefore g_{m2} = \left(\frac{W}{L}\right)_2 (100 \times 10^{-6}) (V_{GS2} - V_{TH})$$

$$\therefore \left(\frac{W}{L}\right)_2 = 2500 //$$

$$b/. \text{ gain } (A_v) = g_{m1} (r_{o1} // 10r_{o1})$$

$$30 = g_{m1} (0.909 r_{o1})$$

$$r_{o1} = \frac{1}{0.1 \times 1.1 \times 10^{-3}}$$

$$= 9009 \Omega$$

$$\therefore g_{m1} = 3.66 \text{ mS}$$

$$\therefore g_{m1} = \sqrt{2(\mu_n C_{ox}) \left(\frac{W}{L}\right)_1 \times I_{D1}}$$

$$\therefore \left(\frac{W}{L}\right)_1 \approx 30.2 //$$

⑥⑥. Power = 1 mW

$$\therefore I_{DS1} = I_{DS2} = \frac{1 \text{ mW}}{1.8 \text{ V}} = 0.556 \text{ mA.}$$

$$\text{Volt. gain (A}_v\text{)} = -\frac{g_{m1}}{g_{m2}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$= -4$$

$$\text{See } V_{GS1} = V_{GS2} = \frac{V_{DD}}{3}$$

$$\therefore I_{DS1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH})^2$$

$$\therefore \left(\frac{W}{L}\right)_1 = 139 //$$

$$\therefore \left(\frac{W}{L}\right)_2 = \frac{139}{16}$$

$$\approx 8.69 //$$

$$\text{and } V_{IN} = \frac{V_{DD}}{3} = 0.6 \text{ V}$$

(67)

$$R_{in} = \frac{1}{g_{m1}} = 50 \Omega$$

$$\therefore g_{m1} = 20 \text{ mS}$$

$$\text{Volt. gain } (A_v) = g_{m1} R_D = 5$$

$$\therefore R_D = 250 \Omega$$

$$\text{Power} = 3 \text{ mW}$$

$$\therefore I_{DS1} = \frac{3 \text{ mW}}{1.8 \text{ V}}$$

$$= 1.67 \text{ mA}$$

$$\therefore g_{m1} = \sqrt{2 \times \mu_n C_{ox} \times \left(\frac{W}{L}\right)_1 I_{DS1}}$$

$$\left(\frac{W}{L}\right)_1 = 600$$

$$\therefore R_D = 250 \Omega, \quad \left(\frac{W}{L}\right)_1 = 600, \quad I_{DS} = 1.67 \text{ mA}$$

(68)

$$\text{Power (P)} = 2 \text{ mW}$$

$$I_{DS1} = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA}$$

$\therefore M_1$ operates 100 mV away from triode,

$$V_{DS} = V_{GS} - V_{TH} + 0.1$$

$$V_D = 1.8 - 0.4 + 0.1 = 1.5 \text{ V}$$

$$\therefore R_D = \frac{1.8 - 1.5}{1.11 \times 10^{-3}} \approx 270 \Omega$$

$$\text{Volt. gain (A}_v) = g_{m1} R_D = 4$$

$$\therefore g_{m1} = 14.8 \text{ mS}$$

$$\therefore I_{DS} = \frac{1}{2} g_{m1} \times (V_{GS1} - V_{TH})$$

$$V_{GS} \approx 0.550 \text{ V}$$

$$\text{Set } V_G = 0.9 \text{ V}, \quad \therefore V_S = (0.9 - 0.55) \text{ V} = 0.35 \text{ V}$$

$$R_S = \frac{0.35}{1.11 \times 10^{-3}} \approx 315 \Omega$$

$$\text{To find } \left(\frac{W}{L}\right)_1: \quad g_{m1} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH})$$

$$\therefore \left(\frac{W}{L}\right)_1 \approx 135$$

$$\therefore \left(\frac{W}{L}\right)_1 = 135, \quad V_{TN} = 0.9 \text{ V}, \quad R_S = 315 \Omega, \quad R_D = 270 \Omega$$

$$I_{DS} = 1.11 \text{ mA}$$

(69)

$$\text{Power} = 5 \text{ mW}$$

$$\therefore I_{DS1} = \frac{5 \times 10^{-3}}{1.8} = 2.78 \text{ mA}$$

$$g_{\text{ain}} (A/V) = g_m R_D = 5$$

$$V_{G1} = V_{OUT} = 1.8 - I R_D$$

$$V_{S1} = I R_S$$

$$\text{Let } R_S = \frac{10}{g_m}$$

$$\therefore V_{S1} = \frac{10 I}{g_m}$$

$$\therefore V_{GS1} = 1.8 - I R_D - \frac{10 I}{g_m}$$

$$\therefore I_{DS} = \frac{1}{2} g_m (V_{GS} - V_{TH})$$

$$\begin{aligned} 2.78 \times 10^{-3} &= \frac{g_m}{2} \left(1.8 - 2.78 \times 10^{-3} R_D - \frac{2.78 \times 10^{-2}}{g_m} \right) \\ &= 0.9 g_m - 1.39 \times 10^{-3} g_m R_D - 1.39 \times 10^{-2} \end{aligned}$$

$$\therefore g_m R_D = A_V = 5$$

$$2.78 \times 10^{-3} = 0.9 g_m - 6.95 \times 10^{-3} - 1.39 \times 10^{-2}$$

$$\therefore g_m \approx 26.3 \text{ mS}$$

$$\text{and } R_D = \frac{5}{26.3 \times 10^{-3}} \approx 190 \Omega //$$

$$R_S = \frac{10}{26.3 \times 10^{-3}} = 380 \Omega //$$

$$\therefore g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L} \right) I_{DS1}} \Rightarrow \left(\frac{W}{L} \right) \approx 622 //$$

(70)

$$\therefore R_s \approx \frac{10}{f_m}$$

$$\therefore R_{in} \approx \frac{1}{f_m} = 50 \Omega$$

$$\text{i.e. } f_m = 20 \text{ mS.} //$$

$$|f_{ain} (A_v)| = \frac{f_m R_D}{1 + f_m R_s} = 4$$

$$f_m R_D = 4 + 4 f_m R_s$$

$$R_D = \frac{4 + 0.08 R_s}{0.02} = 200 + 4 R_s \quad \text{--- (1)}$$

$$\therefore R_s I_D + V_{GS} - V_{TH} + 0.25 = 1.8 - I_D R_D \quad (\text{given})$$

$$\text{and } I_D = \frac{1}{2} f_m (V_{GS} - V_{TH})$$

$$\text{i.e. } V_{GS} - V_{TH} = 100 I_D$$

$$\therefore R_s I_D + 100 I_D + 0.25 = 1.8 - I_D R_D$$

From (1):

$$R_s I_D + 100 I_D + 0.25 = 1.8 - 200 I_D - 4 I_D R_s$$

$$5 R_s I_D + 300 I_D = 1.55$$

$$\text{Set } R_s = \frac{10}{f_m} = 500 \Omega$$

$$\therefore 2500 I_D + 300 I_D = 1.55$$

$$\therefore I_D = 0.554 \text{ mA} //$$

$$\therefore I_D = \frac{1}{2} f_m (V_{GS} - V_{TH})$$

$$0.554 \times 10^{-3} = \frac{1}{2} \times 20 \times 10^{-3} (V_{GS} - 0.4)$$

$$\therefore V_{GS} = 0.455 \text{ V}$$

To find $(\frac{W}{L})$:

$$I_{DS} = \sqrt{2 \left(\frac{W}{L} \right) \mu_n C_{ox} I_{DS}}$$

$$\therefore \left(\frac{W}{L} \right) \approx 1805$$

To find R_D :

$$\therefore R_D = 200 + 4R_S \quad (\text{from (1)})$$

$$R_D = 2200$$

To find R_1 and R_2 ,

$$\therefore R_1 + R_2 = 20 \text{ k}\Omega$$

$$\text{and } V_{GS} = V_G - I_D R_S = 0.455 \text{ V}$$

$$\text{i.e. } V_G = 0.732 \text{ V}$$

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$\therefore R_1 = 8133 \Omega$$

$$R_2 \approx 11.9 \text{ k}\Omega$$

$$\therefore R_1 = 8133 \Omega, R_2 = 11.9 \text{ k}\Omega, R_D = 2200 \Omega, R_S = 500 \Omega$$

$$\left(\frac{W}{L} \right) = 1805 \quad I_{DS} = 0.554 \text{ mA}$$

(71)

$$R_{in} = R_g = 10 \text{ k}\Omega //$$

$$\text{Power} = 2 \text{ mW}$$

$$\therefore I_{DS} = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA} //$$

$$A_v = \frac{R_s}{\frac{1}{g_m} + R_s} = 0.8$$

$$\therefore R_s = \frac{4}{g_m} \quad \text{--- (1)}$$

$$\therefore V_{out} = \frac{V_{DD}}{2} = I_{DS} R_s$$

$$I_{DS} R_s = 0.9 \quad \text{--- (2)}$$

$$\therefore V_G = 1.8 \text{ V and } V_S = 0.9$$

$$\therefore V_{GS} = 0.9 \text{ V}$$

$$\text{From (2), } \therefore I_{DS} = 1.11 \text{ mA}$$

$$R_s = \frac{0.9 \text{ V}}{1.11 \text{ mA}} \approx 810 \Omega //$$

$$\text{From (1), } g_m = \frac{4}{810 \Omega} \approx 4.94 \text{ mS}$$

$$\therefore g_m = \left(\frac{W}{L}\right) (M_n C_{ox}) (V_{GS} - V_{TH})$$

$$\frac{W}{L} \approx 49.4 //$$

(72)

$$R_{in} = R_g = 20 k\Omega$$

$$\therefore \text{Power} = 3 \text{ mW}$$

$$\therefore I_{DS} = \frac{3 \text{ mW}}{1.8 \text{ V}} = 1.67 \text{ mA}$$


$$V_{x, \text{at DC}} = I_{DS} R_S = 0.9 \text{ V}$$

$$\therefore R_S = 540 \Omega$$

$$\text{Load impedance, } Z_L = R_S \parallel \left(\frac{1}{sC_1} + R_L \right)$$

(at 100 MHz)
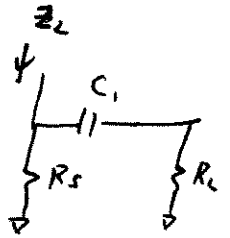
$$= 540 \parallel \left(\frac{1}{2\pi \times 10^8 C_1} + 50 \right)$$



$$\text{Voltage gain } (A_v) = \frac{Z_L}{f_m + Z_L}$$

$$f_m = \frac{2 I_{DS}}{V_{GS} - V_{TH}}$$

$$= \frac{2 \times 1.67 \times 10^{-3}}{(1.8 - 0.9) - 0.4}$$

$$= 6.67 \text{ mS}$$

$$\therefore A_v = \frac{Z_L}{f_m + Z_L} = 0.8$$

$$Z_L = 120 + Z_L (0.8)$$

$$\therefore Z_L = 150$$

$$\therefore 150 = 540 // \left(\frac{1}{2\pi \times 10^8 C_1} + 50 \right)$$

$$= 540 // \left[\frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} \right]$$

$$= \frac{540 \times \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}}{540 + \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}}$$

$$\therefore \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} \approx 208$$

$$\therefore C_1 \approx 10.1 \text{ pF} //$$

To find $(\frac{W}{L})$:

$$\therefore f_m = \left(\frac{W}{L} \right) \mu_n C_{ox} (V_{GS} - V_{TH})$$

$$\frac{W}{L} = 66.7 //$$

$$\therefore \frac{W}{L} = 66.7, C_1 = 10.1 \text{ pF}, R_s = 540 \Omega.$$

(73)

$$\text{Power} = 3 \text{ mW}$$

$$\therefore I_{DS1,2} = \frac{3 \text{ mW}}{1.8 \text{ V}} = 1.67 \text{ mA}$$

$$r_{o2} = \frac{1}{\lambda I_{DS2}}$$

$$= \frac{1}{0.1 \times 1.67 \times 10^{-3}} \approx 5990 \Omega$$

$$= r_{o1}$$

$$\therefore A_v = \frac{r_{o2} \parallel r_{o1}}{\frac{1}{g_{m1}} + r_{o2} \parallel r_{o1}} = 0.9$$

$$\therefore 0.9 = \frac{2995}{\frac{1}{g_{m1}} + 2995}$$

$$g_{m1} \approx 3 \text{ mS}$$

$$\therefore V_{DS2} \geq 0.3 \text{ V. (for } M_2 \text{ to be in saturation)}$$

$$\text{Set } V_{out} \text{ (i.e. } V_{DS2, \text{ nominal}}) = 0.3 \text{ V}$$

$$\therefore g_{m1} = \frac{2 I_{DS1}}{V_{GS1} - V_{TH}}$$

$$3 \times 10^{-3} = \frac{2 \times 1.67 \times 10^{-3}}{V_G - 0.9 - 0.4}$$

$$\therefore V_{IN} = V_G \approx 1.81 \text{ V}$$

$$I_m = \sqrt{2 \left(\frac{W}{L} \right) \mu_n C_{ox} I_{DS}}$$

$$\therefore \frac{W}{L} \approx 13.5$$

$$\therefore \frac{W}{L} = 13.5, \quad V_{TN} = 1.81V, \quad I_{DS} = 1.67mA.$$