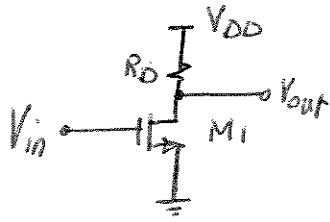


1.

 M_1 operates in the triode region

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right]$$

$$R_D = 10K$$

$$V_{out} = V_{DD} - R_D I_D$$

$$\left(\frac{W}{L} \right)_1 = 3/0.18$$

$$V_{out, min} = ? \text{ when } V_{in} = V_{DD}$$

$$V_{out, min} = V_{DD} - R_D I_{D, max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right] \times R_D$$


If the second term in the square brackets is neglected, then

$$V_{out, min} \approx \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH}) \times R_D}$$

$$= \frac{1.8}{1 + 100 \times 10^{-6} \times \frac{3}{0.18} \times (1.8 - 0.4) \times 10^5}$$

$$V_{out, min} \approx 74 \text{ mV}$$

2.

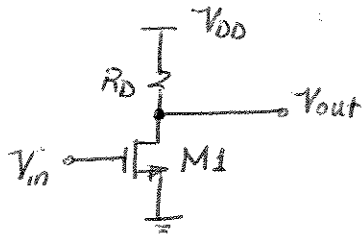

$$V_{out,min} \leq 100 \text{ mV}$$

$$R_D = 5 \text{ k}\Omega$$

$$\left(\frac{W}{L}\right)_{1,min} = ?$$

Output low level establishes for $V_{in} = V_{DD}$, driving M_1 into the triode region.

$$I_{D,max} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2 \right]$$

$$V_{out,min} = V_{DD} - R_D \times I_{D,max}$$


$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2 \right] \times R_D$$

$$\left(\frac{W}{L}\right)_1 = \frac{V_{DD} - V_{out,min}}{\frac{1}{2} \mu_n C_{ox} \left[2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2 \right] \times R_D}$$

$$\left(\frac{W}{L}\right)_{1,min} = \frac{1.8 - 100 \times 10^{-3}}{\frac{1}{2} \times 100 \times 10^{-6} \left[2(1.8 - 0.4) 100 \times 10^{-3} - (100 \times 10^{-3})^2 \right] \times 5 \times 10^3}$$

$$\boxed{\left(\frac{W}{L}\right)_{1,min} = 25}$$

3.

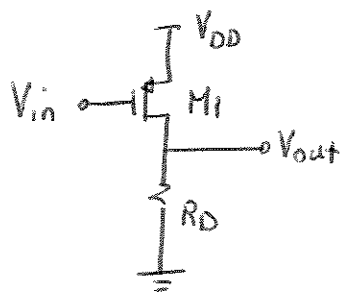

$$\left(\frac{W}{L}\right)_1 = 20/0.18, \quad R_D = 5K$$

$$V_{OL}, V_{OH} = ?$$

$$(1) \quad V_{in} = V_{DD} \rightarrow M_1 \text{ off} \rightarrow I_D = 0 \rightarrow \boxed{V_{out} = V_{OL} = 0}$$

$$(2) \quad V_{in} = 0 \rightarrow M_1 \text{ operates in the triode region}$$

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{SG} - |V_{THP}|) V_{SD} - V_{SD}^2 \right]$$

$$I_{D, \max} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - |V_{THP}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

$$I_{D, \max} = \frac{V_{out}}{R_D} \quad (2)$$

Equating (1) and (2) and neglecting the second order term in the brackets

$$\frac{V_{out}}{R_D} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \times 2(V_{DD} - |V_{THP}|)(-V_{out} + V_{DD})$$


$$V_{out} \left[\frac{1}{R_D} + \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|) \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|) V_{DD}$$

$$V_{out} = \frac{R_D}{R_D + \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|)}} V_{DD}$$

$$V_{out} = \frac{5000}{5000 + \frac{1}{50 \times 10^{-6} \times \left(\frac{20}{0.18}\right) \times (1.8 - 0.5)}} \times 1.8$$

$$V_{out} = V_{OH} = 1.75 \text{ V}$$

4.

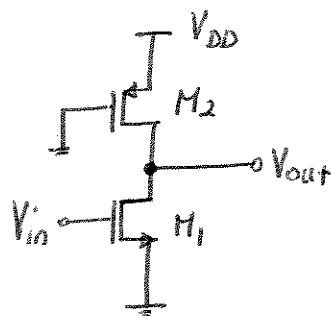

$$\left(\frac{W}{L}\right)_1 = 3/0.18 \quad \left(\frac{W}{L}\right)_2 = 2/0.18$$

(a) if $V_{in} = V_{DD}$, M_2 Saturated $\rightarrow V_{OL} = ?$

(b) if $V_{in} = V_{out} \rightarrow V_{in} = ?$

$$(a) \quad I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{THP}|)^2$$

$$I_{D2} = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (1.8 - 0.5)^2, \text{ Note that } V_{SG} = V_{DD}$$

$$I_{D2} = 4.7 \times 10^{-4} \text{ A}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{GS} - V_{THN}) V_{DS} - V_{DS}^2 \right]$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{THN}) V_{OL} - V_{OL}^2 \right]$$

However $I_{D1} = I_{D2}$

$$4.7 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{3}{0.18}\right) \left[2(1.8 - 0.4) V_{OL} - V_{OL}^2 \right]$$

Neglecting the second-order term yields:

$$\boxed{V_{OL} = 0.2 \text{ V}}$$

$$\text{As } (V_{in} - V_{THN}) = (V_{DD} - V_{THN}) = (1.8 - 0.4) = 1.4 > V_{DS1} = V_{OL} = 0.2 \text{ V}$$

The assumption of M_1 being in Triode region is correct

We define, $V_x = V_{in} - V_{TH,N} \rightarrow V_{in} = V_x + V_{TH,N}$

$$\frac{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2} V_x^2 = 2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{TH,N} - V_x) - (V_{DD} - V_{TH,N} - V_x)^2$$

$$\frac{100}{50} \times \frac{3/0.18}{2/0.18} V_x^2 = 2(1.8 - 0.5)(1.8 - 0.4 - V_x) - (1.8 - 0.4 - V_x)^2$$

$$3V_x^2 = 2.6(1.4 - V_x) - (1.4 - V_x)^2$$

$$3V_x^2 = 3.64 - 2.6V_x - 1.96 + 2.8V_x - V_x^2$$

$$4V_x^2 - 0.2V_x - 1.68 = 0$$

$$V_x = \frac{0.2 \pm \sqrt{0.2^2 + 4 \times 4 \times 1.68}}{8} \rightarrow \boxed{V_x = 0.67 \text{ V}}$$

$$V_{in} = V_x + V_{TH,N} = 0.67 + 0.4 \rightarrow \boxed{V_{in} = V_{out} = 1 \text{ V}}$$

This value of V_{out} guarantees that M_2 operates in the triode region.

Now, let's investigate the region of operation of M_2

$$V_{SD2} = V_{DD} - V_{out}$$

$$= 1.8 - 0.2$$

$$V_{SD2} = 1.6 \text{ V}$$

$$V_{SG2} - |V_{THP}| = V_{DD} - |V_{THP}|$$

$$= 1.8 - 0.5$$

$$V_{SG2} - |V_{THP}| = 1.3$$


As $V_{SD2} > V_{SG2} - |V_{THP}|$, M_2 operates in the saturation region and the initial assumption is valid.

(b) As $V_{in} = V_{out} \rightarrow M_1$ is saturated.

We assume that M_2 is in the triode region and check the validity of this assumption

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{THN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{THP}|) \times (V_{DD} - V_{in}) - (V_{DD} - V_{in})^2 \right]$$

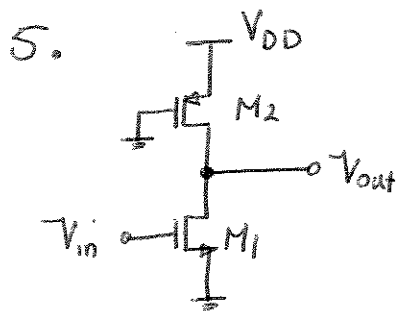

$$V_{OL} \leq 100 \text{ mV}$$

$$\left(\frac{W}{L}\right)_2 = 3/0.18$$

$$\left(\frac{W}{L}\right)_{1, \min} = ?$$

$V_{in} = V_{DD} \rightarrow M_1$ operates in the triode region and M_2 in the saturation.

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{TH,P}|)^2$$

$$= \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{3}{0.18}\right) \times (1.8 - 0.5)^2$$


$$I_{D2} = 7.041 \times 10^{-4} \text{ A}$$

$$I_{D1} = I_{D2} = 7.041 \times 10^{-4} \text{ A}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{GS} - V_{TH,N}) V_{DS} - V_{DS}^2 \right]$$

$$7.041 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L}\right)_1 \left[2(1.8 - 0.4) 0.1 - (0.1)^2 \right]$$
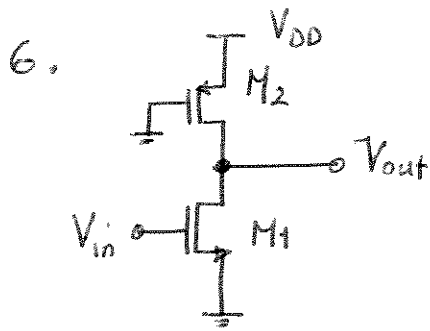
$$\boxed{\left(\frac{W}{L}\right)_{1, \min} = 52.16}$$



$$V_{OL} \leq 80 \text{ mV}$$

$$\left(\frac{W}{L}\right)_1 = 2/0.18$$

$$\left(\frac{W}{L}\right)_{2, \max}$$

$V_{in} = V_{DD} \rightarrow M_1$ operates in the triode region and M_2 in the saturation

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{GS} - V_{TH,N})V_{DS} - V_{DS}^2 \right]$$

$$I_{D1} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) \times \left[2(1.8 - 0.4)0.08 - 0.08^2 \right]$$

$$I_{D1} = 1.2 \times 10^{-4} \text{ A}$$


$$I_{D2} = I_{D1} = 1.2 \times 10^{-4} \text{ A}$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{TH,P}|)^2$$

$$1.2 \times 10^{-4} = \frac{1}{2} \times 50 \times 10^{-6} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)^2$$

$$\left(\frac{W}{L}\right)_{2, \max} = 2.86$$

7.

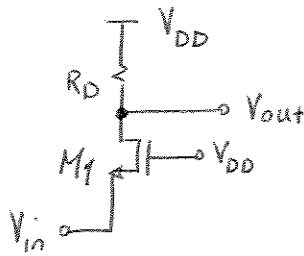

(a) If $V_{in} = 0$, V_{DD} , $V_{out} = ?$

If $V_{in} = 0 \rightarrow M_1$ operates in the triode region.


$$R_{on1} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH,N})}$$


$$V_{out} \cong \frac{R_{on1}}{R_{on1} + R_D} \times V_{DD} \rightarrow V_{out} \cong \frac{1}{1 + \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH,N}) R_D} \times V_{DD}$$

If $V_{in} = V_{DD} \rightarrow V_{out} = V_{DD}$

No, this circuit does not invert.

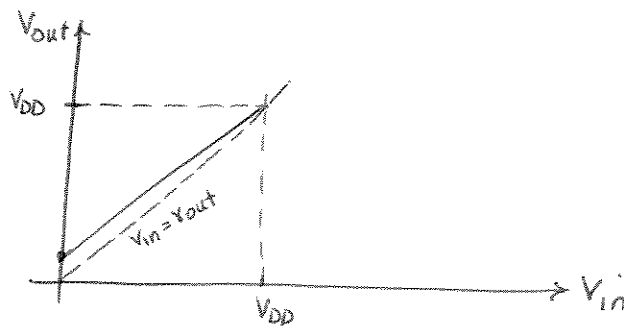(b) A trip point cannot be found for this circuit because $V_{out} = V_{in}$ line does not intersect the transfer characteristic of this buffer.



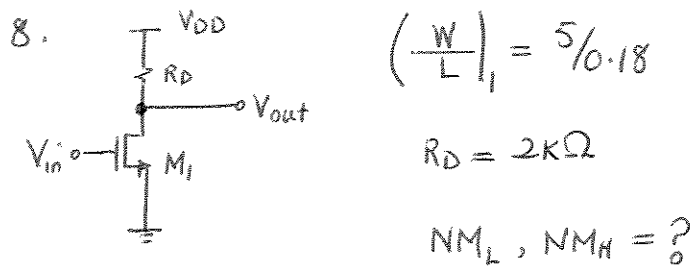

Small signal gain of the circuit is equal to $-g_m R_D$

and $g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N}) R_D = 1$, $V_{GS} = V_{IL}$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 1$

$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH} = \frac{1}{100 \times 10^{-6} \times \frac{5}{0.18} \times 2000} + 0.4$

$V_{IL} = 0.58\text{V}$

To determine NM_H , we note that V_{in} drives M_1 into the triode region

$V_{out} = V_{DD} - R_D I_D$

$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH,N}) V_{out} - V_{out}^2 \right] R_D \quad (1)$

$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH,N}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D$
 $+ 2V_{out}$

$\frac{\partial V_{out}}{\partial V_{in}} = -1 \quad (a) \quad V_{IH}$

$-1 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[-2(V_{in} - V_{TH,N}) + 2V_{out} \right] R_D$

$$I = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[-V_{in}^2 + V_{TH,N} + 2V_{out} \right] R_D$$

$$\frac{I}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_D} = -(V_{in} - V_{TH,N}) + 2V_{out}$$

$$V_{out} = \frac{I}{2\mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{2} \rightarrow V_{out} = 0.5V_{in} - 0.11$$


Substituting This in (1) yields:

$$0.5V_{in} - 0.11 = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \left[2(V_{in} - 0.4)(0.5V_{in} - 0.11) - (0.5V_{in} - 0.11)^2 \right]$$

$$0.75V_{in}^2 - 0.33V_{in} - 0.6117 = 0$$

$$V_{in} = V_{IH} = 1.15$$
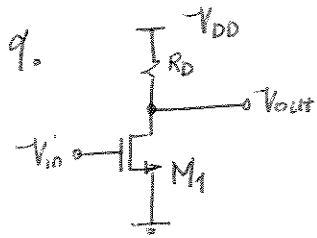
$$NM_H = V_{DD} - V_{IH} = 1.8 - 1.15 \rightarrow \boxed{NM_H = 0.65V}$$



Small signal gain of the inverter is equal to $-g_m R_D$

and $g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N}) R_D = 1$, $V_{GS} = V_{IL}$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 1 \rightarrow V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH,N}$

If we double the value of $\left(\frac{W}{L}\right)_1$ or R_D

$V_{IL} = \frac{1}{100 \times 10^8 \times \frac{5}{0.18} \times 2000 \times 2} + 0.4 \rightarrow \boxed{V_{IL} = 0.49}$

To determine NM_H , we note that V_{in} drives M_1 into the triode region

$V_{out} = V_{DD} - R_D I_D$

$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D \quad (1)$

$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2 V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2 V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right]$

$\frac{\partial V_{out}}{\partial V_{in}} = -1 \quad (a)$

$V_{out} = \frac{1}{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{2}$

Doubling $(\frac{W}{L})_1$ or R_D leads to

$$V_{out} = 0.5V_{in} - 0.155$$


Substituting in (1) yields:

$$0.5V_{in} - 0.155 = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \times 2 \left[2(V_{in} - 0.4)(0.5V_{in} - 0.155) - (0.5V_{in} - 0.155)^2 \right]$$

$$0.75V_{in}^2 - 0.465V_{in} - 0.251925 = 0$$

$$V_{in} = 0.967V \rightarrow NM_H = 1.8 - 0.967$$

$$NM_H = 0.833V$$

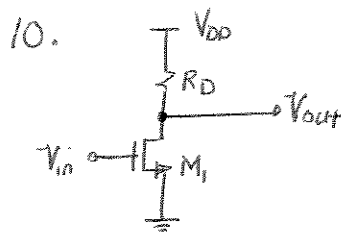

$$\left(\frac{W}{L}\right)_1 = \frac{5}{0.18}$$

$$R_D = 2K$$

$$NM_L \text{ and } NM_H = ? \text{ if } \frac{\partial V_{out}}{\partial V_{in}} = -0.5 \text{ instead of } -1$$

Small signal gain of the inverter is equal to $-g_m R_D$

$$\text{and } g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 0.5$$

$$V_{IL} = \frac{1}{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH,N} = \frac{1}{2 \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000} + 0.4$$

$$\boxed{V_{IL} = 0.49} \text{ which is less than } 0.58 \text{ obtained in problem 8.}$$

To determine NM_H , note that M_1 operates in the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -0.5 \quad \text{at } V_{IH}$$

$$-0.5 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[-(V_{in} - V_{TH,N}) + 3V_{out} \right] R_D$$

$$V_{out} = \frac{1}{3\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{3} \rightarrow V_{out} = -73.33 \times 10^{-3} + 0.33 V_{in}^0$$

$$\text{or } V_{out} = -\frac{0.22}{3} + \frac{V_{in}}{3}$$

Substituting in (1) yields:

$$-\frac{0.22}{3} + \frac{V_{in}}{3} = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \left[2(V_{in} - 0.4) \left(-\frac{0.22}{3} + \frac{V_{in}}{3} \right) - \left(-\frac{0.22}{3} + \frac{V_{in}}{3} \right)^2 \right]$$

$$5V_{in}^2 - 2.2V_{in} - 5.59 = 0$$


$$V_{in} = V_{IH} = 1.3$$

$$NM_H = 1.8 - 1.3$$

$$\boxed{NM_H = 0.5V}$$

less than 0.65V obtained in problem 8 because

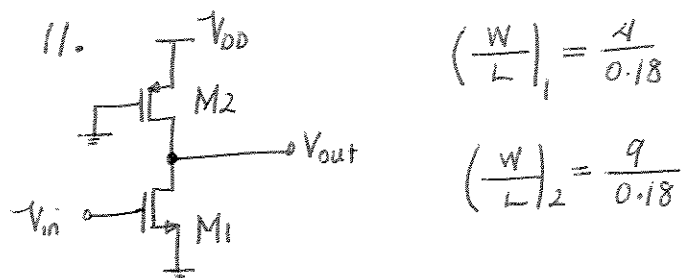V_{IH} is now further pushed up toward V_{DD} .



To calculate V_{IL} , we assume that M_1 and M_2 operate in saturation and triode region respectively.

$$I_{D1} = I_{D2} \quad (1)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH,P}|) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) \right]$$

By substituting $\frac{\partial V_{out}}{\partial V_{in}}$ with "-1" in the above relationship:

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH,P}|) - 2(V_{DD} - V_{out}) \right]$$

$$V_{out} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) + |V_{TH,P}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} = \frac{100 \times 10^{-6} \times 4/0.18}{50 \times 10^{-6} \times 9/0.18} (V_{in} - 0.4) + 0.5$$

$$V_{out} = 0.144 + 0.88 V_{in}^o \quad \text{or} \quad \boxed{V_{out} = \frac{8}{9} V_{in}^o + \frac{1.3}{9}}$$

Substituting V_{out} in (1) by the derivation versus V_{in} gives:

$$136 V_{in}^2 - 108.8 V_{in}^o - 115.13 = 0$$

$$\boxed{V_{in}^o = V_{IL} = NM_L = 1.4 \text{ V}}$$

To calculate V_{IH} , we assume that M_1 and M_2 operate in the triode and saturation region respectively.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{THN}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{THP}|)^2 \quad (2)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 0$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = 0$$

$$V_{out} = \frac{V_{in} - V_{THN}}{2} \text{ Substituted in (2) yields:}$$

$$V_{in} = \sqrt{\frac{3}{2}} (V_{DD} - |V_{THP}|) + V_{THN}$$

$V_{in} = 2 \rightarrow V_{out} = 0.8$ This value of V_{out} puts M_2 into the triode region so our initial assumption is not correct

Now we assume that both M_1 and M_2 operate in the triode region.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{THN}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{THP}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (3)$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \times$$

$$\left[2(V_{DD} - |V_{THP}|) \left(-\frac{\partial V_{out}}{\partial V_{in}} \right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}} \right) \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \times$$

$$\left[2(V_{DD} - |V_{THP}|) - 2(V_{DD} - V_{out}) \right]$$

$$V_{out} = \frac{\frac{\mu_n C_{ox} \left(\frac{W}{L} \right)_1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2} (V_{in} - V_{THN}) - |V_{THP}|}{2 \frac{\mu_n C_{ox} \left(\frac{W}{L} \right)_1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2} - 1}$$

$$V_{out} = \frac{8}{7} V_{in} - 1.1$$

After substituting in (3) it leads to:


$$2.1769 V_{in}^2 - 4.19 V_{in} + 0.576 = 0$$

$$\boxed{V_{in} = 1.77 \text{ V}}$$

$$V_{out} = 0.93 \text{ V} \rightarrow \text{The assumption is correct}$$

$$V_{IH} = 1.77 \text{ V} \rightarrow NM_H = 1.8 - 1.77$$

$$\boxed{NM_H = 0.03 \text{ V}}$$

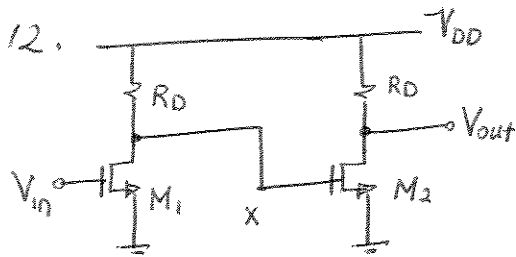

The small signal gain of the circuit is equal to $-g_m R_D$ and since

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{THN})$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{IL} - V_{THN}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_D} + V_{THN} = \frac{2}{5} + 0.4 ; \left(\frac{W}{L} \right)_{1,2} = 5$$

Now we calculate the output of M_1 for $V_{in} = V_{DD}$:

$$V_{DD} - R_D I_D = V_{out}$$

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{THN}) V_{out} - V_{out}^2 \right] R_D = V_{out} ; \left(\frac{W}{L} \right)_{1,2} = 5$$

$$1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times 5 \left[2(1.8 - 0.4) \left(\frac{2}{5} + 0.4 \right) - \left(\frac{2}{5} + 0.4 \right)^2 \right] \times 5000 = \left(\frac{2}{5} + 0.4 \right)$$

$$1.8 - 0.25 \times \left[2.8(2 + 0.45) - 5 \left(\frac{2}{5} + 0.4 \right)^2 \right] = \frac{2}{5} + 0.4$$






$$1.85 - 0.25 \times \left[2.8(2.5 + 0.45^2) - 5 \left(\frac{2}{5} + 0.4 \right)^2 \right] = 2 + 0.45$$

$$1.85 - 0.25 \times \left[5.65 + 1.125^2 - 4 - 1.65 - 0.165^2 \right] = 2 + 0.45$$


$$0.245^2 - 0.45 + 1 = 0$$

$$\Delta < 0!$$

13.

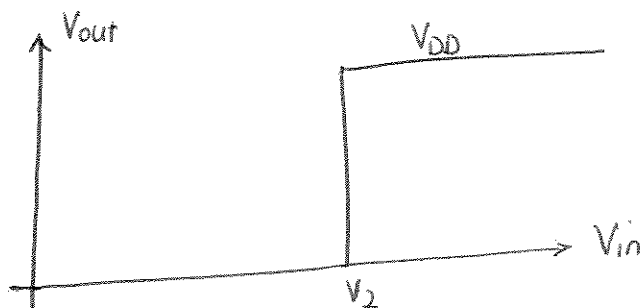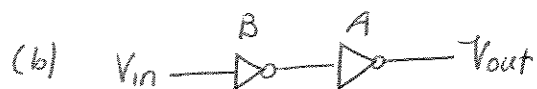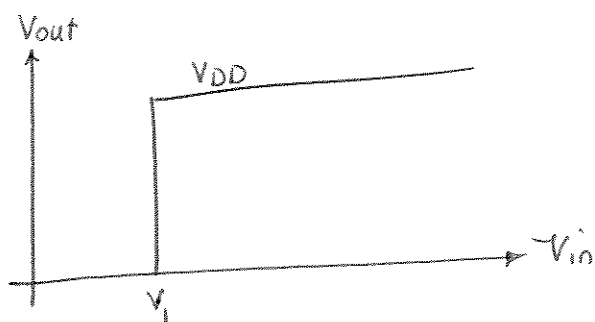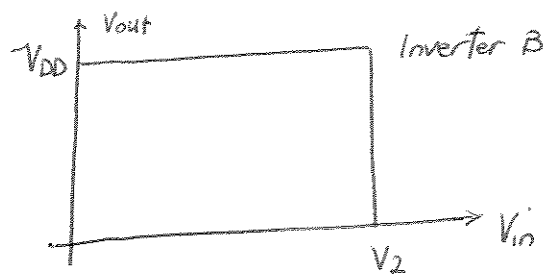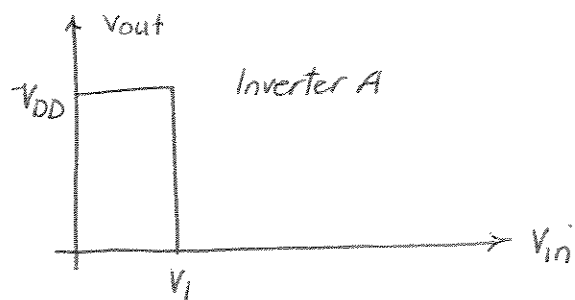

14.

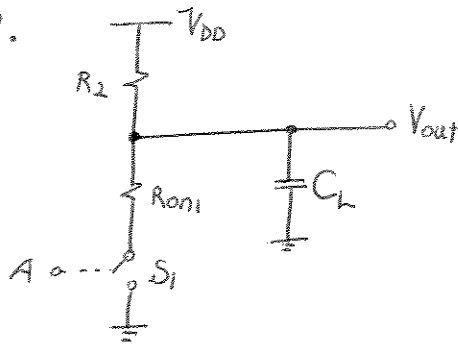

$$R_{on1} \ll R_2 \rightarrow V_{out, min} \approx 0$$

$$(a) \quad V_{out}(t) = V_{out}(\bar{0}) + [V_{DD} - V_{out}(\bar{0})] \left(1 - \exp \frac{-t}{R_2 C_L}\right) \quad t > 0$$

Note that $V_{out}(\bar{0}) = 0$, $V_{out}(\infty) = V_{DD}$

$$V_{out}(t) = V_{DD} \times \left(1 - \exp \frac{-t}{R_2 C_L}\right) \quad t > 0$$

$$0.95 V_{DD} = V_{DD} \times \left(1 - \exp \frac{-T_{95\%}}{R_2 C_L}\right)$$

$$\boxed{T_{95\%} = 3 R_2 C_L}$$

$$(b) \quad V_{out}(t) = V_{out}(\bar{0}) + [V_{out}(\infty) - V_{out}(\bar{0})] \times \left(1 - \exp \frac{-t}{R_2 C_L}\right)$$

$$V_{out}(t) = V_{DD} + [0 - V_{DD}] \times \left(1 - \exp \frac{-t}{R_2 C_L}\right)$$


$$V_{out}(t) = V_{DD} \exp \frac{-t}{R_2 C_L}$$

$$0.05 V_{DD} = V_{DD} \exp \frac{-T_{0.05}}{R_2 C_L}$$

$$\boxed{T_{5\%} = 3 R_2 C_L}$$

If $R_{on1} \ll R_2$, inverter exhibits equal rise and fall time (or low-to-high and high-to-low delay) at the output.

15.

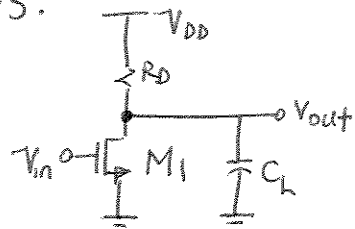

$$C_L = 50 \text{ fF}$$

$$T_R = 100 \text{ pS}$$


$$T_R = 3 \tau_{out}$$

$$R_{D,max} = ?$$

$$T_R = 3 R_D C_L = 100 \text{ pS}$$

$$R_D \leq \frac{100 \text{ pS}}{3 \times 50 \text{ fF}}$$

$$R_D \leq 666.67 \, \Omega$$

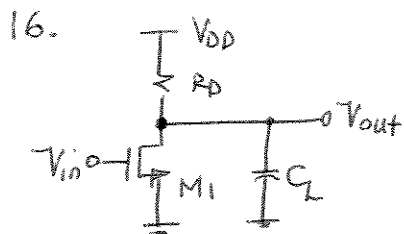

$$C_L = 100 \text{ fF}$$

$$V_{out, \min} = 50 \text{ mV}$$

$$T_R = 200 \text{ pS}$$

$$R_D, \left(\frac{W}{L}\right)_1 = ?$$

$$T_R = 3\tau_{out}$$

$$T_R = 3R_D C_L$$

$$200 \times 10^{-12} = 3 \times R_D \times 100 \times 10^{-15}$$

$$R_D = 666.667 \Omega$$

$V_{in} = V_{DD}$ places M_1 in the triode region

$$V_{out, \min} = V_{DD} - R_D I_{D, \max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D \left[2(V_{DD} - V_{THN}) V_{out, \min} - V_{out, \min}^2 \right]$$


Neglecting the 2nd order term in the square brackets yields:

$$V_{out, \min} = \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D (V_{DD} - V_{TH})}$$

$$50 \times 10^{-3} = \frac{1.8}{1 + 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 \times 666.7 \times (1.8 - 0.4)}$$

$$\left(\frac{W}{L}\right)_1 = 375$$

17.

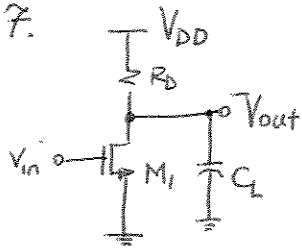

$$C_L = 100 \text{ fF}$$

$$V_{out, min} \approx 0$$

$$I_{D, max} \leq 1 \text{ mA}$$

$$T_{R, min} = 0$$

$$I_{D, max} = \frac{V_{DD} - V_{out, min}}{R_D}$$

$$10^{-3} = \frac{1.8 - 0}{R_D}$$

$$R_D = 1.8 \text{ k}\Omega$$

$$V_{out}(t) = V_{out}(0) + [V_{out}(\infty) - V_{out}(0)] \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$

$$V_{out}(t) = V_{out, min} + [V_{DD} - V_{out, min}] \times \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$


$$V_{out}(t) = V_{DD} \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$

$$0.1 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{10\%}}{R_D C_L}\right)\right) \rightarrow T_{10\%} = 0.105 R_D C_L$$

$$0.9 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{90\%}}{R_D C_L}\right)\right) \rightarrow T_{90\%} = 2.3 R_D C_L$$

$$T_R = T_{90\%} - T_{10\%} = 2.197 R_D C_L = 2.197 \times 1.8 \times 10^3 \times 100 \times 10^{-15}$$

$$T_R = 395.5 \text{ pS}$$

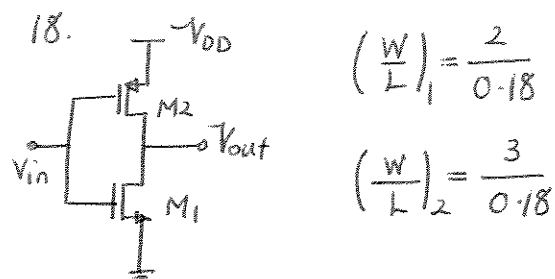

$$I_{D1} = I_{D2}$$

At the trip point $V_{in} = V_{out}$; therefore, both M_1 and M_2 operate in the Saturation region.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in}^0 - V_{THN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in}^0 - |V_{THP}|)^2$$


$$V_{in}^0 = \frac{V_{DD} - |V_{THP}| + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2} \times V_{THN}}}{1 + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}}}$$

$$V_{in}^0 = \frac{1.8 - 0.5 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2} \times 0.4}{1 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2}}$$


$$V_{in} = V_{out} = 0.82 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.82 - 0.4)^2$$

$$I_{D1} = I_{D2} = 97 \mu A$$

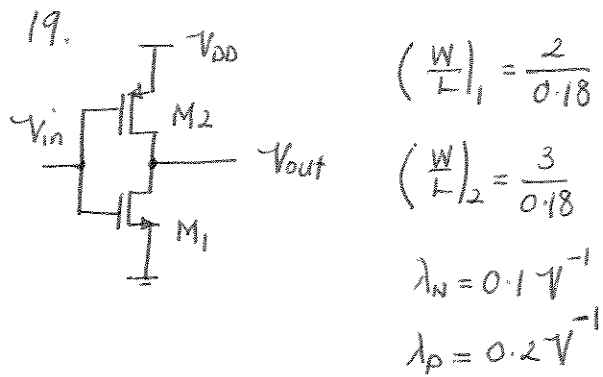

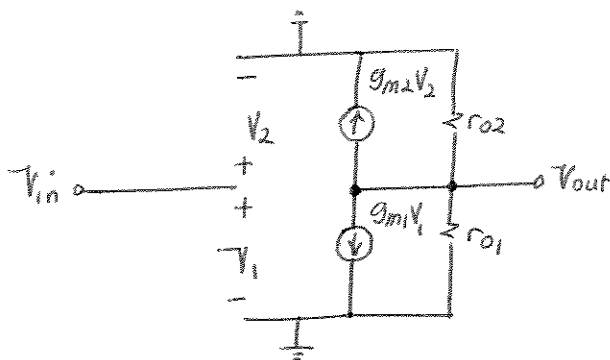Replacing M_1 and M_2 with their small-signal model in the saturation region yields:



$$V_{out} = (-g_{m1}V_1 - g_{m2}V_2)(r_{o1} \parallel r_{o2})$$

$$V_1 = V_2 = V_{in}$$

$$V_{out} = -(g_{m1} + g_{m2})(r_{o1} \parallel r_{o2})V_{in}$$

$$\frac{V_{out}}{V_{in}} = -(g_{m1} + g_{m2})(r_{o1} \parallel r_{o2})$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN})^2$$

$$g_{m1} = \frac{\partial I_{D1}}{\partial V_{in}} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN}) = \frac{2I_{D1}}{V_{in} - V_{THN}}$$

$$g_{m1} = \frac{2 \times 9.7 \times 10^{-5}}{(0.817 - 0.4)} \rightarrow \boxed{g_{m1} = 4.641 \times 10^{-4} \text{ S}}$$

$$g_{m2} = \frac{2I_{D2}}{(V_{SG} - |V_{THP}|)} = \frac{2 \times 9.7 \times 10^{-5}}{(1.8 - 0.817 - 0.5)} \rightarrow \boxed{g_{m2} = 4.02 \times 10^{-4} \text{ V}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 \lambda \simeq \lambda I_D$$

$$r_o \simeq \frac{1}{\lambda I_D}$$

$$r_{oN} \simeq \frac{1}{0.1 \times 9.7 \times 10^{-5}} = 103.17 \text{ K}\Omega$$

$$r_{oP} \simeq \frac{1}{0.2 \times 9.7 \times 10^{-5}} = 51.58 \text{ K}\Omega$$

$$G_{ain} = \frac{V_{out}}{V_{in}} = - (4.64 \times 10^{-4} + 4.02 \times 10^{-4}) (51.58 \text{ K} \parallel 103.17 \text{ K})$$


$$\boxed{G_{ain} = -29.8}$$

20.

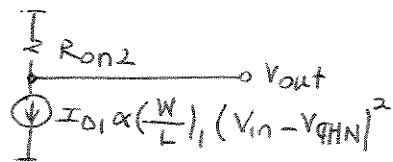(a) Length of M_1 is increased

Let's assume that $V_{in} < V_{TH1}$, as a result M_1 is off and M_2 is on operating in the triode region. As V_{in} increases beyond V_{TH1} , M_1 starts pulling current (conducting) in the saturation region while M_2 is still in the triode region, operating as a resistor; therefore,

CMOS inverter can be modelled as follows:



By increasing L_1 , I_{D1} is weakened due to the inverse proportionality; as a result, an excess V_{in} is required to drop V_{out} to the point where


$V_{out} = V_{in} + |V_{TH2}|$ and M_2 is placed at the edge of saturation.

Therefore characteristic is shifted to the right and it will be steeper at the gain region where both M_1 and M_2 are in saturation region.

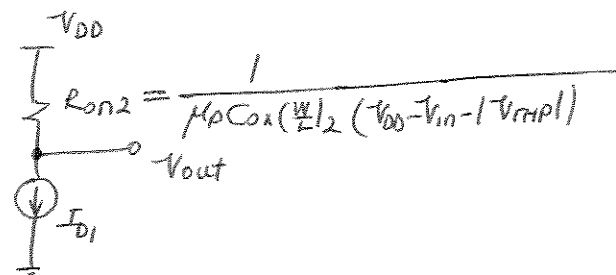
(b) Length of M_2 is increased

Again if we assume that $V_{in} < V_{TH1}$, M_1 is off and M_2 is operating in the triode region with no current. By increasing

V_{in} above V_{TH1} , M_1 conducts in the saturation region while M_2 is operating in the triode region. Using the same model as used in part (a) yields:



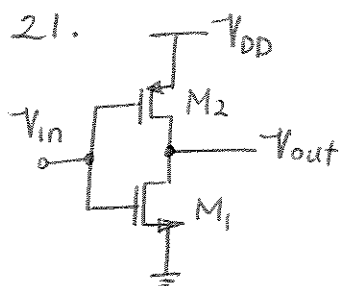
By increasing L_2 , R_{on2} becomes larger; as a result, lower value of I_{D1} causes comparable voltage drop at the output. This will drive M_2 into the saturation with lower current (I_{D1}) and; hence, lower value of V_{in} . Therefore, characteristic is shifted to the left and small signal gain will be higher.



$$\left(\frac{W}{L}\right)_1 = \frac{3}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{7}{0.18}$$

VTC looks like the following figure

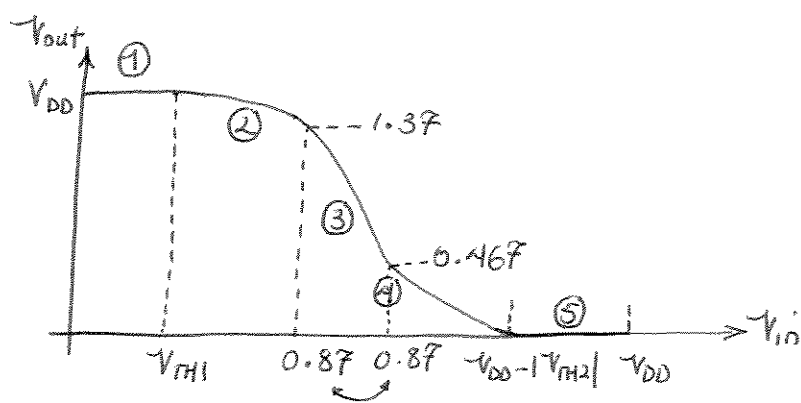

① M_1 off, M_2 in triode region

$$I_{D1} = 0$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|) V_{SD} - V_{SD}^2 \right] = 0$$

$$V_{SD} = 0 \rightarrow V_{out} = V_{DD} \quad (1)$$

② M_1 in saturation, M_2 in triode region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (V_{in} - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{7}{0.18} \times \left[2(1.8 - V_{in} - 0.5) \times (1.8 - V_{out}) - (1.8 - V_{out})^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7 \left[2(1.3 - V_{in})(1.8 - V_{out}) - (1.8 - V_{out})^2 \right] \quad (2)$$

If V_{out} falls significantly, M_2 enters saturation. That is $V_{out} = V_{in} + |V_{TH2}|$. Then M_2 is about to exit the triode region.

Replacing V_{out} by $V_{in} + |V_{TH2}|$ in (2) leads to:

$$6(V_{in} - 0.4)^2 = 7 \left[2(1.3 - V_{in})(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7(1.3 - V_{in})^2 \rightarrow \sqrt{\frac{6}{7}} (V_{in} - 0.4) = (1.3 - V_{in})$$

$$V_{in} = 0.867V, \quad V_{out} = 1.37$$

$$(3) \quad \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_1 V_{out}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 [1 + \lambda_2 (V_{DD} - V_{out})]$$

$$-V_{out} = \frac{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 - \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}{\lambda_2 \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 + \lambda_1 \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}$$

$$V_{out} = \frac{7(1.3 - V_{in})^2 - 6(V_{in} - 0.4)^2}{7\lambda_2(1.3 - V_{in})^2 + 6\lambda_1(V_{in} - 0.4)^2} \quad (3)$$

in region (3) M_1 and M_2 are both in saturation.

④ M_1 in triode region, M_2 in saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \times (V_{DD} - V_{in} - |V_{TH2}|)^2 \quad (4)$$
$$6 \left[2(V_{in} - 0.4)V_{out} - V_{out}^2 \right] = 7(1.3 - V_{in})^2$$

If V_{out} falls sufficiently, M_1 enters the triode region. That is, if

$V_{in} = V_{out} + V_{TH1}$, then M_1 is about to enter the triode region.

By substituting V_{in} with $V_{out} + 0.4$ in (4), we have:

$$6 \left[2V_{out}^2 - V_{out}^2 \right] = 7(0.9 - V_{out})^2$$

$$V_{out} = 0.467, \quad V_{in}^0 = 0.867$$

As channel length modulation has been neglected in this calculation the value of input voltage that makes CMOS inverter transition from region (2) to (3) is

the same as that which makes inverter transition from region (3) to (4).


The slope in region (3) is infinit; however, we assume a finite slope in that region to emphasize the behavior of inverter as to producing a high gain.

⑤ M_1 in triode region, M_2 off

$$I_{D2} = 0, \quad I_{D1} = 0$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = 0 \rightarrow V_{out} = 0$$

22.

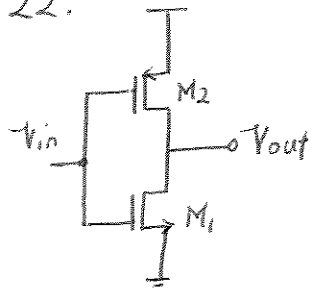

$$V_{in} = V_{out} = 0.5 V$$

M_1 and M_2 are both in saturation region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right)_1 (0.5 - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L} \right)_2 (1.8 - 0.5 - 0.5)^2$$

$$\left(\frac{W}{L} \right)_1 / \left(\frac{W}{L} \right)_2 = 32$$

23. The value of the trip point has to be larger than the threshold voltage of NMOS transistor, 0.4 V . Therefore, 0.3 V Cannot be the trip point of such an inverter.

24.


(a) If the inverter exhibits a very high voltage gain around the trip point, the range of input voltage values which guarantees that M_1 and M_2 are in saturation region is very narrow. Therefore this range can be fairly approximated with only one value of input voltage.

(b) $(W/L)_1 = 3/0.18$ and $(W/L)_2 = 7/0.18$

To calculate the minimum input voltage at which both transistors operate in saturation we assume

M_1 saturation

M_2 triode

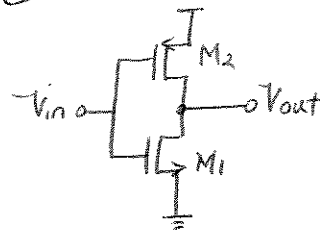

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|)(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2 \right]$$

$V_{out} = V_{in} + |V_{TH2}|$ places M_2 at the edge of saturation

$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times \left[2(1.8 - V_{in} - 0.5)(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)^2 \right]$$

$$\boxed{V_{in, \min} = 0.867}$$

To calculate $V_{in, \max}$, we assume that M_1 and M_2 are in triode and saturation region respectively

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH1})(V_{out} - V_{out}) \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

When M_1 is just going to leave the saturation and enters the triode region

$$V_{in} = V_{out} + 0.4^{(V_{TH1})}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times \left[2(V_{out} + V_{TH1} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{7}{0.18} \times (V_{DD} - V_{in} - |V_{TH2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (V_{DD} - V_{out} - V_{TH1} - |V_{TH2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (0.9 - V_{out})^2$$

$$V_{out} = 0.467 \text{ V}, \quad \boxed{V_{in} = 0.867 \text{ V}_{\max}}$$

To find the trip point, M_1 and M_2 are assumed to be in saturation.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$


$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times (1.8 - V_{in} - 0.5)^2$$

$$\boxed{V_{in}^0 = 0.867 \text{ (a) trip point}}$$







$$V_{in, \text{trip}} - V_{in, \min} = 0$$

$$V_{in, \max} - V_{in, \text{trip}} = 0$$

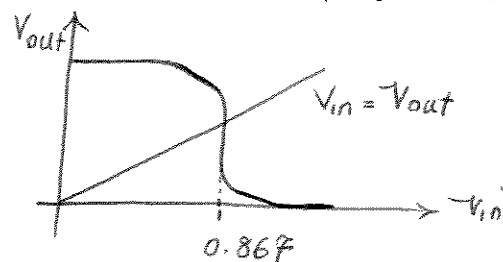
This result is not surprising because VTC of inverter has infinite slope at the region where both M_1 and M_2 are in saturation region



25.

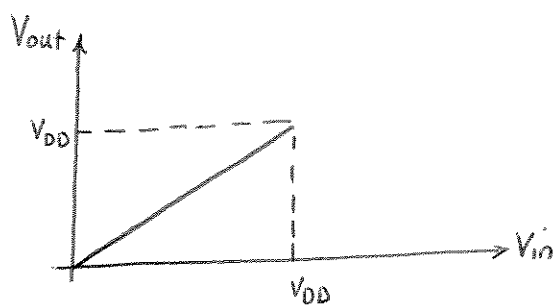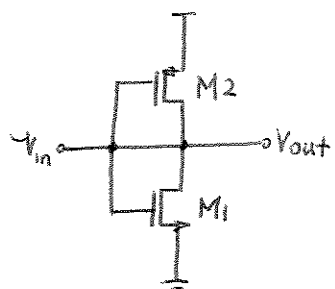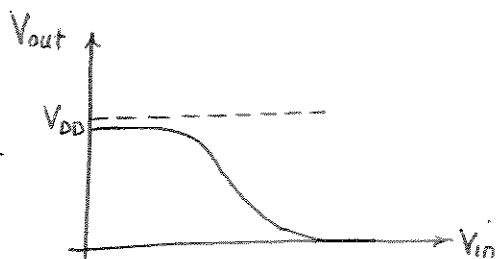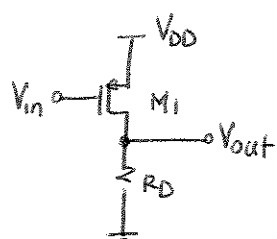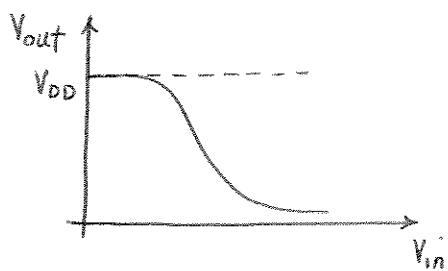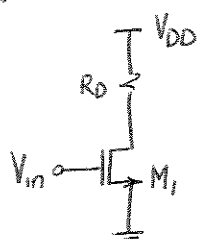

26.

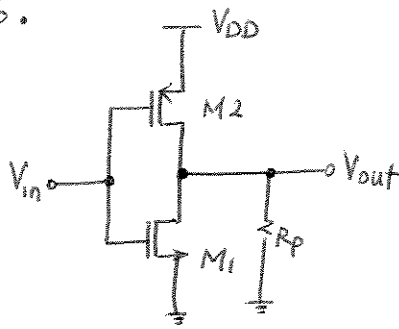


$$R_p = 2K$$

$$V_{OL}, V_{OH}, V_{in, trip} = ?$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

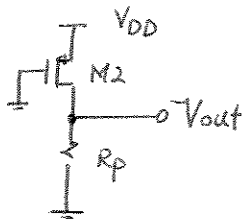To calculate V_{OH} , V_{in} is assumed to be 0V



$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$I_{D2} = \frac{V_{out}}{R_p}$$

$$\frac{V_{out}}{R_p} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$V_{out} - 0.28 V_{out} - 1.44 = 0$$

$$V_{out} = V_{OH} = 1.348 V$$

$$V_{OL} = 0 \text{ because } M_2 \text{ is off for } V_{in} = V_{DD}$$


(a) trip point $V_{in} = V_{out}$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{2000}$$

$$0.05 V_{out}^2 + 0.59 V_{out} - 0.3745 = 0 \rightarrow V_{in} = V_{out} = 0.6 V$$

27.

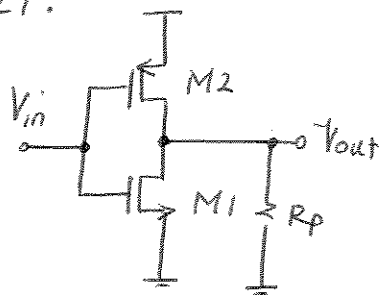

$$R_p = 2K$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

$$V_{in}^0 = V_{out} = 0.6V \text{ (a) trip point}$$

With R_p

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{2000}$$

$$0.05 V_{out}^2 + 0.59 V_{out} - 0.3745 = 0$$

$$V_{in} = V_{out} = 0.6V$$

$$I_{D1} = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (0.6 - 0.4)^2$$

$$I_{D1} = 3.33 \times 10^{-5} A$$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} = 3.33 \times 10^{-5} + \frac{0.6}{2000}$$

$$I_{D2} = 3.35 \times 10^{-4} A$$

$$g_{m1} = \frac{2I_{D1}}{V_{eff1}} = \frac{2 \times 3.33 \times 10^{-5}}{(0.6 - 0.4)} \rightarrow g_{m1} = 3.3 \times 10^{-3} S$$

$$g_{m2} = \frac{2I_{D2}}{V_{eff2}} = \frac{2 \times 3.35 \times 10^{-4}}{(1.8 - 0.6 - 0.5)} \rightarrow g_{m2} = 9.4 \times 10^{-3} S$$

$$A_V = -(g_{m1} + g_{m2}) \times R_p$$


$$A_V = - (3.3 \times 10^{-3} + 9.4 \times 10^{-3}) \times 2000$$

$$A_V = -25.4$$

Without R_p

$$A_V \Rightarrow -\infty$$

28.

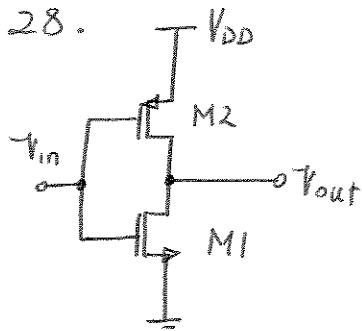

$$\left(\frac{W}{L}\right)_1 = 5/0.18$$

$$\left(\frac{W}{L}\right)_2 = 11/0.18$$

$$NM_L \text{ and } NM_H = ?$$

To calculate NM_L , M_1 and M_2 are assumed to operate in the saturation and triode region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[-2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \times \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right]$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1, \quad V_{in} = V_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] \quad (2)$$

Obtaining V_{OH} from (2) and substituting in (1) yields:

$$V_{IL} = \frac{2\sqrt{\alpha} (V_{DD} - V_{TH1} - |V_{TH2}|)}{(\alpha - 1)\sqrt{\alpha + 3}} - \frac{V_{DD} - \alpha V_{TH1} - |V_{TH2}|}{\alpha - 1}$$

$$\alpha = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} = \frac{100}{50} \times \frac{5}{11} = \frac{10}{11}$$

$$V_{IL} = \frac{2\sqrt{10/11} (1.8 - 0.4 - 0.5)}{(10/11 - 1)\sqrt{10/11 + 3}} - \frac{1.8 - (10/11) \times 0.4 - 0.5}{10/11 - 1}$$

$$\boxed{V_{IL} = 0.7516 \text{ V}}$$

To determine NM_H , M_1 and M_2 are assumed to operate in the triode and saturation region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}| - V_{in})^2 \quad (3)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = -\mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times (V_{DD} - V_{in} - |V_{TH2}|)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \text{ yields}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 [V_{out} - V_{in} + V_{TH1} + V_{out}] = -\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)$$

$$100 \times 5 \times [2V_{out} - (V_{in} - 0.4)] = -50 \times 11 \times (1.8 - 0.5 - V_{in})$$

$$V_{out} = 1.05V_{in} - 0.915 \quad (4)$$

Substituting (4) in (3) yields an equation versus V_{in} as follows:

$$10 \times [2(V_{in} - 0.4)(1.05V_{in} - 0.915) - (1.05V_{in} - 0.915)^2] = 11 \times (1.3 - V_{in})^2$$

$$1.025V_{in}^2 - 21.115V_{in} + 19.64225 = 0$$

$$V_{in} = V_{IH} = 0.9765 \text{ V}$$

$$NM_H = V_{DD} - V_{IH}$$

$$\boxed{NM_H = 0.823 \text{ V}}$$

$$29. \quad NM_L = 0.6 \text{ V}$$

$$(W/L)_1 / (W/L)_2 = ?$$

$$V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}$$

$$0.6 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - a \cdot 0.4 - 0.5}{a-1}$$

$$a = 3\sqrt{\frac{a}{a+3}} - \frac{1.3 - 0.4a}{0.6} + 1$$

$$a = \frac{a+3}{9} \times \left[a-1 + \frac{1.3 - 0.4a}{0.6} \right]^2$$

$$\boxed{a=1}$$

$$(W/L)_1 / (W/L)_2 = \frac{\mu_p C_{ox}}{\mu_n C_{ox}} = \frac{1}{2}$$


$$\boxed{(W/L)_1 / (W/L)_2 = \frac{1}{2}}$$

$$30. V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$

$$a \rightarrow 0 \quad V_{IL} = V_{DD} - |V_{TH2}|$$
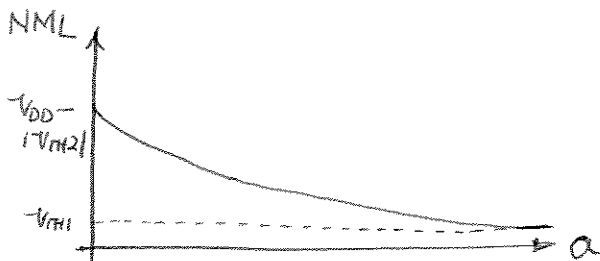
$$a \rightarrow \infty \quad V_{IL} = V_{TH1}$$




If $a = \frac{\mu_n}{\mu_p} \times \frac{(W/L)_1}{(W/L)_2} \rightarrow 0$, it implies that PMOS transistor is


extremely stronger than NMOS. Therefore, as V_{in} increases from

0V, the output of inverter stays at V_{DD} until input reaches $V_{DD} - |V_{TH2}|$.

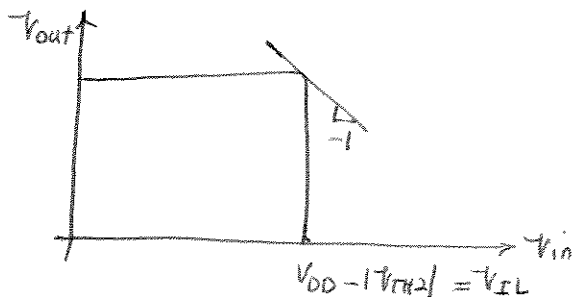At that point, PMOS is cut off and V_{out} sharply drops to 0V.



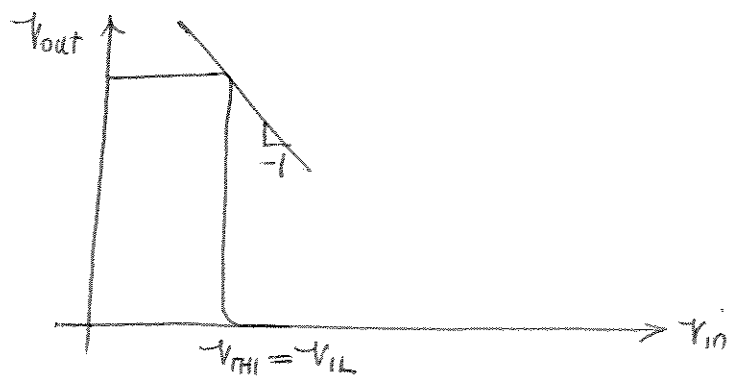When $a \rightarrow \infty$, NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to 0V.




31.

$$NM_H = V_{DD} - \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{1+3a}} + \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$


$$a \rightarrow 0 \quad NM_H = |V_{TH2}|, \quad V_{IH} = V_{DD} - |V_{TH2}|$$
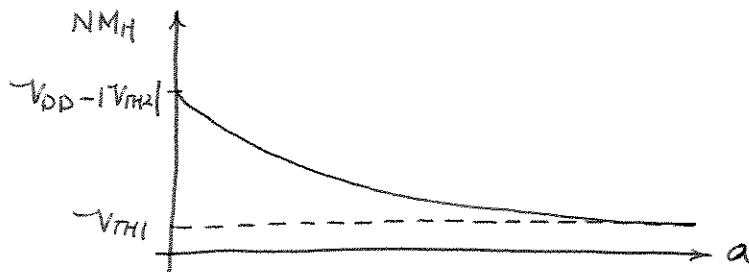
$$a \rightarrow \infty \quad NM_H = V_{DD} - V_{TH1}, \quad V_{IH} = V_{TH1}$$




If $a = \frac{\mu_n}{\mu_p} \times \frac{(W/L)_1}{(W/L)_2} \rightarrow 0$, it implies that PMOS transistor is much

stronger than NMOS. Therefore, as V_{in} increases from 0V, the output of inverter remains at V_{DD} until input reaches $V_{DD} - |V_{TH2}|$. At that point, PMOS is cutoff and V_{out} sharply drops to 0V.

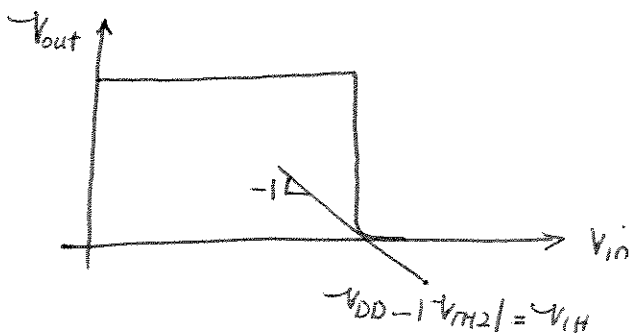


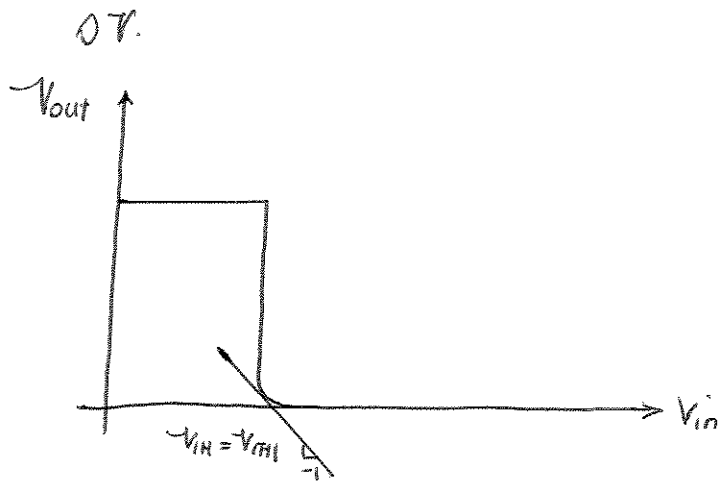When " a " approaches infinity, NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to



Note that the separation between V_{ih} and V_{il} depends on the slope of VTC in the transition region. If " a " approaches either "0" or infinity, VTC exhibits infinite gain in its transition region. Therefore V_{il} and V_{ih} coincide.

32.

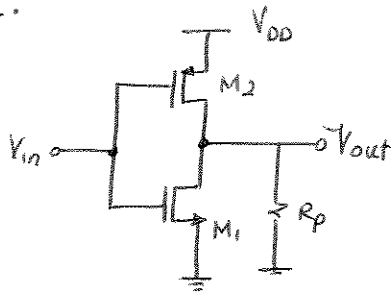

$$R_p = 2K$$

$$NM_L, NM_H = ?$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

To calculate NM_L , M_1 and M_2 are assumed to be in the saturation and triode region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad (V_{in} = V_{IL})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{R_p} \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1, \quad V_{in} = V_{IL}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[-2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right] =$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) + \frac{1}{R_p} \frac{\partial V_{out}}{\partial V_{in}}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) - \frac{1}{R_p} = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] \quad (2)$$

$$\boxed{V_{OH} = 1.01 V_{IL} + 0.73}$$

Replacing V_{out} in (1) with its equivalent versus V_{IL} obtained from (2) yields:

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - V_{IL} - |V_{TH2}|)(V_{DD} - 1.1V_{IL} - 0.73) - (V_{DD} - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{IL} - V_{TH1})^2 + \frac{1.1V_{IL} + 0.73}{R_p}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \left[2(1.8 - V_{IL} - 0.5)(1.8 - 1.1V_{IL} - 0.73) - (1.8 - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} (V_{IL} - 0.4)^2 + \frac{1.1V_{IL} + 0.73}{2000}$$

$$-52.5 \times 10^{-3} V_{IL} - 0.6195 V_{IL} + 0.229875 = 0$$

$$\boxed{V_{IL} = NML = 0.36 V} < V_{TH1} \text{ NOT Acceptable!}$$

This is less than threshold voltage of M_1 ; therefore, this answer is not acceptable. It means that M_1 is off and should be left out in this calculation.

$$I_{D1} = 0, I_{D2} = \frac{V_{out}}{R_p}$$

$$\mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] = -\frac{1}{R_p}$$

$$50 \times 10^{-6} \times \frac{5}{0.18} \times \left[2V_{OH} - V_{IL} - 0.5 - 1.8 \right] = -\frac{1}{2000}$$

$$\boxed{V_{OH} = V_{out} = 0.5V_{IL} + 0.97} \quad (3)$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \times \left[2(1.8 - V_{IL} - 0.5)(1.8 - 0.5V_{IL} - 0.97) - (1.8 - 0.5V_{IL} - 0.97)^2 \right] =$$

$$\frac{0.5V_{IL} + 0.97}{2000}$$

$$0.1875 V_{IL}^2 - 0.6225 V_{IL} + 0.192675 = 0$$

$$\boxed{V_{IL} = NML = 0.345 V}$$

To determine NM_H , M_1 and M_2 are assumed to operate in the triode and Saturation region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad (V_{in} = V_{IH})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] + \frac{V_{out}}{R_p} \quad (4)$$

$$-\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] + \frac{\partial V_{out}}{\partial V_{in}} \frac{1}{R_p}$$

$$-\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[V_{out} - V_{in} + V_{TH1} + V_{out} \right] - \frac{1}{R_p}$$

$$-50 \times 10^{-6} \times \frac{5}{0.18} \times (1.8 - V_{in} - 0.5) = 100 \times 10^{-6} \times \frac{3}{0.18} \times (2V_{out} - V_{in} + 0.4) - \frac{1}{2000}$$

$$\boxed{V_{out} = \frac{0.1V_{in} + 0.59}{1.2}} \quad (5)$$


Combining equs (4) and (5) yields:

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} (1.8 - V_{in} - 0.5)^2 = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \left[2(V_{in} - 0.4) \frac{0.1V_{in} + 0.59}{1.2} - \frac{(0.1V_{in} + 0.59)^2}{1.2^2} \right] + \frac{0.1V_{in} + 0.59}{1.2 \times 2000}$$

$$-0.291 V_{in}^2 + 1.3182 V_{in} - 0.75531 = 0$$

$$V_{in} = V_{IH} = 0.673 \text{ V} \rightarrow \boxed{NM_H = V_{DD} - V_{IH} = 1.127 \text{ V}}$$

33.

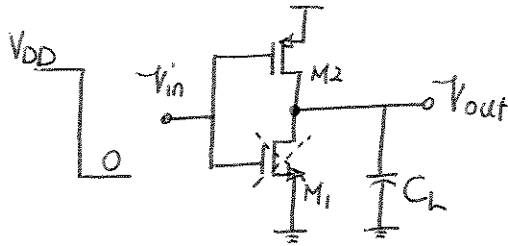

$$V_{out}(t=0) = 0$$

$$(W/L)_2 = 6/0.18$$

$$C_L = 50 \text{ fF}$$

$0 < V_{out} < |V_{TH2}|$; M_2 in the saturation

$$C_L \frac{dV_{out}}{dt} = -I_{D2} = -\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{6}{0.18} (1.8 - 0.5)^2$$

$$= 1.4 \times 10^{-3} \text{ A}$$

$$V_{out}(t) = \frac{I_{D2}}{C_L} \times t$$

$$|V_{TH2}| = \frac{I_{D2}}{C_L} \cdot T_1 \rightarrow T_1 = \frac{C_L \times |V_{TH2}|}{I_{D2}} = 50 \times 10^{-6} \times \frac{1.4 \times 10^{-3}}{1.4 \times 10^{-3}} \times 0.5$$

$$T_1 = 17.75 \text{ pS}$$

$|V_{TH2}| < V_{out} < V_{DD}/2$, M_2 in triode

$$C_L \frac{dV_{out}}{dt} = -I_{D2} = -\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH2}|)(-V_{out} + V_{DD}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(-V_{out} + V_{DD}) - (V_{DD} - V_{out})^2} = -\frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

$$\frac{1}{(V_{DD} - V_{out}) \left[2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out}) \right]} = \frac{1}{2(V_{DD} - |V_{TH2}|)} \left[\frac{1}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{1}{V_{DD} - V_{out}} \right]$$

$$\frac{1}{2(V_{DD} - |V_{TH2}|)} \left[\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{dV_{out}}{V_{DD} - V_{out}} \right] = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 dt$$

$$\ln \frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t + C$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = K \cdot \exp \left[\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t \right]$$

Time origin is assumed to be at $t = T_1 = 17.75 \mu s$

$$V_{out}(t=0) = |V_{TH2}| \rightarrow K=1$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t}$$

$$\begin{aligned} \textcircled{a} V_{out} = V_{DD}/2 \quad T_2 &= \frac{\ln(3 - 4|V_{TH2}|/V_{DD})}{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)} \\ &= \frac{\ln(3 - 4 \times 0.5/1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-15}} \times \frac{6}{0.18} \times (1.8 - 0.5)} \end{aligned}$$

$$\boxed{T_2 = 1.467 \times 10^{-11}}$$

$$T_0 \rightarrow V_{DD/2} = T_1 + T_2 = 17.75 + 14.67$$

$$\boxed{T_0 \rightarrow V_{DD/2} = 32.43 \mu s}$$

34. $|V_{TH2}| < V_{out} < 0.95V_{DD}$ M_2 in Triode

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|) t}$$

$$\begin{aligned} \textcircled{a} V_{out} = 0.95V_{DD}, \quad T_2 &= \frac{\ln(39 - 40|V_{TH2}|/V_{DD})}{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \\ &= \frac{\ln(39 - 40 \times 0.5/1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-15}} \times \frac{6}{0.18} \times (1.8 - 0.5)} \end{aligned}$$

$$T_2 = 7.68 \times 10^{-11}$$


$T_1 = 17.75 \text{ ps}$ from previous problem

$$T_{0 \rightarrow 0.95V_{DD}} = T_1 + T_2 = 17.75 + 76.8$$

$$T_{0 \rightarrow 0.95V_{DD}} = 94.55 \text{ ps}$$

$$(T_{0 \rightarrow 0.95V_{DD}}) / (T_{0 \rightarrow V_{DD}/2}) \approx 3$$

35.

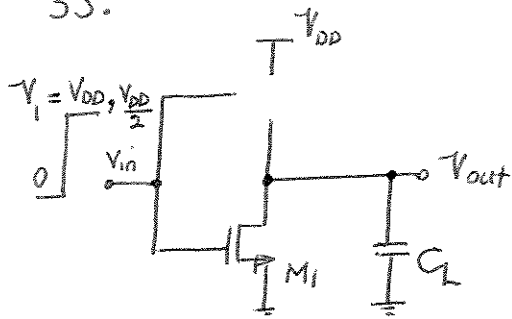

$$V_{out}(t=0) = V_{DD}$$

$$C_L = 30 \text{ fF}$$

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$


$$T_{V_{DD} \rightarrow V_{DD/2}} = ?$$

$$\left(\frac{W}{L}\right)_2 = \text{Not necessary}$$

$$V_i = V_{DD} \nmid V_{DD/2}$$

$$(a) V_i = V_{DD}$$
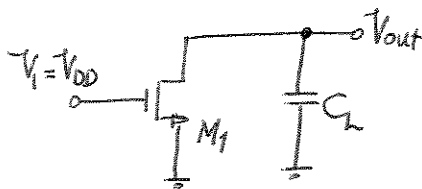
$$V_{DD} - V_{TH1} \leq V_{out} \leq V_{DD} \quad M_1 \text{ Saturation}$$



$$\frac{V_{DD}}{2} \leq V_{out} \leq V_{DD} - V_{TH1} \quad M_1 \text{ Triode}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2 = 5.44 \times 10^{-4} \text{ A}$$

$$dV_{out} = -\frac{I_{D1}}{C_L} \cdot dt$$

$$V_{out}(t) - V_{DD} = -\frac{I_{D1}}{C_L} t \rightarrow V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} \text{ s}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2} = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 dt$$

$$\frac{1}{[2(V_{DD} - V_{TH1}) - V_{out}] V_{out}} = \frac{1}{2(V_{DD} - V_{TH1})} \left[\frac{1}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{1}{V_{out}} \right]$$

$$\frac{1}{2(V_{DD}-V_{TH1})} \left[\frac{dV_{out}}{2(V_{DD}-V_{TH1})-V_{out}} + \frac{dV_{out}}{V_{out}} \right] = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 dt$$

$$-\ln \left[2(V_{DD}-V_{TH1})-V_{out} \right] + \ln V_{out} = -\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 (V_{DD}-V_{TH1}) t + C$$

$$\frac{V_{out}}{2(V_{DD}-V_{TH1})-V_{out}} = K \cdot \exp \left[-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 (V_{DD}-V_{TH1}) t \right]$$

$$V_{out}(t=0) = V_{DD}-V_{TH1} \quad \text{Note that time origin is assumed to be } 2.2 \times 10^{-11}$$

$$K=1 \rightarrow$$

$$\frac{V_{out}}{2(V_{DD}-V_{TH1})-V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 (V_{DD}-V_{TH1}) t}$$

$$V_{out} = V_{DD}/2 \rightarrow \frac{V_{DD}/2}{2(V_{DD}-V_{TH1})-V_{DD}/2} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 (V_{DD}-V_{TH1}) T_{(V_{DD}-V_{TH1}) \rightarrow V_{DD}/2}}$$


$$T_{(V_{DD}-V_{TH1}) \rightarrow V_{DD}/2} = \frac{\ln \left(3 - \frac{4V_{TH1}}{V_{DD}} \right)}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 (V_{DD}-V_{TH1})}$$

$$= \frac{\ln(3 - 4 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} \times (1.8 - 0.4)} = 2.88 \times 10^{-11} \text{ s}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = T_{V_{DD} \rightarrow V_{DD}-V_{TH1}} + T_{(V_{DD}-V_{TH1}) \rightarrow V_{DD}/2}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = 5 \times 10^{-11} = 50.86 \text{ pS}$$

$$(b) V_i = V_{DD}/2$$

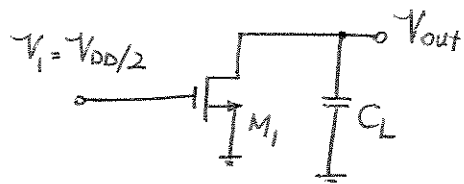

$$V_{DD}/2 - V_{TH1} < V_{out} < V_{DD} \quad M_1 \text{ in Saturation}$$

$$V_{DD}/2 < V_{out} < V_{DD} \quad M_1 \text{ in Saturation}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD}/2 - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (0.9 - 0.4)^2$$


$$= 6.944 \times 10^{-5}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD}/2 = V_{DD} - \frac{I_{D1}}{C_L} \times T_{(V_{DD} \rightarrow V_{DD}/2)} \Rightarrow T_{(V_{DD} \rightarrow V_{DD}/2)} = \frac{(V_{DD}/2) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD}/2)} = 3.888 \times 10^{-10}$$

36.

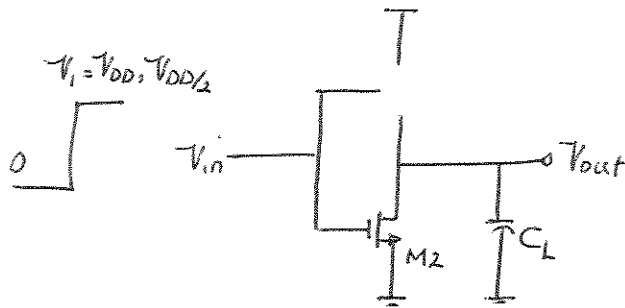

$$V_{out}(0) = V_{DD}$$

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$

$$C_L = 30 \text{ fF}$$

$$T_{V_{DD}} \rightarrow 0.05 V_{DD} = ?$$

(a) $V_i = V_{DD}$ $V_{DD} - V_{TH1} < V_{out} < V_{DD}$ M_1 in Saturation

$0.05 V_{DD} < V_{out} < V_{DD} - V_{TH1}$ M_1 in Triode

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2$$

$$= 5.44 \times 10^{-4} \text{ A}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} \text{ s}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \left[\frac{dV_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{dV_{out}}{V_{out}} \right] = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 dt$$

$V_{out}(t=0) = V_{DD} - V_{TH1}$ Note that time origin is assumed to be $2.2 \times 10^{-11} \text{ s}$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1}) t}$$

$$V_{out} = 0.05 V_{DD}$$

$$\frac{0.05 V_{DD}}{2(V_{DD} - V_{TH1}) - 0.05 V_{DD}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1}) T_{(V_{DD} - V_{TH1}) \rightarrow 0.05 V_{DD}}}$$

$$T_{(V_{DD} - V_{TH1}) \rightarrow 0.05 V_{DD}} = \frac{\ln(39 - 40 V_{TH1} / V_{DD})}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})}$$

$$= \frac{\ln(39 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{-15} \times \frac{1}{0.18} (1.8 - 0.4)}$$

$$T_{(V_{DD} - V_{TH1}) \rightarrow 0.05 V_{DD}} = 131.33 \text{ pS}$$

$$T_{(V_{DD} \rightarrow 0.05 V_{DD})} = T_{(V_{DD} \rightarrow V_{DD} - V_{TH1})} - T_{(V_{DD} - V_{TH1} \rightarrow 0.05 V_{DD})}$$

$$= 2.2 \times 10^{-11} + 1.3133 \times 10^{-10}$$

$$T_{(V_{DD} \rightarrow 0.05 V_{DD})} = 153.33 \text{ pS}$$

(b) $V_i = V_{DD}/2$ $V_{DD/2} - V_{TH1} < V_{out} < V_{DD}$ M_1 in Saturation

$0.05 V_{DD} < V_{out} < V_{DD/2} - V_{TH1}$ M_1 in Triode

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (0.9 - 0.4)^2$$

$$= 6.944 \times 10^{-5} \text{ A}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD/2} - V_{TH1} = V_{DD} - \frac{I_{D1}}{C_L} T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} = \frac{(V_{DD/2} + V_{TH1}) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} = 5.616 \times 10^{-10}$$

$$\text{for } 0.05V_{DD} < V_{out} < V_{DD/2} - V_{TH1}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD/2} - V_{TH1})V_{out} - V_{out}^2 \right]$$

$$\frac{V_{out}}{2(V_{DD/2} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1}) t}$$

$$V_{out} = 0.05V_{DD} \rightarrow \frac{0.05V_{DD}}{2(V_{DD/2} - V_{TH1}) - 0.05V_{DD}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1}) \times T}$$

$$\begin{aligned} T_{(V_{DD/2} - V_{TH1} \rightarrow 0.05V_{DD})} &= \frac{\ln(19 - 40V_{TH1}/V_{DD})}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1})} \\ &= \frac{\ln(19 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} (0.9 - 0.4)} \\ &= 2.5 \times 10^{-10} \end{aligned}$$


$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} + T_{(V_{DD/2} - V_{TH1} \rightarrow 0.05V_{DD})}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = 5.616 \times 10^{-10} + 2.5 \times 10^{-10} = 811.5 \text{ pS}$$

By decreasing V_{in} from V_{DD} to $V_{DD}/2$, the time it takes the output to reach $0.05V_{DD}$ will be 5.3 time larger!

$$\frac{T(V_{DD} \rightarrow 0.05V_{DD})(V_{in}=V_{DD})}{T(V_{DD} \rightarrow 0.05V_{DD})(V_{in}=V_{DD}/2)} = \frac{811.5 \text{ p}}{153.33 \text{ p}} \approx 5.3$$

37.

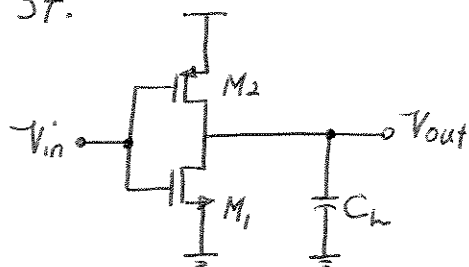

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$

$$\left(\frac{W}{L}\right)_2 = 3/0.18$$

$$C_L = 80 \text{ fF}$$

$$T_{PHL}, T_{PLH} = ?$$

To calculate T_{PLH}

$$0 < V_{out} < |V_{TH2}| \quad M_2 \text{ in Saturation}$$

$$|V_{TH2}| < V_{out} < V_{DD}/2 \quad M_2 \text{ in Triode}$$

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$V_{out}(t) = \frac{|I_{D2}|}{C_L} t$$

$$= \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2 t$$

$$V_{out}(T_{PLH1}) = |V_{TH2}|$$

$$T_{PLH1} = \frac{|V_{TH2}| \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

for M_2 operating in Triode region

$$C_L \frac{dV_{out}}{dt} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

Defining $V_{DD} - V_{out} = u$ and noting that $\int \frac{du}{au - u^2} = \frac{1}{a} \ln \frac{u}{a-u}$,

$$\left. \frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \right|_{V_{out}=V_{DD/2}}^{V_{out}=|V_{TH2}|} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 T_{PLH2}$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}}\right)$$

$$T_{PLH} = T_{PLH1} + T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}}\right) \right]$$

$$T_{PLH} = \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} (1.8 - 0.5)} \left[\frac{2 \times 0.5}{1.8 - 0.5} + \ln \left(3 - 4 \frac{0.5}{1.8}\right) \right]$$

$$T_{PLH} = 1.0377 \times 10^{-10}$$

To calculate T_{PHL}

$V_{DD} - V_{TH1} < -V_{out} < V_{DD}$ M_1 in Saturation

$V_{DD/2} < V_{out} < V_{DD} - V_{TH1}$ M_1 in Triode

$$T_{PHL1} = \frac{-\Delta V_{out} \times C_L}{I_{D1}} = \frac{-V_{TH1} \times C_L}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2}$$

after this point in time.

$$C_L \frac{dV_{out}}{dt} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$V_{out}(t=0) = V_{DD} - V_{TH1}$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ V_{out} = V_{DD} - V_{TH1} \end{array} \right. = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 T_{HL2}$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})} \times \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})} \times \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$T_{PHL} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)} \times \left[\frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \frac{0.4}{1.8} \right) \right]$$

$$T_{PHL} = 1.3563 \times 10^{-10}$$

$$38. \quad V_{DD} = 1.8 + 1.8 \times 0.1 = 1.98$$

$$T_{PLH} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} \times (1.98 - 0.5)} \left[\frac{2 \times 0.5}{1.98 - 0.5} + \ln \left(3 - 4 \times \frac{0.5}{1.98} \right) \right]$$

$$\boxed{T_{PLH} = 8.846 \times 10^{-11}}$$

$$\text{Decrease in } T_{PLH} = \left| \frac{8.846 \times 10^{-11} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100$$

$$= 14.75\%$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (1.98 - 0.4)} \left[\frac{2 \times 0.4}{1.98 - 0.4} + \ln \left(3 - 4 \frac{0.4}{1.98} \right) \right]$$

$$\boxed{T_{PHL} = 1.1767 \times 10^{-10}}$$

$$\text{Decrease in } T_{PHL} = \left| \frac{1.1767 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100$$

$$= 13.24\%$$

$$39. V_{DD} = 0.9 \text{ V}$$

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$T_{PLH} = \frac{\Delta V_{out} \times C_L}{I_{D2}} = \frac{(V_{DD}/2) \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2}$$

$$= \frac{0.45 \times 80 \times 10^{-15}}{\frac{1}{2} \times 50 \times 10^{-6} \times \frac{3}{0.18} \times (0.9 - 0.5)^2}$$

$$T_{PLH} = 5.4 \times 10^{-10} = 540 \text{ pS}$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (0.9 - 0.4)} \times \left[\frac{2 \times 0.4}{0.9 - 0.4} + \ln \left(3 - 4 \frac{0.4}{0.9} \right) \right]$$

$$T_{PHL} = 5.186 \times 10^{-10} = 518.6 \text{ pS}$$

$$\text{Increase in } T_{PLH} = \left| \frac{5.4 \times 10^{-10} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100$$

$$= 420.38\%$$

$$\text{Increase in } T_{PHL} = \left| \frac{5.186 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100$$

$$= 282.36\%$$

$$40. T_{PLH} = T_{PHL} = 80 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

$$\left(\frac{W}{L}\right)_1, \left(\frac{W}{L}\right)_2 = ?$$

$$T_{PLH} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{50 \times 10^{-6} \times (1.8 - 0.5) \times \left(\frac{W}{L}\right)_2} \times \left[\frac{2 \times 0.5}{1.8 - 0.5} + \ln \left(3 - 4 \times \frac{0.5}{1.8} \right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{2.4}{0.18}}$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{100 \times 10^{-6} \times (1.8 - 0.4) \times \left(\frac{W}{L}\right)_1} \times \left[\frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \times \frac{0.4}{1.8} \right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_1 = \frac{1}{0.18}}$$

41.

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$V_{TH1} = 0.4$$

$$\frac{2V_{TH1}}{V_{DD} - V_{TH1}} = \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \rightarrow V_{DD} = V_{TH1} \left[1 + \frac{2}{\ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right)} \right]$$

$$V_{TH1} = 0.4 \rightarrow \boxed{V_{DD} = 1.57}$$

$$\frac{2V_{TH1}}{V_{DD} - V_{TH1}} = 0.1 \times \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \rightarrow V_{DD} = V_{TH1} \left[1 + \frac{20}{\ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right)} \right]$$

$$V_{TH1} = 0.4 \rightarrow \boxed{V_{DD} = 8.16}$$

$$42. \left(\frac{W}{L} \right)_1 = 1/0.18 \quad T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$T_{PHL} = 100 \text{ pS}$$

$$C_L = 80 \text{ fF}$$

$$V_{DD} = ?$$

$$100 \times 10^{-12} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (V_{DD} - 0.4)} \times \left[\frac{2 \times 0.4}{V_{DD} - 0.4} + \ln \left(3 - 4 \frac{0.4}{V_{DD}} \right) \right]$$

$$V_{DD} = 0.4 + 1.44 \left[\frac{0.8}{V_{DD} - 0.4} + \ln \left(3 - \frac{1.6}{V_{DD}} \right) \right]$$

$$\boxed{V_{DD} = 2.22}$$

43. $T_{PHL} = 120 \text{ ps}$ $(W/L)_1 = ?$

$C_L = 90 \text{ fF}$ $V_{TH1} = ?$

$V_{DD} = 1.8$

$T_{PHL} = 160 \text{ ps}$ $T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$

$V_{DD} = 1.5 \text{ V}$

$C_L = 90 \text{ fF}$

$$120 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.8 - V_{TH1})} \times \left[\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.8} \right) \right] \quad (1)$$

$$160 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.5 - V_{TH1})} \times \left[\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right) \right] \quad (2)$$

Dividing Equations (1) and (2) yields:

$$0.75 = \frac{1.5 - V_{TH1}}{1.8 - V_{TH1}} \times \frac{\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.8} \right)}{\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right)}$$

$$V_{TH1} = 1.8 - \left(\frac{1.5 - V_{TH1}}{0.75} \right) \times \frac{\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.8} \right)}{\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right)}$$

This equation does not lead to a real value for V_{TH1} so we use another derivation

$$V_{TH1} = 0.45 \times \left\{ 3 - e^{\left[0.75 \frac{1.8 - V_{TH1}}{1.5 - V_{TH1}} \times \left[\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right) \right] - \frac{2V_{TH1}}{1.8 - V_{TH1}} \right]} \right\}$$

$$V_{TH1} = 0.39$$

$$\left(\frac{W}{L}\right)_1 = \frac{1.26}{0.18}$$

44.

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$\ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right)$ is meaningless if $V_{DD} < 4V_{TH1}/3$.

Let's consider the case where $V_{DD} = \frac{4}{3}V_{TH1}$; then, T_{PHL} is the time it takes

for the output to drop from $V_{DD} = \frac{4}{3}V_{TH1}$ to $\frac{V_{DD}}{2} = \frac{2}{3}V_{TH1}$. However,


$$(V_{in}^0 = V_{DD} = \frac{4}{3}V_{TH1}) - (V_{out} = \frac{2}{3}V_{TH1}) = \frac{2}{3}V_{TH1} < V_{TH1}. \text{ In other words, } M_1$$

never enters the triode region in the region where T_{PHL} is calculated. The

logarithmic term is derived from equation in which M_1 was assumed to be in

Triode region. Therefore the logarithmic term is meaningless for $V_{DD} < \frac{4}{3}V_{TH1}$.

45.

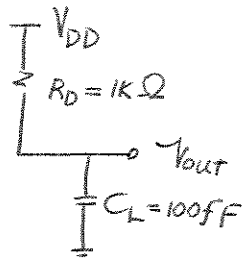

$$V_{R_D} = (V_{DD} - V_{out})$$

$$I_{R_D} = C_L \frac{dV_{out}}{dt}$$

$$P_{R_D}(t) = V_{R_D} \cdot I_{R_D} = C_L (V_{DD} - V_{out}) \frac{dV_{out}}{dt}$$

$$\begin{aligned} E_{R_D} &= \int_{t=0}^{\infty} P_{R_D}(t) dt = \int_{V_{out}=0}^{V_{DD}} (V_{DD} - V_{out}) dV_{out} = \frac{1}{2} C_L V_{DD}^2 \\ &= \frac{1}{2} \times 100 \times 10^{-15} \times (1.8)^2 \end{aligned}$$

$$E_{R_D} = 0.162 \text{ pJ}$$

46. 10^6 Gates

$$f = 2 \text{ GHz}$$

20% of gates switch in every clock cycle

$C_L = 20 \text{ fF}$ for each gate

$$P_{av} = ?$$

$$P_{av, \text{gate}} = f_{in} C_L V_{DD}^2$$

$$P_{av, \text{total}} = 0.2 \times 10^6 \times f_{in} C_L V_{DD}^2$$

$$= 0.2 \times 10^6 \times 2 \times 10^9 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av, \text{total}} = 25.92 \text{ W}$$

$$47. f = 2 \text{ GHz}$$

5×10^6 Transistors with $W = 1 \mu\text{m}$, $L = 0.18 \mu\text{m}$, $C_{ox} = 10 \text{ fF}/\mu\text{m}^2$

$$C_{\text{gate}} = WLC_{ox}$$

$$C_{\text{Load}} = 5 \times 10^6 C_{\text{gate}}$$

$$= 5 \times 10^6 \times WLC_{ox}$$

$$= 5 \times 10^6 \times 1 \mu\text{m} \times 0.18 \mu\text{m} \times 10 \text{ fF}/\mu\text{m}^2$$

$$C_{\text{Load}} = 9 \text{ pF}$$

$$P_{av} = f_{in} C_L V_{DD}^2$$

$$= 2 \times 10^9 \times 9 \times 10^{-9} \times (1.8)^2$$

$$P_{av} = 58.32 \text{ W}$$

48.

$$V_{DD} = V_{DD} + 0.1 V_{DD} = 1.98$$

$$\left(\frac{W}{L}\right)_1 = 2/0.18$$

$$\left(\frac{W}{L}\right)_2 = 4/0.18$$

$$I_{Peak} \Big|_{V_{DD}=1.8} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{V_{DD}}{2} - V_{TH1}\right)^2 \left(1 + \lambda_1 \frac{V_{DD}}{2}\right)$$

$$= \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.9 - 0.4)^2$$

$$I_{Peak} \Big|_{V_{DD}=1.8} = 1.388 \times 10^{-4}$$


$$I_{Peak} \Big|_{V_{DD}=1.98} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.99 - 0.4)^2$$

$$I_{Peak} \Big|_{V_{DD}=1.98} = 1.9338 \times 10^{-4}$$

$$\text{Change in Crowbar Current} = \frac{1.9338 \times 10^{-4} - 1.388 \times 10^{-4}}{1.388 \times 10^{-4}}$$

$$\text{Change in Crowbar Current} = 39.24\%$$

49.

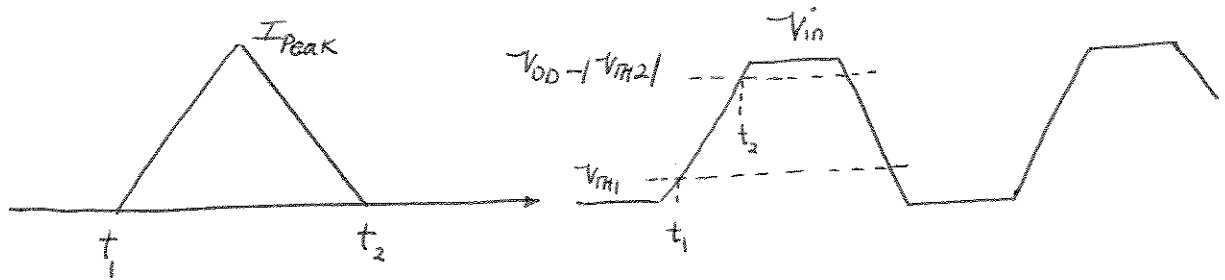

Total Energy drawn from V_{DD} during the interval $[t_1, t_2]$ is:

$$E = V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

In a periode the total energy is:

$$E_{tot} = 2 \times V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

$$P_{av} = V_{DD} I_{Peak} (t_2 - t_1) f_i$$

$$\text{Slope of input voltage} = \frac{0.9V_{DD} - 0.1V_{DD}}{t_r} = \frac{0.8V_{DD}}{t_r}$$


$$(t_2 - t_1) = \frac{(V_{DD} - V_{TH1} - |V_{TH2}|)}{0.8V_{DD}} \times t_r$$

$$P_{av} = V_{DD} \times \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left(\frac{V_{DD}}{2} - V_{TH1} \right)^2 \times \frac{(V_{DD} - V_{TH1} - |V_{TH2}|)}{0.8V_{DD}} t_r \times f_i$$

$$P_{av} = \frac{1}{1.6} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left(\frac{V_{DD}}{2} - V_{TH1} \right)^2 (V_{DD} - V_{TH1} - |V_{TH2}|) f_i \cdot t_r$$

$$P_{av} = 1.4 \times 10^{-5} \left(\frac{W}{L} \right)_1 \times t_r \times f_i$$


50.

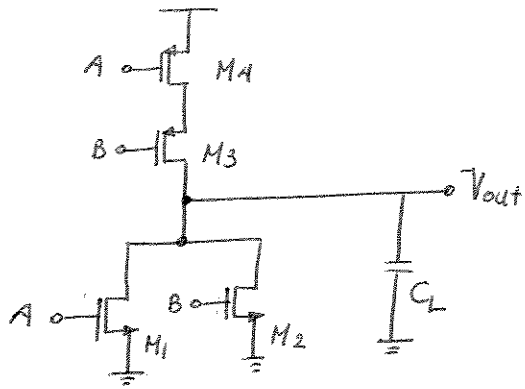

$$C_L = 20 \text{ fF}$$

$$f_i = 500 \text{ MHz}$$

$$P_{av} = ?$$


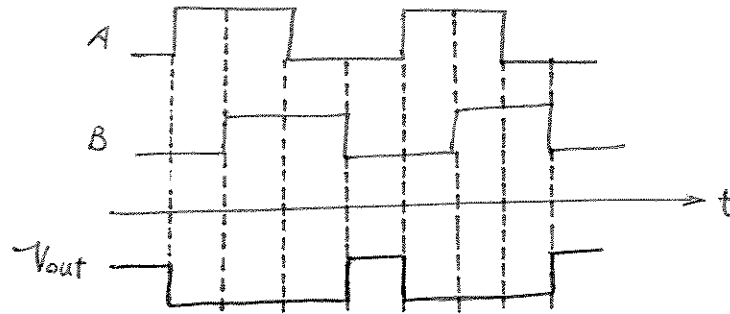


$$P_{av} = f_{in} C_L V_{DD}^2$$

$$= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av} = 3.24 \times 10^{-5} \text{ W}$$

51.

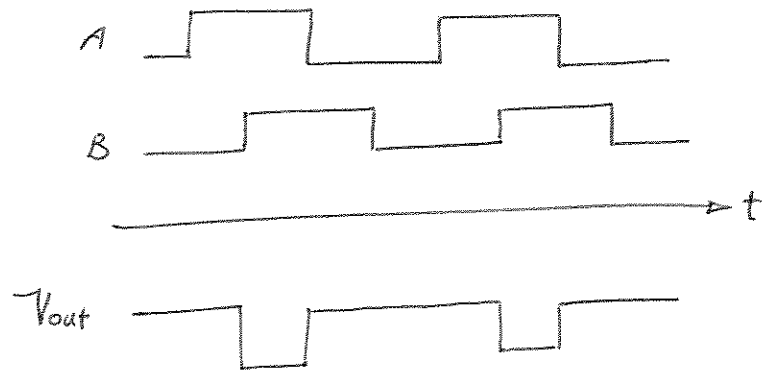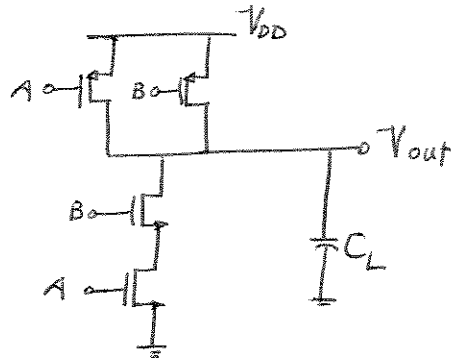


$$P_{av} = f_{in} C_L V_{DD}^2$$


$$= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av} = 3.24 \times 10^{-5} \text{ W}$$


52.

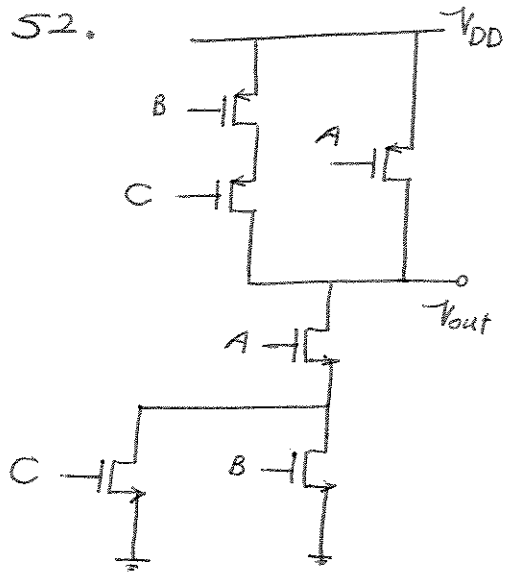


$$V_{out} = \overline{(B+C)A}$$

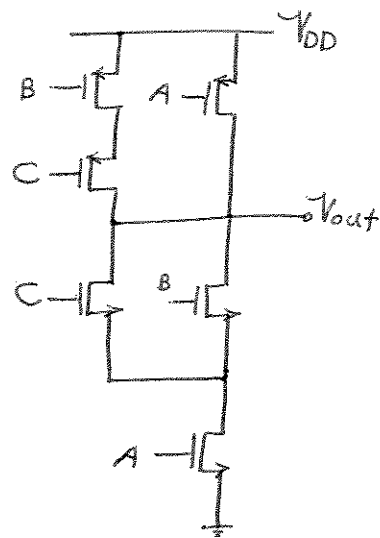


$$V_{out} = \overline{(B+C).A}$$

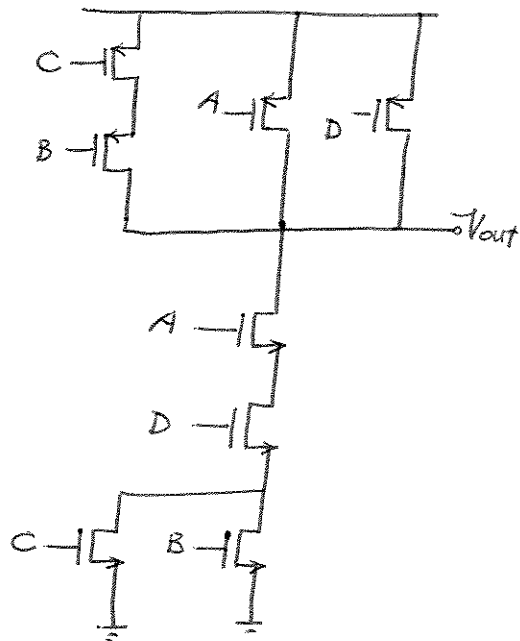

$$V_{out} = \overline{(B+C) D . A}$$

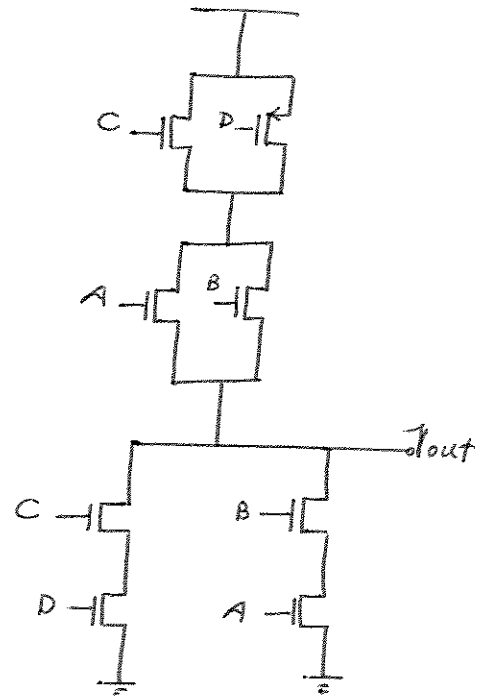


$$V_{out} = \overline{A.B + C.D}$$

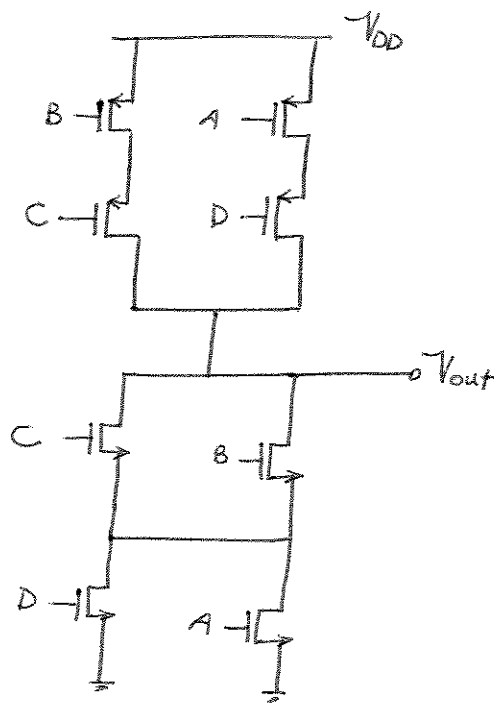

$$V_{out} = \overline{(A+D) \cdot (B+C)}$$

53.

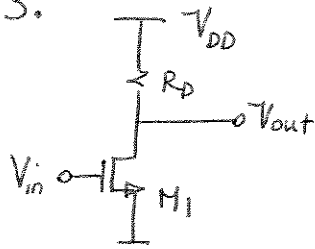

$$P_{\text{static}} = 0.5 \text{ mW}$$

$$V_{OL} = 100 \text{ mV}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{(1.8 - 0.1)^2}{R_D} + 0.1 \times \frac{1.8 - 0.1}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{1}{R_D} \times 3.06 = 0.5 \times 10^{-3}$$


$$R_D = 6120 \, \Omega$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{TH1})V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right)_1 \times \left[2(1.8 - 0.4)0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{6120}$$

$$\left(\frac{W}{L} \right)_1 = \frac{3.7}{0.18}$$

54.

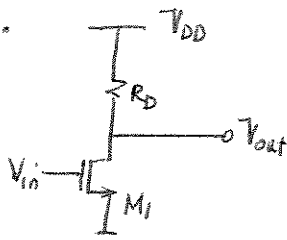

$$P_{Static} = 0.25 \text{ mW}$$

$$NM_L = 600 \text{ mV}$$

$$\text{Small Signal gain} = -g_m R_D$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})$$

$$\mu_n C_{ox} \frac{W}{L} (V_{IL} - V_{TH}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} + V_{TH}$$

$$NM_L = V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} + V_{TH}$$

$$\frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} = (NM_L - V_{TH}) \rightarrow \left(\frac{W}{L}\right) R_D = \frac{1}{\mu_n C_{ox} (NM_L - V_{TH})}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \mu_n C_{ox} \frac{1}{\mu_n C_{ox} (NM_L - V_{TH})} \times \left[2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = (V_{DD} - V_{OL})$$

$$2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 = 2(NM_L - V_{TH}) (V_{DD} - V_{OL})$$

$$-V_{OL}^2 - 2(V_{DD} - V_{TH}) V_{OL} - 2(NM_L - V_{TH}) V_{OL} + 2(NM_L - V_{TH}) V_{DD} = 0$$

$$-V_{OL}^2 - 2(V_{DD} + NM_L - 2V_{TH}) V_{OL} + 2(NM_L - V_{TH}) V_{DD} = 0$$

$$V_{OL}^2 + 3.2 V_{OL} + 0.72 = 0$$

$$V_{OL} = 0.2435$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.25 \times 10^{-3}$$

$$\frac{(1.8 - 0.24)^2 + 0.24 \times (1.8 - 0.24)}{R_D} = 0.25 \times 10^{-3}$$


$$R_D = 11206.55 \Omega$$

$$\left(\frac{W}{L}\right) = \frac{1}{\mu_n C_{ox} (N_{ML} - V_{TH}) R_D}$$

$$\left(\frac{W}{L}\right) = \frac{0.8}{0.18}$$

$$\left(\frac{W}{L}\right) = \frac{1}{100 \times 10^{-6} (0.6 - 0.4) 11206.55}$$

55.

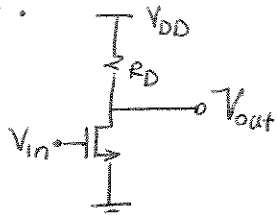

$$V_{OL} = 100\text{mV}$$

$$P_{av} = 0.25\text{mW}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + \frac{V_{OL}(V_{DD} - V_{OL})}{R_D} = P_{av}$$

$$\frac{(1.8 - 0.1)^2 + 0.1 \times (1.8 - 0.1)}{0.25 \times 10^{-3}} = R_D$$


$$R_D = 12240$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left[2(V_{DD} - V_{TH1})V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right) \times \left[2(1.8 - 0.4) \times 0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{12240}$$

$$\left(\frac{W}{L} \right) = \frac{1.85}{0.18}$$

56.

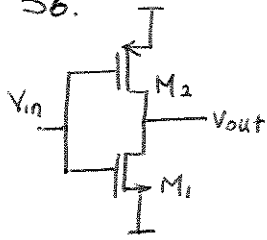

$$V_{in} = V_{out} = 0.8V, \quad I_{D1} = I_{D2} = 0.5mA$$

$$\lambda_n = 0.1V^{-1}$$

$$\lambda_p = 0.2V^{-1}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_n V_{out}) = I_{D1}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right)_1 (0.8 - 0.4)^2 (1 + 0.1 \times 0.8) = 0.5 \times 10^{-3}$$


$$\boxed{\left(\frac{W}{L} \right)_1 = \frac{10.4}{0.18}}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 [1 + \lambda_p (V_{DD} - V_{out})] = I_{D2}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L} \right)_2 (1.8 - 0.8 - 0.5)^2 [1 + 0.2 \times (1.8 - 0.8)] = 0.5 \times 10^{-3}$$

$$\boxed{\left(\frac{W}{L} \right)_2 = \frac{12}{0.18}}$$

57.

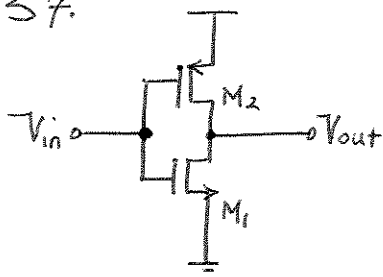

$$NM_L = NM_H = 0.7V$$

NM_L : M_1 in Saturation and M_2 in triode

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

Differentiating both sides with respect to V_{in}

$$2\mu_n \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1}) = \mu_p \left(\frac{W}{L} \right)_2 \left[-2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right]$$

$$(a) \quad V_{in} = V_{IL} \quad , \quad \frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\mu_n \left(\frac{W}{L} \right)_1 (V_{IL} - V_{TH1}) = \mu_p \left(\frac{W}{L} \right)_2 (2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD}) \quad (2)$$

obtaining V_{OH} from (2), substituting in (1), we arrive at

$$V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L} \right)_1}{\mu_p \left(\frac{W}{L} \right)_2}$$

NM_H , M_1 in triode and M_2 in Saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

Differentiating both sides with respect to V_{in} .

$$\mu_n \left(\frac{W}{L} \right)_1 \left[2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 2\mu_p \left(\frac{W}{L} \right)_2 \times (V_{in} - V_{DD} - |V_{TH2}|)$$

Assuming $\frac{\partial V_{out}}{\partial V_{in}} = -1$, $V_{in} = V_{IH}$, and $V_{out} = V_{OL}$ obtaining

$$V_{IH} = \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{1+3a}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$V_{IL} = NM_L = 0.7$$

$$V_{IH} = V_{DD} - NM_H = 1.8 - 0.7 = 1.1$$

$$0.7 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - 0.4a - 0.5}{a-1}$$

$$0.7(a-1) = \frac{1.8\sqrt{a}}{\sqrt{a+3}} - \frac{1.3 - 0.4a}{1}$$

$$0.7a - 0.7 + 1.3 - 0.4a = \sqrt{\frac{a}{a+3}} \times 1.8$$

$$\frac{0.6 + 0.3a}{1.8} = \sqrt{\frac{a}{a+3}} \rightarrow a^3 + 7a^2 - 20a + 12 = 0$$

$$a = \begin{cases} -9.3 \\ 1.3 \\ 1 \end{cases} \rightarrow \boxed{a = 1.3}$$

$$1.1 = \frac{2a(1.8-0.4-0.5)}{(a-1)\sqrt{1+3a}} - \frac{1.8-0.4a-0.5}{a-1}$$

$$1.1(a-1) = \frac{1.8a}{\sqrt{1+3a}} - 1.3 + 0.4a$$

$$1.1a - 1.1 + 1.3 - 0.4a = \frac{1.8a}{\sqrt{1+3a}}$$

$$0.2 + 0.7a = \frac{1.8a}{\sqrt{1+3a}}$$


$$147a^3 - 191a^2 + 40a + 4 = 0 \rightarrow \begin{cases} a_1 = 1 \\ a_2 = 0.37 \\ a_3 = -0.073 \end{cases} \rightarrow \boxed{a = 0.37}$$

No it is not possible to design a CMOS inverter with $NM_L = NM_H = 0.7$.

The reason is that each value of $a = \frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}$ specifies a unique set of noise margins (NM_L, NM_H).

Remember, the relative strength of NMOS and PMOS determines the noise margins interdependently.

58.

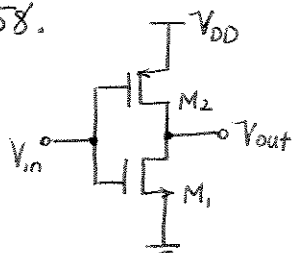

$$T_{PLH} = T_{PHL} = 100 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

 T_{PLH}

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$V_{out}(t) = -\frac{|I_{D2}|}{C_L} t$$

$$= -\frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2 t$$

$$T_{PLH1} = \frac{2|V_{TH2}|/C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

$$|I_{D2}| = C_L \frac{dV_{out}}{dt}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] = C_L \frac{dV_{out}}{dt}$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

$$\frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \bigg|_{V_{out}=|V_{TH2}|}^{V_{out}=V_{DD}/2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 T_{PLH2}$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$

$$T_{PLH} = T_{PLH1} + T_{PLH2}$$

$$= \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$100 \times 10^{-12} = \frac{50 \times 10^{-15}}{50 \times 10^{-6} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)} \left[\frac{2 \times 0.5}{1.8 - 0.5} + \ln \left(3 - 4 \frac{0.5}{1.8} \right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{1.9}{0.18}}$$

$$T_{PHL}$$

$$T_{PHL1} = \frac{2V_{TH1}C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH1})V_{out} - V_{out}^2 \right] = -C_L \frac{dV_{out}}{dt}$$

$$\frac{-1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \bigg|_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}-V_{TH1}} = \frac{1}{2} \mu_n C_{ox} / C_L \left(\frac{W}{L}\right)_1 T_{PHL2}$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$100 \times 10^{-12} = \frac{50 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 \times (1.8 - 0.4)} \times \left[\frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \times \frac{0.4}{1.8} \right) \right] \cdot \boxed{\left(\frac{W}{L}\right)_1 = \frac{0.85}{0.18}}$$