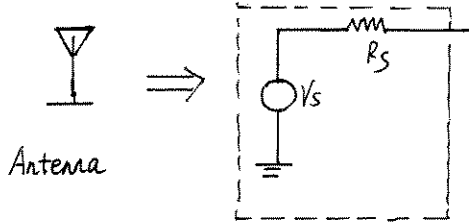



1)



Thevenin Equivalent:

$$V_s = V_0 \cos \omega t$$

$$R_s = R_{out}$$

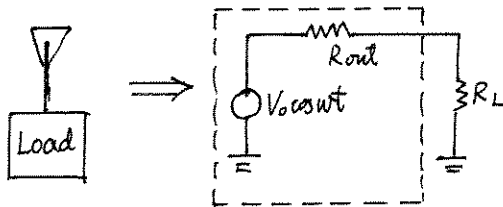

Average power delivered to load = $(I_{rms})^2 R_L$,

$$I_{rms} = \frac{V_{rms}}{R_{out} + R_L}, \quad V_{rms} = \frac{V_0}{\sqrt{2}} \Rightarrow I_{rms} = \frac{V_0}{\sqrt{2}(R_{out} + R_L)}$$

$$\text{Average power} = (I_{rms})^2 R_L = \frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \quad (\text{Eq. 1})$$

Plot of Average Power

When R_L is small, Eq. 1 is small.

When R_L is large, Eq. 1 is also small.


So for some R_L between zero and infinity, the average power will reach its peak. Let's take the derivative of Eq. 1 with respect to R_L to find the optimum R_L .

$$\frac{\partial}{\partial R_L} \left[\frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \right] = \frac{V_0^2}{2(R_{out} + R_L)^2} - \frac{V_0^2 R_L}{(R_{out} + R_L)^3}$$


Setting it to zero and solve for R_L

$$\frac{V_0^2}{2(R_{out} + R_L)^2} = \frac{V_0^2 R_L}{(R_{out} + R_L)^3} \Rightarrow \frac{(R_{out} + R_L)}{2} = R_L$$

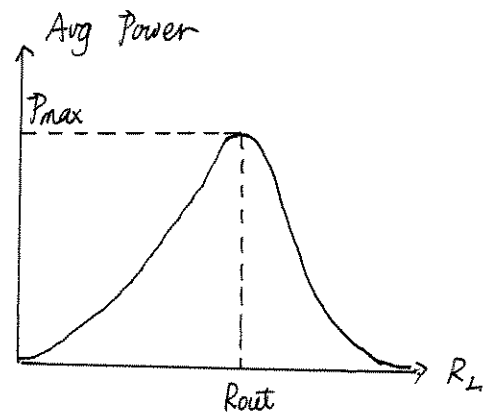
$$\Rightarrow R_{out} + R_L = 2R_L \Rightarrow R_L = R_{out}$$



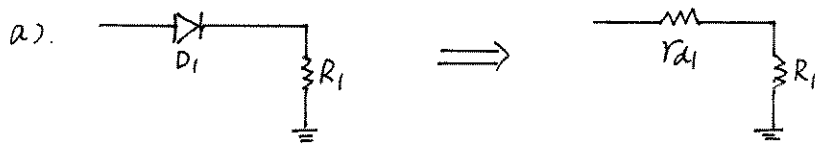
2) In small signal operation, a diode can be replaced by a linear resistor if charges are small.



$$R_{in} = r_{d1} + R_1$$

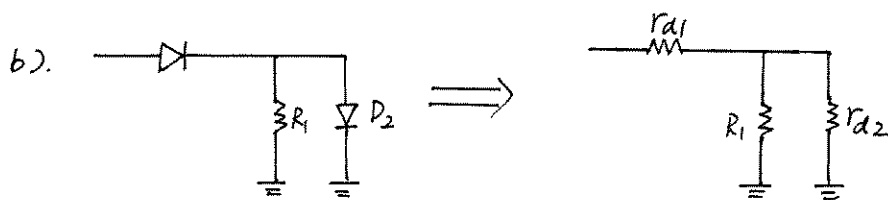

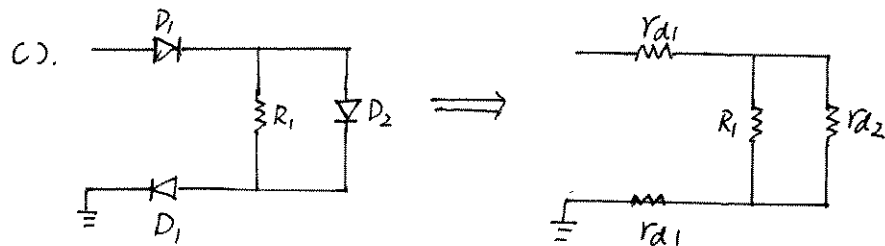
$$R_{in} = r_{d1} + R_1 // r_{d2} \quad (// \text{ means in parallel })$$




$$R_{in} = 2r_{d1} + R_1 // r_{d2}$$

3). When $V_A = \infty$, $V_O = \infty$.


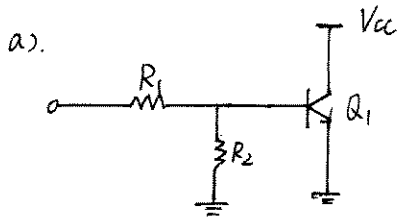


\Rightarrow

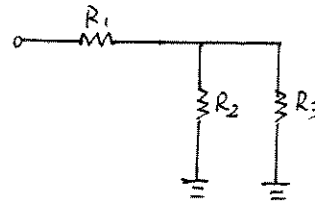


Replacing Q_1 by its equivalent resistance seen at base
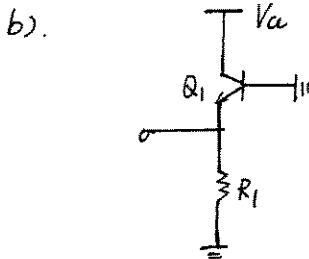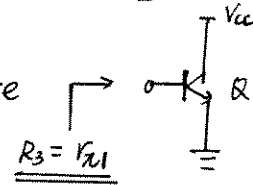
$$\text{So } R_{in} = R_1 + R_2 \parallel R_3 = R_1 + R_2 \parallel r_{\pi 1}$$





\Rightarrow

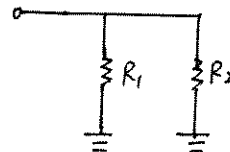


Replacing Q_1 by its equivalent resistance seen at emitter
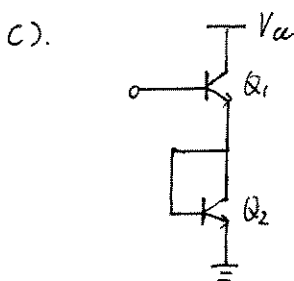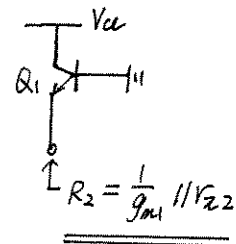
$$\text{So } R_{in} = R_1 \parallel R_2 = R_{in} \parallel \left(\frac{1}{g_{m1}} \parallel r_{\pi 1} \right)$$




\Rightarrow

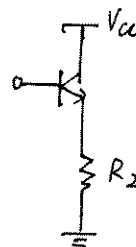


Replacing Q_2 by its equivalent diode-connected resistance
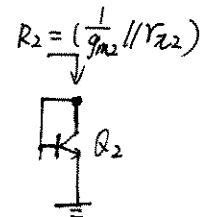
$$\text{So } R_{in} = r_{\pi 1} + (1 + \beta) R_2 = r_{\pi 1} + (1 + \beta) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$




3).

d).

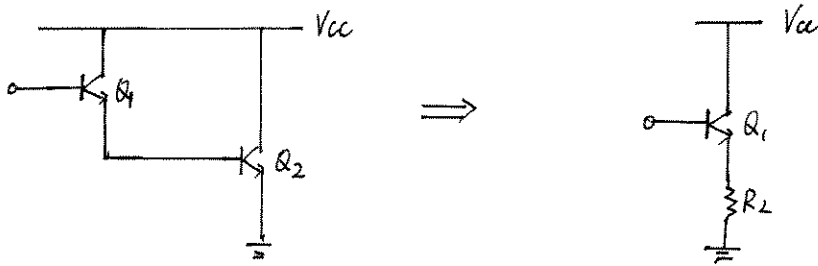

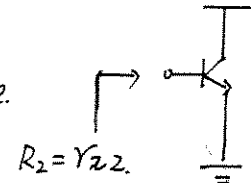Replacing Q_2 by its equivalent resistance seen at base.



$$\text{So } R_{in} = r_{\pi 1} + (1 + \beta) R_2 = r_{\pi 1} + (1 + \beta) r_{z2}.$$

(Please refer to the textbook for all the equivalent resistances.)


4). Since the problem doesn't say $V_A = \infty$, r_o must be considered in derivation.

a). Short V_B since it's a DC source, and replace Q_1 with an ideal transistor with its output resistance.



$$So \quad R_{out} = R_1 // r_o // \infty = R_1 // r_o$$


b).

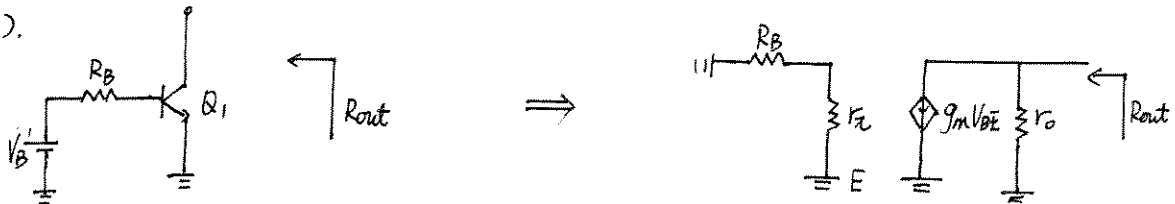

By drawing the small-signal model, it's easy to tell $V_{BE} = 0$ and $R_{out} = r_o$

c). Replace Q_1 with an ideal transistor and an output impedance r_{o1} .

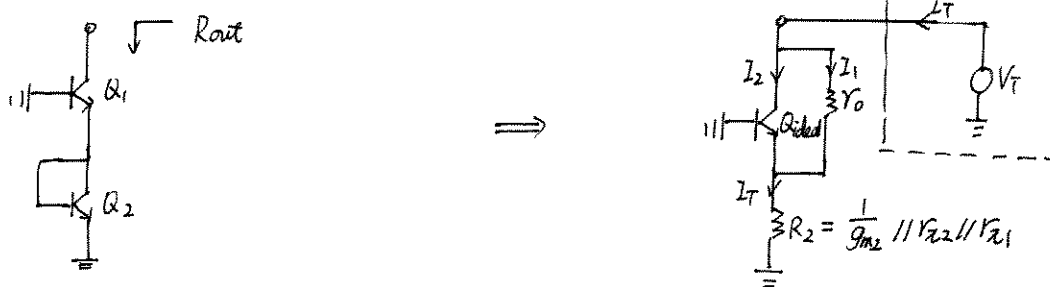Replace Q_2 with a resistor $\frac{1}{g_{m2}} // r_{a2} // r_{a1}$



Here, r_{a1} is included in R_2 because it is also connected from emitter to ground and it accounts for the base current of Q_1 .

$$4) I_1 = \frac{V_T - I_T R_2}{r_o}, \quad I_2 = g_{m1} (0 - I_T R_2)$$

$$I_T = I_1 + I_2 = \frac{V_T - I_T R_2}{r_o} - g_{m1} I_T R_2$$

$$\Rightarrow I_T + \frac{I_T R_2}{r_o} + g_{m1} I_T R_2 = \frac{V_T}{r_o}$$

$$\Rightarrow \frac{V_T}{I_T} = r_o \left(1 + \frac{R_2}{r_o} + g_{m1} R_2 \right)$$

$$\Rightarrow R_{out} = \frac{V_T}{I_T} = r_o (1 + g_{m1} R_2) + R_2$$


$$= r_o \left[1 + g_{m1} \left(\frac{1}{g_{m2} \parallel r_{\pi 2} \parallel r_{\pi 1}} \right) \right] + \frac{1}{g_{m2} \parallel r_{\pi 2} \parallel r_{\pi 1}}$$

Usually $\frac{1}{g_m} \ll r_{\pi}$, and if $\beta_1 = \beta_2$

$$R_{out} \approx \frac{1}{g_m} + 2r_o$$


5). $V_A = \infty$, $r_o = \infty$

a).

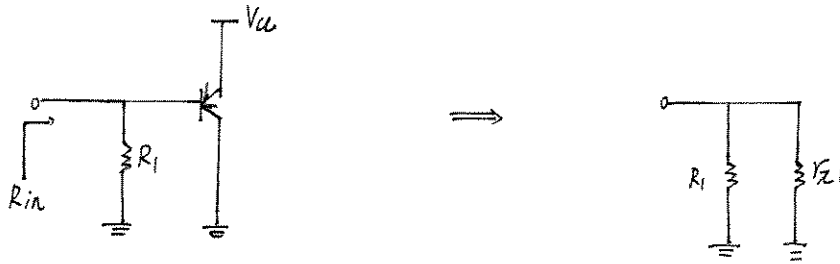


$$R_{in} = R_1 \parallel R_2$$

b).

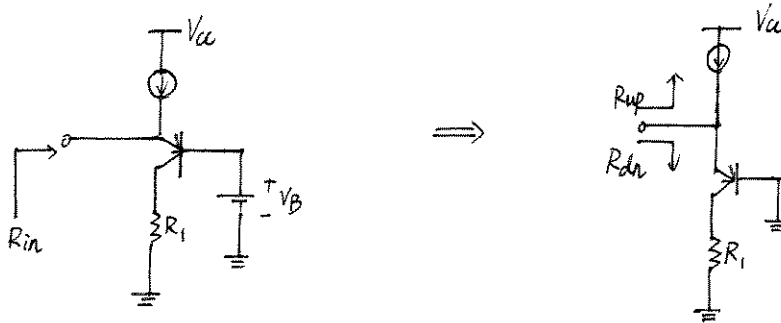

$$R_{in} = R_{up} \parallel R_{dn}, \quad R_{up} = \infty, \text{ since a DC current source is open.}$$

Finding R_{dn} :

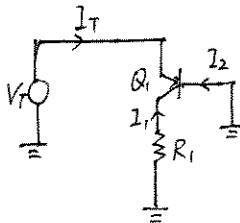

$$I_T = -(I_1 + I_2)$$

$$I_1 = g_m (0 - V_T) = -g_m V_T$$

$$I_2 = \frac{I_1}{\beta}$$



$$\text{So } I_T = -(-g_m V_T - \frac{g_m V_T}{\beta}) = (g_m + \frac{g_m}{\beta}) V_T$$

$$\frac{V_T}{I_T} = \frac{1}{(g_m + \frac{g_m}{\beta})} = \frac{1}{g_m} \parallel r_e$$


$$R_{dn} = \frac{V_T}{I_T} = \frac{1}{g_m} \parallel r_e$$

$$\text{So } R_{in} = R_{up} \parallel R_{dn} = \infty \parallel \frac{1}{g_m} \parallel r_e = \frac{1}{g_m} \parallel r_e$$

5). c).

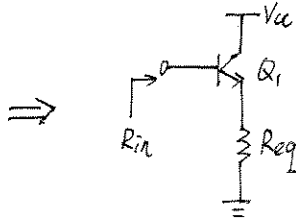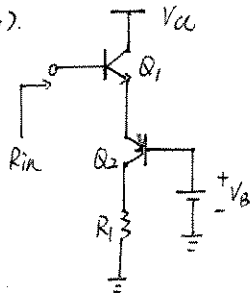




From b), we know that

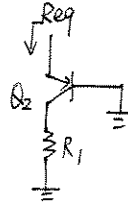

$$R_{eq} = \frac{1}{g_{m2}} \parallel r_{\pi 2}.$$


$$\text{So } R_{in} = r_{\pi 1} + (1 + \beta) R_{eq} = r_{\pi 1} + (1 + \beta) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right).$$

d).

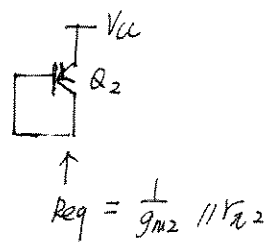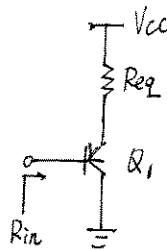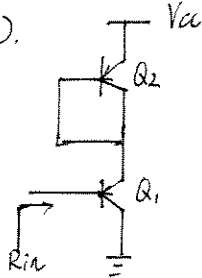



$$R_{in} = r_{\pi 1} + (1 + \beta) R_{eq} = r_{\pi 1} + (1 + \beta) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

e)

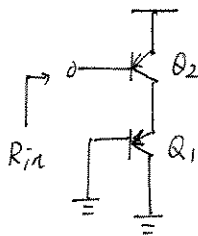

$R_{in} = r_{\pi 2}$. Q_1 plays no role here since it's connected to the collector of Q_2 .
It can not be seen from the base of Q_2 .

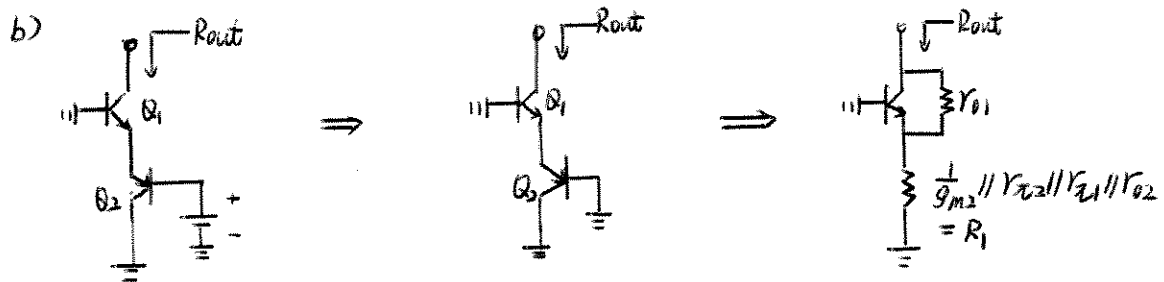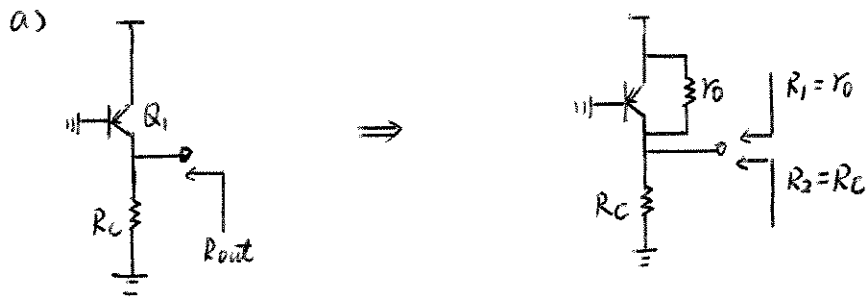
b) Since the problem doesn't state $V_A = \infty$, r_o is not ∞ .



As shown in problem 4) c).

$$R_{out} = R_1 + r_{o1} + g_{m2} r_{o1} R_1 = r_{o1} + (1 + g_{m1} r_{o1}) R_1$$

$$= r_{o1} + (1 + g_{m1} r_{o1}) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{\pi 1} \parallel R_{o2} \right)$$

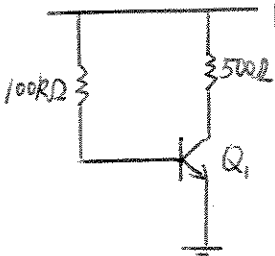7) a).  $V_{CC} = 2.5V$ $I_B = \frac{V_{CC} - V_{BE}}{100\text{ k}\Omega}$, $I_C = \beta I_B$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

Guess $V_{BE} = 0.7V$,

$$I = \beta \left(\frac{V_{CC} - V_{BE}}{100\text{ k}\Omega} \right) = 1.8\text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.747V, \text{ not } 0.7V, \text{ Iterate}$$

$$V_{BE} = 0.747V, I_C = 1.753\text{ mA}$$

Verify V_{BE} , $V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.746V$, converged

$$V_{CE} = 2.5 - (1.753)(0.5\text{ k}) = 1.62V$$

$V_{CE} > V_{BE}$, Q_1 in forward active region.

$$I_C = 1.754\text{ mA}$$


$$V_{CE} = 1.62V$$

$$I_B = 17.54\text{ }\mu\text{A}$$

$$V_{BE} = 0.746V$$

↑
operating point

7). b).

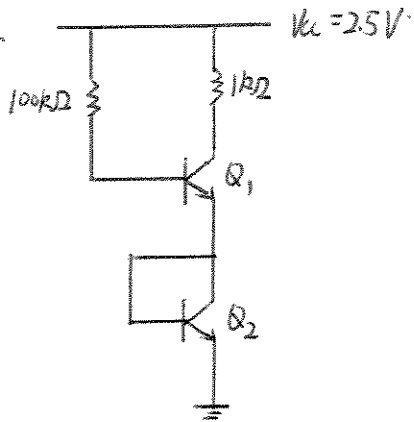

$$I_{B1} = \frac{2.5 - (V_{BE1} + V_{BE2})}{100k\Omega}$$

$$I_{C1} = \beta I_{B1}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right), V_{BE2} = V_T \ln\left(\frac{I_{C2}}{I_S}\right)$$

Assume $V_{BE1} = V_{BE2} = 0.8V$

$$I_{C1} = \beta \left(\frac{2.5 - 1.6}{100k} \right) = 0.9mA$$

$$V_{BE1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.728V, \text{ not } 0.8V, \text{ reiterate}$$

$I_{C2} = 0.9mA$, Since β 's are the same

$$V_{BE2} = 0.728V$$

$$I_{C1} = \beta \left(\frac{2.5 - (2)(0.728)}{100k\Omega} \right) = 1.042mA = I_{C2}$$

$$V_{BE1} = V_{BE2} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.733V, \text{ iterate once more}$$

$$I_{C1} = I_{C2} = \beta \left(\frac{2.5 - (2)(0.733)}{100k\Omega} \right) = 1.034mA$$

7) b)

$$I_{C1} = I_2 = 1.034 \text{ mA}$$

$$V_{BE1} = V_{BE2} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.733, \text{ Converges.}$$

$$V_{CE1} = 2.5 - 0.733 - (1.034)(1 \text{ k}\Omega) = 0.733 \text{ V}$$

$V_{CE} = V_{BE}$, Q_2 at the edge of active region.

$$V_{BE2} = V_{CE2} = 0.733 \text{ V}$$

Operating Point:

$$I_{C1} = 1.034 \text{ mA}$$

$$I_{B1} = 0.01 \text{ mA}$$

$$V_{BE1} = 0.733 \text{ V}$$

$$V_{CE1} = 0.733 \text{ V}$$


$$I_{C2} = 1.034 \text{ mA}$$

$$I_{B2} = 0.01 \text{ mA}$$

$$V_{BE2} = 0.733 \text{ V}$$

$$V_{CE2} = 0.733 \text{ V}$$

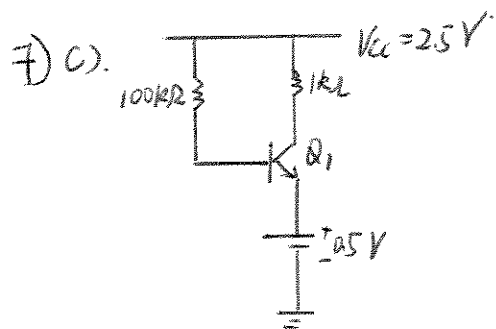Although, for Q_2 $V_{BE} = V_{CE}$, it is at the edge of active region, the situation is not as severe as Q_1 's. Since Q_2 's configuration will always render $V_{BE} = V_{CE}$, whereas for Q_1 , V_{CE} may drop below V_{BE} .



$$I_B = \frac{V_{CC} - (V_{BE} + 0.5)}{100K}$$

$$I_C = \beta I_B$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

Guess $V_{BE} = 0.8V$,

$$I_C = \beta \left(\frac{2.5 - 1.3}{100K} \right) = 1.2mA$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.736V, \text{ not } 0.8, \text{ reiterate}$$

$$V_{BE} = 0.736V, I_C = \beta \left(\frac{2.5 - (0.736 + 0.5)}{100K\Omega} \right) = 1.26mA$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.738V, \text{ converges.}$$


$$V_{CE} = (2.5 - 0.5) - (1.26)(1K\Omega) = 0.74$$

$V_{CE} > V_{BE}$, Q_1 in forward active region


Operating point

$$I_C = 1.26mA \quad V_{BE} = 0.738V$$

$$I_B = 0.0126mA \quad V_{CE} = 0.74V$$

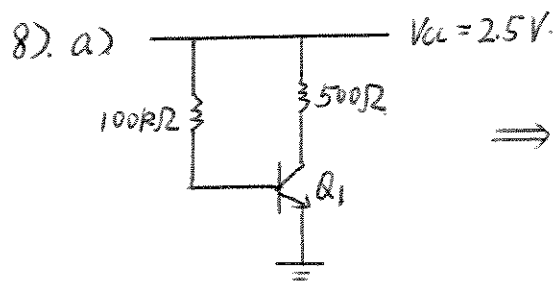


\Rightarrow

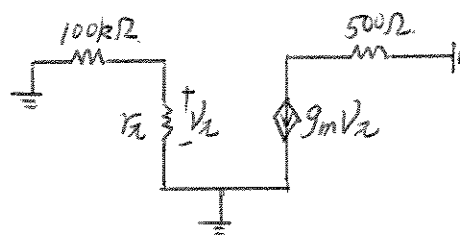


$$g_m = \frac{I_C}{V_T} = \frac{1.754 \text{ mA}}{26 \text{ mV}} = 0.0675 \text{ S}$$
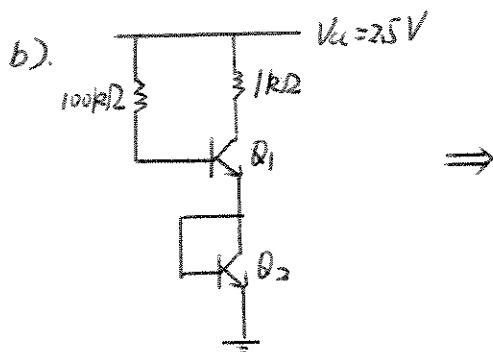
$$r_{\pi 1} = \frac{\beta}{g_m} = \frac{100}{0.0675} \Omega = 1482.3 \Omega$$



\Rightarrow

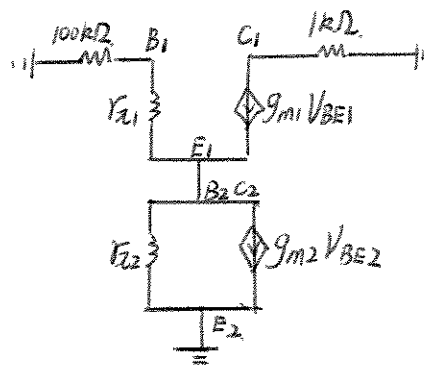


$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{1.034 \text{ mA}}{26 \text{ mV}} = 0.04 \text{ S}$$


$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{0.04} \Omega = 2500 \Omega$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{1.034 \text{ mA}}{26 \text{ mV}} = 0.04 \text{ S}$$
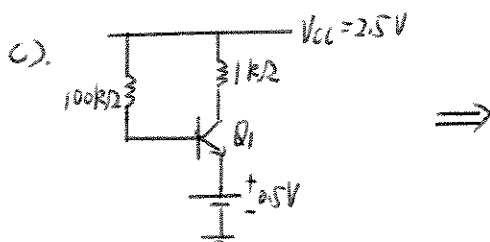
$$r_{\pi 2} = \frac{\beta}{g_{m2}} = \frac{100}{0.04} \Omega = 2500 \Omega$$




\Rightarrow

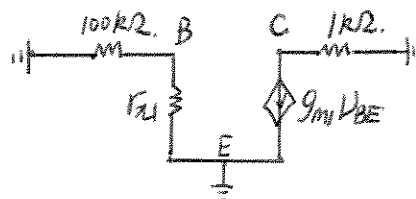

$$g_{m1} = \frac{I_C}{V_T} = \frac{1.26 \text{ mA}}{26 \text{ mV}} = 0.048 \text{ S}$$
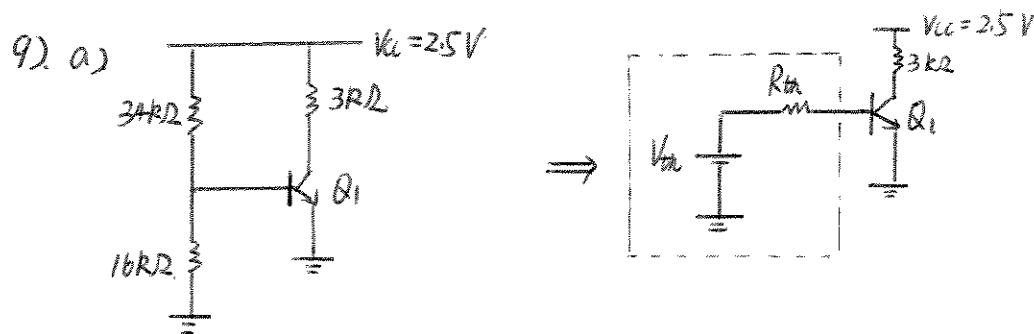
$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{0.048} \Omega = 2083 \Omega$$



Thevenin Equivalent $R_{th} = \frac{34 \times 16}{34 + 16} k\Omega = 10.88 k\Omega$

$$V_{th} = \frac{2.5V \times 16}{34 + 16} = 0.8V$$

$$I_c = \beta \left(\frac{0.8 - V_{BE}}{10.88k} \right), \quad V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right)$$

Assume $V_{BE} = 0.7$,

$$I_c = \beta \left(\frac{0.8 - 0.7}{10.88k\Omega} \right) = 0.92mA$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.734V$$

Iterate, $V_{BE} = 0.734V$

$$I_c = \beta \left(\frac{0.8 - 0.734}{10.88k\Omega} \right) = 0.61mA$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.724V$$

Iterate, $V_{BE} = 0.724V$

$$I_c = \beta \left(\frac{0.8 - 0.724}{10.88k\Omega} \right) = 0.699mA$$

9) a) $I_c = 0.699 \text{ mA}$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.727 \text{ V}$$

Iterate, $V_{BE} = 0.727 \text{ V}$

$$I_c = \beta \left(\frac{0.8 - 0.727}{10.88 \text{ k}\Omega} \right) = 0.67 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.726 \text{ V}, \text{ Converged!!}$$

$$V_{CE} = 2.5 - (0.67)(3 \text{ k}\Omega) = 0.49$$


$$V_{BE} - V_{CE} = 0.236 \text{ V}, \text{ Soft-saturation, still OK.}$$

Operating point:

$$I_c = 0.67 \text{ mA} \quad V_{BE} = 0.726 \text{ V}$$

$$I_B = 6.7 \mu\text{A} \quad V_{CE} = 0.49 \text{ V}$$

9) b).

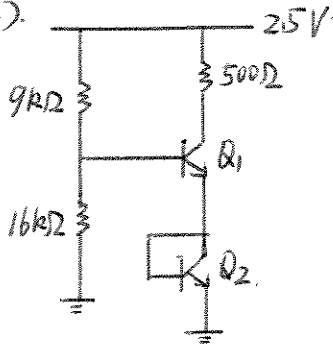


\Rightarrow

$$R_{th} = \frac{9 \times 16}{9 + 16} \text{ k}\Omega = 5.76 \text{ k}\Omega$$

$$V_{th} = 25 \text{ V} \times \frac{16}{9 + 16} = 1.6 \text{ V}$$

\Downarrow

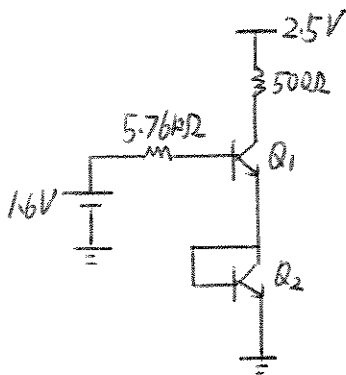

$$I_{C1} = \beta \left(\frac{1.6 - (V_{BE1} + V_{BE2})}{5.76 \text{ k}\Omega} \right)$$

$$V_{BE} = V_{BE1} = V_{BE2} = V_T \ln \left(\frac{I_C}{I_S} \right)$$

$$I_{C1} = I_{C2} = I_C$$

Guess $V_{BE1} = V_{BE2} = 0.7 \text{ V}$

$$I_C = \beta \left(\frac{1.6 - 1.4}{5.76 \text{ k}\Omega} \right) = 3.47 \text{ mA}$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.769 \text{ V}$$

Iterate, $V_{BE} = 0.769 \text{ V}$

$$I_C = \beta \left(\frac{1.6 - 2(0.769)}{5.76 \text{ k}\Omega} \right) = 1.08 \text{ mA}$$

9)

b)

$$I_c = 1.08 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.738 \text{ V}$$

Iterate, $V_{BE} = 0.738 \text{ V}$

$$I_c = \beta \left(\frac{1.6 - 2(0.738)}{5.76 \text{ k}\Omega} \right) = 2.15 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.756 \text{ V}$$

Iterate, $V_{BE} = 0.756 \text{ V}$

$$I_c = \beta \left(\frac{1.6 - 2(0.756)}{5.76 \text{ k}\Omega} \right) = 1.53 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.747 \text{ V}$$

Iterate ... (for 3 more times)

$$V_{BE} = 0.75 \text{ V}, I_c = 1.74 \text{ mA} \quad \text{converged}$$

$$V_{CE} = 2.5 - 0.75 - (1.74)(0.5) = 0.88 \text{ V}$$

Operating Point

$$I_{c1} = 1.74 \text{ mA}$$

$$I_{B1} = 17.4 \mu\text{A}$$

$$V_{BE} = 0.75 \text{ V} \quad (\text{Forward active})$$


$$V_{CE} = 0.88 \text{ V}$$

$$I_{c2} = 1.74 \text{ mA}$$

$$I_{B2} = 17.4 \mu\text{A}$$


$$V_{BE2} = 0.75 \text{ V} \quad (\text{Edge of forward active})$$
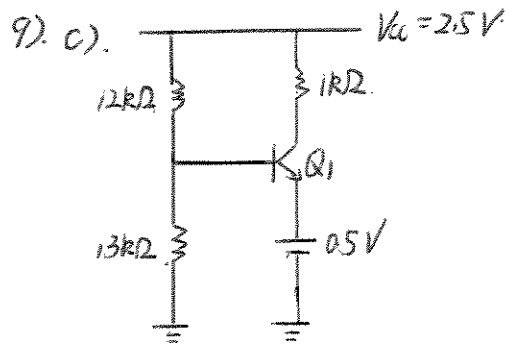
$$V_{CE2} = 0.75 \text{ V} \quad (\text{active})$$



$$V_{th} = 2.5V \times \frac{13}{12+13} = 1.3V$$
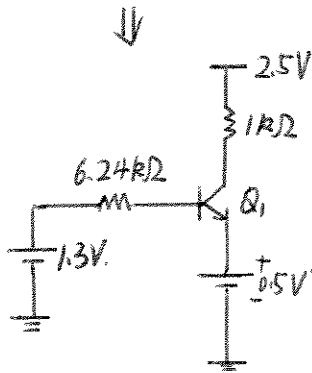
$$\Rightarrow R_{th} = \frac{12 \times 13}{12+13} k\Omega = 6.24k\Omega$$



$$I_c = \beta \left(\frac{1.3 - (V_{BE} + 0.5)}{6.24 k\Omega} \right)$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right)$$

Guess $V_{BE} = 0.743V$

$$I_c = \beta \left(\frac{1.3 - (0.743 + 0.5)}{6.24 k\Omega} \right) = 0.913 mA$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.734V$$

Iterate, $V_{BE} = 0.734V$

$$I_c = \beta \left(\frac{1.3 - (0.734 + 0.5)}{6.24 k\Omega} \right) = 1.06 mA$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.738V$$

9)

c)

Iterate, $V_{BE} = 0.738V$

$$I_C = \beta \left(\frac{1.3 - (0.738 + 0.5)}{6.24k\Omega} \right) = 0.99mA$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.736V$$

$$V_{CE} = 2.5 - 0.5 - (0.99)(1k\Omega) = 1.01V$$

$V_{CE} > V_{BE} \Rightarrow$ Forward Active Region

operating point



$$I_C = 0.99mA$$

$$V_{BE} = 0.736V$$

$$I_B = 9.9\mu A$$

$$V_{CE} = 1.01V$$



10). a). $V_{CC} = 2.5V$

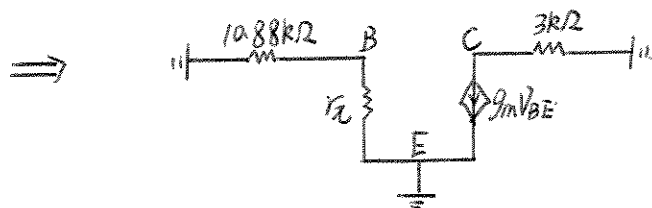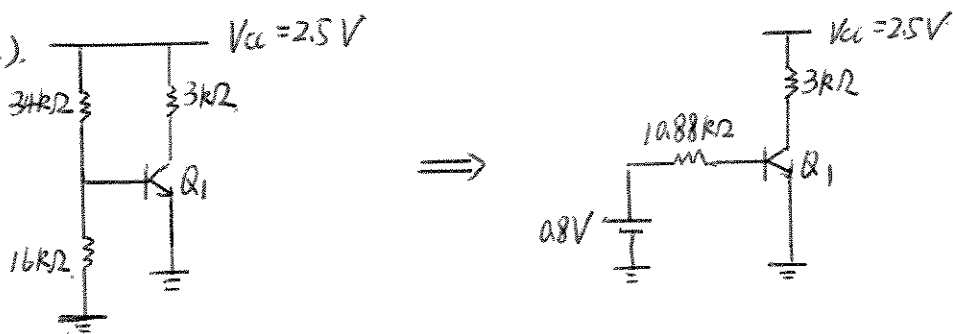

$$g_m = \frac{I_C}{V_T} = \frac{0.67mA}{26mV} = 0.026S$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.026} \Omega = 3846\Omega$$

b). $V_{CC} = 2.5V$

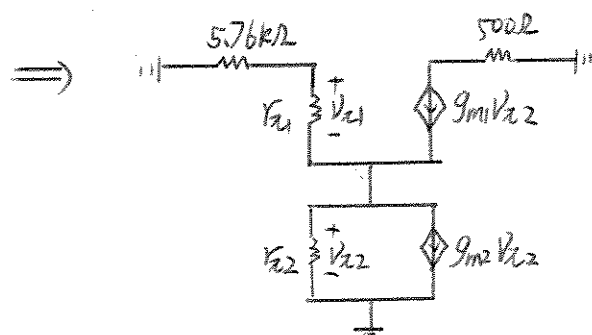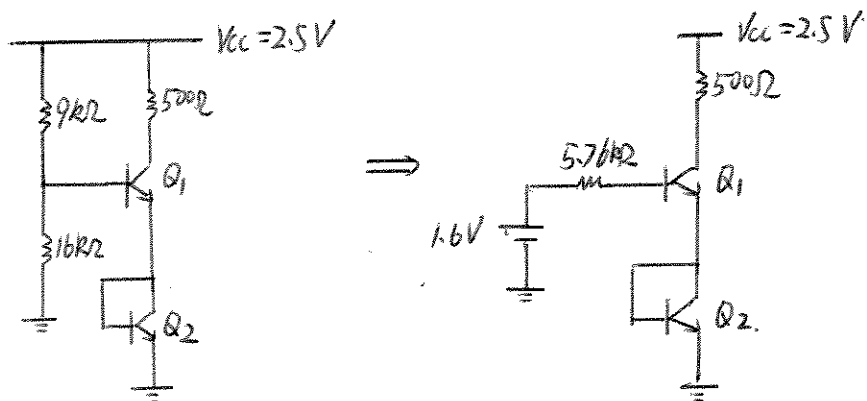


$$g_{m1} = \frac{1.74mA}{26mV} = 0.067S$$

$$r_{\pi1} = \frac{\beta_1}{g_{m1}} = 1494.3\Omega$$



$$g_{m2} = 0.067S$$

$$r_{\pi2} = 1494.3\Omega$$

10) c).

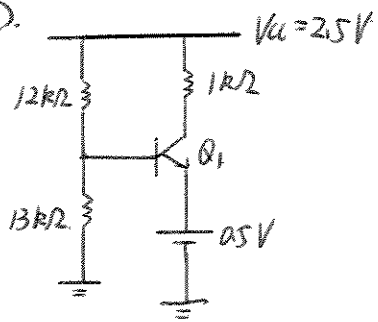


\Rightarrow

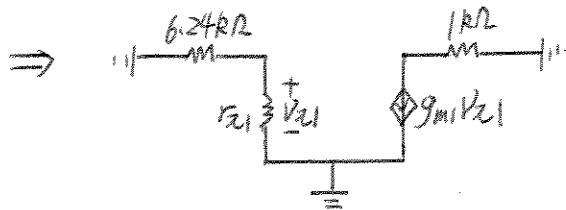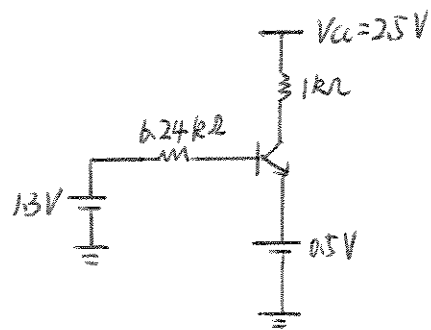

$$g_{m1} = \frac{I_C}{V_T} = \frac{0.99 \text{ mA}}{26 \text{ mV}} = 0.038 \text{ S}$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{0.038} \Omega = 2632 \Omega$$

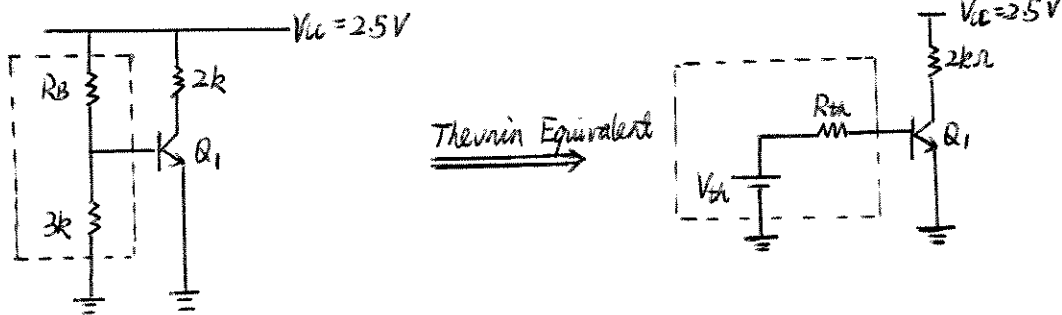11) a). Find the minimum R_B that guarantees forward active region.



$$R_{th} = \frac{R_B \times 3}{R_B + 3}, \quad V_{th} = \frac{25 \times 3}{R_B + 3}$$

To maintain Q_1 in forward-active region, $V_{CE} \geq V_{BE}$ (*)

$$V_{CE} = V_{CC} - I_C \cdot 2k, \quad I_C = \beta I_B, \quad I_B = \frac{V_{th} - V_{BE}}{R_{th}}$$

$$\text{So } V_{CE} = V_{CC} - \beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot 2k$$

From (*)

$$V_{CC} - \beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot 2k \geq V_{BE} \quad (1)$$

$$\text{And } V_{BE} = V_T \ln(I_C/I_S) = V_T \ln[\beta(V_{th} - V_{BE})/R_{th}/I_S] \quad (2)$$

Find the minimum R_B by iteration. Guess $V_{BE} = 0.8$ as initial condition.

Use $V_{BE} = 0.8$, and substitute R_{th} and V_{th} into (1), it can be calculated

$$R_B \geq 6.178k$$

Check the validity of V_{BE} . With $R_B \geq 6.178k$, from (2)

$$V_{BE} = 0.727V$$

So the initial guess of V_{BE} is not accurate.

Reiterate with $V_{BE} = 0.727$, it can be calculated from (1)

$$R_B \geq 7.058k$$

11) With $R_B \geq 706k$, from ②

$$V_{BE} = 0.728$$

It's very close to 0.727. So the results have converged. (Satisfy both ① & ②)

The final answer is

$$R_B \geq 706k$$

b). β changes from 100 to 200, so $\partial\beta$ is 100

$$V_{CB} = 2.5 - I_C(2k) - V_{BE} = 2.5 - \left(\frac{V_{TH} - V_{BE}}{R_{TH}} \right) \beta \cdot (2k) - V_{BE}$$

$$\frac{\partial V_{CB}}{\partial \beta} = - \left(\frac{V_{TH} - V_{BE}}{R_{TH}} \right) \cdot 2k$$



$$\partial V_{CB} = - \left(\frac{V_{TH} - V_{BE}}{R_{TH}} \right) \cdot 2k \cdot (\partial\beta) = -1.6627$$

(Forward bias sustained during β 's rising : 1.663V)

$$\text{Original } V_{CB} = 0.01428$$

Total net forward bias after β has rose to 200 :

$$1 - 1.6627 + 0.01428 = 1.648 (V)$$

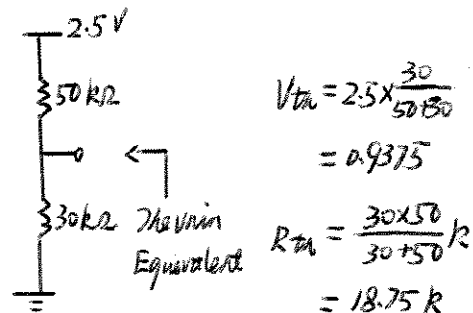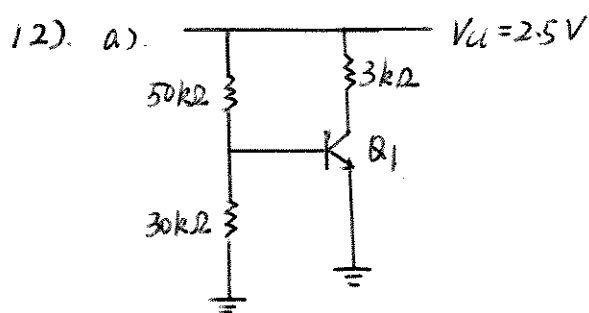

Since $I_C = 0.5mA$, $I_B = \frac{I_C}{\beta} = 0.005mA$.

$$I_B = \frac{V_{th} - V_{BE}}{R_{th}} \Rightarrow V_{BE} = V_{th} - I_B \cdot R_{th} = 0.84375$$

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \Rightarrow I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 4.03 \times 10^{-15} (mA)$$

b). At the edge of saturation means $V_{BE} - V_{CE} = 0$.

(soft saturation not allowed)


$$V_{CE} = 2.5 - I_C \cdot (3k), \text{ in which } I_C = \beta I_B = \beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right)$$

$$\text{SO } V_{BE} = 2.5 - \beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot (3k)$$

Solve this equation:

$$V_{BE} = 0.83.$$
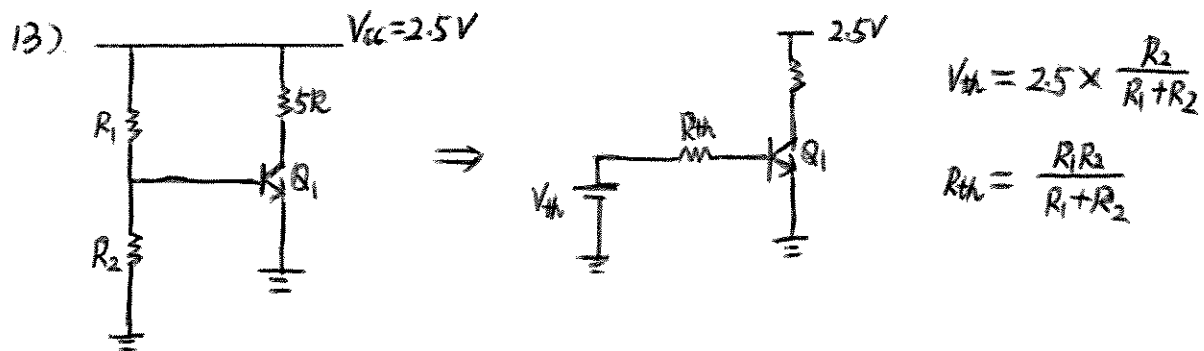
$$I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = \frac{\beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right)}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 7.84 \times 10^{-15} (mA)$$



$$R_{in} = R_{th} \parallel \frac{\beta}{g_m} = R_{th} \parallel \frac{V_T \beta}{I_C} > 10k\Omega$$

$$g_m \geq \frac{1}{260\Omega} = 0.0038S$$

Let's choose g_m to be $0.0038S$

$$g_m = \frac{I_C}{V_T} \Rightarrow I_C = g_m V_T = 0.104(mA)$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.761(V)$$

Let $R_{in} = 10k\Omega$

$$R_{in} = R_{th} \parallel \frac{\beta}{g_m} \Rightarrow R_{th} = 16.13k\Omega \quad (1)$$

$$I_B = \frac{I_C}{\beta} = \frac{V_{th} - V_{BE}}{R_{th}} \Rightarrow V_{th} = V_{BE} + \frac{I_C (R_{th})}{\beta} = 0.78V \quad (2)$$

$$(2) \Rightarrow 2.5 \times \frac{R_2}{R_1 + R_2} = 0.78V$$

$$(1) \Rightarrow \frac{R_1 R_2}{R_1 + R_2} = 16.13k\Omega$$

It can be solved that $R_1 = 51.7k\Omega$, $R_2 = 23.44k\Omega$

This is only one possible solution set. The thought process is more important.

14). If g_m at least $\frac{1}{26} = 0.03848 (\Omega^{-1})$

$$\text{Let } g_m = 0.03848 = \frac{I_c}{V_T} \Rightarrow I_c = 0.99996 \text{ (mA)}$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_S} \right) = 0.82 \text{ V}$$

$$V_{CE} = V_{CC} - I_c \cdot 5k = -2.5$$

No solution exists because the transistor is in saturation mode where g_m is essentially zero.


Whereas for problem 13),

$$V_{CE} = V_{CC} - I_c \cdot 5k = 2.5 - 0.104 \times 5 = 1.98 \text{ V}$$

$$V_{BE} = 0.76 \text{ V}$$

$$V_{CE} > V_{BE}$$

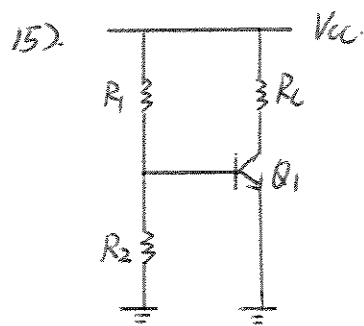So Q_1 is still in forward-active region.



$$\text{Gain} = A_o$$

$$R_{out} = R_o = R_c$$

$$R_{in} = \frac{R_1 R_2}{R_1 + R_2} \parallel r_{\pi}, \quad r_{\pi} = \frac{\beta}{g_m}$$

$$R_{in} = \frac{R_1 R_2}{R_1 + R_2} \parallel \frac{\beta}{g_m}$$

$$\text{Gain} = A_o = g_m R_o \Rightarrow g_m = \frac{A_o}{R_o} = \frac{I_c}{V_T} \Rightarrow I_c = \frac{A_o V_T}{R_o}$$

(I_c is set)

Bias point analysis:

$$\frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_{BE}}{\frac{R_1 R_2}{R_1 + R_2}} = \frac{A_o V_T}{R_o}$$


$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = V_T \ln\left(\frac{A_o V_T}{R_o I_s}\right)$$

$$15) \quad \frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)}{\frac{R_1 R_2}{R_1 + R_2}} = \frac{A_0 V_T}{R_0}$$


$$\frac{R_1 R_2}{R_1 + R_2} = \frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)}{\frac{A_0 V_T}{R_0}}$$

Max R_{in} :
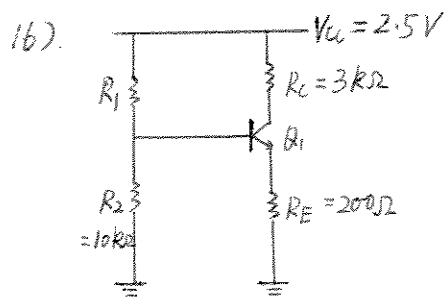
$$\frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)}{\frac{A_0 V_T}{R_0}} // \beta \frac{R_0}{A_0}$$



\Rightarrow

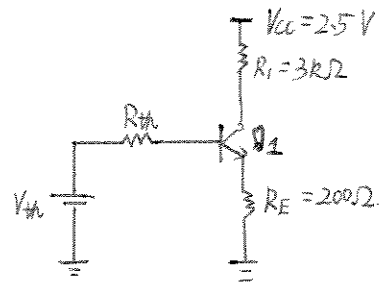

$$a) V_{th} = V_{cc} \cdot \frac{R_2}{R_1 + R_2} = 2.5 \times \frac{10k}{10k + R_1},$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{R_1 (10k)}{R_1 + 10k}$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E \quad (*)$$

Since $I_E = 0.25 \text{ mA}$, $I_B = 0.0025 \text{ mA}$, $I_E = \frac{0.25 \text{ mA}}{99} = 0.2525 \text{ mA}$.

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.696 \text{ V}.$$

$(*)$ becomes

$$2.5 \times \frac{10k}{10k + R_1} = 0.0025 \times \frac{R_1 (10k)}{R_1 + 10k} + 0.696 + 0.2525 \times 0.2$$

So

$$R_1 = 22.73 \text{ k}.$$

b) If R_E deviates by 5%, changes in R_E is 10Ω .

$$I_B = \frac{V_{th} - (V_{BE} + I_E R_E)}{R_{th}} \Rightarrow \frac{I_C}{\beta} = \frac{V_{th} - (V_{BE} + \frac{I_C}{\alpha} R_E)}{R_{th}}$$

$$\Rightarrow I_C = \frac{\beta \alpha (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E}$$


$$\Rightarrow \partial I_C = - \frac{\beta^2 \alpha (V_{th} - V_{BE})}{(\alpha R_{th} + \beta R_E)^2} \partial R_E$$

$$16) \partial R_E = 10, V_{th} = 0.764, V_{BE} = 0.7465, R_{th} = 6.94k, \alpha = 0.99, \beta = 100$$

$$\text{So } \partial I_C = -0.0024 \text{ (mA)}$$

$$\text{The error is } \frac{0.0024}{0.25} \times 100\% = 0.96\% \text{ in } I_C.$$

17).

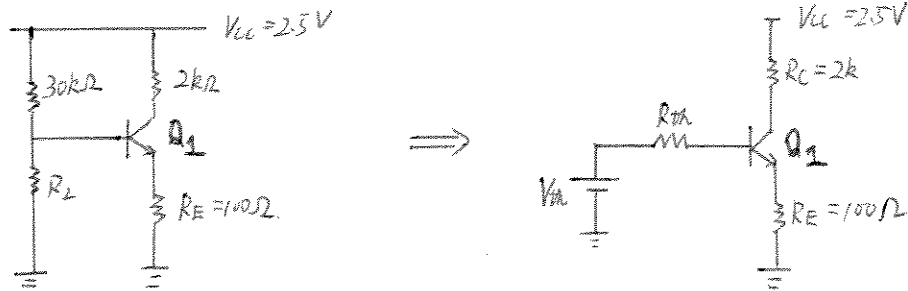

$$V_{th} = \frac{R_2 \times 2.5}{30k + R_2}, \quad R_{th} = \frac{30k \times R_2}{30k + R_2}$$

$V_{CE} \geq V_{BE}$ (To be guaranteed in active mode, soft saturation is not allowed.)

$$V_{CE} = V_{CC} - (I_C \cdot 2k + I_E \cdot 100)$$

$$I_C = \frac{\beta \alpha (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E} \quad \left(\because I_C = \frac{V_{th} - (V_{BE} + \frac{I_C}{\alpha} R_E)}{R_{th}} \right)$$

$$\text{So } V_{CE} = V_{CC} - \left[\frac{\beta \alpha (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E} \cdot 2k + \frac{\beta (V_{th} - V_{BE})}{\alpha R_{th} + \beta R_E} \times 100 \right]$$

$V_{CE} \geq V_{BE}$ means

$$2.5 - \left[\frac{99 \left(\frac{R_2 \times 2.5}{30k + R_2} - V_{BE} \right)}{0.99 \times \frac{30k \times R_2}{30k + R_2} + 100 \times 100} \times 2k + \frac{100 \left(\frac{R_2 \times 2.5}{30k + R_2} - V_{BE} \right)}{0.99 \times \frac{30k \times R_2}{30k + R_2} + 100 \times 100} \times 100 \right] \geq V_{BE} \quad (1)$$

And


$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = V_T \ln \left[\frac{\beta \alpha (V_{th} - V_{BE})}{I_S (\alpha R_{th} + \beta R_E)} \right] \quad (2)$$

There are two unknowns (R_2 and V_{BE}) and two equations (1 and 2)

Since (2) is a nonlinear equation, the problem can be solved by iteration.

$$\text{Maximum } R_2 = 20.343k.$$

18b)

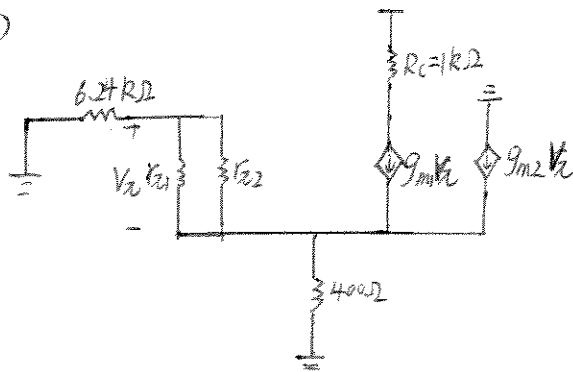


Small - Signal


$$g_{m1} = \frac{I_c}{V_T} = 0.02855 \text{ (S)}$$

$$g_{m2} = 0.0142 \text{ (S)}$$

$$r_{x1} = 3571.4 \text{ (}\Omega\text{)}$$
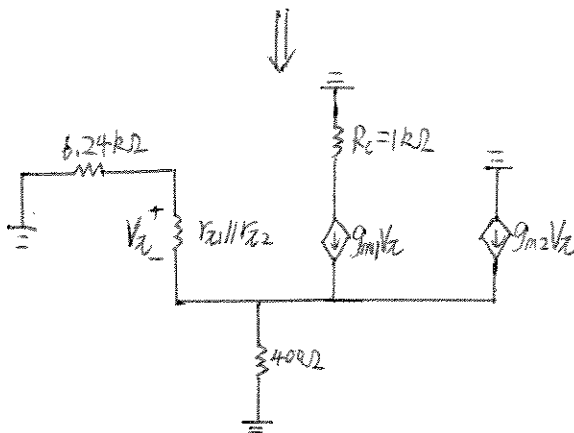
$$r_{x2} = 7042.3 \text{ (}\Omega\text{)}$$



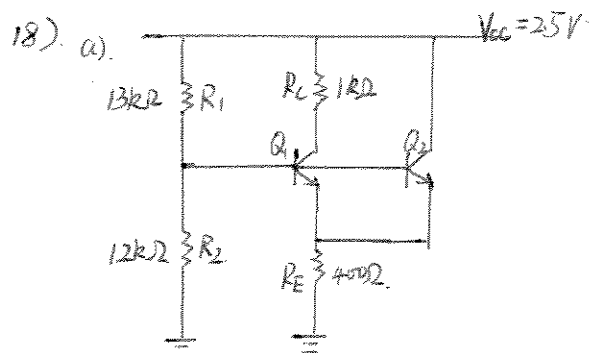


$$I_{S1} = 2 I_{S2} = 5 \times 10^{-16} \text{ A}$$

$$\beta_1 = \beta_2 = 100$$

$$I_{S2} = 2.5 \times 10^{-16} \text{ A}$$

$$V_{th} = V_{cc} \times \frac{R_2}{R_1 + R_2} = 1.2 \text{ V}$$
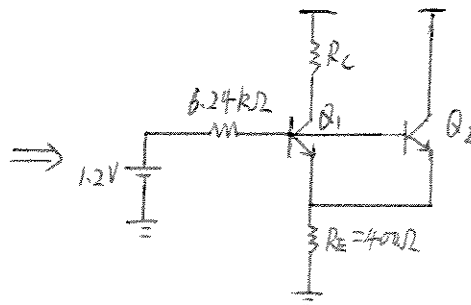
$$R_{th} = R_1 \parallel R_2 = 6.24 \text{ k}\Omega$$



$$I_{B2} = \frac{1.2 - (V_{BE} + 3 I_{E2} \cdot R_E)}{6.24 \text{ k}\Omega}, \quad \text{and} \quad I_{B2} = \frac{I_{C2}}{\beta}$$

$$\text{so } \frac{I_{C2}}{\beta} = \frac{1.2 - (V_{BE} + 3 I_{C2} / \alpha \cdot 0.4 \text{ k}\Omega)}{6.24 \text{ k}\Omega}$$

$$\beta = 100, \quad \alpha = 0.99$$

$$\Rightarrow I_{C2} = \frac{(1.2 - V_{BE}) \cdot (\beta \alpha)}{(\alpha \cdot 6.24 \text{ k}\Omega + 3 \beta \cdot 0.4 \text{ k}\Omega)} = \frac{(1.2 - V_{BE})(99)}{126.1776} \text{ (mA)}$$


$$\text{GUESS } V_{BE} = 0.8, \quad I_{C2} = 0.314 \text{ mA}$$

$$V_{BE} = V_T \ln \left(\frac{I_{C2}}{I_{S2}} \right) = 0.724, \text{ not } 0.8, \text{ so reiterate.}$$

$$I_{C2} = \frac{(1.2 - 0.724)(99)}{126.1776} = 0.3735$$

$$V_{BE} = 26 \ln \left(\frac{0.3735}{2.5 \times 10^{-16}} \right) = 0.728, \text{ close, iterate again}$$
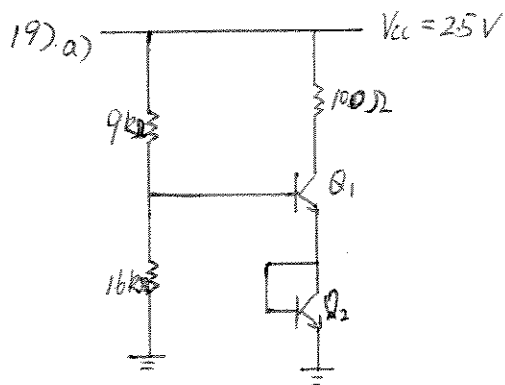
$$\Rightarrow V_{BE} \approx 0.729 \text{ (V)}, \quad I_{C2} = 0.371 \text{ (mA)}, \quad I_{C1} = 0.74 \text{ (mA)}$$




$$I_{S1} = I_{S2} = 4 \times 10^{-16} \text{ A}$$

$$\beta_1 = \beta_2 = 100$$

$$V_A = \infty$$

$$V_{th} = \frac{(2.5)(16k)}{9k + 16k} = 1.6 \text{ V}$$

$$R_{th} = 9k // 16k = 5.76k (\Omega)$$

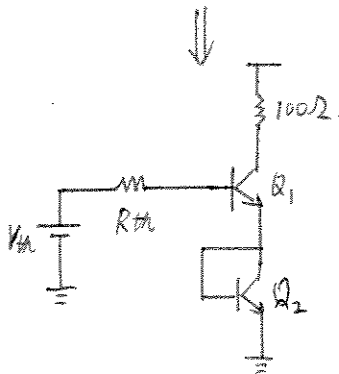

$$I_{B1} = \frac{V_{th} - 2(V_{BE})}{R_{th}}, \quad I_{C1} = \beta I_{B1} = \beta \frac{V_{th} - 2(V_{BE})}{R_{th}} \quad (1)$$

$$V_{BE} = V_T \ln \left(\frac{I_{C1}}{I_{S1}} \right) \quad (2)$$

$$\text{Guess } V_{BE} = 0.7,$$

$$(1) \Rightarrow I_{C1} = 100 \times \frac{1.6 - 2 \times 0.7}{5.76} = 3.47 \text{ (mA)}$$

$$(2) \Rightarrow V_{BE} = V_T \ln \left(\frac{3.47}{4 \times 10^{-16}} \right) = 0.7746, \text{ not } 0.7, \text{ reiterate}$$

$$(1) \Rightarrow I_{C1} = 0.8819$$

$$(2) \Rightarrow V_{BE} = 0.739, \text{ not } 0.7746, \text{ reiterate } \dots$$

After several iterations, V_{BE} converges to 0.755

19) a) $V_{BE} = 0.755 \text{ (V)}$

$$I_{B1} = \frac{V_{Th} - 2V_{BE}}{R_{Th}} = 0.0156 \text{ (mA)}$$

$$I_{C2} = \beta I_{B1} = 1.56 \text{ (mA)}$$


$$V_{CE} = V_{CC} - [I_C \cdot (0.1) + V_{BE}] = 1.589 \text{ (V)}$$

$$I_{C2} = 1.56 \text{ (mA)}$$

$$I_{B2} = (1/\beta) I_{C2} = 0.0156 \text{ (mA)}$$

$$V_{CE2} = V_{BE} = 0.755 \text{ (V)}$$


b).

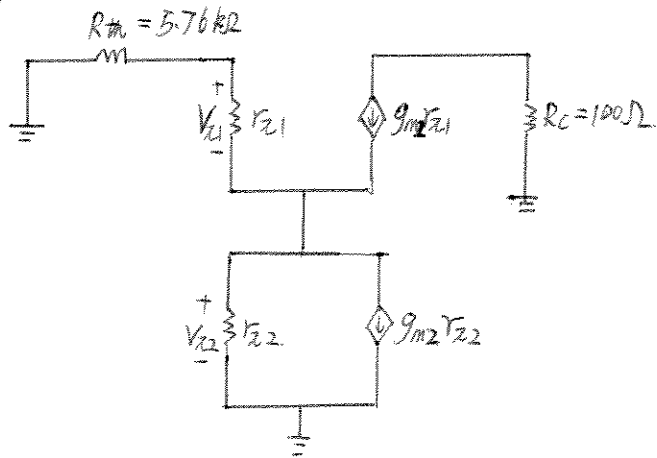

$$g_{m1} = g_{m2} = \frac{I_C}{V_T} = 0.065 \text{ (S)}$$

$$r_{x1} = r_{x2} = \frac{\beta}{g_m} = 1666.7 \text{ (}\Omega\text{)}$$

20)

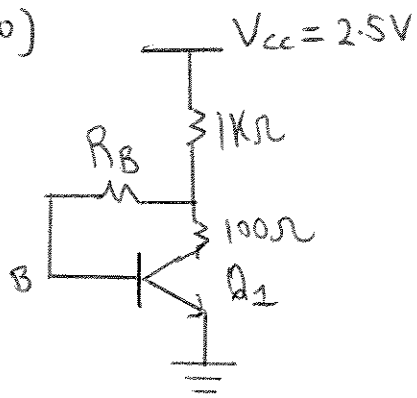

$$I_c = 1 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.750 \text{ V}$$

$$V_B = 2.5 - (I_E (1 \text{ k}\Omega) + I_B R_B) = 0.750 \text{ V}$$

$$I_E = 1.01 \text{ mA}$$


$$I_B = 0.01 \text{ mA}$$

$$V_B = 2.5 - 1.01 - 0.01 R_B = 0.750$$

$$0.74 = 0.01 R_B$$

$$R_B = 74 \text{ k}\Omega$$

21)

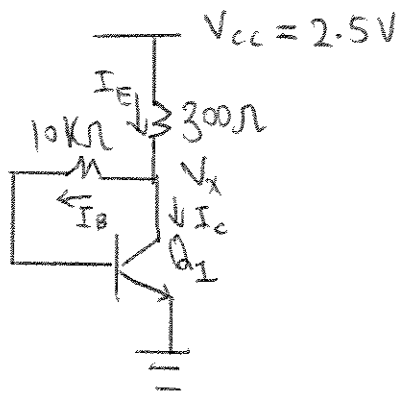

$$V_x = 1.1V$$

$$\beta = 100$$

$$I_s = ?$$

$$I_E = I_B + I_C$$

$$I_E = \frac{2.5 - 1.1}{300\Omega} = 4.67 \text{ mA}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_E = \frac{I_C}{\beta} + I_C = 4.67 \text{ mA}$$


$$I_C = 4.624 \text{ mA}$$

$$I_s = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}}, \quad V_{BE} = 1.1 - \frac{4.624(10K)}{100} = 0.6376V$$

$$I_s = 1.035 \times 10^{-10} \text{ mA}$$

$$I_s = 1.035 \times 10^{-13} \text{ A}$$

22.

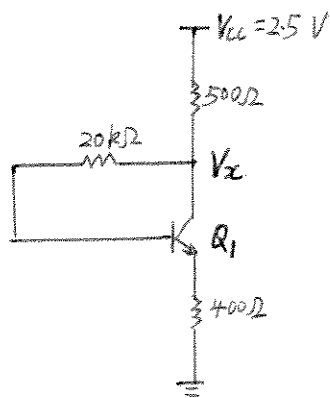

$$I_S = 6 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = \infty$$

$$\frac{V_{CC} - V_X}{0.5k} = I_C + I_B = I_C \left(1 + \frac{1}{\beta}\right) \Rightarrow V_X = 2.5 - 0.5k \cdot \frac{I_C}{\alpha} \quad (1)$$

$$\frac{V_X - (V_{BE} + I_E \cdot 0.4k)}{20k} = \frac{I_C}{\beta} \Rightarrow V_X = (20k) \left(\frac{I_C}{\beta}\right) + V_{BE} + \frac{I_C}{\alpha} \cdot (0.4k) \quad (2)$$

Equating V_X in (1) and (2)

$$2.5 - (0.5k) \left(\frac{I_C}{\alpha}\right) = (20k) \left(\frac{I_C}{\beta}\right) + V_{BE} + \frac{I_C}{\alpha} (0.4k)$$

$$I_C = \frac{2.5 - V_{BE}}{\frac{0.9k}{\alpha} + \frac{20k}{\beta}} = \frac{2.5 - V_{BE}}{1.11k} \quad (3)$$

First iteration $V_{BE} = 0.8$.

$$(3) \Rightarrow I_C = 1.53 \text{ (mA)}$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S}\right) = 0.743, \text{ not } 0.8, \text{ reiterate}$$


$$(3) \Rightarrow I_C = \frac{2.5 - 0.743}{1.11} = 1.583 \text{ (mA)}$$

$$V_{BE} = V_T \ln \left(\frac{1.583}{I_S}\right) = 0.744, \text{ converged.}$$

$$\text{So, } V_{BE} = 0.74 \text{ (V)} \quad I_C = 1.58 \text{ (mA)}, \quad I_B = I_C / \beta = 0.0158 \text{ (mA)}$$

$$V_C = 2.5 - \frac{1.583}{0.99} \times 0.5 = 1.7 \text{ (V)}, \quad V_E = V_C - (I_B \cdot 20k + V_{BE}) = 0.644 \text{ (V)}, \quad V_{CE} = V_C - V_E = 1.056 \text{ (V)}$$

23).

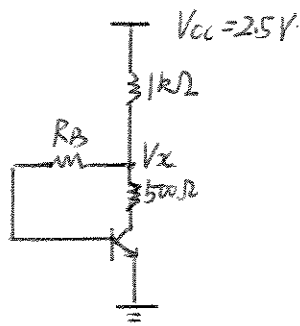

$$I_c = \beta \left(\frac{2.5 - I_E(1k) - V_{BE}}{R_B} \right)$$

$$\frac{I_c R_B}{\beta} = 2.5 - I_E(1k) - V_{BE}$$

$(I_E = \frac{I_c}{\alpha})$

$$I_c = \frac{2.5 - V_{BE}}{\frac{R_B}{\beta} + \frac{1k}{\alpha}} \quad (1)$$

$$V_{BC} \leq 0.2V$$

$$(V_x - I_B R_B) - (V_x - I_c 0.5) \leq 0.2V$$

$$I_c \left(0.5 - \frac{R_B}{\beta} \right) \leq 0.2V$$

$$\left(\frac{2.5 - V_{BE}}{\frac{R_B}{\beta} + \frac{1k}{\alpha}} \right) \left(0.5 - \frac{R_B}{\beta} \right) \leq 0.2V \quad (2)$$

Guess $V_{BE} = 0.75V \Rightarrow R_B \geq 34.513k\Omega$ (From (2))

Let $R_B = 34.513k\Omega$

$$I_c = 1.291mA, \text{ (From (1))}$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.7564V, \text{ not } 0.75, \text{ Iterate}$$

$$V_{BE} = 0.7564V. \Rightarrow R_B \geq 34.461k\Omega$$

23)

$$\text{Let } R_B = 34.461 \text{ k}\Omega$$

$$I_C = 1.287 \text{ mA (From (1))}$$


$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.7563 \text{ V, Converged!!}$$

$$\text{So } I_C = 1.287 \text{ mA, } R_B = 34.46 \text{ k}\Omega$$

$$\text{Check } V_{BC} : V_{BC} = (1.287)(0.5) - \left(\frac{1.287}{100} \right)(34.46)$$

$$V_{BC} = 0.1999998, \text{ less than } 0.2 \text{ V}$$

24). a).

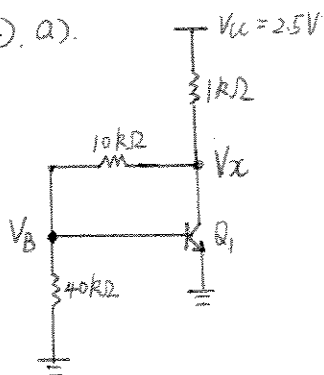

$$I_S = 8 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = \infty$$

$$V_X = 2.5 - \left(\frac{I_C}{\alpha} + \frac{V_B}{40k} \right) \cdot 1k$$

$$V_X = \left(\frac{V_B}{40k} + I_B \right) 10k + V_B = \left(\frac{V_B}{40k} + \frac{I_C}{\beta} \right) 10k + V_B$$

$$\text{Equating } V_X \Rightarrow 2.5 - \left(V_B + \frac{V_B \cdot 1k}{40k} + \frac{V_B \cdot 10k}{40k} \right) = \frac{I_C}{\alpha} \cdot 1k + \frac{I_C}{\beta} \cdot 10k.$$

$$\Rightarrow I_C = \frac{2.5 - 1.275V_B}{\frac{1k}{\alpha} + \frac{10k}{\beta}}$$

Guess $V_B = 0.8$

$$I_C = \frac{1.48}{\frac{1k}{0.99} + \frac{10k}{100}} = 1.33 \text{ mA}$$

Then

$$V_B = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.732, \text{ not } 0.8.$$

Reiterate

$$I_C = \frac{1.5667}{1.11} = 1.413 \text{ mA}$$

$$V_B = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.733$$

So V_B converges to 0.73V


$$I_C = 1.41 \text{ mA}$$

$$I_B = 14.1 \mu\text{A}$$

$$V_{CE} = 2.5V - \left(\frac{1.41}{0.99} + \frac{0.73}{40} \right) \times 1V = 1.06V.$$

$$V_{BE} = 0.73V$$


24 b) Small Signal

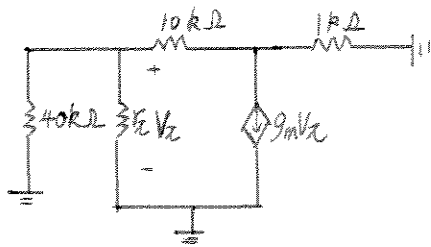

$$g_m = \frac{I_C}{V_T} = 0.054 \text{ S}$$

$$r_x = \frac{\beta}{g_m} = 1844 \Omega$$

25)

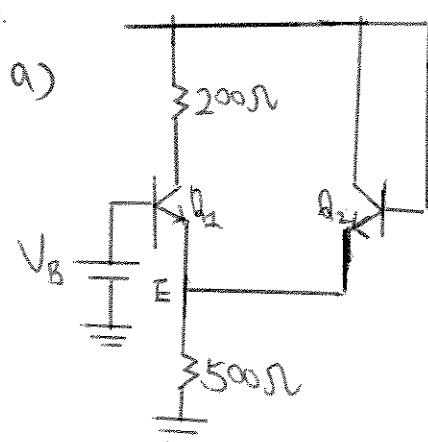

$$I_{C1} = 1\text{mA}, I_{E1} = 1.01\text{mA}$$

$$I_{S1} = I_{S2} = 3 \times 10^{-16}\text{A}$$

$$V_A = \infty$$

$$\beta = 100$$

$$V_E = (I_{E1} + I_{E2}) 0.5\text{k}, V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right) = 0.75\text{V}$$

$$V_E = 2.5 - V_{BE2}$$

$$V_B - (1.01 + I_{E2}) 0.5 = 0.75\text{V}$$

$$\text{Guess } V_{BE2} = 0.7\text{V}$$

$$V_E = 1.8 \Rightarrow I_{E1} + I_{E2} = 3.6\text{mA} \Rightarrow I_{E2} = 2.59\text{mA}$$

$$I_{C2} = 2.5641\text{mA} \Rightarrow V_{BE2} = V_T \ln\left(\frac{I_{C2}}{I_S}\right) = 0.774\text{V}$$

Reiterate

$$V_E = 1.726 \Rightarrow I_{E2} = 2.442\text{mA}, I_{C2} = 2.4176\text{mA}$$

$$V_{BE2} = V_T \ln\left(\frac{I_{C2}}{I_S}\right) = 0.773, \text{ converged!!}$$

$$V_{BE} = 0.773\text{V}, I_{C2} = 2.42\text{mA}, I_{E2} = 2.44\text{mA}$$

$$V_B = 0.75 + (1.01 + 2.44) 0.5 = 2.475\text{V}$$


$$V_C = 2.5 - (1 \times 0.2) = 2.3$$

Q_1 in soft-saturation region.

25

b)

Small Signal Model

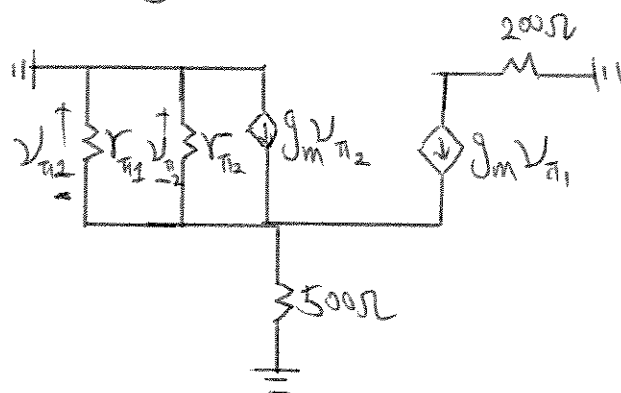

$$g_{m1} = \frac{1 \text{ mA}}{26 \text{ mV}} = 0.0385 \left(\frac{1}{\Omega} \right) \text{ S}$$

$$r_{\pi1} = \frac{100}{0.0385} = 2.6 \text{ k}\Omega$$


$$g_{m2} = \frac{2.42 \text{ mA}}{26 \text{ mV}} = 0.0931 \left(\frac{1}{\Omega} \right) \text{ S}$$

$$r_{\pi2} = \frac{100}{0.0931} = 1.07 \text{ k}\Omega$$


$$2b). \beta_{npn} = 2\beta_{mp} = 100$$

$$I_S = 9 \times 10^{-16} \text{ A}$$

$$V_A = \infty$$

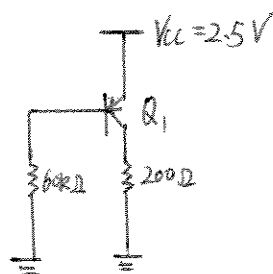

(a)

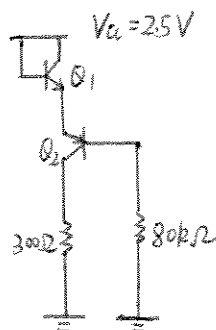

(b)

$$a) I_C = \frac{2.5 - |V_{BE}|}{60k} \beta_{npn}, \quad V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

$$\text{Guess } |V_{BE}| = 0.8 \Rightarrow I_C = 1.42 \text{ mA}$$

$$|V_{BE}| = 26 \times 10^{-3} \ln\left(\frac{1.42}{9 \times 10^{-16}}\right) = 0.730 \text{ (V)}, \text{ not } 0.8$$

$$\text{Reiterate, } I_C = \frac{2.5 - 0.73}{60k} \times 50 = 1.475 \text{ mA}$$

$$|V_{BE}| = 26 \times 10^{-3} \ln\left(\frac{1.42}{9 \times 10^{-16}}\right) = 0.731 \text{ (V)}$$

$$\text{Reiterate, } I_C = \frac{2.5 - 0.731}{60k} \times 50 = 1.474 \text{ mA}$$

$$|V_{BE}| = 26 \times 10^{-3} \ln\left(\frac{1.474}{9 \times 10^{-16}}\right) = 0.731 \text{ (V)}, \text{ converged.}$$

$$Q_1: |V_{BE}| = 0.731 \text{ V}, I_C = 1.47 \text{ mA}, I_B = 29.4 \mu\text{A}$$

$$|V_{CE}| = 2.206 \text{ V}$$

In forward active region.

26)

$$b). \quad I_{C2} = \frac{2.5 - (V_{BE1} + |V_{BE2}|)}{80k} \quad (1)$$

$$I_{C2} \cdot \frac{\beta_{npn} + 1}{\beta_{npn}} = \frac{I_{C1} (\beta_{npn} + 1)}{\beta_{npn}} \quad \Rightarrow \quad I_{C1} = \frac{2(\beta_{npn} + 1)}{2\beta_{npn} + 1} I_{C2} = 1.0099 I_{C2} \quad (2)$$

$$\beta_{npn} = 2\beta_{pnp} = 100$$

$$V_{BE1} = V_T \ln \left(\frac{I_{C1}}{I_S} \right) \quad (3)$$

$$V_{BE2} = V_T \ln \left(\frac{I_{C2}}{I_S} \right) \quad (4)$$

Four unknowns: I_{C1} , I_{C2} , V_{BE1} , V_{BE2} . Four equations: (1), (2), (3), (4)

Solve by iteration since (3) and (4) are exponential equations.

Guess $V_{BE2} = V_{BE1} = 0.8$

$$(1) \Rightarrow I_{C2} = 50 \times \left(\frac{2.5 - 1.6}{80k} \right) A = 0.5625 mA$$

$$(2) \Rightarrow I_{C1} = 0.568 mA$$

$$(3) \Rightarrow V_{BE1} = V_T \ln \left(\frac{0.568}{9 \times 10^{-13}} \right) V = 0.706 V$$

$$(4) \Rightarrow V_{BE2} = V_T \ln \left(\frac{0.5625}{9 \times 10^{-13}} \right) V = 0.706 V$$

Reiterate,

$$I_{C2} = 0.68 mA, \quad I_{C1} = 0.6867 mA, \quad V_{BE1} = 0.711 V, \quad V_{BE2} = 0.711 V$$

Reiterate,

$$I_{C2} = 0.674 mA, \quad I_{C1} = 0.680 mA, \quad V_{BE1} = 0.711 V, \quad V_{BE2} = 0.711 V$$

So,

$$I_{C1} = 0.680 mA$$

$$I_{B1} = 0.8 \mu A$$

$$V_{BE1} = 0.711 V$$

$$V_{CE1} = 0.711 V$$



$$I_{C2} = 0.674 mA$$

$$I_{B2} = 13.48 \mu A$$

$$|V_{BE2}| = 0.711 V$$

$$|V_{CE2}| = 2.5 V - 0.711 V - (0.674)(0.3) V = 1.5868 V$$


27. a)

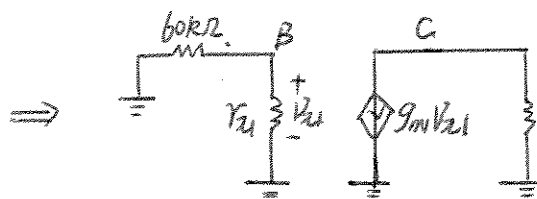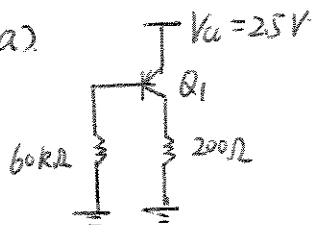


$$g_{m1} = \frac{I_C}{V_T} = \frac{1.47 \text{ mA}}{26 \text{ mV}} = 0.0565 \text{ S}$$

$$r_{e1} = \frac{\beta}{g_{m1}} = 884 \Omega$$

b)

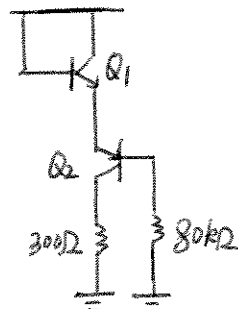

\Rightarrow

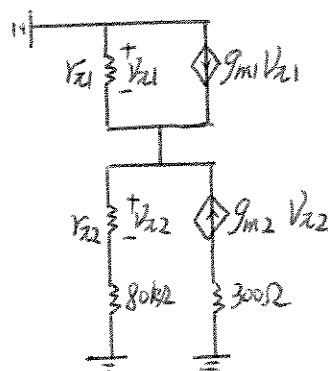

$$g_{m1} = \frac{I_{C1}}{V_T} = 0.02615 \text{ S}$$


$$r_{e1} = 3823.5 \Omega$$

$$g_{m2} = \frac{I_{C2}}{V_T} = 0.0259 \text{ S}$$

$$r_{e2} = 1928.8 \Omega$$

28)

a)

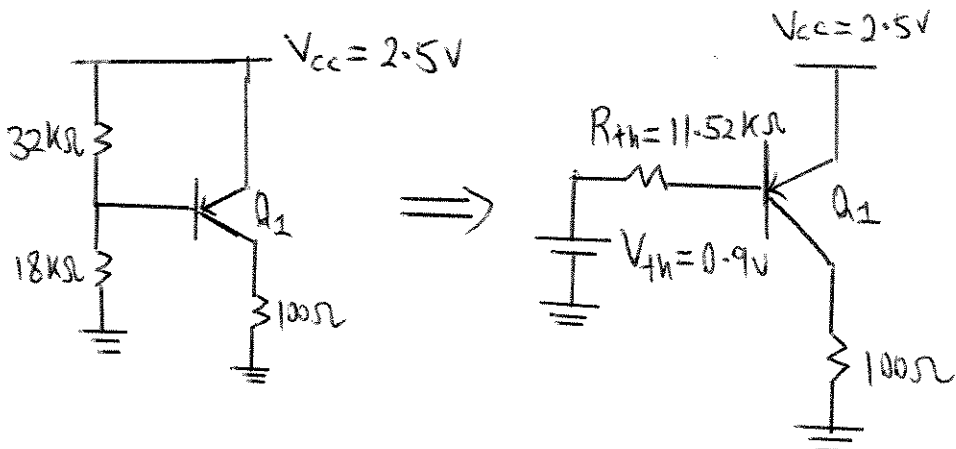

$$I_c = \beta_{npn} \left(\frac{2.5 - |V_{BE}| - V_{th}}{R_{th}} \right)$$

Guess $|V_{BE}| = 0.7 \text{ V}$, $I_c = 3.91 \text{ mA}$

$$|V_{BE}| = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.757 \text{ V}$$

Reiterate, $|V_{BE}| = 0.757 \text{ V}$, $I_c = 3.66 \text{ mA}$

$$|V_{BE}| = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.755 \text{ V}$$

Reiterate, $|V_{BE}| = 0.755 \text{ V}$, $I_c = 3.67 \text{ mA}$

$$|V_{BE}| = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.755 \text{ V, Converged!!}$$

$$V_c = (3.67 \text{ mA})(0.1 \text{ k}\Omega) = 0.367 \text{ V}, \quad V_b = 2.5 - 0.755 = 1.745 \text{ V}$$


Q_1 in forward active.

Bias point:

$$I_c = 3.67 \text{ mA} \quad |V_{BE}| = 0.755$$

$$I_B = 73.4 \text{ }\mu\text{A} \quad |V_{CE}| = 2.5 - 0.367 = 2.133 \text{ V}$$

28)
b)

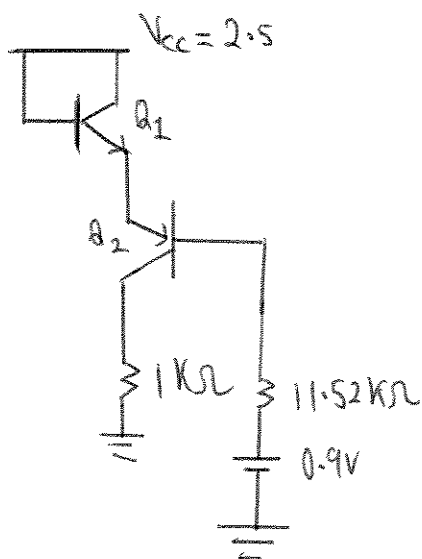

$$I_{C2} = \frac{2.5 - (V_{BE1} + V_{BE2}) - 0.9}{11.52 \text{ k}} 50$$

$$I_{C1} = I_{C2} (1.0099)$$

(From β relation)

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right)$$

$$|V_{BE2}| = V_T \ln\left(\frac{I_{C2}}{I_S}\right)$$

Guess, $V_{BE1} = V_{BE2} = 0.7 \text{ V}$

$$I_{C2} = 0.868 \text{ mA}, \quad I_{C1} = 0.877 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right) = 0.718 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{C2}}{I_S}\right) = 0.717$$

Reiterate, $V_{BE1} = 0.718 \text{ V}, \quad |V_{BE2}| = 0.717 \text{ V}$

$$I_{C2} = 0.716 \text{ mA}, \quad I_{C1} = 0.723 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right) = 0.713 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{C2}}{I_S}\right) = 0.712 \text{ V}$$

Reiterate, $V_{BE1} = 0.713 \text{ V}, \quad |V_{BE2}| = 0.712 \text{ V}$

$$I_{C2} = 0.760 \text{ mA}, \quad I_{C1} = 0.767 \text{ mA}$$

$$V_{BE1} = 0.714 \text{ V}, \quad |V_{BE2}| = 0.714 \text{ V}$$

28)

b)

Reiterate, $V_{BE1} = 0.714 \text{ V}$, $|V_{BE2}| = 0.714 \text{ V}$

$$I_{C2} = 0.747 \text{ mA}, I_{C1} = 0.754 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.714 \text{ V},$$

$$|V_{BE2}| = 0.714 \text{ V}$$

$$V_{B2} = \frac{(0.747 \text{ mA}) (11.52 \text{ k}\Omega)}{50} + 0.9 = 1.07 \text{ V}$$

$$V_{C2} = (0.747 \text{ mA})(1 \text{ k}\Omega) = 0.747 \text{ V}$$

Q₂ is in forward-active region. Q₁ is always in forward-active region.

Bias point:

$$V_{BE1} = 0.714 \text{ V}$$

$$I_{C1} = 0.754 \text{ mA}$$

$$I_{B1} = 7.54 \mu\text{A}$$

$$V_{CE1} = 0.714 \text{ V}$$

$$|V_{BE2}| = 0.714 \text{ V}$$


$$I_{C2} = 0.747 \text{ mA}$$

$$I_{B2} = 14.94 \mu\text{A}$$


$$|V_{CE2}| = 2.5 - 0.714 - 0.747 = 1.039 \text{ V}$$

29)


a)

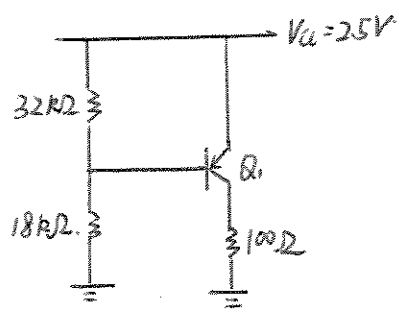

\Rightarrow

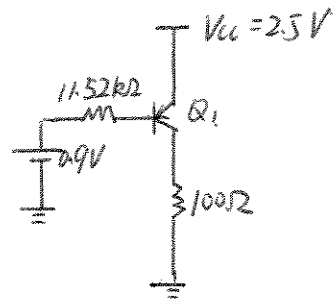


Small Signal:

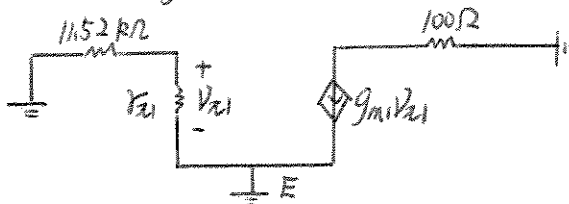


$$g_{m1} = \frac{3.67 \text{ mA}}{26 \text{ mV}} = 0.141 \text{ S}$$

$$r_{e1} = \frac{50}{0.141} \Omega = 354.2 \Omega$$

b)

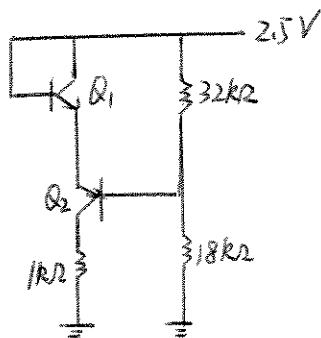

\Rightarrow

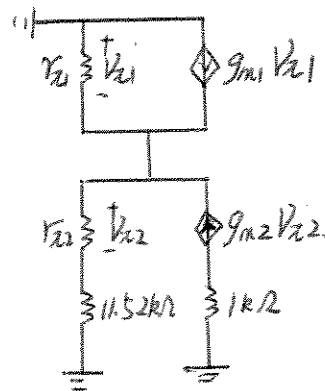


$$g_{m1} = 0.029 \text{ S}$$

$$r_{e1} = 3448.3 \Omega$$

$$g_{m2} = 0.0287 \text{ S}$$


$$r_{e2} = 17403 \Omega$$

30)

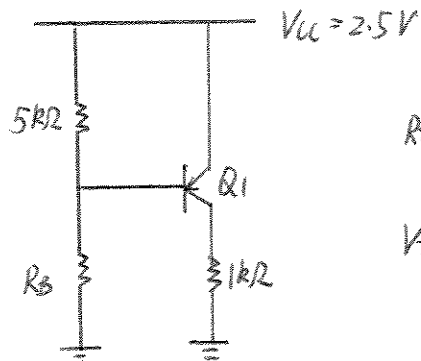

$$R_{th} = \frac{(R_B)(5k\Omega)}{R_B + 5k\Omega}$$
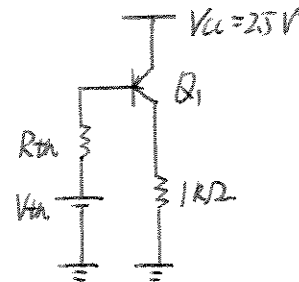
$$V_{th} = \frac{R_B}{R_B + 5k\Omega} \cdot 2.5V$$



$$\beta = 50, I_s = 8 \times 10^{-16} A, V_A = \infty$$

Edge of saturation: $|V_{BE}| = |V_{CE}|$

$$I_c = \frac{50(2.5 - |V_{BE}| - V_{th})}{R_{th}}, |V_{CE}| = 2.5 - I_c(1k\Omega) = |V_{BE}|$$

$$2.5 - \frac{50(2.5 - |V_{BE}| - V_{th})(1k\Omega)}{R_{th}} = |V_{BE}|$$

Substitute in R_{th} and V_{th} and rearrange:

$$12.5R_B + 50|V_{BE}|R_B - |V_{BE}|(5k)R_B = 625 - |V_{BE}|250 \quad (1)$$

Guess $|V_{BE}| = 0.7V$, $(1) \Rightarrow 44R_B = 450 \Rightarrow R_B = 10.23k\Omega$

$$V_{th} = 1.68V, I_c = 1.7857mA$$

$$R_{th} = 3.36k\Omega, |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.739V, \text{ not } 0.7V, \text{ Iterate}$$

$$|V_{BE}| = 0.739V, (1) \Rightarrow 45.755R_B = 440.25$$

$$R_B = 9.62k\Omega$$

$$V_{th} = 1.645V, I_c = 1.763mA$$

$$R_{th} = 3.29k\Omega, |V_{BE}| = 0.739V, \text{ Converged.}$$

3°)

So $\pm 5\%$ of $9.62 \text{ k}\Omega$.

+5% Case:

$$9.62 \text{ k}\Omega + 5\% = 10.101 \text{ k}\Omega$$

$$V_{th} = 1.67 \text{ V}, R_{th} = 3.345 \text{ k}\Omega$$

$$I_c = \frac{(2.5 - 0.74 - 1.67)}{3.345} 50 = 1.3455 \text{ mA} \quad (\text{Assume } |V_{BE}| = 0.74 \text{ V})$$

$$\text{check for } |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.732 \text{ V}, \text{ iterate once}$$

$$I_c = 1.4651 \text{ mA}, |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.734 \text{ V}, \text{ converged}$$

$$|V_{BE}| \approx 0.734, |V_{CE}| = 2.5 - 1.4651(1 \text{ k}\Omega) = 1.0349 \text{ V}$$

$$V_{BC} = 0.3009 \text{ V} \quad (\text{Reverse bias})$$

-5% Case:

$$9.62 \text{ k}\Omega - 5\% = 9.139 \text{ k}\Omega$$

$$V_{th} = 1.616 \text{ V}, R_{th} = 3.23184 \text{ k}\Omega$$


$$I_c = \frac{(2.5 - 0.74 - 1.616)}{(3.23184)} 50 = 2.228 \text{ mA}, |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.745 \text{ V}$$

$$\text{reiterate: } |V_{BE}| = 0.745 \text{ V}, I_c = 2.150 \text{ mA}$$

$$\text{Verify } V_{BE}, |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.744 \text{ V}, \text{ converged}$$

$$|V_{CE}| = 2.5 - 2.150(1 \text{ k}\Omega) = 0.35, |V_{BE}| = 0.744 \text{ V}, V_{BC} = -0.394 \text{ V} \quad (\text{Forward Bias})$$

31)

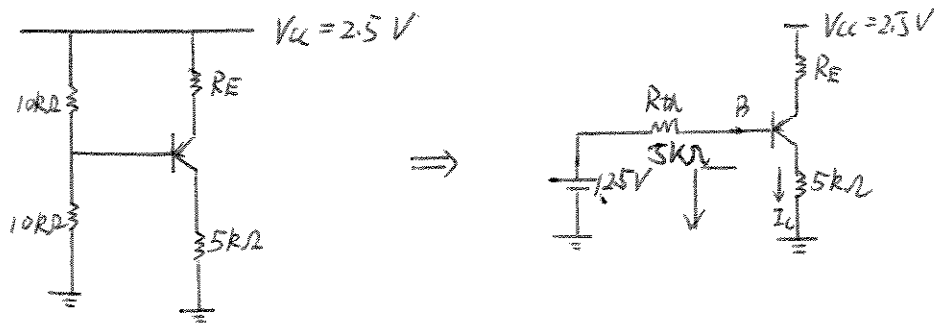

$$V_{BC} = 1.25 + I_B R_{th} - I_C 5k = 0.3$$

$$1.25 + \frac{I_C 5}{\beta} - I_C 5k = 0.3$$

$$\beta = 50 \Rightarrow I_C = 0.1939 \text{ mA}$$

$$|V_{BE}| = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.682 \text{ V}$$

$$I_B = \frac{(2.5 - \frac{I_C R_E}{\alpha} - |V_{BE}|) - 1.25}{5k}$$

$$\alpha = 0.9804$$

$$I_B = 0.003878 \text{ mA}$$

$$|V_{BE}| = 0.682 \text{ V}$$

$$I_C = 0.1939 \text{ mA}$$

$$R_E = 2.89 \text{ k}\Omega$$

If R_E is halved $\Rightarrow R_E = 1.44 \text{ k}\Omega$

$$I_C = \beta \left(\frac{2.5 - |V_{BE}| - 1.25 - \alpha I_C R_E}{5k} \right)$$

$$I_C = \frac{62.5 - 50|V_{BE}|}{78.44}, \text{ Guess } |V_{BE}| = 0.682 \text{ V}$$

31)

$$I_c = 0.3621 \text{ mA}$$

$$\text{Verify } |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.698 \text{ V, not } 0.682 \text{ V}$$

reiterate

$$I_c = \frac{62.5 - 50(0.698)}{78.44} = 0.352 \text{ mA}$$


$$\text{Verify } |V_{BE}| = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.697 \text{ V, converged}$$

so $I_c = 0.352 \text{ mA}$, which is 1.82 times of 0.1939 mA

$$V_{BC} = 1.25 + \frac{(0.352)(5 \text{ k}\Omega)}{50} - (0.352)(5 \text{ k}\Omega) = -0.4748 \text{ V}$$

which drive Q_1 into saturation.

322

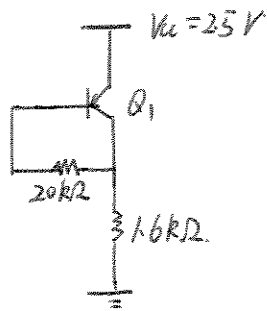

$$\beta = 80$$

$$V_A = \infty$$

$$V_B = (I_B)(20k\Omega) + I_E(16k\Omega)$$

$$I_C = 1mA$$

$$I_B = \frac{1}{80}mA, \quad I_E = \frac{1}{0.98765}mA = 1.0125mA$$

$$V_B = \left(\frac{1}{80}\right)(20)V + (1.0125)(1.6)V$$


$$= 1.87V$$

$$|V_{BE}| = 25V - 1.87V = 0.63V$$

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \Rightarrow I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = \frac{1mA}{e^{\left(\frac{0.63}{0.026}\right)}}$$

$$I_S = 3 \times 10^{-11}mA$$

33)

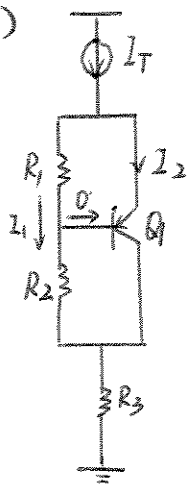

If Base current is neglected, $I_C = I_E$


$$I_1 = \frac{V_E - V_C}{R_1 + R_2}$$

$$|V_{BE}| = I_1 R_1 = \frac{V_E - V_C}{R_1 + R_2} R_1 = \frac{|V_{CE}|}{R_1 + R_2} R_1$$

$$\text{So } \frac{|V_{CE}|}{|V_{BE}|} = \frac{R_1 + R_2}{R_1}$$

Let $A = \frac{R_1 + R_2}{R_1}$, $|V_{CE}| = A |V_{BE}|$, thus $|V_{BE}|$ is multiplied.

34)

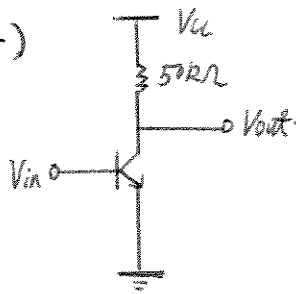

$$A_V = g_m R_C = 20$$


$$\frac{I_C R_C}{V_T} = 20 \Rightarrow I_C = \frac{20 V_T}{R_C}$$

$$I_C = 0.0104 \text{ mA}$$

$$V_{CC} - (50 \text{ k}\Omega) (0.0104 \text{ mA}) = V_{BE}$$

$$\Rightarrow V_{CC} - 50 \times 0.0104 \text{ V} = 0.8 \text{ V}$$

$$\Rightarrow V_{CC} = 1.32 \text{ V}$$

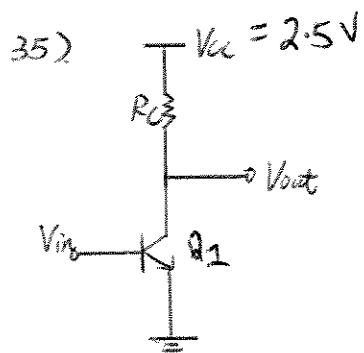

$$V_A = 10V, r_o = \frac{V_A}{I_C}, g_m = \frac{I_C}{V_T}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = g_m (R_C // r_o) = g_m \left(\frac{R_C r_o}{R_C + r_o} \right) = \frac{R_C V_A}{V_T (R_C + \frac{V_A}{I_C})}$$


As the equation above shows, a large gain means a large I_C . However, a large I_C will drive Q_1 into saturation. So a tradeoff must be made. The maximum limit for I_C is when it drives Q_1 into the edge of saturation, namely, $V_{BE} = V_{CE}$.

$$V_{CE} = V_{CC} - I_C (1K)$$

$$V_{BE} = 0.8V, V_{CC} = 2.5V$$

$$0.8 = 2.5 - I_C 1K$$

$$I_C = 1.7mA$$

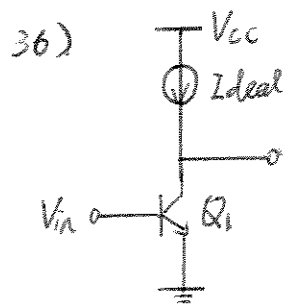


$$A_v = 50$$

$$R_{out} = R_o = 10k\Omega$$

$$A_v = g_m R_{out} = \frac{I_c}{V_T} R_{out} = 50$$

$$I_c = 50 \left(\frac{V_T}{R_{out}} \right) = 0.13mA$$

37).

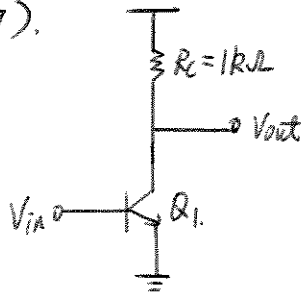


$$I_c = I_s \exp \left(\frac{V_{BE}}{2V_T} \right)$$

$$g_m = \frac{\partial I_c}{\partial V_{BE}} = \frac{I_c}{2V_T}$$

$$R_{out} = R_c$$

$$\left| \frac{V_{out}}{V_{in}} \right| = g_m R_{out} = \frac{I_c R_c}{2V_T} = \frac{(1mA)(1k\Omega)}{(2)(0.026V)} = 19.23$$

38). (Find A_v , R_{in} , R_{out})

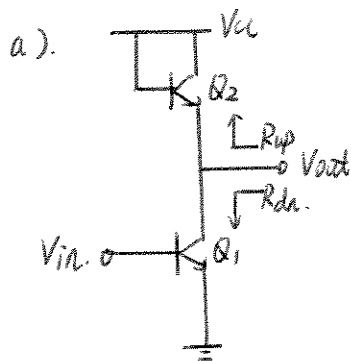

$$V_A = \infty$$


$$R_{out} = R_{up} // R_{dn}$$

$$R_{up} = \frac{1}{g_{m2}} // r_{\pi 2}, R_{dn} = \infty$$

$$R_{out} = \frac{1}{g_{m2}} // r_{\pi 2}$$

$$R_{in} = r_{\pi 1}$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left(\frac{1}{g_{m2}} // r_{\pi 2} \right)$$

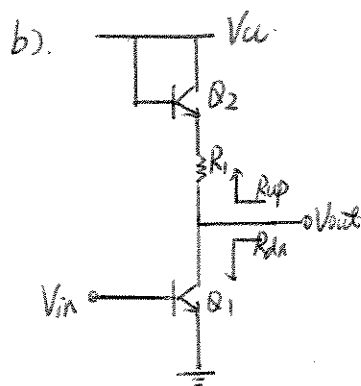

$$V_A = \infty$$

$$R_{up} = R_1 + \frac{1}{g_{m2}} // r_{\pi 2}$$


$$R_{dn} = \infty$$

$$R_{out} = R_{up} // R_{dn} = R_1 + \frac{1}{g_{m2}} // r_{\pi 2}$$

$$R_{in} = r_{\pi 1}$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left(R_1 + \frac{1}{g_{m2}} // r_{\pi 2} \right)$$

38
c).

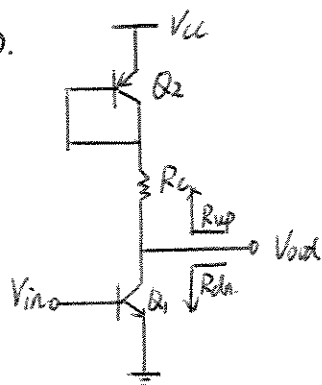


$$V_A = \infty$$


$$R_{up} = R_C + \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right), R_{dn} = \infty$$

$$R_{out} = R_C + \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right), R_{in} = r_{\pi 1}$$
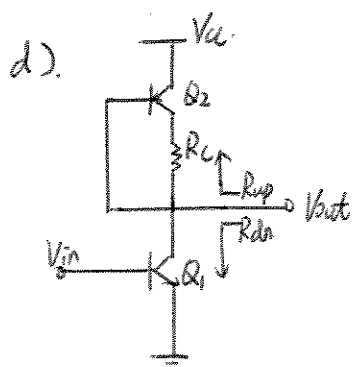
$$A_v = g_{m2} \left(R_C + \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right) \right)$$



Find R_{up} :

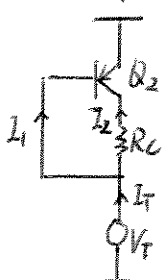

$$I_T = I_1 + I_2 = \frac{I_2}{\beta} + I_2$$

$$I_2 = g_m V_T, I_T = \frac{g_m V_T}{\beta} + g_m V_T$$

$$\frac{V_T}{I_T} = R_{up} = \frac{1}{\left(\frac{g_m}{\beta} + g_m \right)} = r_{\pi 2} \parallel \frac{1}{g_{m2}}$$

$$R_{dn} = \infty$$


$$R_{out} = R_{up} \parallel R_{dn} = r_{\pi 2} \parallel \frac{1}{g_{m2}}$$

$$R_{in} = r_{\pi 1}$$

$$A_v = g_{m2} \left(r_{\pi 2} \parallel \frac{1}{g_{m2}} \right)$$

38).

c).

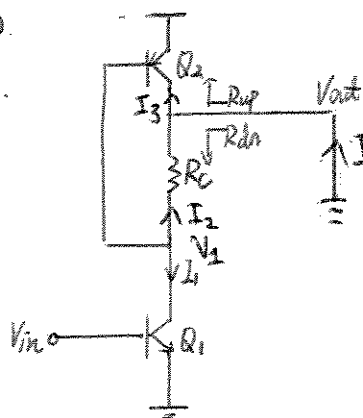

$$R_{up} = \infty$$

$$R_{dn} = R_c + r_{\pi 2}$$

$$R_{out} = R_c + r_{\pi 2}$$

$$|A_v| = G_m R_{out}$$

$$\text{where } G_m = \left| \frac{I_{out}}{V_{in}} \right|$$

$$I_{out} + I_2 = I_3, \quad I_2 = \frac{V_1}{R_c}$$

$$I_3 = V_1 g_{m2}$$

$$V_1 = -I_1 (R_c \parallel r_{\pi 2}) = -g_{m1} V_{in} (R_c \parallel r_{\pi 2})$$


$$I_{out} = I_3 - I_2 = V_1 \left(g_{m2} - \frac{1}{R_c} \right)$$

$$I_{out} = -g_{m1} V_{in} (R_c \parallel r_{\pi 2}) \left(g_{m2} - \frac{1}{R_c} \right)$$

$$G_m = \left| \frac{I_{out}}{V_{in}} \right| = g_{m1} (R_c \parallel r_{\pi 2}) \left(g_{m2} - \frac{1}{R_c} \right)$$

$$|A_v| = g_{m1} (R_c \parallel r_{\pi 2}) \left(g_{m2} - \frac{1}{R_c} \right) (R_c + r_{\pi 2})$$

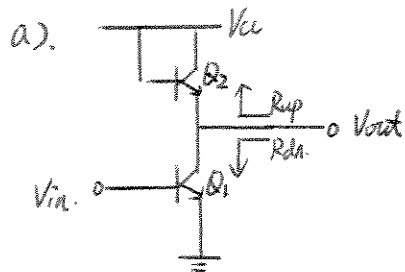39). $V_A < \infty$, find A_v , R_{in} , R_{out}




$$R_{up} = \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}, \quad R_{dn} = r_{o1}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o1} \parallel r_{o2}$$

$$R_{in} = r_{\pi 1}$$

$$|A_v| = g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{\pi 1} \parallel r_{o1} \parallel r_{o2} \right)$$

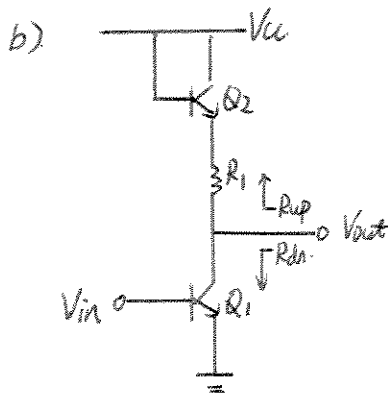


$$R_{up} = R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$$

$$R_{dn} = r_{o1}$$

$$R_{out} = r_{o1} \parallel \left(R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$|A_v| = g_{m1} \left[r_{o1} \parallel \left(R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right) \right]$$

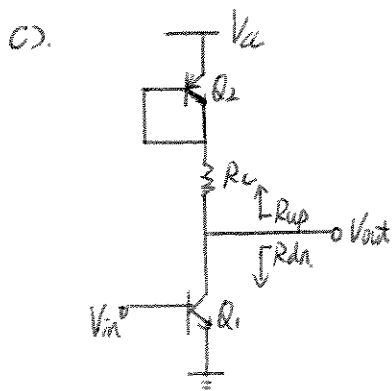

$$R_{up} = R_c + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$$


$$R_{dn} = r_{o1}$$

$$R_{in} = r_{\pi 1}$$


$$R_{out} = r_{o1} \parallel \left(R_c + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

$$|A_v| = g_{m1} \left[r_{o1} \parallel \left(R_c + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right) \right]$$

39d)

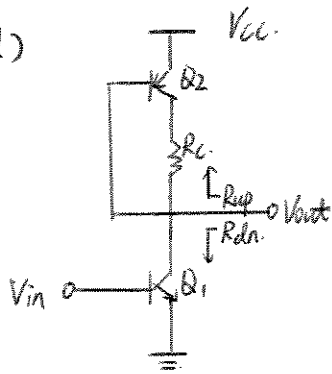

Find R_{up} :

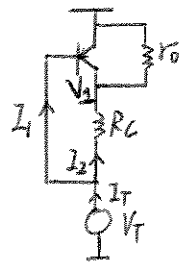

$$I_T = I_1 + I_2$$

$$I_2 = \frac{V_T - V_1}{R_c}, \quad I_1 = \frac{g_m V_T}{\beta}$$

$$V_1 = (I_2 - g_m V_T) r_o$$

$$I_2 = \frac{V_T - (I_2 - g_m V_T) r_o}{R_c}$$

$$I_2 = \frac{(1 + g_m r_o) V_T}{R_c + r_o}$$

$$I_T = \frac{g_m V_T}{\beta} + \frac{(1 + g_m r_o) V_T}{R_c + r_o}$$

$$\frac{V_T}{I_T} = R_{up} = \frac{1}{\frac{g_m}{\beta} + \frac{(1 + g_m r_o)}{R_c + r_o}}$$

$$R_{up} = Y_{\pi 2} \parallel \frac{(R_c + r_{o2})}{1 + g_{m2} r_{o2}}$$

$$R_{dn} = r_{o1}$$


$$R_{out} = Y_{\pi 2} \parallel \frac{(R_c + r_{o2})}{1 + g_{m2} r_{o2}} \parallel r_{o1}$$

$$R_{in} = Y_{\pi 2}$$

$$|A_v| = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left(Y_{\pi 2} \parallel \frac{(R_c + r_{o2})}{1 + g_{m2} r_{o2}} \parallel r_{o1} \right)$$

$$R_{up} = Y_{\pi 2} \parallel \frac{R_c + r_o}{(1 + g_m r_o)}$$

39 e).

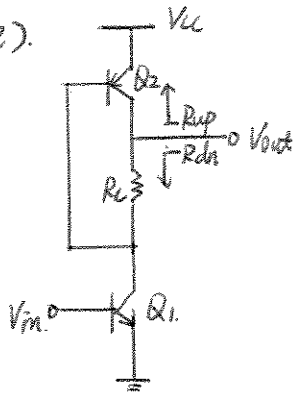

$$R_{up} = r_{o2}$$


$$R_{dn} = R_c + (r_{o1} \parallel r_{z2})$$

$$R_{in} = r_{z1}$$

$$R_{out} = r_{o2} \parallel [R_c + (r_{o1} \parallel r_{z2})]$$

$$|A_v| = G_m R_{out}$$

Finding G_m :

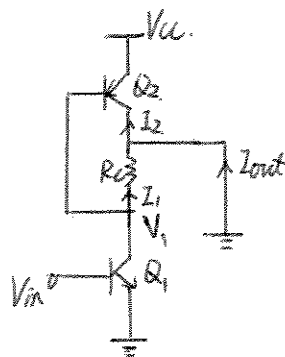

$$G_m = \left| \frac{I_{out}}{V_{in}} \right|$$

$$I_{out} + I_1 = I_2$$

$$I_{out} = I_2 - I_1$$

$$I_1 = \frac{V_1}{R_c} \quad I_2 = V_1 g_{m2}$$

$$V_1 = -(g_{m1} V_{in}) (r_{o1} \parallel R_c \parallel r_{z2})$$

$$I_{out} = V_1 \left(g_{m2} - \frac{1}{R_c} \right) = -g_{m1} V_{in} (r_{o1} \parallel R_c \parallel r_{z2}) \left(g_{m2} - \frac{1}{R_c} \right)$$

$$G_m = \left| \frac{I_{out}}{V_{in}} \right| = g_{m1} (r_{o1} \parallel R_c \parallel r_{z2}) \left(g_{m2} - \frac{1}{R_c} \right)$$

$$|A_v| = g_{m1} (r_{o1} \parallel R_c \parallel r_{z2}) \left(g_{m2} - \frac{1}{R_c} \right) \left[r_{o2} \parallel [R_c + (r_{o1} \parallel r_{z2})] \right]$$

40)

Gain of a degenerated CE stage ($V_A = \infty$)

$$A_v = \frac{-R_c}{\frac{1}{g_m} + R_E} = \frac{-R_c g_m}{1 + R_E g_m}$$

$$\frac{\partial A_v}{\partial I_c} = R_c \left(\frac{g_m R_E}{(1 + R_E g_m)^2} \frac{\partial g_m}{\partial I_c} - \frac{\partial g_m / \partial I_c}{1 + g_m R_E} \right)$$

$$\frac{\partial g_m}{\partial I_c} = \frac{1}{V_T} = \frac{1}{26 \text{ mV}} = 38.46 \left(\frac{1}{V} \right)$$

a) $g_m R_E = 3$

$$\frac{\partial A_v}{\partial I_c} = R_c (-2.404) \quad , \quad \partial I_c = 0.1 I_c$$

$$\partial A_v = -R_c I_c (0.24)$$

$$\text{Relative change in gain} = \frac{\partial A_v}{A_v} = \frac{-0.24 (R_c I_c)}{-\frac{R_c I_c}{V_T (1 + R_E g_m)}} = 2.5\%$$

40)


$$b) \quad g_m R_E = 7$$

$$\frac{\partial A_v}{\partial I_c} = -R_c 0.6$$

$$\partial A_v = -R_c I_c (0.06)$$

Relative change in gain
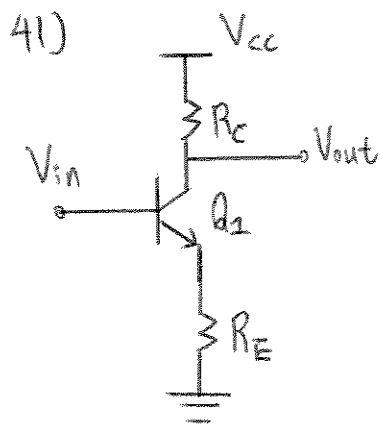
$$\frac{\partial A_v}{A_v} = \frac{-0.06 (R_c I_c)}{\frac{-R_c I_c}{V_T (1 + R_E g_m)}} = 1.25\%$$



$$V_A = \infty$$

$$R_C I_C = 20 V_T$$


$$R_E I_C = 5 V_T$$

$$|A_v| = \frac{R_C}{R_E + \frac{1}{g_m}} = \frac{R_C}{R_E + \frac{V_T}{I_C}} = \frac{R_C I_C}{R_E I_C + V_T}$$

Assume β is large, so $I_C = I_E$.

$$R_C I_C = 20 V_T, \quad R_E I_C = 5 V_T$$

$$|A_v| = \frac{20 V_T}{5 V_T + V_T} = \frac{20 V_T}{6 V_T} = 3.33$$

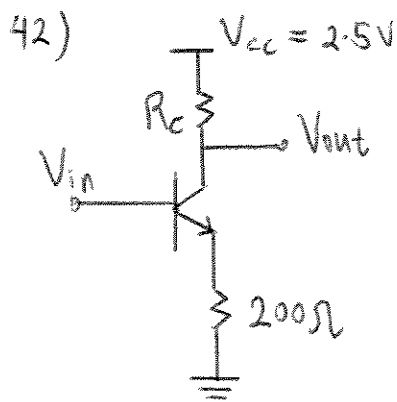

$$|A_v| = \frac{R_c I_c}{R_E I_c + V_T} = 10$$

Edge of Saturation

$$V_{CE} = V_{BE} = 2.5 - I_c(R_c + R_E)$$

$$V_{BE} = 0.8 \text{ V} \Rightarrow I_c R_c = 1.7 - I_c 0.2 \quad (\text{operating point})$$

$$|A_v| = 10 \Rightarrow R_c I_c = 10(R_E I_c + V_T) \quad (\text{Gain Equation})$$

Equating the two equations above \Rightarrow

$$1.7 - 0.2 I_c = 2 I_c + 0.26 \Rightarrow I_c = 0.655 \text{ mA}$$

$$\text{Check for } V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.725, \text{ not } 0.8, \text{ Reiterate}$$

$$I_c R_c = 1.775 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$

$$\text{Equating the two equations} \Rightarrow I_c = 0.689 \text{ mA}$$

$$\text{Check for } V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.727 \text{ V, iterate 1 more time}$$

$$I_c R_c = 1.773 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$

42)

Equating the two equations $\Rightarrow I_c = 0.688 \text{ mA}$

Check for $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.727 \text{ V}$, converged

$$I_c = 0.688 \text{ mA}$$


$$R_c = \frac{2I_c + 0.26}{I_c} = \frac{(2 \times 0.688) + 0.26}{0.688}$$

$$R_c = 2.38 \text{ k}\Omega$$

$$R_{in} = r_{\pi} + (1 + \beta) R_E$$

$$R_{in} = \frac{\beta}{g_m} + (101)(0.2) = 24.0 \text{ k}\Omega$$

43)

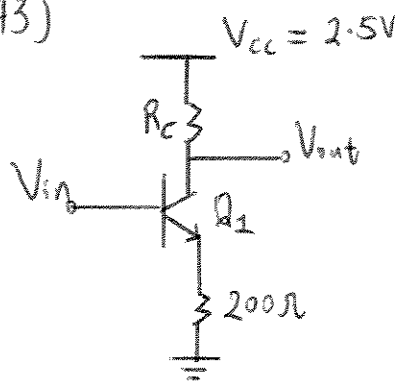

$|A_v| = 100$
(Voltage gain)

$$|A_v| = 100 \Rightarrow R_C I_C = 100 (R_E I_C + V_T)$$

$$R_C I_C = 20 I_C + 2.6 \quad (1)$$

$$R_C I_C = 1.7 - I_C 0.2 \quad (2) \quad (\text{Assume } V_{BE} = 0.8)$$

Equating (1) and (2) yield

$$1.7 - I_C 0.2 = 20 I_C + 2.6 \Rightarrow I_C = -0.04455 \text{ mA}$$

A negative I_C in forward active region is impossible, therefore, a solution does not exist. The reason is because $R_C I_C$ is too large to produce a gain of 100 that drive Q_1 into saturation region.

Maximum gain achievable:

$$\frac{R_C I_C}{R_E I_C + V_T} = |A_v| \quad (\text{Gain Equation})$$

$$2.5 = R_C I_C + V_{CE} + R_C I_C \quad (\text{Operating Point Equation})$$

Let $A = \text{Maximum gain}$

43)

$$AI_c 0.2 + A 0.026 = 1.7 - I_c 0.2$$

$$\Rightarrow I_c = \frac{1.7 - A 0.026}{A 0.2 + 0.2}$$

Since I_c cannot be zero, set



$$\frac{1.7 - A 0.026}{A 0.2 + 0.2} > 0$$

$$1.7 - A 0.026 > 0$$

$$1.7 > A 0.026$$

$$A < \frac{1.7}{0.026} = 65.4 \text{ (Maximum gain achievable)}$$

44) $V_A = \infty$

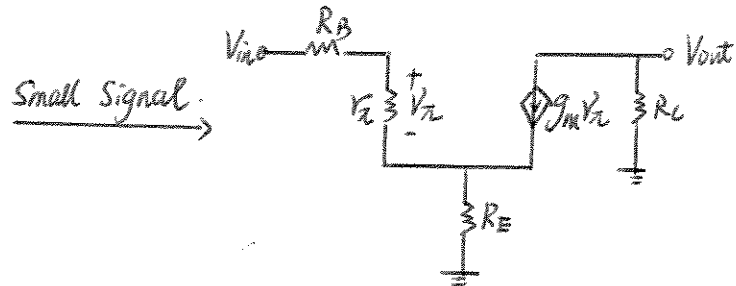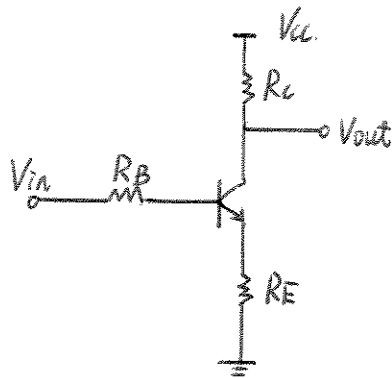


$$V_{out} = -g_m v_{\pi} R_C$$

$$v_{\pi} = \frac{V_{in} R_C}{R_B + r_{\pi} + (\beta + 1) R_E}$$


$$V_{out} = \frac{-g_m R_C V_{in}}{R_B + r_{\pi} + (\beta + 1) R_E} = \frac{-\beta R_C V_{in}}{R_B + r_{\pi} + (\beta + 1) R_E} = \frac{-R_C V_{in}}{\frac{R_B}{\beta} + \frac{1}{g_m} + \frac{\beta + 1}{\beta} R_E}$$

$$\frac{V_{out}}{V_{in}} \approx \frac{-R_C}{\frac{R_B}{\beta + 1} + \frac{1}{g_m} + R_E}$$

45)

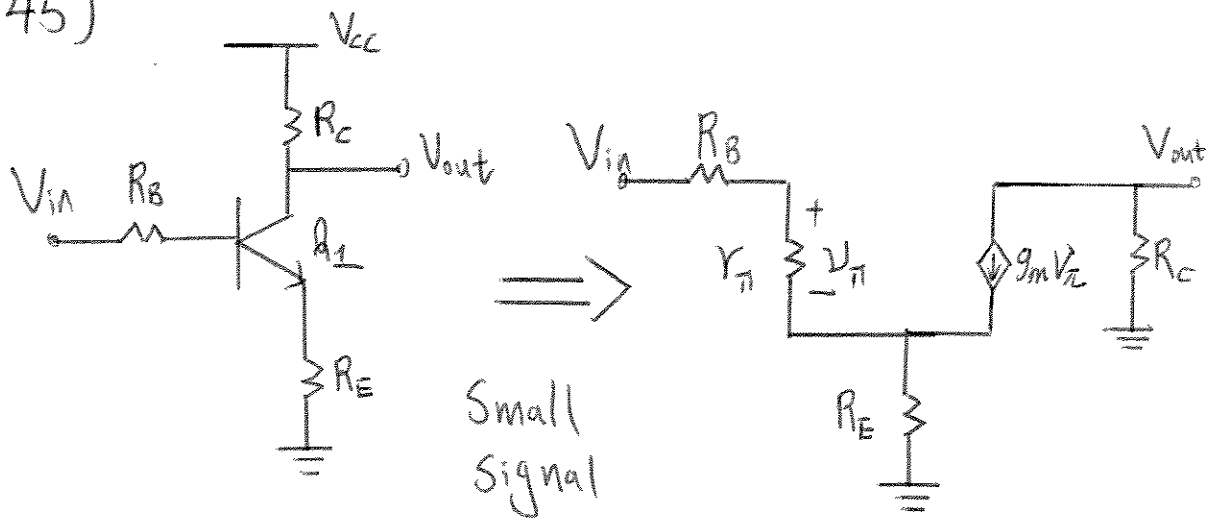

R_{out} Calculation:

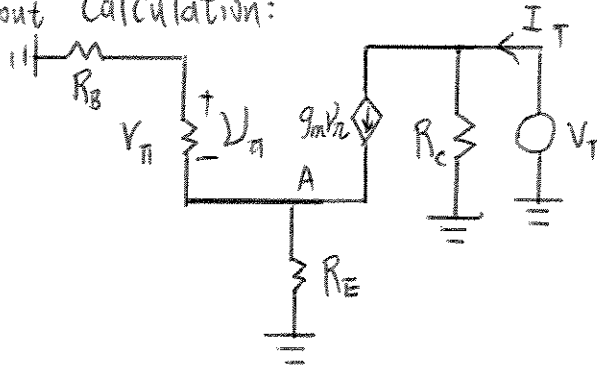

$$V_A = g_m V_{\pi} (R_E \parallel R_B + r_{\pi}) \quad (1)$$


$$V_{\pi} = -\frac{V_A r_{\pi}}{r_{\pi} + R_B} \Rightarrow V_A = -\frac{V_{\pi} (r_{\pi} + R_B)}{r_{\pi}} \quad (2)$$

The only possible solution for 1) and 2) is $V_{\pi} = V_A = 0$,
 Since 1) is positive and 2) is negative.

$$V_{\pi} = 0 \Rightarrow g_m V_{\pi} \Rightarrow 0 \Rightarrow \frac{V_T}{I_T} = R_C$$

Therefore, $R_{out} = R_C$

4b) $V_A = \infty$

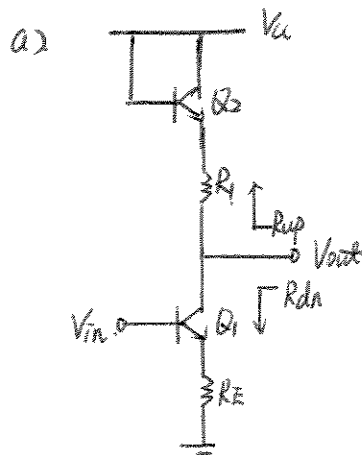


$$R_{up} = R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{dn} = \infty$$

$$R_{out} = R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{in} = r_{\pi 1} + (1 + \beta) R_E$$

$$|A_v| = \frac{R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{R_E + \frac{1}{g_{m1}}}$$

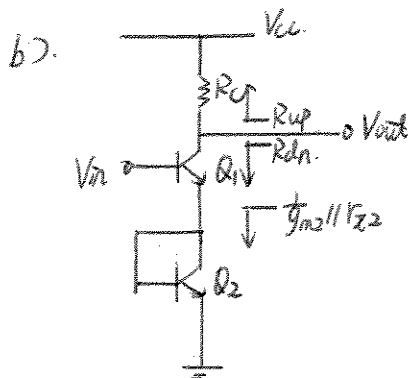


$$R_{up} = R_C$$

$$R_{dn} = \infty$$

$$R_{out} = R_C$$

$$R_{in} = r_{\pi 1} + (\beta + 1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{1}{g_{m1}}}$$

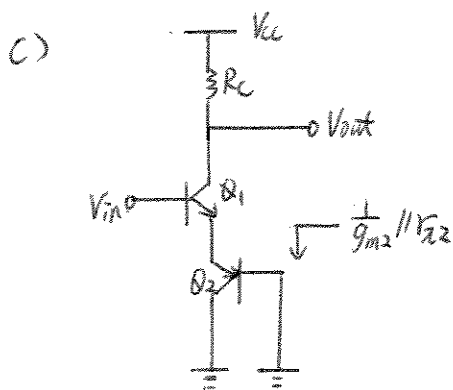


$$R_{out} = R_C$$

$$R_{in} = r_{\pi 1} + (\beta + 1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{1}{g_{m1}}}$$

4b).

d).

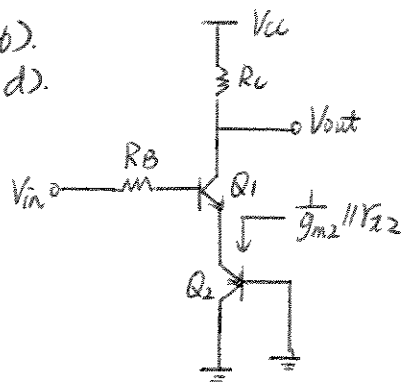


$$R_{out} = R_C$$


$$R_{in} = R_B + r_{z1} + (\beta + 1) \left(\frac{1}{g_{m2}} \parallel r_{z2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{z2} + \frac{1}{g_{m1}} + \frac{R_B}{\beta + 1}}$$

e)

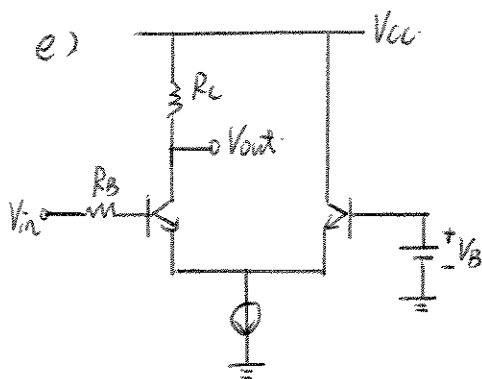

⇒

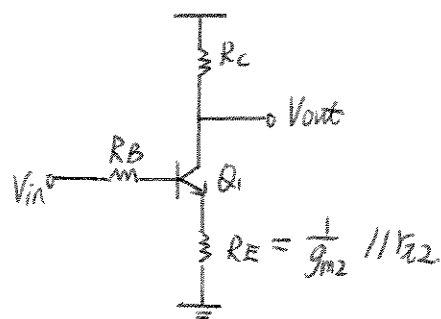


$$R_{out} = R_C$$

$$R_{in} = R_B + r_{z1} + (\beta + 1) \left(\frac{1}{g_{m2}} \parallel r_{z2} \right)$$

$$|A_v| = \frac{R_C}{\frac{1}{g_{m2}} \parallel r_{z2} + \frac{1}{g_{m1}} + \frac{R_B}{\beta + 1}}$$

47). $V_A = \infty$.

a).

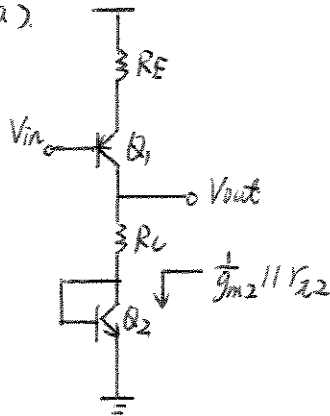

$$R_{out} = R_C + \frac{1}{g_{m2} \parallel r_{A2}}$$


$$R_{in} = r_{A1} + (1 + \beta) R_E$$

$$|A_v| = \frac{R_C + \frac{1}{g_{m2} \parallel r_{A2}}}{R_E + \frac{1}{g_{m1}}}$$


b). $R_{out} = \frac{1}{g_{m2}} \parallel r_{A2}$

$$R_{in} = r_{A1} + (1 + \beta) R_E$$

$$|A_v| = \frac{\frac{1}{g_{m2}} \parallel r_{A2}}{R_E + \frac{1}{g_{m1}}}$$

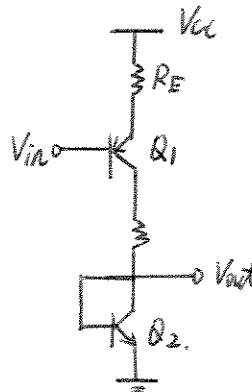

c).

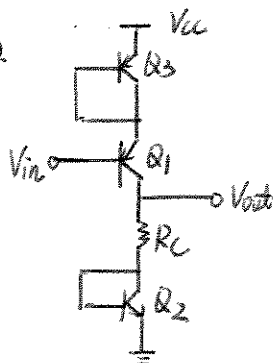

$$R_{out} = R_C + \frac{1}{g_{m2} \parallel r_{A2}}$$


$$R_{in} = r_{A1} + (1 + \beta) \left(\frac{1}{g_{m3}} \parallel r_{A3} \right)$$

$$|A_v| = \frac{R_C + \frac{1}{g_{m2} \parallel r_{A2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m3}} \parallel r_{A3}}$$


d). $R_{out} = R_C \parallel r_{A2}$

$$R_{in} = r_{A1} + (\beta + 1) R_E$$

$$|A_v| = \frac{R_C \parallel r_{A2}}{R_E + \frac{1}{g_{m1}}}$$

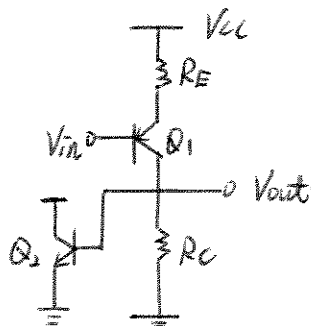


48).

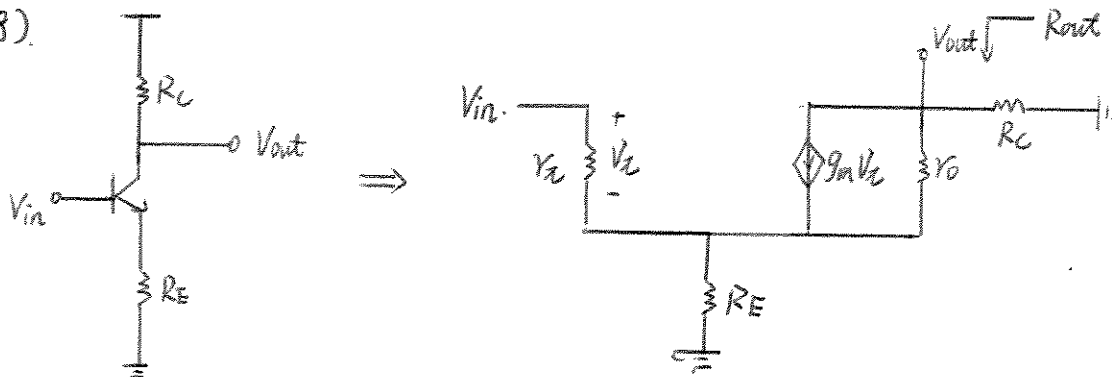

$$R_{out} = R_C \parallel R_{eq}$$

Solve for R_{eq} .

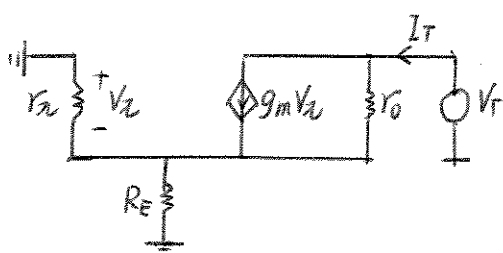

$$I_T = g_m v_{\pi} + \frac{(V_T + v_{\pi})}{r_o}$$

$$v_{\pi} = -I_T (r_{\pi} \parallel R_E)$$

$$I_T = -g_m I_T (r_{\pi} \parallel R_E) + \frac{(V_T - I_T (r_{\pi} \parallel R_E))}{r_o}$$

$$\frac{V_T}{I_T} = r_o \left(1 + \frac{(r_{\pi} \parallel R_E)}{r_o} \right) + g_m (r_{\pi} \parallel R_E)$$

$$\frac{V_T}{I_T} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$


$$R_{eq} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{out} = R_C \parallel r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{out} \approx R_C \parallel r_o (1 + g_m (r_{\pi} \parallel R_E)) \quad \text{since } g_m r_o \gg 1$$

49). $\beta \gg 1$ and $V_A < \infty$ to have meaningful result.

a).

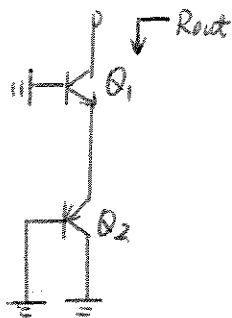


$$\frac{1}{g_{m2}} \parallel r_{\pi 2} \approx \frac{1}{g_{m2}}, \text{ since } \beta \gg 1$$

$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$= r_{o1} (1 + g_{m1} / g_{m2})$$

b).

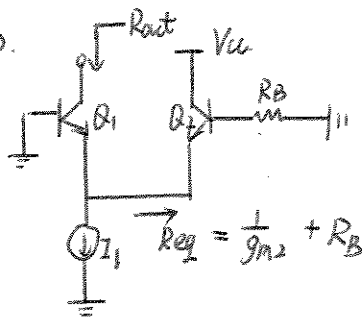


$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) \left[\left(\frac{1}{g_{m2}} + \frac{R_B}{\beta + 1} \right) \parallel r_{\pi 1} \right]$$

$$\approx r_{o1} + (1 + g_{m1} r_{o1}) \left(\frac{1}{g_{m2}} + \frac{R_B}{\beta} \right)$$

$$\approx r_{o1} \left[1 + g_{m1} \left(\frac{1}{g_{m2}} + \frac{R_B}{\beta} \right) \right]$$

c).

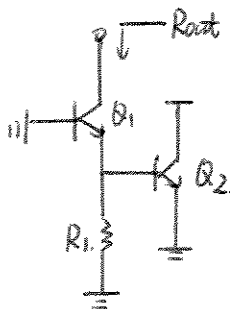


$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) (R_1 \parallel r_{\pi 2} \parallel r_{\pi 1})$$

$$R_1 \parallel r_{\pi 1} \parallel r_{\pi 2} \approx R_1, \text{ since } \beta \gg 1.$$


$$R_{out} \approx r_{o1} (1 + g_{m1} R_1)$$

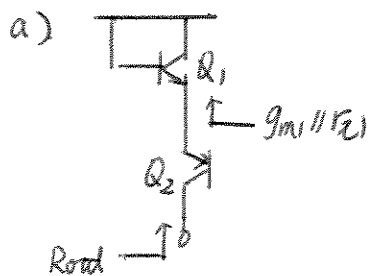50) $\beta \gg 1$, $V_A \gg \infty$, for meaningful results



$$R_{out} = r_{O2} + (1 + g_{m2} r_{O2}) \left(\frac{1}{g_{m1}} \parallel r_{O1} \right)$$

$$\approx r_{O2} (1 + g_{m2} / g_{m1})$$

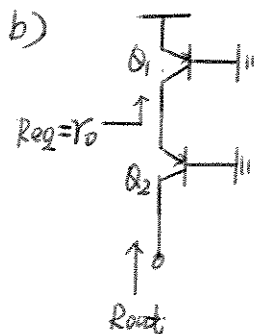

$$R_{out} = r_{O2} + (1 + g_{m2} r_{O2}) (r_{O1} \parallel r_{O2})$$

$$\approx r_{O2} [1 + g_{m2} (r_{O1} \parallel r_{O2})]$$

The output impedance in b) is larger than a) because Q_2 's connected for a high impedance load, whereas in a) it's connected to a low impedance load.


$$51). r_2 = \beta V_T / I_C.$$

$$R_{in} = r_2 // R_B = \frac{\frac{\beta V_T}{I_C} R_B}{\frac{\beta V_T}{I_C} + R_B} = \frac{V_T R_B}{V_T + \frac{I_C}{\beta} R_B} = \frac{V_T R_B}{V_T + I_B R_B}$$


$$\text{Since } I_B R_B \gg V_T \Rightarrow R_{in} \approx \frac{V_T R_B}{I_B R_B} = \frac{V_T}{I_B} = \frac{V_T}{\frac{I_C}{\beta}} = \frac{\beta V_T}{I_C} \approx r_2$$

$$\text{So } R_{in} = r_2 // R_B \approx r_2.$$

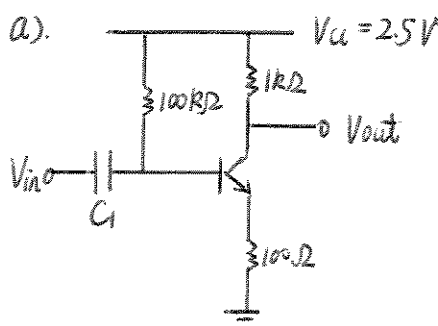52). $I_S = 8 \times 10^{-6} \text{ A}$, $\beta = 100$, $V_A = \infty$



DC Analysis

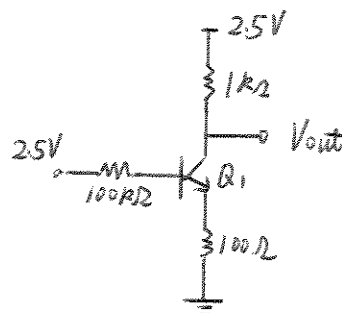

$$I_C = \frac{\beta(2.5 - (V_{BE} + \frac{I_C}{\alpha} 0.1))}{100K} \Rightarrow I_C = \frac{100(2.5 - V_{BE})}{100K + 10.1K}$$

Guess $V_{BE} = 0.75 \text{ V}$, $I_C = 1.59 \text{ mA}$

Verify $V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.736 \text{ V}$, not 0.75 V , reiterate


$V_{BE} = 0.736 \text{ V}$, $I_C = 1.60 \text{ mA}$

Verify $V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.736 \text{ V}$, converged !!

$I_C = 1.60 \text{ mA}$

$g_m = \frac{I_C}{V_T} = \frac{1.60 \text{ mA}}{26 \text{ mV}} = 0.0615 \left(\frac{1}{\Omega}\right) \text{ S}$

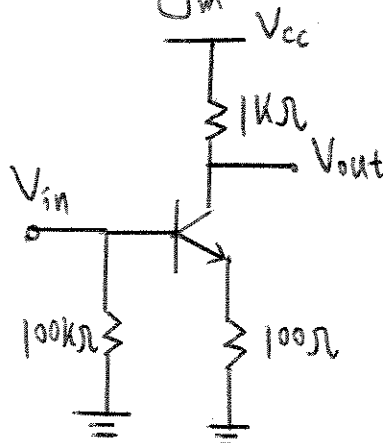
$r_{\pi} = \frac{\beta}{g_m} = 1.63 \text{ k}\Omega$



$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = \frac{1K}{0.1 + \frac{1}{g_m}} = 8.6$$

52)

b)

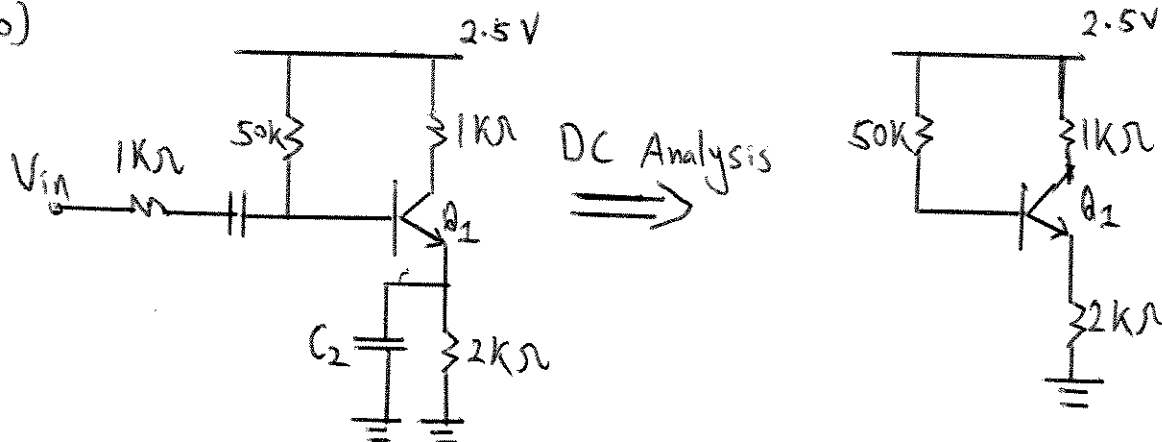

$$I_c = \beta \left(\frac{2.5 - (V_{BE} + I_E 2K)}{50K} \right) \Rightarrow I_c = \frac{100(2.5 - V_{BE})}{50K + 202K}$$

Guess $V_{BE} = 0.7V$, $I_c = 0.714mA$

Verify $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.7155V$, reiterate.

$V_{BE} = 0.7155V$, $I_c = 0.708mA$


Verify $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.715V$, converged!!

$I_c = 0.708mA$

$g_m = \frac{I_c}{V_T} = 0.02723 \left(\frac{1}{\Omega}\right) S$

$V_{BE} = 0.715V$

AC Analysis:

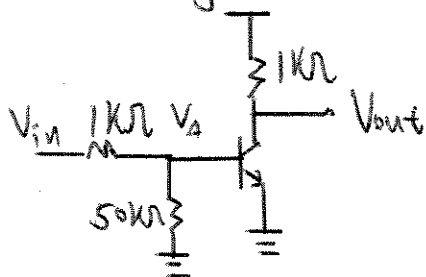


$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right| = 21.1$$

$$\left| \frac{V_{out}}{V_A} \right| = g_m 1K\Omega = 27.23$$

$$\left| \frac{V_A}{V_{in}} \right| = \frac{50K // V_{\pi}}{50K // V_{\pi} + 1K} = 0.77$$

52)

c)

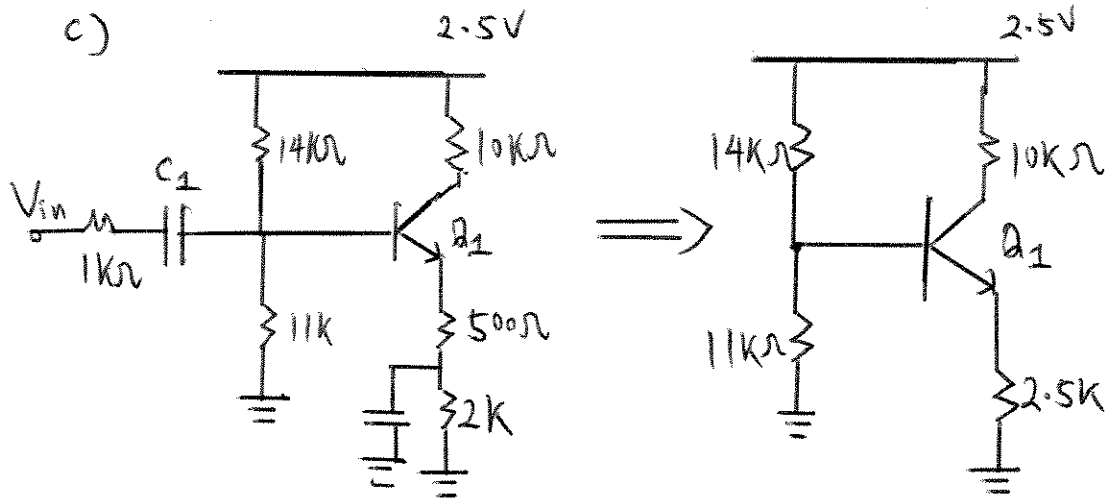

$$I_c = \beta \left(\frac{1.1 - (V_{BE} + \frac{I_c \cdot 2.5}{\alpha})}{14k\Omega // 11k\Omega} \right) \Rightarrow I_c = \frac{100 \cdot (1.1 - V_{BE})}{6.16 + 252.53}$$

Guess $V_{BE} = 0.7V$, $I_c = 0.1546mA$

Verify $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.676V$, not $0.7V$, reiterate
 $V_{BE} = 0.676V$, $I_c = 0.164mA$

Verify $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.677V$, converged !!

$I_c = 0.164mA$, $V_{BE} = 0.677V$, $g_m = 0.00631 \left(\frac{1}{\Omega}\right)S$,
 $r_{\pi} = 15.85k$


AC Analysis:

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right| = 12.9$$

$$\left| \frac{V_{out}}{V_A} \right| = \frac{10k}{\frac{1}{g_m} + 0.5} = 15.2$$

$$\left| \frac{V_A}{V_{in}} \right| = \frac{6.16k // (15.85k + 10 // 0.5)}{6.16k // (15.85k + 10 // 0.5) + 1k} = 0.85$$

53).

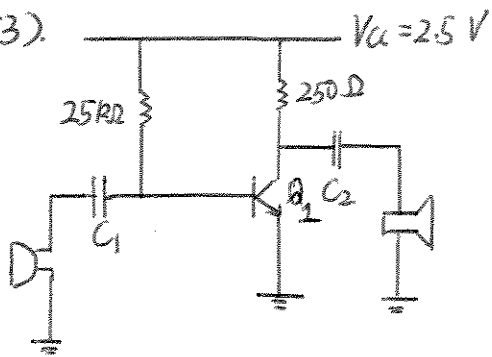

$$R_B = 25 \text{ k}\Omega$$

$$R_C = 250 \Omega$$

$$I_S = 5 \times 10^{-17} \text{ A}$$

$$V_A = \infty$$

DC Analysis: Assume collector bias voltage is still 1.5 V. So 1 V across $R_C \Rightarrow I_C = 4 \text{ mA}$.

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.832$$


$$I_B = \frac{2.5 - V_{BE}}{25 \text{ k}} = 0.06673 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = \frac{0.832 \text{ mA}}{0.06673 \text{ mA}} = 60$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_m (250 \Omega // 8 \Omega) = 1.2, (\text{Greater than unity})$$

$$g_m = \frac{4 \text{ mA}}{26 \text{ mV}} = 0.1538 \left(\frac{1}{\Omega} \right) \text{ S}$$

54)

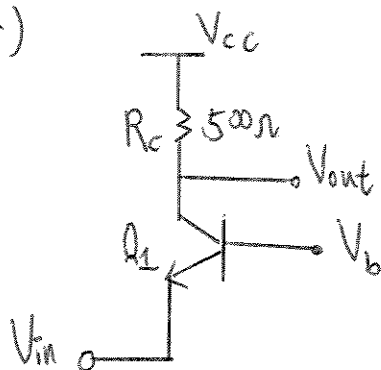

$$I_c = 2 \text{ mA}$$

$$V_A = \infty$$

$$g_m = \frac{I_c}{V_T} = 0.0769 \left(\frac{1}{\text{V}} \right) \text{ S}, \quad \frac{1}{g_m} = 13 \Omega$$


$$a) |A_v| = g_m R_c = \frac{0.5}{0.013} = 38.5$$

$$R_{in} = \frac{1}{g_m} \parallel r_{\pi} \approx \frac{1}{g_m} = 13 \Omega \quad (\text{Since } \beta \text{ is usually large})$$

$$R_{out} = 500 \Omega$$


b) Since $|A_v| = g_m R_c$, and g_m is fixed by I_c . The only way to maximize $|A_v|$ is to maximize R_c . However a large R_c will push Q_1 into saturation, losing its gain altogether. Therefore, V_B has to be as small as possible to provide enough room for V_C to drop \Rightarrow large $R_c \Rightarrow$ large gain.

55) $V_A = \infty$

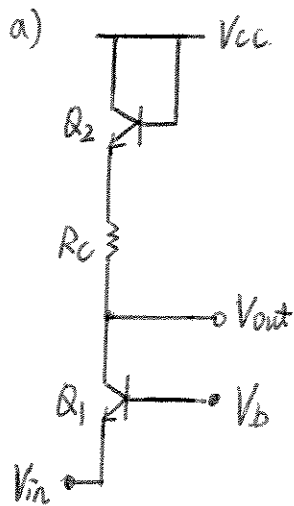


$$|A_v| = \frac{R_c + \frac{1}{g_{m2} \parallel r_{\pi 2}}}{\frac{1}{g_{m1}}}$$
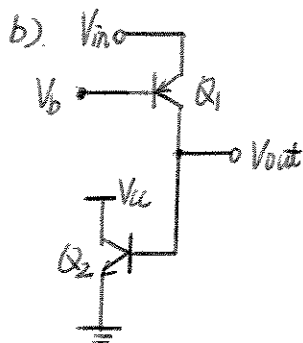
$$= g_{m1} (R_c + \frac{1}{g_{m2} \parallel r_{\pi 2}})$$



$$|A_v| = \frac{r_{\pi 2}}{\frac{1}{g_{m1}}} = g_{m1} r_{\pi 2}$$

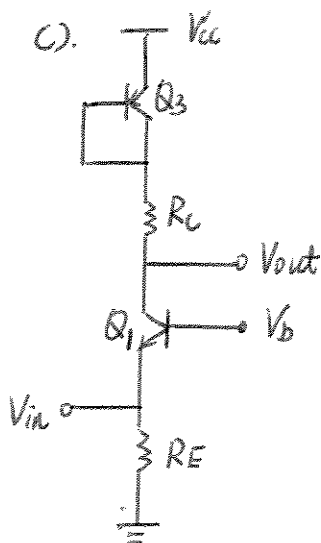


$$|A_v| = \frac{R_c + \frac{1}{g_{m3} \parallel r_{\pi 3}}}{\frac{1}{g_{m1}}}$$

$$= g_{m1} (R_c + \frac{1}{g_{m3} \parallel r_{\pi 3}})$$

55).


d).

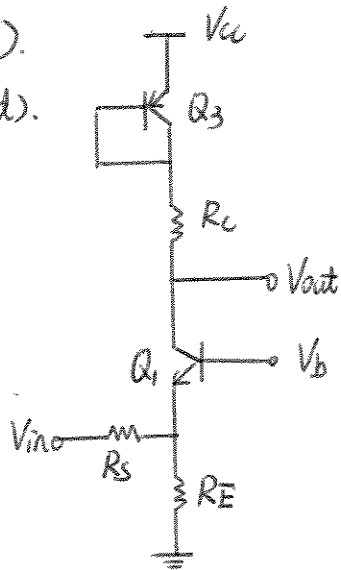

$$|A_v| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right|$$

$$= \left[g_{m1} (R_C + \frac{1}{g_{m3} || r_{\pi 3}}) \right] \left(\frac{R_E || \frac{1}{g_{m1}}}{R_E || \frac{1}{g_{m1}} + R_S} \right)$$


56) $V_A = \infty$

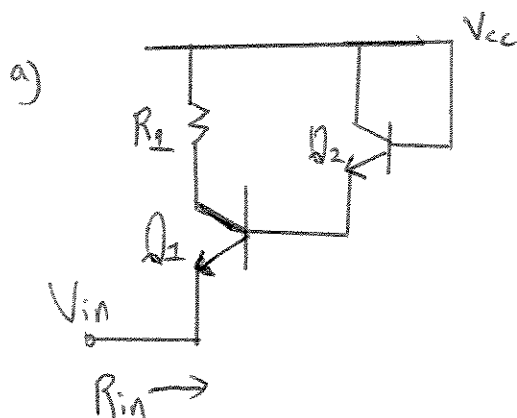

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\beta_1 + 1}$$

Since β is usually very large
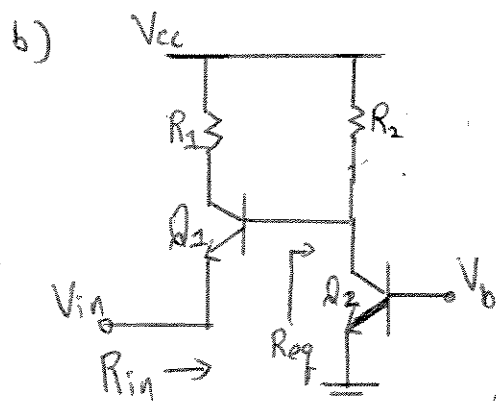
$$R_{in} \approx \frac{1}{g_{m1}} + \frac{1}{g_{m2}(\beta_1 + 1)}$$




$$R_{eq} = R_2 \parallel \infty = R_2$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_2}{\beta_1 + 1}$$

Since β is usually very large

$$R_{in} = \frac{1}{g_{m1}} + \frac{R_2}{\beta_1 + 1}$$

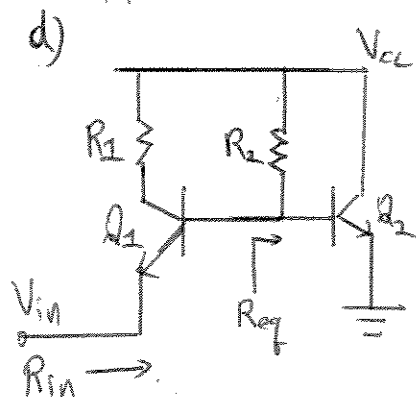* Note, part c) and d) have swapped places.



$$R_{eq} = R_2 \parallel r_{\pi 2}$$


$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_2 \parallel r_{\pi 2}}{\beta_1 + 1}$$

Since β is usually very large

$$R_{in} \approx \frac{1}{g_{m1}} + \frac{R_2 \parallel r_{\pi 2}}{\beta_1 + 1}$$

56) * Note, part c) and d) have swapped places

c)

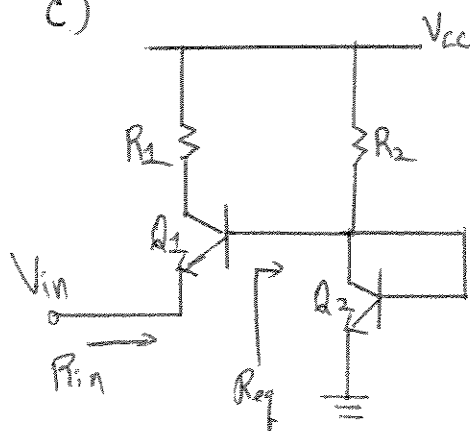


$$R_{eq} = R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\beta_1 + 1}$$

Since β is usually very large
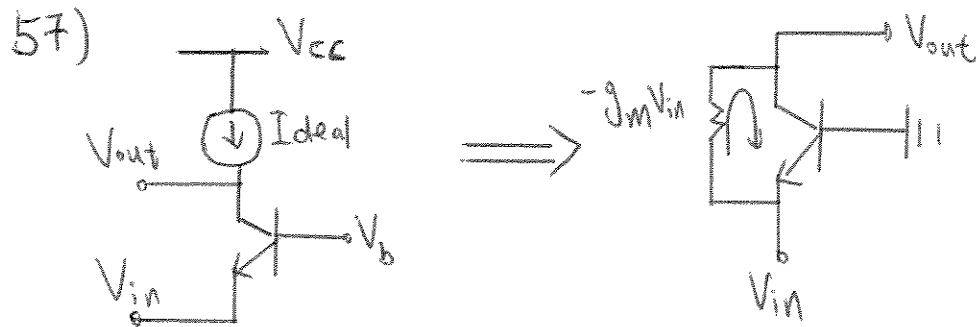
$$R_{in} \approx \frac{1}{g_{m1}} + \frac{R_2 \parallel \frac{1}{g_{m2}}}{\beta + 1}$$



Since an ideal current source is an open circuit, the signal current produced by the transistor has nowhere to go but R_o .

$$\text{So } V_{out} = -(g_m(0 - V_{in}))R_o + V_{in}$$


$$V_{out} = g_m R_o V_{in} + V_{in}$$

$$V_{out} = V_{in}(g_m R_o + 1)$$

$$\frac{V_{out}}{V_{in}} = 1 + g_m R_o$$

58)

b) AC Analysis

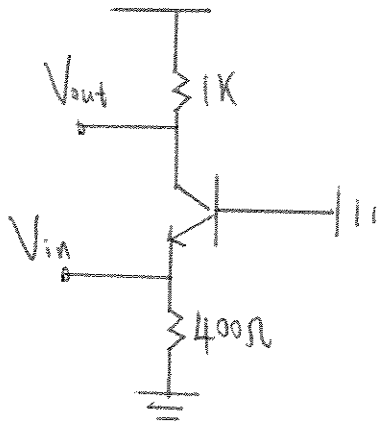

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_m 1K$$


$$g_m = 0.0391 \left(\frac{1}{\Omega} \right) S$$

$$A_v = 39.1$$

$$R_{in} = 400\Omega \parallel \frac{1}{g_m} = 400\Omega \parallel 25.583\Omega = 24.0\Omega$$

$$R_{out} = 1K$$

58)

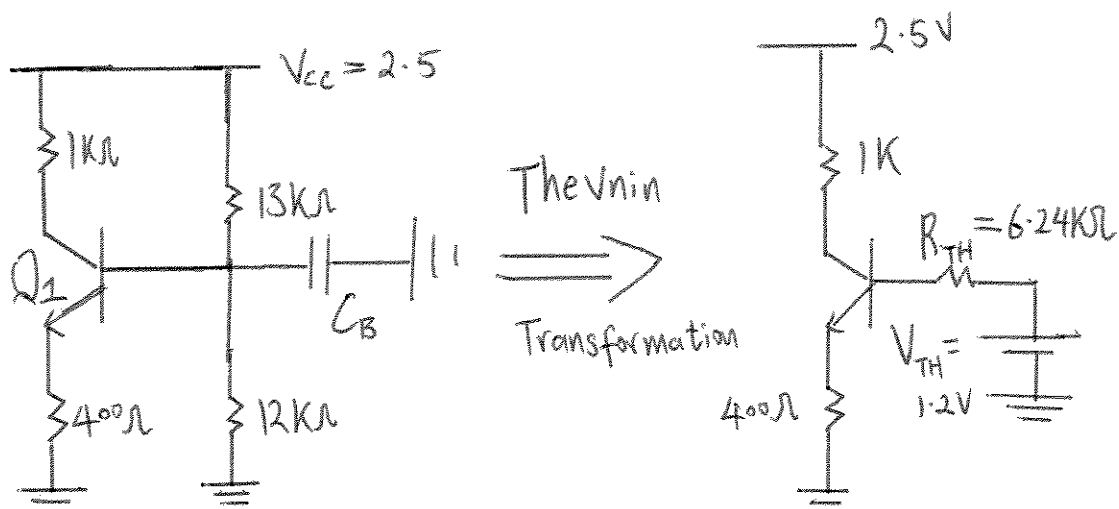

$$\beta = 100, \quad I_s = 8 \times 10^{-16} A, \quad V_A = \infty, \quad C_B = \text{Very large}$$

a) DC Analysis:

$$I_c = \beta \left(\frac{1.2 - (V_{BE} + I_E 0.4)}{6.24} \right) \Rightarrow \frac{\beta (1.2 - V_{BE})}{6.24 + \frac{0.4\beta}{\alpha}}$$

$$\text{Guess } V_{BE} = 0.7 \Rightarrow I_c = 1.072 \text{ mA}$$

$$\text{Verify } V_{BE}: V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.726 \text{ V, not } 0.7 \text{ V, reiterate.}$$

$$V_{BE} = 0.726 \text{ V, } I_c = 1.0163 \text{ mA}$$

$$\text{Verify } V_{BE}: V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.725 \text{ V, converged!!}$$

$$V_{BE} = 0.725, \quad V_{CE} = 2.5 - \left[(0.0163)(1k) + 0.4 \left(\frac{1.0163}{0.99} \right) \right]$$

$$V_{CE} = 1.07$$

$$I_c = 1.0163 \text{ mA, } I_B = 10.163 \text{ } \mu\text{A}$$

59)

$$C_B = 0$$

a) Since C_B was not considered during DC analysis, it has no effect on operating point analysis. So it is still the same as 58).


$$V_{BE} = 0.725 \text{ V}$$

$$I_C = 1.0163 \text{ mA}$$

$$I_B = 10.163 \mu\text{A}$$

$$V_{CE} = 1.07 \text{ V}$$

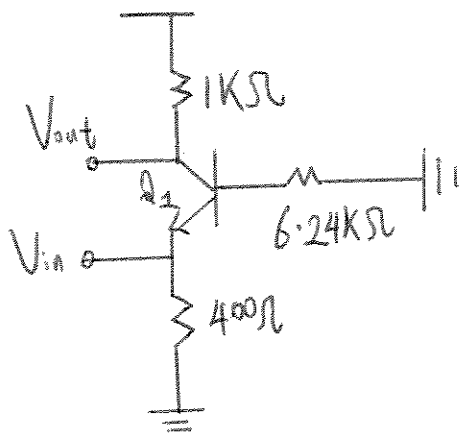b) Since capacitor is frequency dependent, the circuit's AC analysis will be different.



$$|A_v| = \frac{1\text{K}}{\frac{1}{g_m} + \frac{6.24\text{K}\Omega}{\beta+1}} = 11.4$$


$$R_{in} = 400\Omega \parallel \left(\frac{1}{g_m} + \frac{6.24\text{K}\Omega}{\beta+1} \right)$$

$$R_{in} = 71.7\Omega$$

Note: $6.24\text{K}\Omega$ is R_{THEV} of $13\text{K}\Omega$ and $12\text{K}\Omega$ combination.

$$R_{out} = 1\text{K}\Omega$$

60)

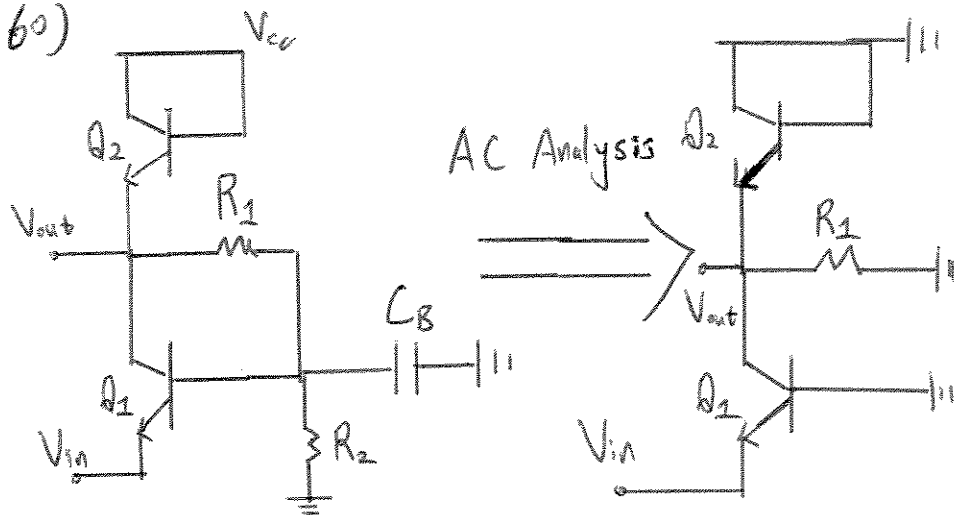


$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \approx \frac{1}{g_{m2}} \parallel R_1$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \right) \approx g_{m1} \left(\frac{1}{g_{m2}} \parallel R_1 \right)$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \approx \frac{1}{g_{m1}}$$


61)

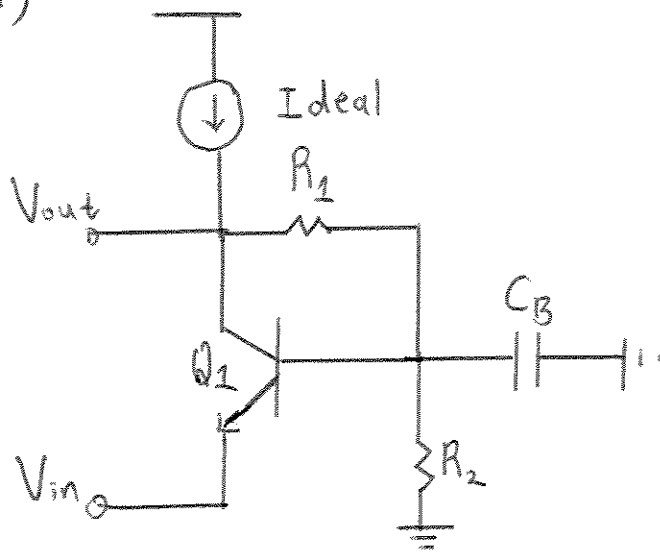

$$V_A = \infty$$

$$C_B \text{ large}$$

AC Analysis

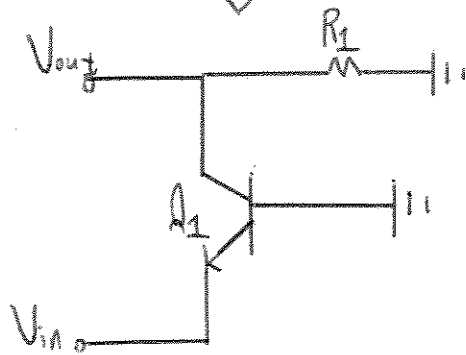


(R_2 shorted out)

$$R_{out} = R_1$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \approx \frac{1}{g_{m1}}$$

$$|A_v| = g_{m1} R_1$$

62)

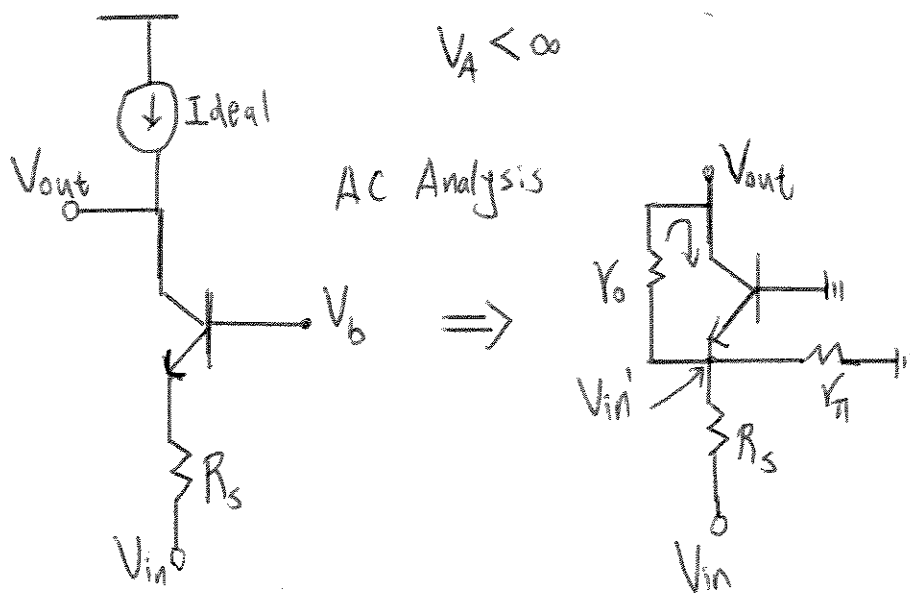

$$A_v = \frac{V_{out}}{V_{in}} = \left(\frac{V_{in'}}{V_{in}} \right) \left(\frac{V_{out}}{V_{in'}} \right), \quad \left(\frac{V_{in'}}{V_{in}} \right) = \frac{r_{\pi}}{r_{\pi} + R_s}$$


Since V_{out} is float, so looking at emitter and V_o , we will

see an infinite impedance.

$$\frac{V_{out}}{V_{in'}} \Rightarrow -g_m(-V_{in'})V_o + V_{in'} = V_{out} \Rightarrow \frac{V_{out}}{V_{in'}} = (g_m V_o + 1)$$

$$A_v = (g_m V_o + 1) \left(\frac{r_{\pi}}{r_{\pi} + R_s} \right)$$

63)

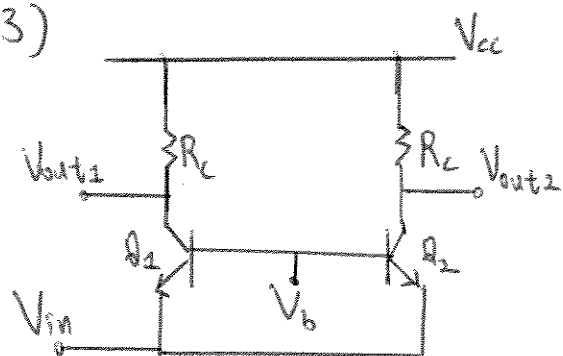

$$V_A = \infty$$

$$I_{S1} = 2I_{S2}$$

$$\left| \frac{V_{out1}}{V_{in}} \right| = g_{m1} R_c, \quad \left| \frac{V_{out2}}{V_{in}} \right| = g_{m2} R_c$$


$$g_{m1} = \frac{V_T}{I_{c1}} = \frac{V_T}{2I_{S2} e^{(V_{BE}/V_T)}}, \quad \text{Since } I_{S1} = 2I_{S2}$$

$$g_{m2} = \frac{V_T}{I_{c2}} = \frac{V_T}{I_{S2} e^{(V_{BE}/V_T)}}$$

$$(V_{BE1} = V_{BE2} = V_{BE})$$

$$\Rightarrow g_{m1} = \frac{g_{m2}}{2} \Rightarrow \left| \frac{V_{out1}}{V_{in}} \right| = \frac{1}{2} \left| \frac{V_{out2}}{V_{in}} \right|$$

64)

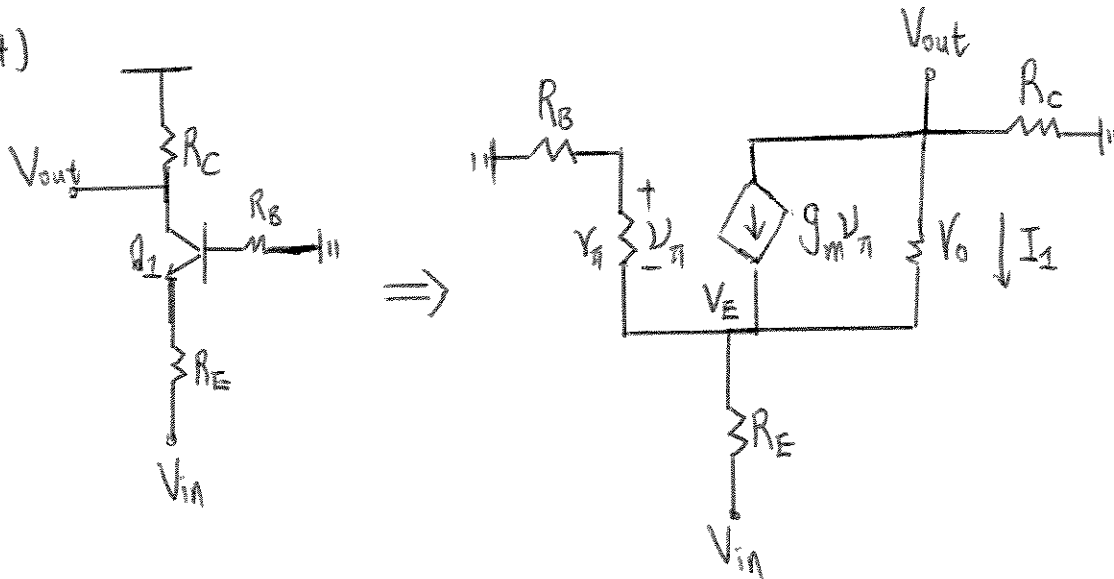

$$V_{out} = -(I_1 + g_m v_\pi) R_C, \quad I_1 = \frac{V_{out} - V_E}{r_o}$$

$$V_{out} = -\left(\frac{V_{out} - V_E}{r_o} + g_m v_\pi\right) R_C, \quad V_E = -\frac{g_m v_\pi}{\beta} (r_\pi + R_B)$$

$$V_{out} = -\left(\frac{V_{out} + \frac{g_m v_\pi (r_\pi + R_B)}{\beta}}{r_o} + g_m v_\pi\right) R_C$$

Rearranging

$$v_\pi = -\frac{\left(1 + \frac{R_C}{r_o}\right)}{\frac{g_m (r_\pi + R_B) R_C}{\beta r_o} + g_m R_C} V_{out} = A V_{out}$$

Summing the voltage at node E.

$$V_E - \left(\left(1 + \frac{1}{\beta}\right) g_m v_\pi + \frac{V_{out} - V_E}{r_o}\right) R_E = V_{in} \quad (1)$$

64) Writing V_E in terms of V_{π} , and V_{π} in terms of V_{out}

1) becomes


$$-\frac{g_m A V_{out}}{\beta} (r_{\pi} + R_B) \left(1 + \frac{R_E}{Y_o}\right) - \left(1 + \frac{1}{\beta}\right) g_m A V_{out} R_E - \frac{V_{out} R_E}{Y_o} = V_{in}$$

Solving $V_{out} / V_{in} \Rightarrow$

$$\frac{V_{out}}{V_{in}} = \frac{1}{-\frac{g_m A}{\beta} (r_{\pi} + R_B) \left(1 + \frac{R_E}{Y_o}\right) - \left(1 + \frac{1}{\beta}\right) g_m A R_E - \frac{R_E}{Y_o}}$$

substituting A into equation
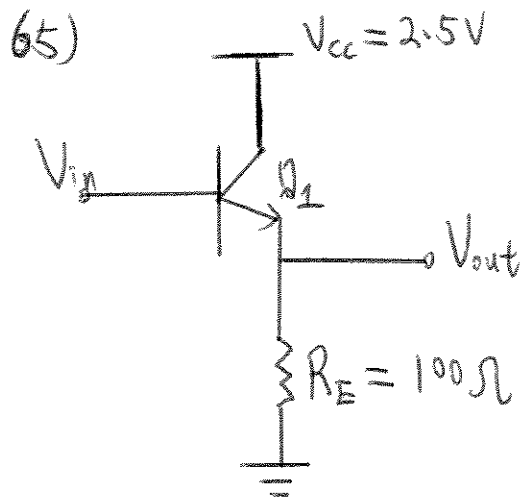
$$\frac{V_{out}}{V_{in}} = \frac{\frac{g_m (r_{\pi} + R_B) R_C}{\beta Y_o} + g_m R_C}{g_m \left(1 + \frac{R_E}{Y_o}\right) (r_{\pi} + R_B) \left(1 + \frac{R_E}{Y_o}\right) + \left(1 + \frac{1}{\beta}\right) g_m \left(1 + \frac{R_C}{Y_o}\right) R_E - \frac{R_E}{Y_o} \left(\frac{g_m (r_{\pi} + R_B) R_C}{\beta Y_o} + g_m R_C\right)}$$



$$R_E = 100\Omega$$

$$V_A = \infty$$

$$|A_v| = 0.8$$


$$|A_v| = \frac{R_E}{R_E + \frac{1}{g_m}} = \frac{R_E I_c}{R_E I_c + V_T} = 0.8$$

$$\Rightarrow R_E I_c = 0.8(R_E I_c + V_T), \quad R_E = 100\Omega$$

$$\Rightarrow 0.1 I_c = 0.08 I_c + 0.0208 \Rightarrow 0.02 I_c = 0.0208$$

$$\Rightarrow I_c = 1.04 \text{ mA}$$

6b)

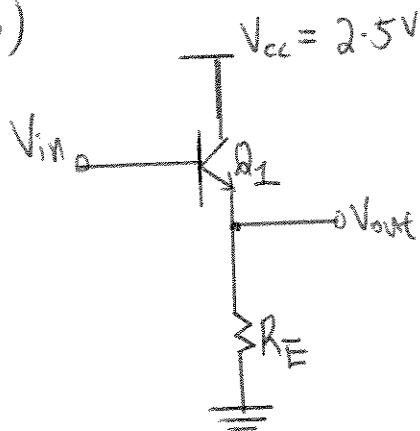

$$|A_v| > 0.9$$

$$R_{in} > 10\text{K}\Omega$$

$$|A_v| = \frac{R_E I_C}{R_E I_C + V_T} > 0.9 \Rightarrow R_E I_C > 0.9[R_E I_C + V_T]$$

$$\Rightarrow R_E I_C > 9V_T = 234\text{mV}, \text{ Let } R_E I_C = 240\text{mV}$$

$$R_{in} = r_{\pi} + (1+\beta)R_E > 10\text{K} \Rightarrow 100V_T + (101)R_E I_C > 10\text{K}\Omega I_C$$

Substituting $R_E I_C = 240\text{mV} \Rightarrow I_C < 2.684\text{mA}$


$$\text{Choose } I_C \text{ to be } 2.5\text{mA} \Rightarrow R_E = 96\Omega$$

To Verify:

$$R_{in} = \frac{100(0.026)}{2.5} + (101)0.096 = 10.74\text{K}\Omega$$

$$|A_v| = \frac{(0.096)(2.5)}{(0.096)(2.5) + 0.026} = 0.902$$

67)

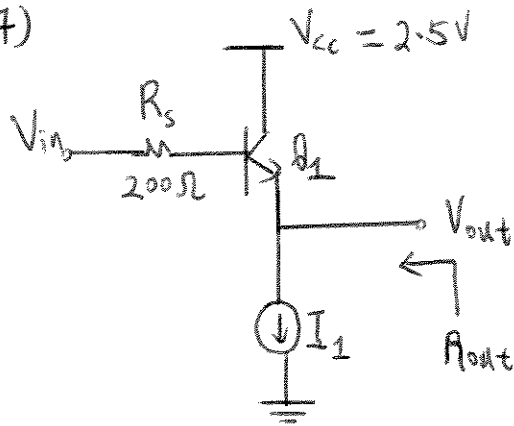

$$\beta = 100$$

$$V_A = \infty$$

$$R_{out} = \frac{1}{g_m} + \frac{R_s}{(\beta+1)} \leq 5\Omega \quad (\text{Assuming } r_{\pi} \gg \frac{1}{g_m})$$


$$R_{out} = 0.026 + \frac{200\Omega I_c}{101} \leq 5\Omega I_c$$

$$\Rightarrow I_c \geq 0.0086A$$

$$\text{pick } I_c = 0.009A$$


$$R_{out} = \frac{0.026V}{0.009A} + \frac{200}{101} = 4.87\Omega$$

68). a).

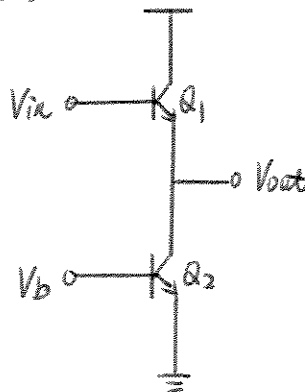

$$V_A = \infty$$

\Rightarrow

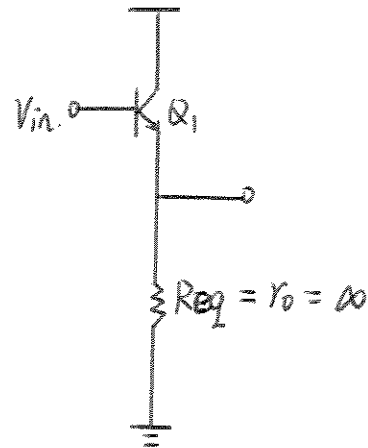


$$|A_v| = \frac{r_o}{r_o + \frac{1}{g_m}}, \quad \text{Since } r_o = \infty$$


$$|A_v| = 1.$$

$$R_{in} = \infty \quad (\text{since } r_o = \infty)$$
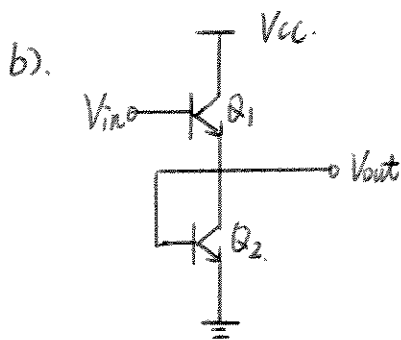
$$R_{out} = \infty \parallel \frac{1}{g_{m1}} \parallel r_{\lambda 1} = \frac{1}{g_{m1}} \parallel r_{\lambda 1}$$



\Rightarrow

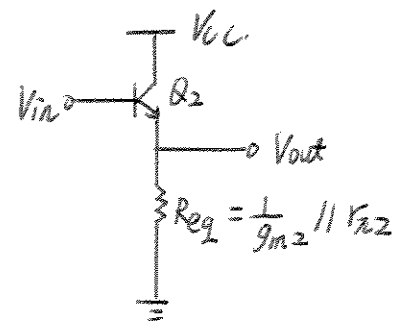


$$|A_v| = \frac{\frac{1}{g_{m2}} \parallel r_{\lambda 2}}{\frac{1}{g_{m2}} \parallel r_{\lambda 2} + \frac{1}{g_{m1}}}$$

$$R_{in} = r_{\lambda 1} + (1 + \beta) \frac{1}{g_{m2}} \parallel r_{\lambda 2}$$


$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\lambda 2} \parallel \frac{1}{g_{m1}} \parallel r_{\lambda 1}$$

$$(\text{If } I_{S1} = I_{S2}, g_{m1} = g_{m2} = g_m, r_{\lambda 1} = r_{\lambda 2} = r_{\lambda}, R_{out} = \frac{1}{2g_m} \parallel \frac{r_{\lambda}}{2})$$

c).

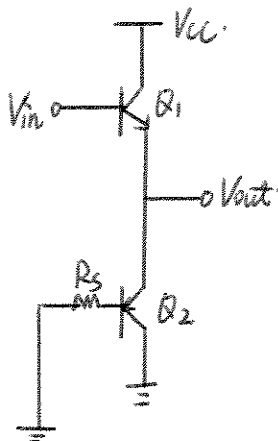

\Rightarrow

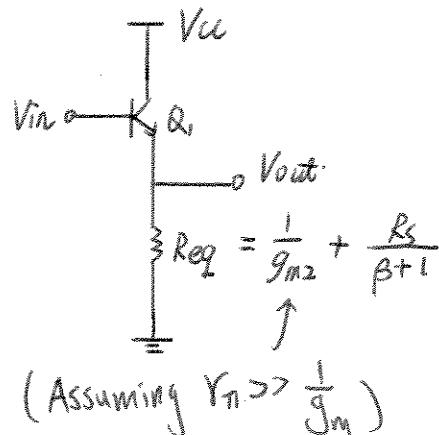


$$|A_v| = \frac{\frac{1}{g_{m2}} + \frac{R_s}{\beta+1}}{\frac{1}{g_{m2}} + \frac{R_s}{\beta+1} + \frac{1}{g_{m1}}}$$

$$R_{in} = R_1 + (1+\beta) \left(\frac{1}{g_{m2}} + \frac{R_s}{\beta+1} \right)$$


$$R_{out} = \left(\frac{1}{g_{m2}} + \frac{R_s}{\beta+1} \right) \parallel \left(\frac{1}{g_{m1}} \parallel R_{c1} \right)$$

$$R_{out} \approx \left(\frac{1}{g_{m2}} + \frac{R_s}{\beta+1} \right) \parallel \frac{1}{g_{m1}}$$

d).

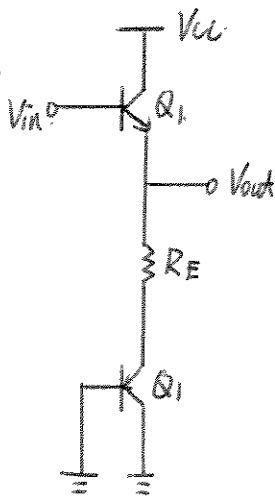

\Rightarrow

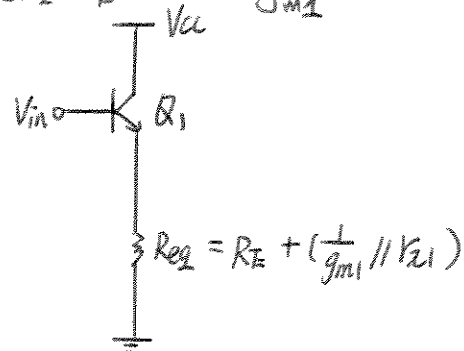


$$|A_v| = \frac{R_E + \left(\frac{1}{g_{m1}} \parallel R_{c1} \right)}{R_E + \left(\frac{1}{g_{m1}} \parallel R_{c1} \right) + \frac{1}{g_{m1}}}$$


$$R_{in} = R_1 + (1+\beta) \left[R_E + \left(\frac{1}{g_{m1}} \parallel R_{c1} \right) \right]$$

$$R_{out} = \left[R_E + \left(\frac{1}{g_{m1}} \parallel R_{c1} \right) \right] \parallel \left(\frac{1}{g_{m1}} \parallel R_{c1} \right)$$

68). e).

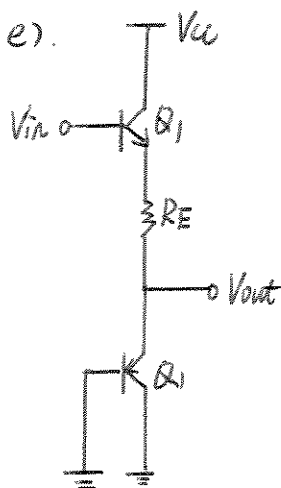

\Rightarrow

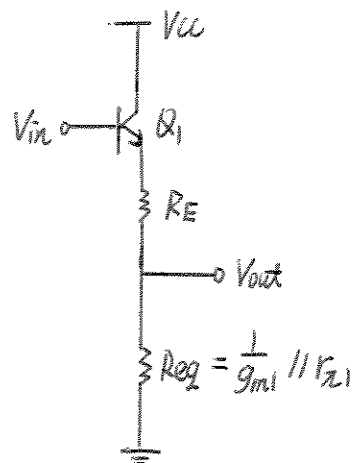


$$|A_v| = \frac{\frac{1}{g_{m1}} \parallel r_{L1}}{\frac{1}{g_{m1}} \parallel r_{L1} + R_E + \frac{1}{g_{m1}}}$$

$$R_{in} = r_{L1} + (1 + \beta) [R_E + \frac{1}{g_{m1}} \parallel r_{L1}]$$


$$R_{out} = (\frac{1}{g_{m1}} \parallel r_{L1}) \parallel (R_E + \frac{1}{g_{m1}} \parallel r_{L1}).$$

69 a)

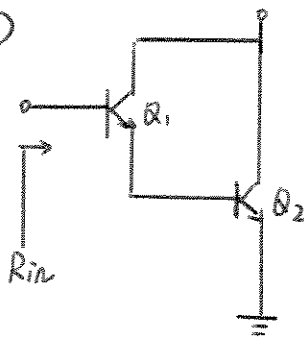

$$R_{in} = r_{\pi 1} + (1 + \beta) r_{\pi 2}$$

b).

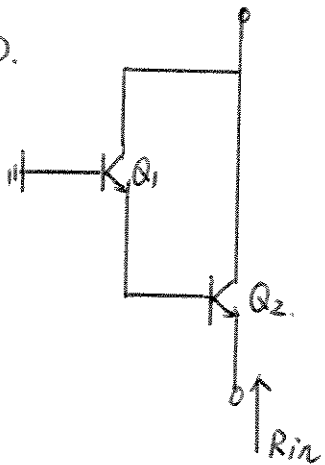


$$R_{in} = \frac{1}{g_{m2}} + \frac{1/g_{m1}}{(\beta + 1)} \quad (\text{Assume } r_{\pi} \gg \frac{1}{g_m})$$

$$c) \text{ Current Gain} = \frac{(I_{c1} + I_{c2})}{I_{B1}} = \beta + \frac{I_{c2}}{I_{B1}} = \beta + \frac{\beta I_{B2}}{I_{B1}}$$

$$\text{Since } I_{B2} = I_{c1} = \beta I_{B1}$$


$$\text{Current Gain} = \beta + \beta^2 = \beta(\beta + 1), \quad (\text{Assuming } \beta_1 = \beta_2 = \beta)$$

70).

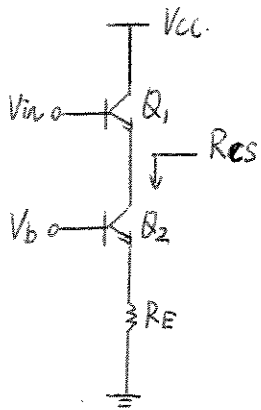


$$u) R_{cs} = Y_{o2} + (1 + g_{m2} Y_{o2})(R_E // Y_{\pi 2})$$

b).

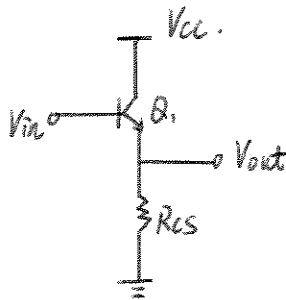

$$A_v = \frac{R_{cs} // Y_{o1}}{R_{cs} // Y_{o1} + \frac{1}{g_{m1}}}$$
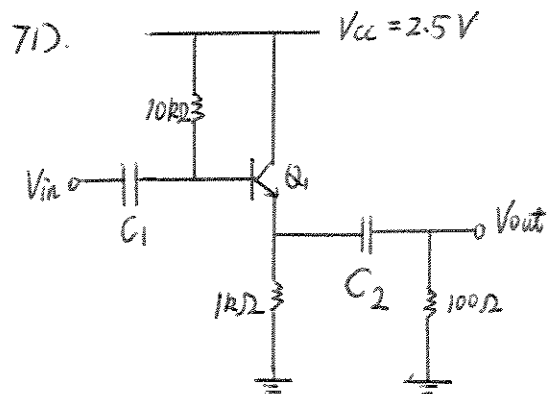
$$A_v = \frac{(Y_{o2} + (1 + g_{m2} Y_{o2})(R_E // Y_{\pi 2})) // Y_{o1}}{(Y_{o2} + (1 + g_{m2} Y_{o2})(R_E // Y_{\pi 2})) // Y_{o1} + \frac{1}{g_{m1}}}$$




$$I_s = 7 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = 5 \text{ V}$$

DC Analysis: (Ignore V_o 's effect).

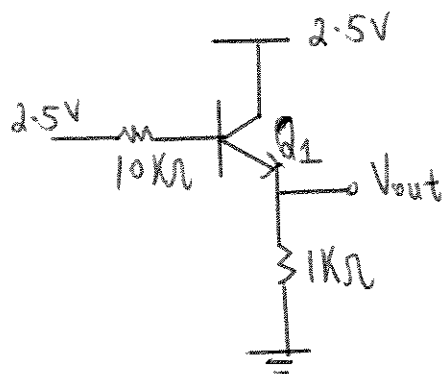

$$I_c = \beta \left(\frac{2.5 - (V_{BE} + \frac{I_c}{\alpha} 1 \text{ k}\Omega)}{10 \text{ k}\Omega} \right)$$

Rearrange

$$I_c = \frac{2.5 - V_{BE}}{\frac{10 \text{ k}\Omega}{\beta} + \frac{1 \text{ k}\Omega}{\alpha}}$$

Guess: $V_{BE} = 0.7 \text{ V}$, $I_c = 1.621 \text{ mA}$

check for V_{BE} : $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$, not 0.7, reiterate


$$V_{BE} = 0.740 \text{ V}, I_c = 1.59 \text{ mA}$$

check for V_{BE} : $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$, Converged.

So $I_c = 1.59 \text{ mA}$, $g_m = 0.0612 \left(\frac{1}{\Omega}\right) \text{ S}$, $\frac{1}{g_m} = 16.34 \Omega$,
 $r_o = 3.14 \text{ k}\Omega$


71)

AC Analysis: (Include V_o)

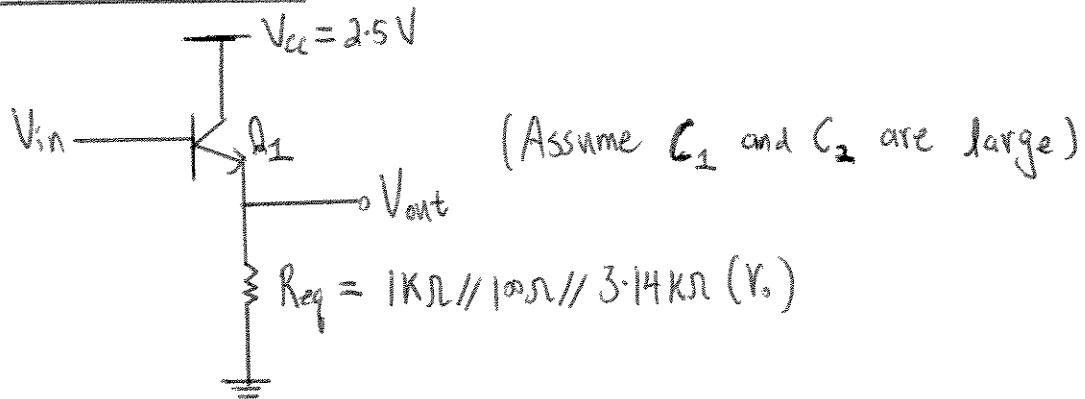

$$A_v = \frac{(1K\Omega // 100\Omega // 3.14K\Omega)}{16.34\Omega + (1K\Omega // 100\Omega // 3.14K\Omega)} = 0.84$$

72).

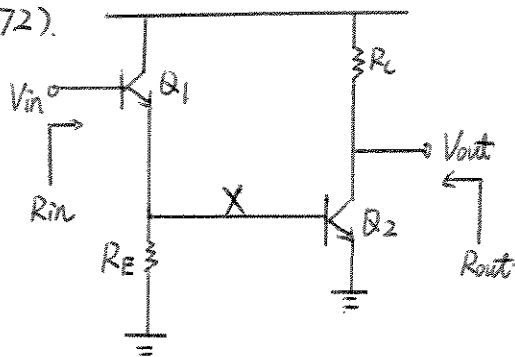

$$V_A < \infty$$


$$a) R_{in} = r_{\pi 1} + (1 + \beta)(R_E \parallel r_{\pi 2} \parallel r_{o 1})$$

$$R_{out} = R_C \parallel r_{o 2}$$

$$b) \left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_x}{V_{in}} \right| \left| \frac{V_{out}}{V_x} \right|$$

$$\left| \frac{V_x}{V_{in}} \right| = \frac{(R_E \parallel r_{\pi 2} \parallel r_{o 1})}{\frac{1}{g_{m 1}} + R_E \parallel r_{\pi 2} \parallel r_{o 1}}, \quad \left| \frac{V_{out}}{V_x} \right| = g_{m 2} R_C$$

$$\left| \frac{V_{out}}{V_{in}} \right| = (g_{m 2} R_C) \left[\frac{R_E \parallel r_{\pi 2} \parallel r_{o 1}}{\frac{1}{g_{m 1}} + R_E \parallel r_{\pi 2} \parallel r_{o 1}} \right]$$

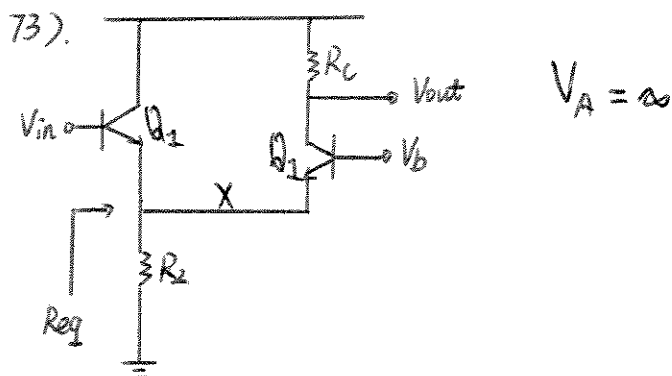

$$a) R_{eq} = R_E \parallel r_{\pi 1} \parallel \frac{1}{g_{m1}}$$


$$R_{in} = r_{\pi 1} + (1 + \beta) \left[R_E \parallel r_{\pi 1} \parallel \frac{1}{g_{m1}} \right]$$

$$R_{out} = R_C$$

$$b) \left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{V_x}{V_{in}} \right| \left| \frac{V_{out}}{V_x} \right|$$

$$\left| \frac{V_x}{V_{in}} \right| = \frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 1}}{\frac{1}{g_{m1}} + R_E \parallel \frac{1}{g_{m1}} \parallel r_{\pi 1}}, \quad \left| \frac{V_{out}}{V_x} \right| = g_{m2} R_C$$

$$\left| \frac{V_{out}}{V_{in}} \right| = (g_{m2} R_C) \left(\frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 1}}{R_E \parallel \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{1}{g_{m1}}} \right)$$

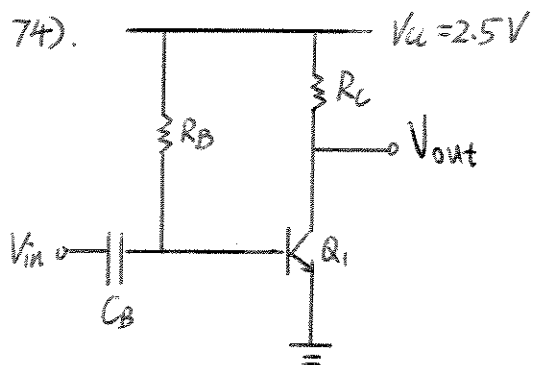

$$A_v = 10$$

$$R_{in} > 5k\Omega$$

$$R_{out} = 1k, R_c = 1k\Omega$$

$$A_v = \frac{R_c}{\frac{1}{g_m}} = 10 = \frac{I_c R_c}{V_T} \Rightarrow I_c = 0.26mA$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.697V.$$

$$I_c = 100 \left(\frac{2.5 - 0.697}{R_B} \right) \Rightarrow R_B = 693k\Omega, r_{\pi} = \beta \frac{V_T}{I_c} = 10k\Omega$$

$$R_{in} = 693k // 10k = 9.86k\Omega$$

$$\frac{1}{2\pi(200)C_B} = \frac{1}{10} \frac{1}{g_m} = 10\Omega \Rightarrow C_B = 80\mu f$$

(To avoid gain degradation).

$$R_c = 1k\Omega$$


$$R_B = 693k$$

$$C_B = 80\mu f$$

$$A_v = 10$$

$$\Rightarrow R_{out} = 1k\Omega$$

$$R_{in} = 9.86k\Omega$$

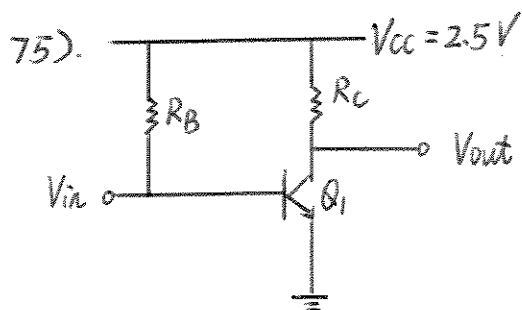

$$A_v = \text{Maximum}$$

$$R_{out} \leq 500\Omega$$

$$V_{bc} \leq 400\text{ mV}$$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T}, \text{ gain is maximized by maximize } I_c R_c$$

$$R_{out} = R_c \leq 500\Omega, \text{ choose } R_c = 450\Omega, R_{out} = 450\Omega$$

$$V_{bc} = V_{BE} - (2.5 - I_c R_c) \leq 400\text{ mV}$$

Guess $V_{BE} = 0.7$, and let $V_{bc} = 400\text{ mV}$ to maximize $I_c R_c$.

$$0.7 - (2.5 - I_c \cdot 0.450) = 0.4$$

$$I_c = 4.89\text{ mA}, V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.773$$

Not 0.7, Iterate.

$$0.773 - 2.5 + I_c \cdot 0.450 = 0.4$$


$$I_c = 4.73\text{ mA}, V_{BE} = 0.772 \text{ converged!!}$$

$$A_v = \left(\frac{I_c}{V_T}\right) R_c = \left(\frac{4.73}{26}\right) (450) = 81.9$$

$$R_B = 100 \left(\frac{2.5 - 0.772}{4.73} \right) = 36.5\text{ K}$$

$$\begin{aligned} R_B = 36.5\text{ K} &\Rightarrow A_v = 81.9 \\ R_c = 450\Omega &V_{bc} = 0.4\text{ V} \\ &R_{out} = 450\Omega \end{aligned}$$

76)

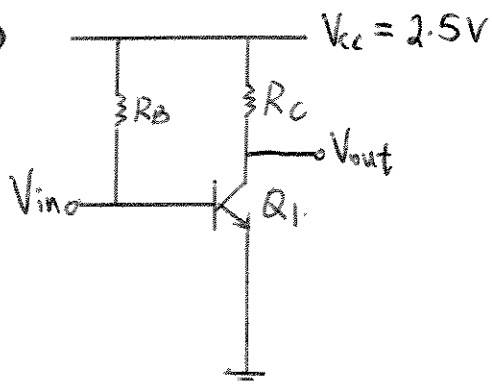 R_{in} : Maximum

$$A_v \geq 20$$

$$R_{out} = R_c = 1K$$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T} \geq 20 \Rightarrow I_c \geq 0.52 \text{ mA}$$

$$R_{in} = R_B // r_{\pi} = \frac{\beta R_B V_T}{R_B I_c + V_T \beta} \quad 1), \quad I_c = \beta \left(\frac{2.5 - V_{BE}}{R_B} \right) \quad 2)$$

As we can see from 1), higher I_c means lower R_{in} .


So set I_c as low as possible, $I_c = 0.52 \text{ mA}$.

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.715 \text{ V}$$

$$\text{From 2), } R_B = \frac{100(2.5 - 0.715)}{0.52} = 343.3K\Omega, \quad V_{\pi} = 5K\Omega$$

$$R_{in} = 4.93K\Omega$$
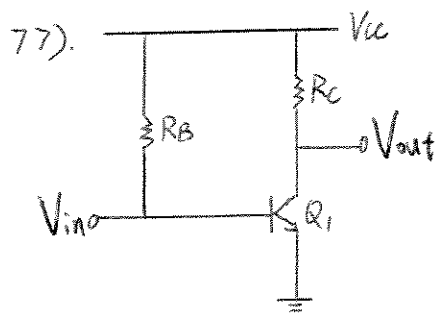
$$\begin{aligned} R_c = 1K\Omega & \Rightarrow A_v = 20 \\ R_B = 343.3K\Omega & \Rightarrow R_{in} = 4.93K\Omega \\ & R_{out} = 1K\Omega \end{aligned}$$



Minimum Supply

$$A_v = 15$$

$$R_{out} = 2\text{K}\Omega, R_c = 2\text{K}\Omega$$

$$V_{BC} \leq 0.4\text{V}$$

$$A_v = g_m R_c = \frac{I_c}{V_T} R_c = 15 \Rightarrow I_c = 0.195\text{mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.689\text{V}$$

$$V_{BC} = V_{BE} - (V_{cc} - I_c R_c) \leq 0.4\text{V}, I_c R_c = 0.39\text{V}$$

$$V_{cc} \geq 0.689 + 0.39 - 0.4 = 0.679\text{V}$$

Since the problem is concerned with minimum power supply, let $V_{cc} = 0.69\text{V}$, Since $V_{BE} = 0.679\text{V}$ ($V_{cc} > V_{BE}$)

$$I_c = \beta \left(\frac{V_{cc} - 0.689}{R_B} \right) \Rightarrow R_B = 100 \left(\frac{0.69 - 0.689}{0.195} \right) = 512.8\Omega$$


$$R_c = 2\text{K}\Omega$$

$$R_B = 512.8\Omega$$

$$V_{cc} = 0.69\text{V}$$

$$\Rightarrow A_v = 15$$

$$R_{out} = 2\text{K}\Omega$$

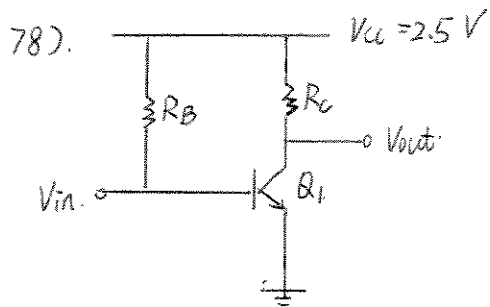


$$A_o = g_m R_c$$

$$A_o = \frac{I_c R_c}{V_T}, \quad \text{Power Dissipation} = I_c V_{cc}$$

$$R_{out} = R_c = \frac{A_o V_T}{I_c}$$

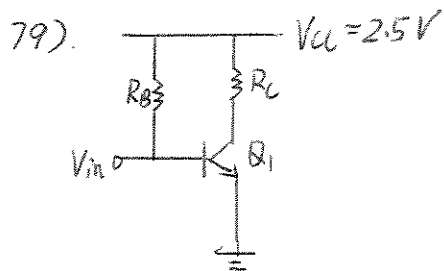For large R_{out} , I_c has to be small, which decreases power.
 So small power dissipation and small output impedance cannot be satisfied simultaneously.



Power Budget = 1mW
 $A_v = 20$


$$A_v = g_m R_c = \frac{I_c R_c}{V_T} = 20, \quad V_{cc} I_c = 1\text{mW}$$

$$I_c = 0.4\text{mA}, \quad R_c = 1.3\text{K}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.708\text{V}, \quad I_c = \beta \left(\frac{V_{cc} - V_{BE}}{R_B} \right) = 100 \left(\frac{2.5 - 0.708}{R_B} \right)$$

$$\Rightarrow R_B = 448\text{K}, \quad R_{in} = 448 // (100 \times \frac{26}{0.4}) = 6.4\text{K}$$
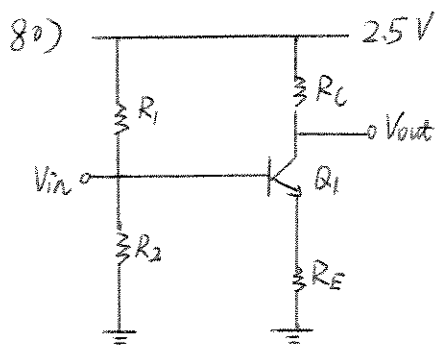
$$R_B = 448\text{K} \Rightarrow \begin{aligned} A_v &= 20 \\ \text{Power Budget} &= 1\text{mW} \\ R_{out} &= 1.3\text{K}\Omega \\ R_{in} &= 6.4\text{K} \end{aligned}$$



$$A_v = 5$$

$$R_{out} = R_c = 500\Omega$$

$$R_E I_c \approx 300\text{mV}$$

$$A_v = \frac{R_c I_c}{R_E I_c + V_T} = \frac{R_c I_c}{300 + 26} \Rightarrow R_c I_c = 1.63\text{V} \Rightarrow I_c = 3.26\text{mA}$$

$$R_E I_c \approx 300\text{mV} \Rightarrow R_E = 92\Omega$$

$$R_1 = \frac{2.5 - (V_{BE} + 0.3)}{10 I_B}, \quad V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.7624$$

$$10 I_B = 0.326\text{mA}$$

$$R_1 = \frac{2.5 - (0.7624 + 0.3)}{0.326} = 4.41\text{k}\Omega$$

$$R_2 = \frac{(0.7624 + 0.3)}{(9 \times 0.0326)} = 3.62\text{k}\Omega$$

$$V_{CE} = 2.5 - 1.63 - 0.3 = 0.57, \quad V_{BE} = 0.7624.$$

Q_1 is in soft saturation region, so active region characteristics

still apply.

$$R_c = 500\Omega$$


$$R_1 = 4.41\text{k}\Omega$$

$$R_2 = 3.62\text{k}\Omega$$

$$R_E = 92\Omega$$

$$\Rightarrow A_v = 5$$

$$R_{out} = 500\Omega$$

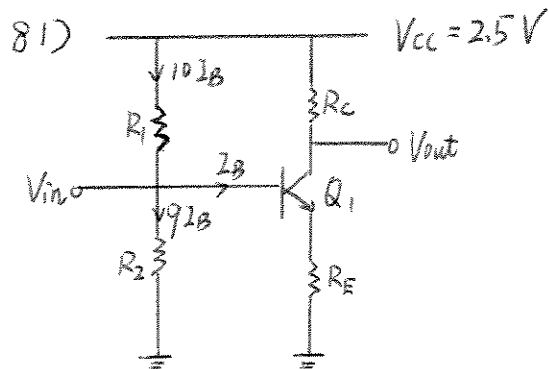

$$A_v = \text{Maximum}$$

$$R_{out} = R_c \leq 1\text{K}\Omega$$

$$V_{BC} = 0.4\text{V}$$

$$R_E I_c \approx 200\text{mV}$$

$$V_{BC} = (V_{BE} + 0.2) - (2.5 - I_c R_c) = 0.4 \quad 1)$$

$$A_v = \frac{R_c I_c}{R_E I_c + V_T} = \frac{R_c I_c}{0.226}$$

Rearrange, 1) becomes $I_c R_c = 0.4 + 2.5 - (V_{BE} + 0.2)$

Guess $V_{BE} = 0.7 \Rightarrow I_c R_c = 2\text{V}$

Let $R_c = 1\text{K} \Rightarrow I_c = 2\text{mA}$

check for V_{BE} : $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.750$, not 0.7, reiterate

$$V_{BE} = 0.75 \Rightarrow I_c R_c = 1.95\text{V}$$

$$R_c = 1\text{K} \Rightarrow I_c = 1.95\text{mA}$$

check for V_{BE} : $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.750$, Converged!!

$$I_c = 1.95\text{mA}, R_E I_c = 200\text{mV} \Rightarrow R_E = 103\Omega$$

$$I_B = 0.0195\text{mA}$$

$$R_1 = \frac{2.5 - (0.750 + 0.2)}{(10)(0.0195)} = 7.95\text{K}$$

$$R_2 = \frac{(0.750 + 0.2)}{(9)(0.0195)} = 5.41\text{K}$$

81)

$$A_v = \frac{R_c I_c}{R_E I_c + V_T} = \frac{1.95}{0.226} = 8.63$$

This is the maximum gain we would get
when R_{out} is $1\text{K}\Omega$ and V_{ce} is at 0.4V .

Since anything larger will violate either requirement.


$$R_c = 1\text{K}\Omega$$

$$R_E = 103\Omega$$

$$R_1 = 7.95\text{K}\Omega$$

$$R_2 = 5.41\text{K}\Omega$$
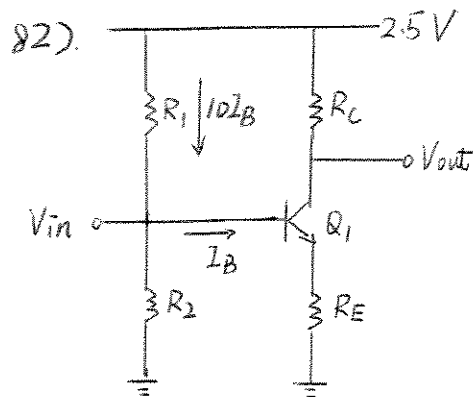
$$\Rightarrow \begin{matrix} A_v = 8.63 \\ R_{out} = 1\text{K}\Omega \end{matrix}$$



Power budget = 5 mW

$$A_v = 5$$

$$R_E I_c \approx 200 \text{ mV}$$

$$V_{cc} \left(I_c + \frac{I_c}{10} \right) = 5 \text{ mW} \Rightarrow I_c = 1.82 \text{ mA}, I_B = 0.0182 \text{ mA}$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.747$$

$$A_v = \frac{R_c I_c}{R_E I_c + V_T} = \frac{R_c I_c}{0.226} = 5 \Rightarrow R_c I_c = 1.13 \text{ V} \Rightarrow R_c = 621 \Omega$$

$$R_1 = \frac{2.5 - (0.747 + 0.2)}{(10)(0.0182)} = 8.53 \text{ K}\Omega$$

$$R_2 = \frac{(0.747 + 0.2)}{(9)(0.0182)} = 5.78 \text{ K}\Omega$$

$$R_E I_c \approx 200 \text{ mV} \Rightarrow R_E = 110 \Omega$$

$$R_c = 621 \Omega$$


$$R_E = 110 \Omega$$

$$R_1 = 8.53 \text{ K}\Omega$$

$$R_2 = 5.78 \text{ K}\Omega$$

$$\Rightarrow A_v = 5$$

Power Budget = 5 mW

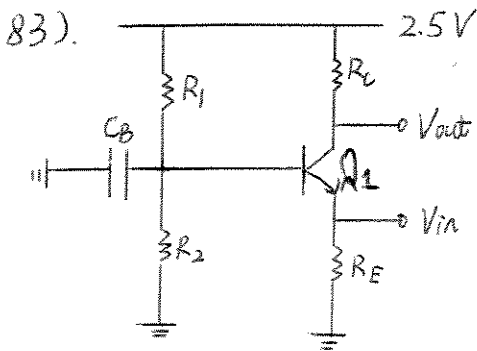

$$A_v = 20$$

$$R_{in} = 50\Omega$$

$$R_E I_C \approx 10 V_T = 260 \text{ mV}$$

$$R_{in} = \frac{1}{g_m} = 50\Omega, \text{ since } R_E \text{ doesn't affect input impedance.}$$

$$\frac{V_T}{I_C} = 50\Omega \Rightarrow I_C = \frac{V_T}{50\Omega} = 0.52 \text{ mA}, I_B = 0.0052 \text{ mA}$$

$$A_v = \frac{R_C}{1/g_m} = \frac{I_C R_C}{V_T} = 20 \Rightarrow R_C = 1\text{ k}\Omega$$

$$R_1 = \frac{2.5 - (0.715 + 0.260)}{(10)(0.0052)} = 29.3\text{ K}$$

$$R_2 = \frac{(0.715 + 0.260)}{(9)(0.0052)} = 20.83\text{ K}$$


$$R_E I_C \approx 260 \text{ mV} \Rightarrow R_E \approx 500\Omega$$

$$\frac{1}{C_B (2\pi)(200)} = \frac{1}{10} \frac{1}{g_m} = 5\Omega \Rightarrow C_B = 159.1 \mu\text{f}$$

$$R_C = 1\text{ k}\Omega, R_E = 500\Omega, R_1 = 29.3\text{ K}\Omega, R_2 = 20.83\text{ K}\Omega, C_B = 159.1 \mu\text{f}$$

$$\Rightarrow A_v = 20, R_{in} = 50\Omega$$

84)

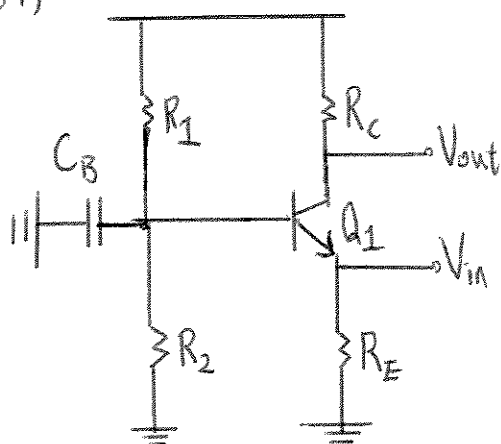

$$A_v = 8$$

$$R_{out} = 500\Omega$$

$$R_{out} = R_c = 500\Omega$$

$$A_v = \frac{I_c R_c}{V_T} = 8 \Rightarrow I_c = 0.416 \text{ mA}, I_B = 0.00416 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.709$$

$$R_E \approx \frac{260 \text{ mV}}{I_c} = 625\Omega, R_1 = \frac{2.5 - (0.709 + 0.260)}{(10)(0.00416)} = 36.8 \text{ K}\Omega$$

$$R_2 = \frac{(0.709 + 0.260)}{(9)(0.00416)} = 25.9 \text{ K}\Omega$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = 62.5\Omega, \frac{1}{C_B 200(2\pi)} = \frac{62.5}{10} \Rightarrow C_B = 127.3 \text{ }\mu\text{f}$$

$$C_B = 127.3 \text{ }\mu\text{f}$$

$$R_1 = 36.8 \text{ K}$$

$$R_2 = 25.9 \text{ K}$$


$$R_c = 500\Omega$$

$$R_E = 625\Omega$$

$$\Rightarrow A_v = 8$$

$$R_{out} = 500\Omega$$

85)

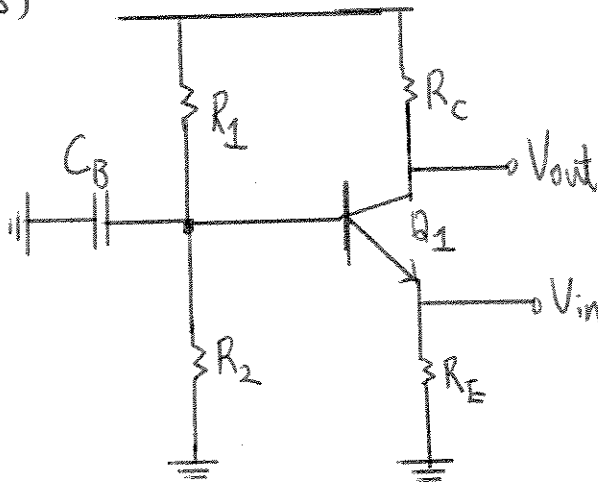

$$A_v = 20$$

$$R_c = 200\Omega$$

$$(R_c = R_{out})$$


$$A_v = \frac{I_c R_c}{V_T} = 20 \Rightarrow I_c = 2.6 \text{ mA}$$

$$I_B = 0.026 \text{ mA}, 10I_B = 0.26 \text{ mA}$$

$$\text{Power} = V_{cc} (I_c + 10I_B) = 2.5 (0.26 \text{ mA} + 2.6 \text{ mA}) = 7.15 \text{ mW}$$

This is the minimum power dissipation, since anything lower will lower the voltage gain.

86)

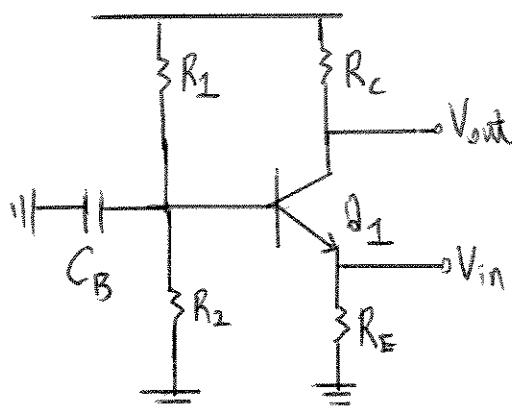

$$Power = 5mW$$

$$A_v = 10$$

$$V_{cc} I_c + V_{cc} \frac{I_c}{10} = 5mW, \quad V_{cc} I_c \cdot 1.1 = 5mW, \quad I_c = 1.82mA$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.747$$

$$A_v = g_m R_c = \frac{I_c R_c}{V_T} = 10 \Rightarrow R_c = 0.143K\Omega$$


$$I_c R_E \approx 260mV, \quad R_E \approx 142.9\Omega$$

$$R_1 = \frac{2.5 - (0.747 + 0.260)}{(10)(0.0182)} = 8.2K, \quad R_2 = \frac{(0.747 + 0.260)}{(9)(0.0182)} = 6.15K$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = 14.3\Omega, \quad \frac{1}{C_B 2\pi(200)} = \frac{14.3}{10} \Rightarrow C_B = 556.5\mu f$$

$$R_c = 143\Omega, \quad R_E = 143\Omega, \quad R_1 = 8.2K, \quad R_2 = 6.15K, \quad C_B = 556.5\mu f.$$
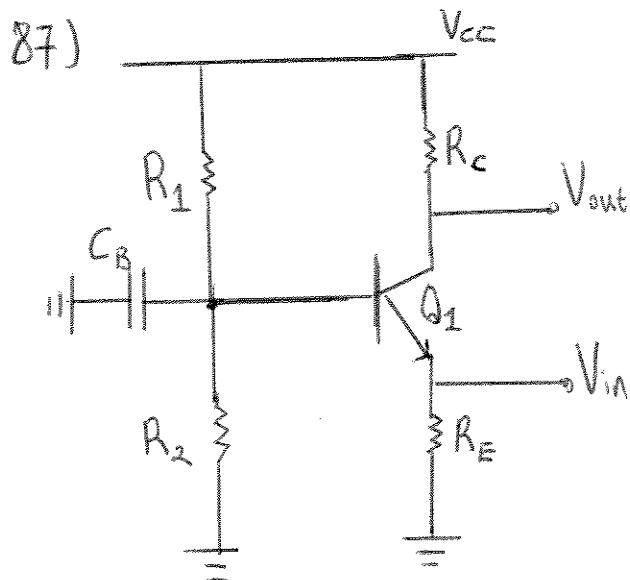
$$\Rightarrow A_v = 10, \quad Power = 5mW$$



$$R_{in} = 50 \Omega$$

$$A_v = 20$$

Assume R_E doesn't affect R_{in} significantly,
 $R_{in} \approx \frac{1}{g_m} = 50 \Omega$

$$A_v = \frac{R_c}{1/g_m} = 20 \Rightarrow R_c = 1K\Omega, \quad \frac{1}{g_m} = \frac{V_T}{I_c} \Rightarrow I_c = \frac{26mV}{50\Omega} = 0.52 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.715V, \quad R_E I_c = 260mV \Rightarrow R_E = 500\Omega$$

$$V_{cc} = I_c R_c + V_{CE} + I_c R_E = 0.52 + V_{CE} + 0.260$$

$$V_{BC} \text{ is forward biased to } 0.4V, \quad V_{CE} = V_{BE} - 0.4 = 0.315V$$

$$V_{cc} = 0.52 + 0.315 + 0.260 = 1.1V. \quad (\text{Minimum Supply Voltage})$$


$$R_1 = \frac{1.1 - (0.715 + 0.260)}{0.052} = 2.4K, \quad R_2 = \frac{(0.715 + 0.260)}{(1)(0.0052)} = 20.83K$$

$$\frac{1}{C_B 2\pi 200} = \frac{1}{10} \frac{1}{g_m} = 5 \Rightarrow C_B = 159.2 \mu f$$

$$V_{cc} = 1.1V, \quad R_1 = 2.4K, \quad R_2 = 20.83K, \quad R_c = 1K, \quad R_E = 500\Omega, \quad C_B = 159.2\mu f$$

$$\Rightarrow R_{in} = 50\Omega, \quad A_v = 20$$

88)

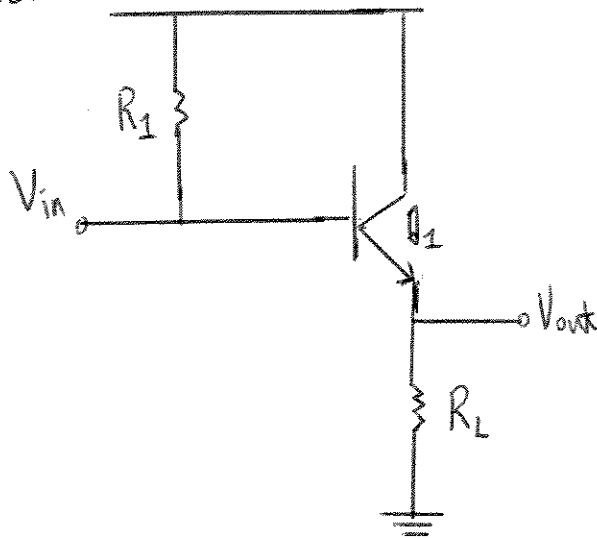

$$A_v = 0.85$$

$$R_{in} > 10\text{K}\Omega$$

$$R_L = 200\Omega$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.85 \Rightarrow \frac{200}{200 + \frac{1}{g_m}} = 0.85$$

$$\Rightarrow 200 = 0.85 \left(200 + \frac{1}{g_m} \right) \Rightarrow \frac{1}{g_m} = 35.294\Omega$$

$$\Rightarrow I_c = \frac{26\text{mV}}{35.294\Omega} = 0.737\text{mA}, \quad V_{BE} = V_T \ln\left(\frac{0.737}{6 \times 10^{-8}}\right) = 0.724\text{V}$$

$$R_{in} = R_1 \parallel (r_{\pi} + (1 + \beta)(200\Omega))$$

$$R_{in} = R_1 \parallel 23.73\text{K}$$

$$R_{in} = \frac{R_1 \cdot 23.73\text{K}}{R_1 + 23.73\text{K}} > 10\text{K} \Rightarrow R_1 > 17.28\text{K} \text{ (Input Impedance Requirement)}$$

To support an I_c of 0.737, R_1 must be determined.

88)

$$R_1 = \frac{2.5 - (0.724 + (0.737 \times 0.2) / 0.99)}{0.737 / 100}$$

$$R_1 = 220.77 \text{ k}\Omega$$

$$R_1 = 220.77 \text{ k}\Omega \Rightarrow R_{in} = 220.77 \text{ k}\Omega // 23.73 \text{ k}\Omega$$

$$R_{in} = 21.43 \text{ k}\Omega > 10 \text{ k}\Omega$$

$$R_1 = 220.77 \text{ k}\Omega$$


$$R_L = 200 \Omega$$

\Rightarrow

$$A_v = 0.85$$

$$R_{in} = 21.43 \text{ k}\Omega$$

89)

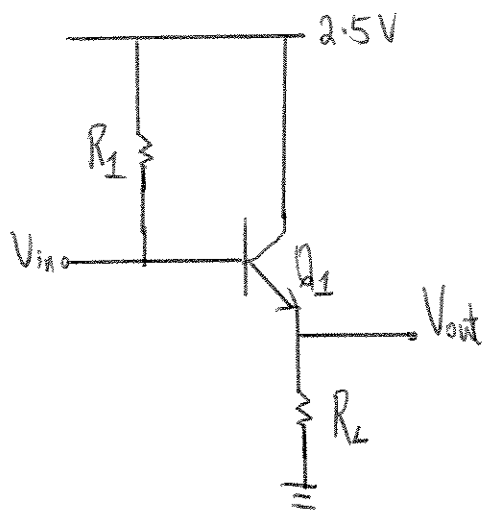

$$P_{\text{Power}} = 5 \text{ mW}$$

$$A_v = 0.9$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.9 \Rightarrow R_L = 0.9(R_L + \frac{1}{g_m})$$


$$R_L = 9 \frac{1}{g_m}$$

$$P_{\text{Power}} = 2.5 \left(I_c + \frac{I_c}{\beta} \right) \Rightarrow I_c = 1.98 \text{ mA}$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = \frac{26 \text{ mV}}{1.98 \text{ mA}} = 13.13 \Omega$$

$$R_L = (9)(13.13) = 118.17 \Omega$$

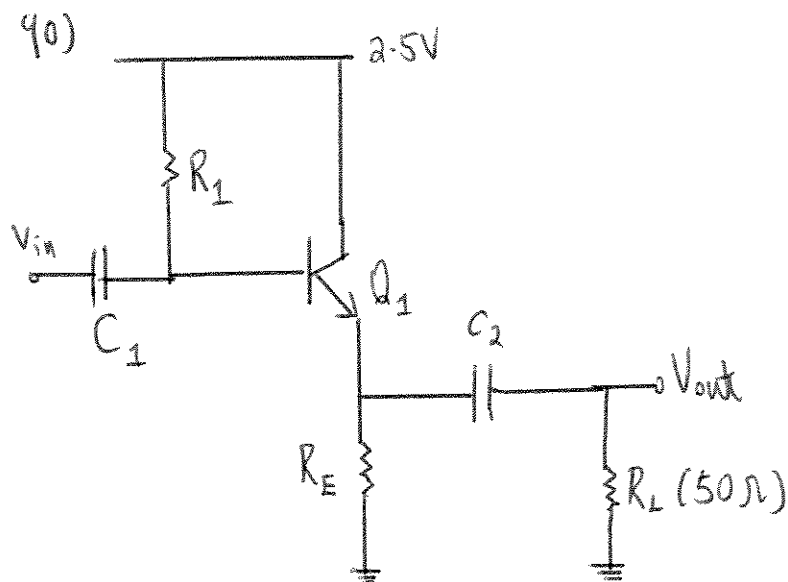This is the minimum load resistance, since anything lower will lower the voltage gain.



$A_v = 0.8$
 Since R_E doesn't
 affect Voltage gain
 significantly.

$$A_v \approx \frac{R_L}{R_L + \frac{1}{g_m}} = 0.8$$

$$R_L = 0.8 \left(R_L + \frac{1}{g_m} \right)$$

$$0.2 R_L = 0.8 \frac{1}{g_m}$$

$$R_L = 4 \frac{1}{g_m} \Rightarrow \frac{R_L}{4} = \frac{1}{g_m} = 12.5 = \frac{V_T}{I_c}$$

$$I_c = \frac{26 \text{ mV}}{12.5 \Omega} = 2.08 \text{ mA}$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.751 \text{ V}$$

$$\text{Let } R_E I_c = 20 V_T, \quad R_E = \frac{20}{g_m} = 250 \Omega$$

(0.52V)

$$R_L = \frac{2.5 - (0.751 + 0.52)}{0.0208 \text{ mA}} = 59.1 \text{ K}$$

90)

$$\frac{1}{(2\pi)(100 \times 10^6)C_1} = \frac{1}{10} \frac{1}{g_m} \Rightarrow C_1 = 1.27 \text{ nf}$$

$$\frac{1}{(2\pi)(100 \times 10^6)C_2} = \frac{1}{10} 50 \Rightarrow C_2 = 0.32 \text{ nf}$$

Cs. C2 will not load Q1.

$$C_1 = 1.27 \text{ nf}$$

$$C_2 = 0.32 \text{ nf}$$

$$R_1 = 59.1 \text{ k}\Omega \Rightarrow A_v = 0.8$$

$$R_E = 250 \Omega$$

$$R_L = 50 \Omega$$