
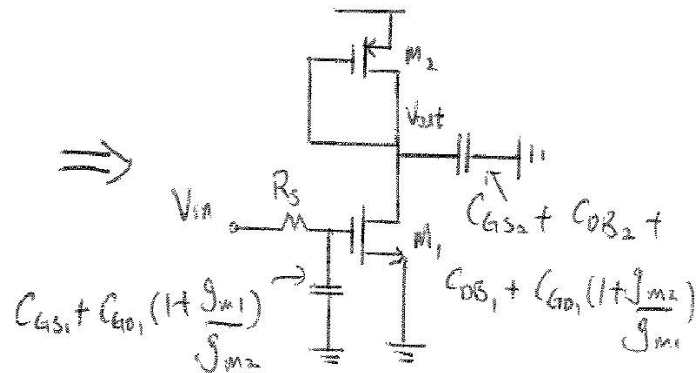


38)

a)


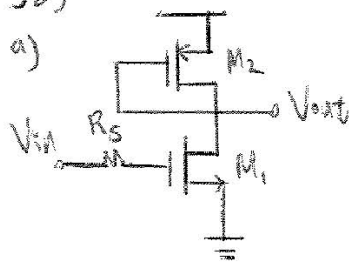


$$DC \text{ gain} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{pin} = \frac{1}{R_S (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{pout} = \frac{g_{m2}}{(C_{GS2} + C_{DB2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}}))}$$

b)

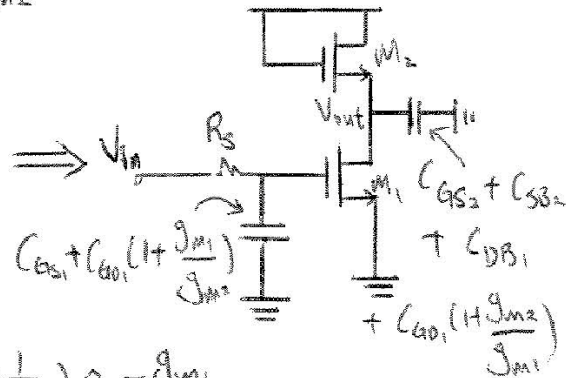
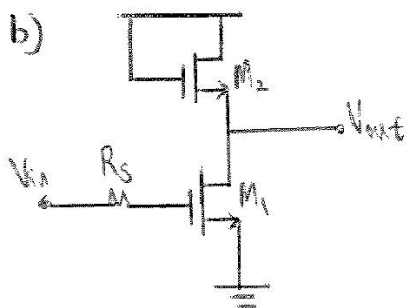


$$DC \text{ gain} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{pin} = \frac{1}{R_S (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{pout} = \frac{g_{m2}}{C_{SB2} + C_{GS2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}})}$$

38)

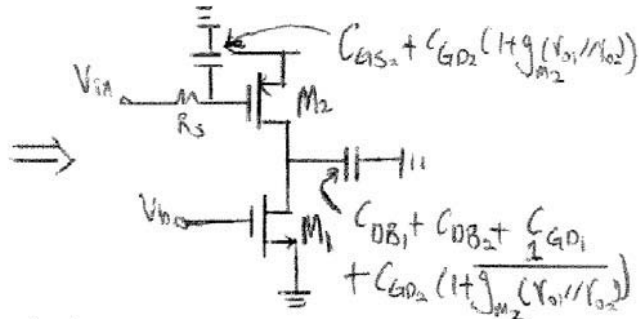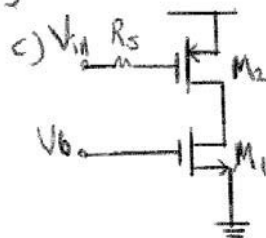

DC gain: $-g_{m2} (V_{O1} // V_{O2})$


$$\omega_{pin} = \frac{1}{R_S (C_{GS2} + C_{GD2} (1 + g_{m2} (V_{O1} // V_{O2})))}$$

$$\omega_{pout} = \frac{1}{(V_{O1} // V_{O2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2} (1 + \frac{1}{g_{m2} (V_{O1} // V_{O2})})]}$$

$$\omega_{pout} \approx \frac{1}{(V_{O1} // V_{O2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2}]}$$

Since $g_{m2} (V_{O1} // V_{O2}) \gg 1$

42)

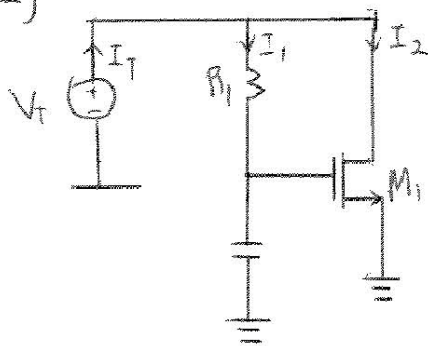

$\lambda = 0$, and neglect other capacitances.

$$I_T = I_1 + I_2$$


$$I_1 = \frac{V_T}{R_1 + \frac{1}{C_1 s}}, \quad I_2 = \frac{g_{m1} V_T}{C_1 R_1 s + 1}$$

$$I_T = \frac{C_1 s V_T}{C_1 R_1 s + 1} + \frac{g_{m1} V_T}{C_1 R_1 s + 1} \Rightarrow \frac{V_T}{I_T} = \frac{C_1 R_1 s + 1}{C_1 s + g_{m1}}$$

$$s \rightarrow j\omega \Rightarrow \frac{C_1 R_1 (j\omega) + 1}{C_1 j\omega + g_{m1}} = Z_T(j\omega)$$

$$|Z_T| = |Z_{in}| = \frac{\sqrt{(C_1 R_1 \omega)^2 + 1}}{\sqrt{C_1^2 \omega^2 + g_{m1}^2}} = \frac{\sqrt{C_1 R_1 \omega^2 + 1}}{g_{m1} \sqrt{\left(\frac{C_1 \omega}{g_{m1}}\right)^2 + 1}}$$

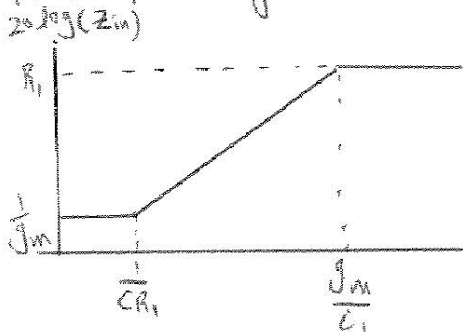
At $\omega = \frac{1}{C_1 R_1}$, we have a zero, at $\omega = \frac{g_{m1}}{C_1}$, we have a pole. If $R_1 > \frac{1}{g_{m1}}$, the zero $\frac{1}{C_1 R_1}$ is at a lower frequency than the pole, and the bode-plot for magnitude would look like the following.



The bode-plot shows an impedance that increases with frequency, an inductive behavior.

46)

a)

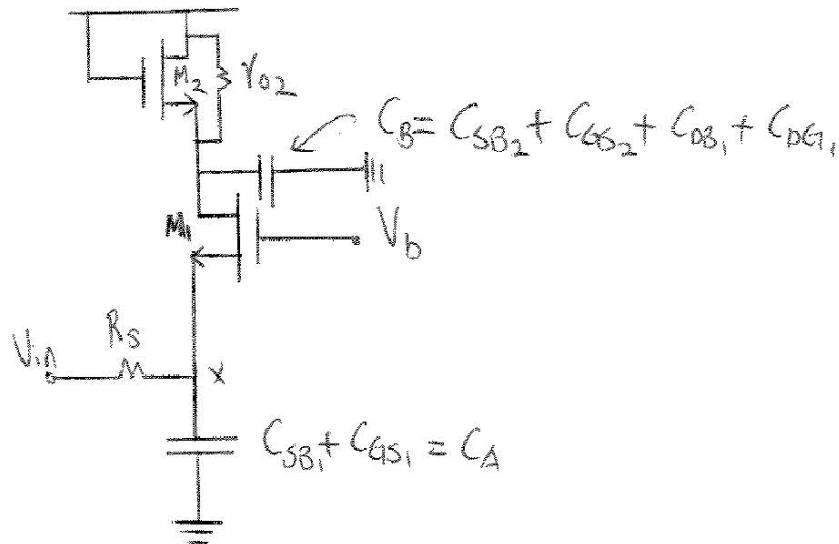

$$V_{out} = -(0 - V_x) g_{m1} \left[\frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right] = V_x g_{m1} \left[\frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]$$

Node equation at X, $\frac{V_x - V_{in}}{R_s} + V_x C_A s - g_{m1} (0 - V_x) = 0$

$$V_x \left(\frac{1}{R_s} + C_A s + g_{m1} \right) = \frac{V_{in}}{R_s} \Rightarrow V_x = \frac{V_{in}}{(1 + R_s C_A s + R_s g_{m1})}$$

substitute in V_x and solving for $V_{out}/V_{in} \Rightarrow$


$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} \left[\frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]}{(1 + R_s C_A s + R_s g_{m1})}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_s C_A s + R_s g_{m1})}$$

Where $C_B = C_{SB2} + C_{DS2} + C_{DB1} + C_{DB3}$

$C_A = C_{SB1} + C_{DS1}$

46)

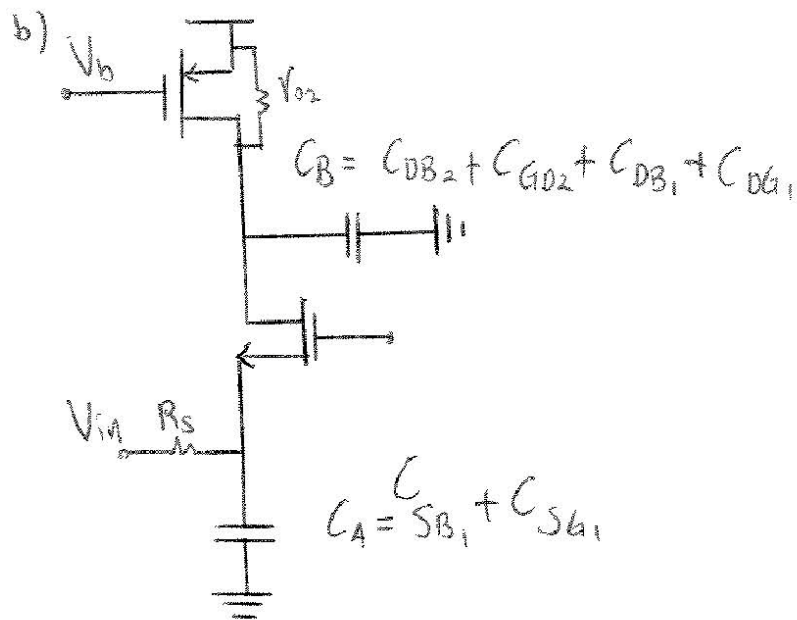

Similar to part a), with $\frac{1}{g_{m2}}$ replaced by V_{o2} ,
and different C_B .


$$\text{So } \frac{V_{out}}{V_{in}} = \frac{g_{m1} V_{o2}}{(C_B V_{o2} s + 1)(1 + R_s C_A s + R_s g_{m1})}$$

Where $C_B = C_{DB2} + C_{GD2} + C_{DB1} + C_{GD1}$

$$C_A = C_{SB1} + C_{SS1}$$

46)

c)

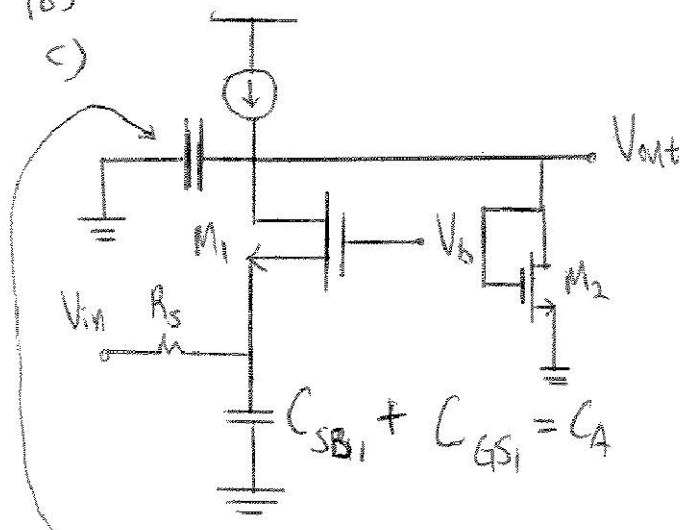

$$C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$$


AC-wise, this circuit is very similar to part a). Its transfer function is the same as part a), except for C_B .

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_S C_A s + R_S g_{m1})}$$

Where $C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$

$$C_A = C_{SB1} + C_{GS1}$$

50)

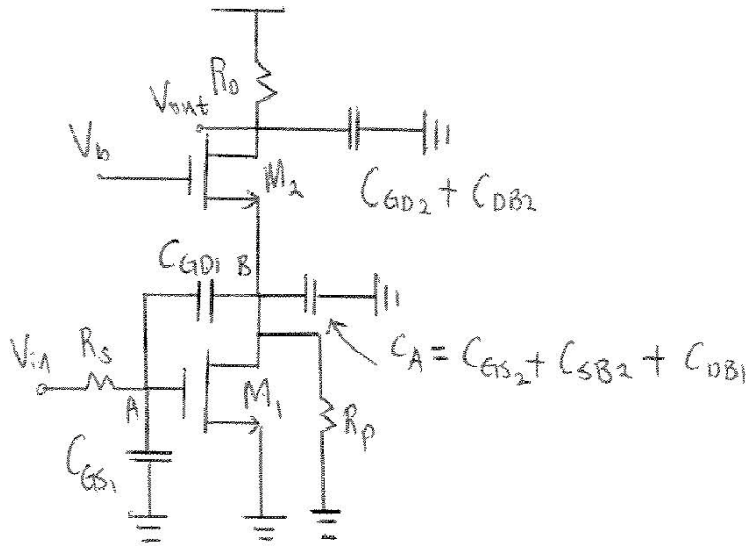

Dc gain from A to B is $-g_{m1}(R_p \parallel \frac{1}{g_{m2}})$


Applying Miller's Theorem:

$$\omega_{pin}(\omega_{pA}) = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + g_{m1}(R_p \parallel \frac{1}{g_{m2}})))}$$

$$\omega_{pB} = \frac{1}{R_p \parallel \frac{1}{g_{m2}} [C_{GS2} + C_{SB2} + C_{DB1} + C_{GD1} (1 + 1/g_{m1}(R_p \parallel \frac{1}{g_{m2}}))]}$$

$$\omega_{pout} = \frac{1}{R_o (C_{GD2} + C_{DB2})}$$


1. (a)

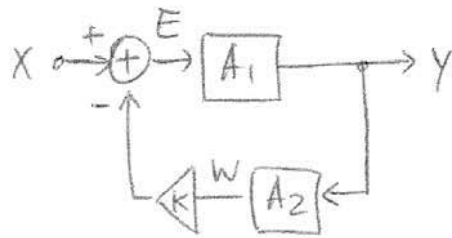

$$Y = A_1 E_1 - A_1 [X - Y A_2 K]$$

$$\Rightarrow \frac{Y}{X} = \frac{A_1}{1 + K A_1 A_2}$$

(b)

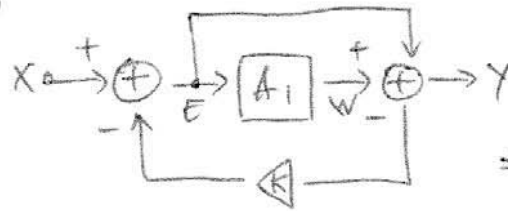


$$Y = E - A_1 W$$

$$= (X - KY) - A_1 (X - KY)$$

$$\Rightarrow \frac{Y}{X} = \frac{1 - A_1}{1 + (1 - A_1)K}$$

(c)

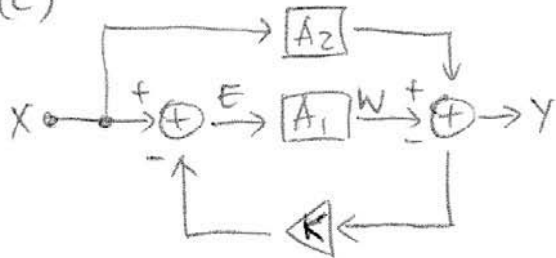


$$Y = X A_2 - W$$

$$= X A_2 - A_1 (X - Y K)$$

$$\Rightarrow \frac{Y}{X} = \frac{A_2 - A_1}{1 - A_1 K}$$

(d)

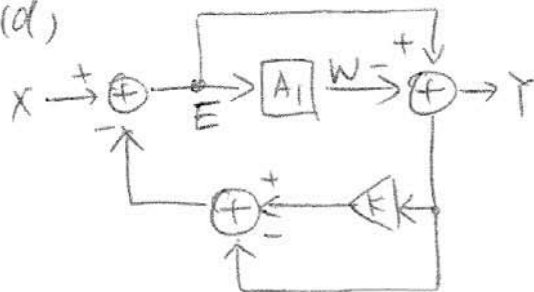

$$Y = E - W$$


$$= (X - (KY - Y)) - A_1 [X - (KY - Y)]$$

$$\Rightarrow \frac{Y}{X} = \frac{(1 - A_1)}{1 + (K - 1)(1 - A_1)}$$

$$(c) \frac{Y}{X} = \frac{A_2 - A_1}{1 - A_1 K}$$

4.

(a)

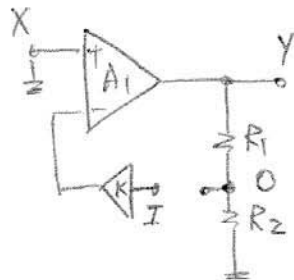


(X is grounded
in loop-gain calculation)

$$0 = Y \frac{R_2}{R_1 + R_2} = (-IK)A_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} \\ = +KA_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

(b)

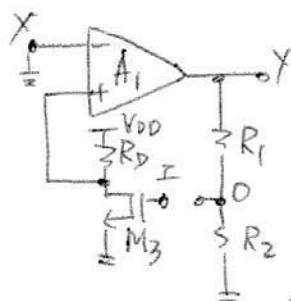


(X is grounded)

$$0 = Y \left(\frac{R_2}{R_1 + R_2} \right)$$

$$= -I g_{m3} R_D A_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} \\ = +g_{m3} R_D A_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

(c)

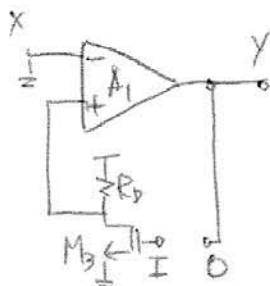


(X is grounded)

$$0 = Y = -I g_{m3} R_D A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} \\ = +g_{m3} R_D A_1$$

(d)

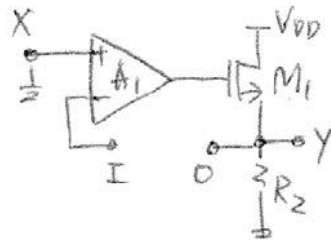

(X is grounded)

$$0 = V = -I \times \frac{g_{m1} R_2}{1 + g_{m1} R_2} \times A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain}$$
$$= + A_1 \frac{g_{m1} R_2}{1 + g_{m1} R_2}$$

5.

$$(a) \frac{Y}{X} = \frac{A_{o.L.}}{1 + \text{Loop Gain}} = \frac{A_1}{1 + A_1 K \left(\frac{R_2}{R_1 + R_2} \right)}$$

$$(b) \frac{Y}{X} = \frac{A_1}{1 + g_{m3} R_D A_1 \left(\frac{R_2}{R_1 + R_2} \right)}$$

$$(c) \frac{Y}{X} = \frac{A_1}{1 + g_{m3} R_D A_1}$$

$$(d) \frac{Y}{X} = \frac{A_1}{1 + A_1 \left(\frac{g_{m1} R_2}{1 + g_{m1} R_2} \right)}$$