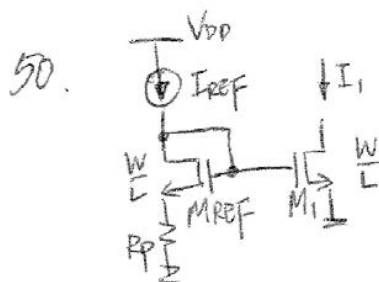


Chapter 9



Determine R_p such that $I_1 = 2I_{REF}$.

First calculate V_{gs1} :

$$V_{gs1} = \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} = 2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} \quad \text{--- (1)}$$

Assuming I_1 is in saturation:


$$\begin{aligned} I_{REF} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs,REF} - V_{TH})^2 \\ &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) [V_{gs1} - I_{REF} R_p - V_{TH}]^2 \end{aligned}$$

Substitute (1) into I_{REF} :

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} - I_{REF} R_p \right]^2 \quad \text{--- (2)}$$

$$\text{Solve for } R_p: \quad R_p = \frac{(2 - \sqrt{2})}{\sqrt{I_{REF}} \cdot \mu_n C_{ox} \left(\frac{W}{L}\right)}$$

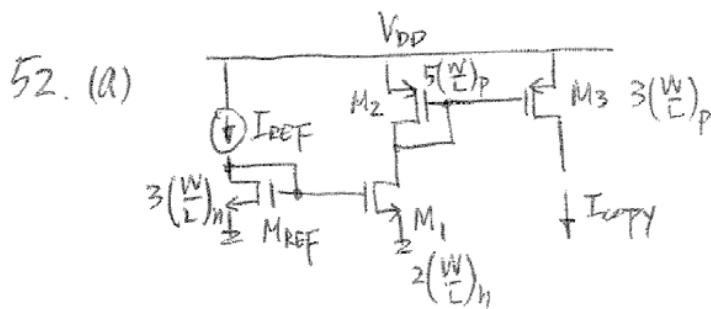
From (2), we find that R_p is independent of any change in V_{TH} , ΔV !!



$$V_{GS, REF} = V_{GS, 1} : \Rightarrow I_{D, 1} = \frac{2}{3} I_{REF}$$

$$V_{GS, 2} = V_{GS, 3} : \Rightarrow I_{COPY} = \frac{3}{5} I_{D, 2} = \frac{3}{5} I_{D, 1}$$
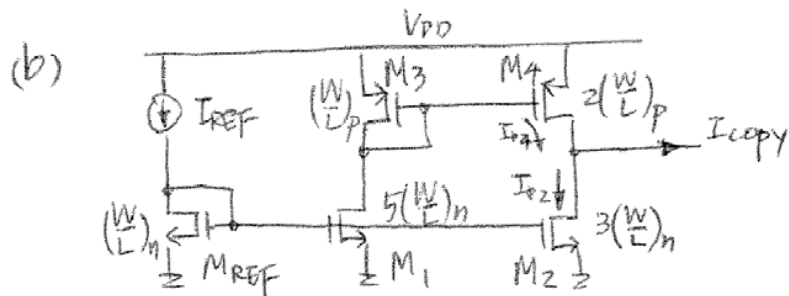
$$= \frac{3}{5} \cdot \left(\frac{2}{3} I_{REF} \right) = \frac{2}{5} I_{REF}$$







$$V_{GS, REF} = V_{GS, 1} : I_{D, 1} = 5 I_{REF}$$

$$V_{GS, 3} = V_{GS, 4} : I_{D, 4} = 2 I_{D, 3} = 2 I_{D, 1} = 10 I_{REF}$$


$$V_{GS, REF} = V_{GS, 2} : I_{D, 2} = 3 I_{REF}$$

$$\therefore I_{COPY} = I_{D, 4} - I_{D, 2} = 7 I_{REF}$$

Chapter 10

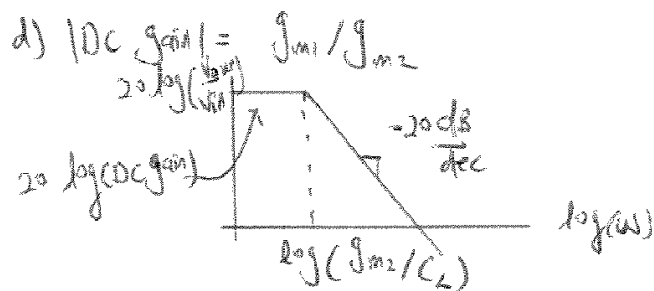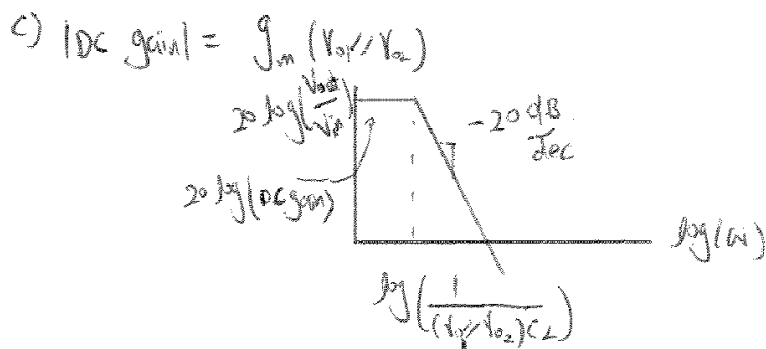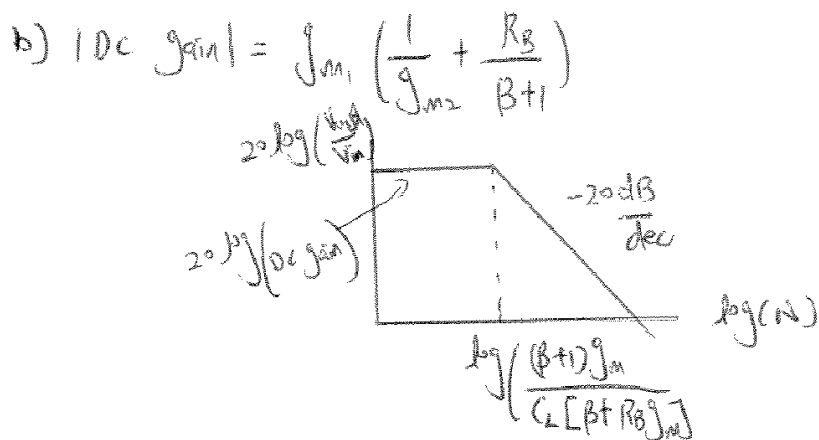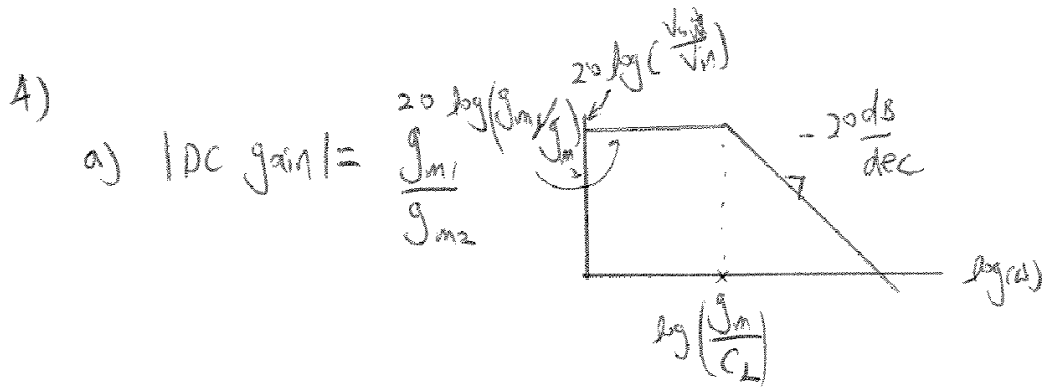

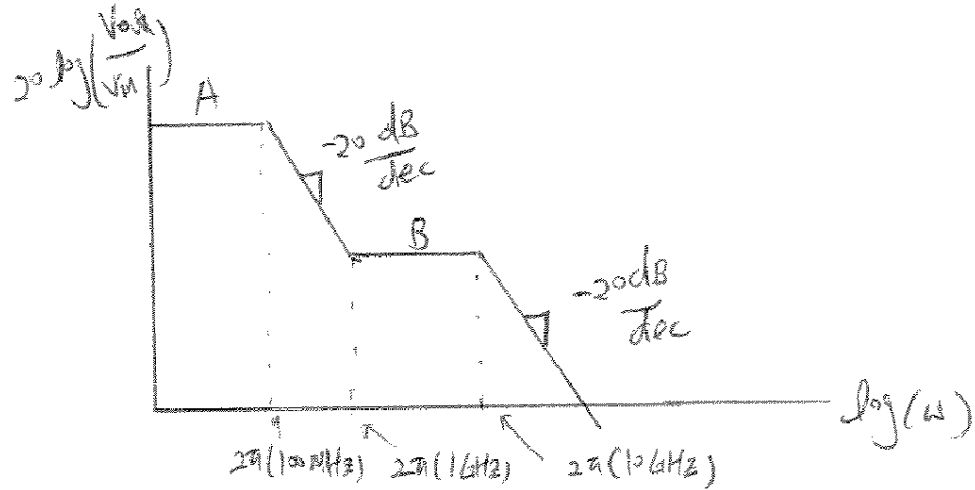6)
Poles at 100 MHz, 10 GHz
Zero at 1 GHz.




$$A(100\text{MHz}) = B(1\text{GHz})$$

$$B = 0.1A$$

图中横坐标应为 $\log(2\pi \cdot 10^8)$, $\log(2\pi \cdot 10^9)$, $\log(2\pi \cdot 10^{10})$.

12)

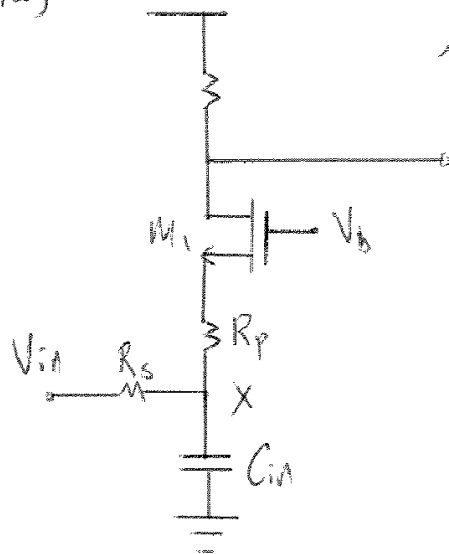

$$\lambda = 0$$


To find input pole,
let $V_{in} = 0$ and
find the equivalent
resistance and capacitance
from node X to
ground.

$$R_x = R_s \parallel \left(R_p + \frac{1}{g_{m_1}} \right), \quad C_x = C_{in}$$

$$\omega_{p.in} = \frac{1}{C_{in} \left[R_s \parallel \left(R_p + \frac{1}{g_{m_1}} \right) \right]}$$

$$\omega_{p.out} = \frac{1}{R_o C_L}$$

13)

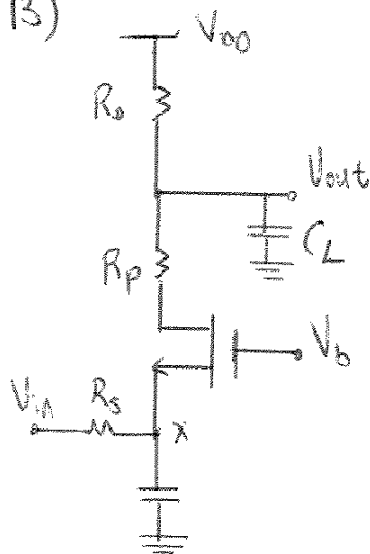

$\lambda=0$, neglect all other caps.

$$R_x = R_s \parallel \frac{1}{g_m}$$

$$C_x = C_{in}$$


$$R_{out} = R_0 \quad (\text{Since } r_o = \infty)$$

$$C_{out} = C_L$$

$$\omega_{psn} = \frac{1}{(R_s \parallel \frac{1}{g_m}) C_{in}}$$

$$\omega_{pout} = \frac{1}{R_0 C_L}$$

14)

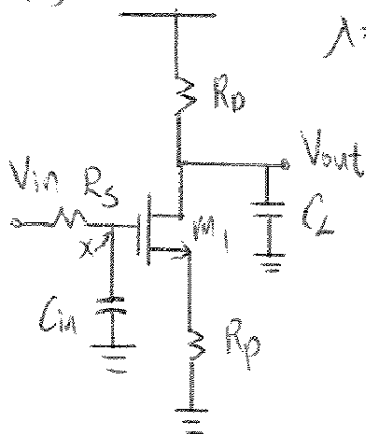


$\lambda=0$

$$R_x = R_s, \quad R_{out} = R_0$$


$$C_x = C_{in}, \quad C_{out} = C_L$$

$$\omega_{psn} = \frac{1}{R_s C_{in}}$$

$$\omega_{pout} = \frac{1}{R_0 C_L}$$

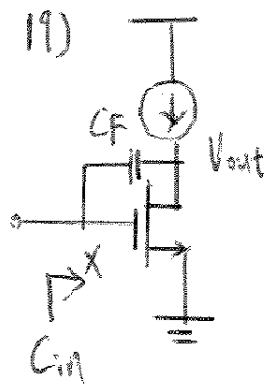
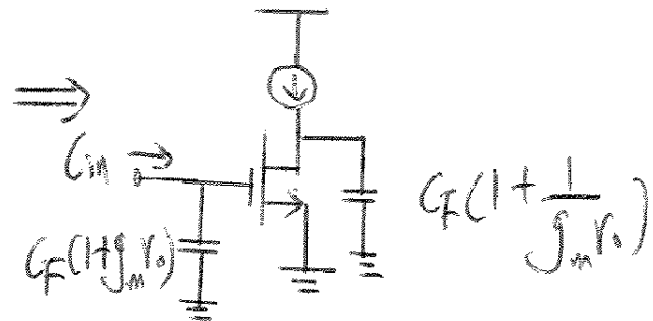
$$\lambda > 0, \text{ DC gain} = -g_m V_o$$



$$C_{in} = C_F (1 + g_m r_o), \text{ neglecting other caps.}$$

$$\text{As } \lambda \rightarrow 0, r_o \rightarrow \infty, \text{ DC gain} \rightarrow \infty,$$

$$C_{in} \rightarrow \infty, \text{ this bandwidth will } \rightarrow 0.$$