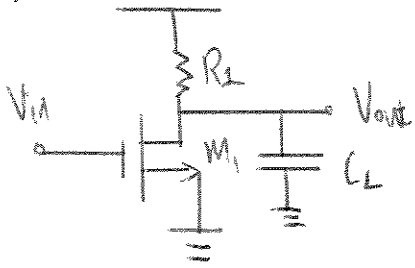


1)



$$R_1 = 1 \text{ k}\Omega$$

$$C_L = 1 \text{ pF}$$

$$V_{out} = -g_{m1} R_1 \parallel \frac{1}{C_L s} V_{in} \Rightarrow \frac{V_{out}}{V_{in}} = -g_{m1} R_1 \parallel \frac{1}{C_L s}$$


$$\frac{V_{out}}{V_{in}} = -g_{m1} \left(\frac{R_1}{R_1 C_L s + 1} \right), \quad s \rightarrow j\omega, \quad \frac{V_{out}}{V_{in}}(j\omega) = -g_{m1} \left(\frac{R_1}{R_1 C_L j\omega + 1} \right)$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_{m1} R_1}{\sqrt{1 + (\omega R_1 C_L)^2}}, \quad \text{Fall by } 10\% = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} R_1 \cdot 0.9$$

$$\Rightarrow \frac{g_{m1} R_1}{\sqrt{1 + (\omega R_1 C_L)^2}} = g_{m1} R_1 \cdot 0.9 \Rightarrow \omega_{-10\%} = 4.84 \times 10^9 \text{ rad/s}$$

$$2\pi f = 4.84 \times 10^9 \Rightarrow f_{-10\%} = 7.708 \times 10^8 \text{ Hz}$$

2)

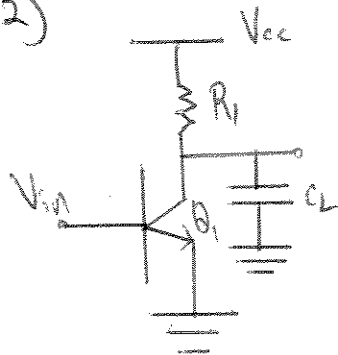

-3dB bandwidth = 1 GHz

$C_L = 2 \text{ pF}$

Power = 2 mW

Low freq gain?

$$\text{Power} = 2.5 \text{ V } I_c, \quad I_c = 0.8 \text{ mA}$$


$$\text{Dominant Pole at the output} = \frac{1}{R_L C_L} = 2\pi (1 \text{ GHz})$$

$$R_L = 79.58 \text{ Ohm}$$

$$\text{Low Freq gain: } -g_m R_L = \frac{-I_c R_L}{V_T} = \frac{(79.58)(0.8)}{26}$$


$$A_v \Big|_{\text{low freq}} = -2.45$$

3)

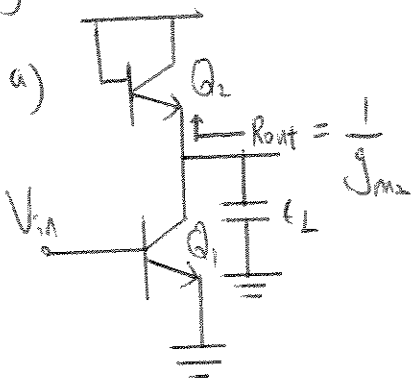


Assume $\beta \gg 1$

$$-3dB = \frac{g_{m2}}{C_L}$$

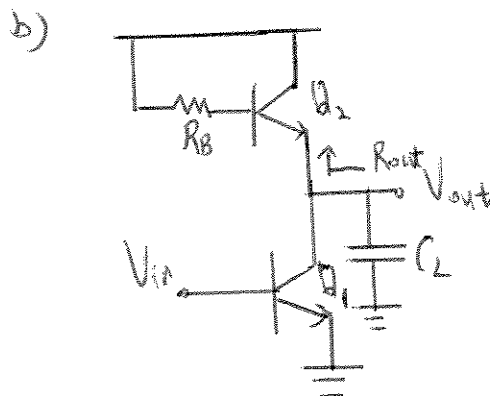


$$R_{out} = \frac{1}{g_{m2}} + \frac{R_B}{\beta + 1}$$
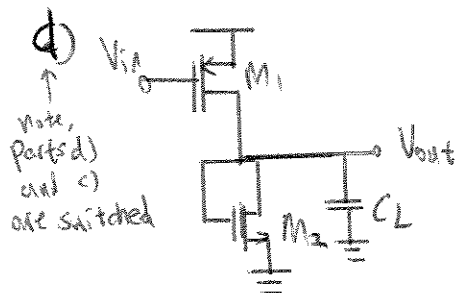
$$-3dB = \frac{(\beta + 1)g_{m2}}{C_L [\beta + R_B g_{m2}]}$$



$$R_{out} = \frac{1}{g_{m2} \parallel Y_{02} \parallel Y_{01}} \approx \frac{1}{g_{m2}}$$


$$-3dB = \frac{g_{m2}}{C_L}$$

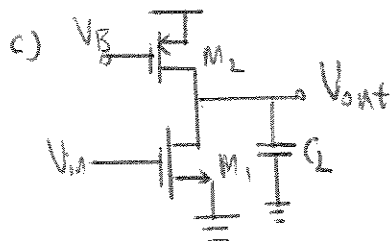


$$R_{out} = Y_{01} \parallel Y_{02}$$

$$-3dB = \frac{1}{(Y_{01} \parallel Y_{02}) C_L}$$


4)

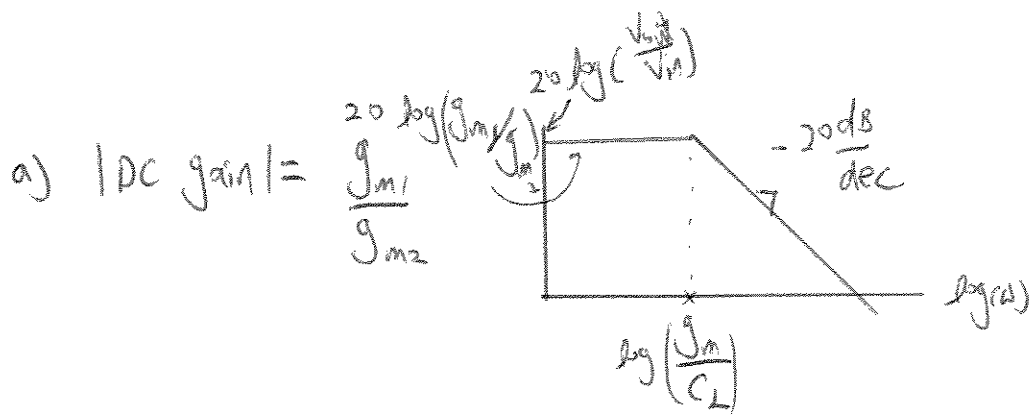


b) $|DC \text{ gain}| = g_{m1} \left(\frac{1}{g_{m2}} + \frac{R_B}{\beta + 1} \right)$

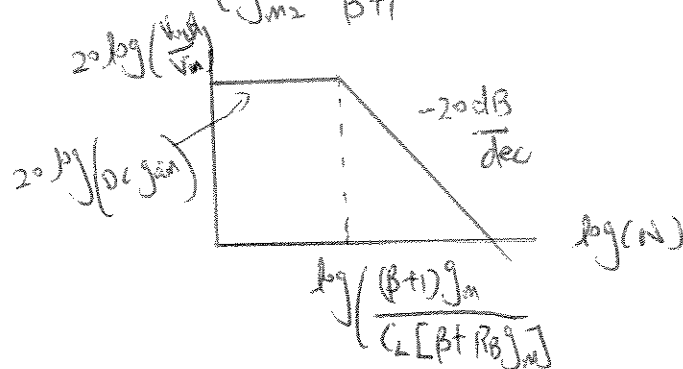


c) $|DC \text{ gain}| = g_{m1} (V_{o1}/V_{o2})$

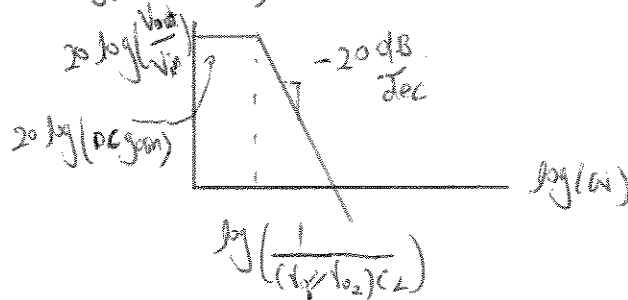

d) $|DC \text{ gain}| = g_{m1}/g_{m2}$

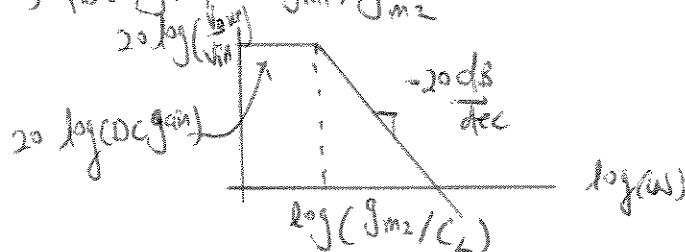

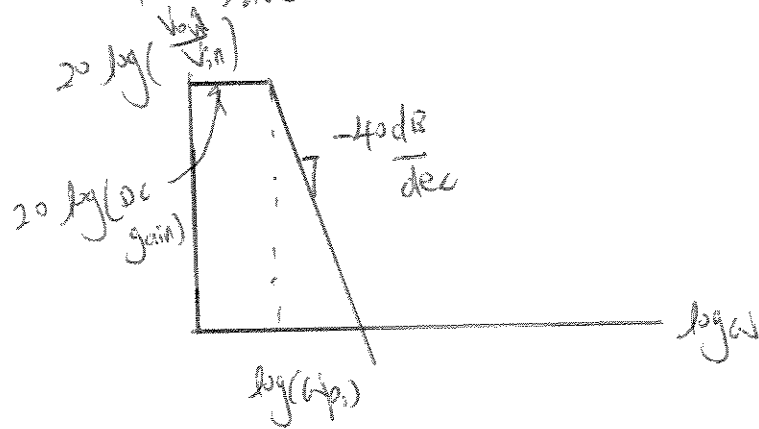
5) 2 poles at ω_{p2} , means slope is -40 dB/dec



* Assuming transfer function is in the form of

$$\frac{A}{\left(\sqrt{\left(\frac{\omega}{\omega_{p1}}\right)^2 + 1}\right)^2}$$

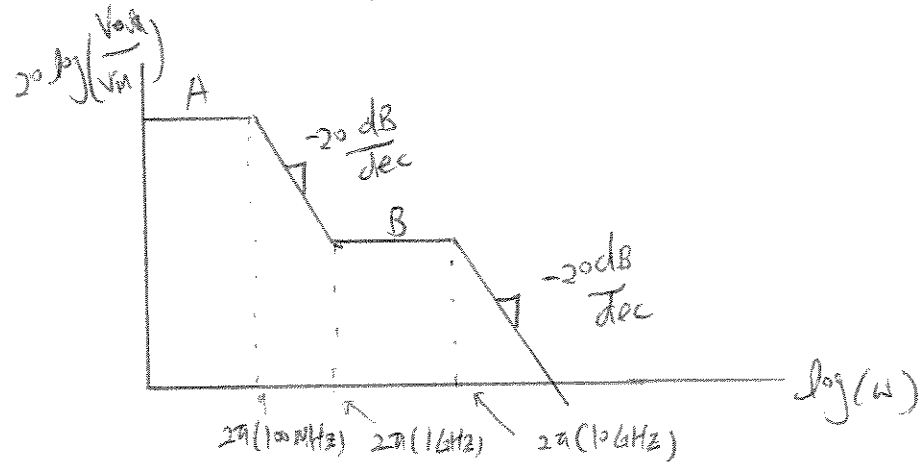6)
 Poles at 100 MHz, 10 GHz
 Zero at 1 GHz.




$$A(100 \text{ MHz}) = B(1 \text{ GHz})$$

$$B = 0.1A$$


7) Ideal Integrator: $\frac{V_{out}(s)}{V_{in}} = \frac{1}{s}$

$$\left| \frac{V_{out}(\omega)}{V_{in}} \right| = \frac{1}{\omega}$$

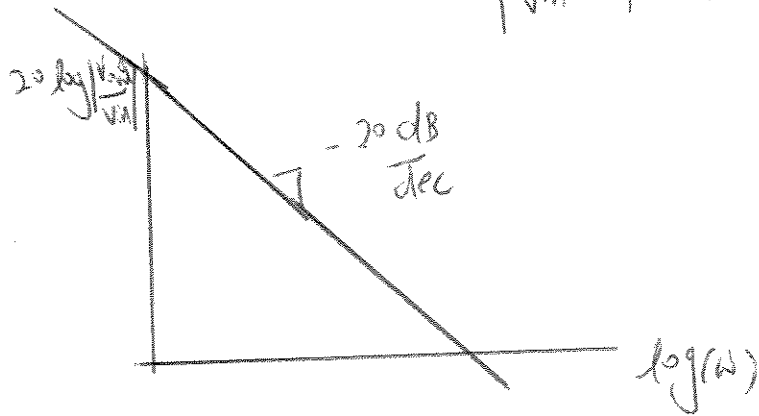


For an integrator, the gain at arbitrary low freq approaches infinity.

8) Ideal differentiator: $S = \frac{V_{out}}{V_{in}}$, $\left| \frac{V_{out}}{V_{in}}(j\omega) \right| = \omega$
 $\omega_z = 0$

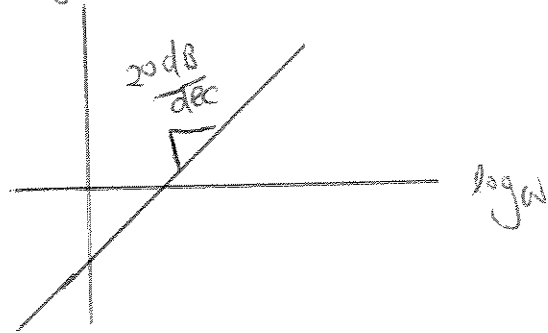

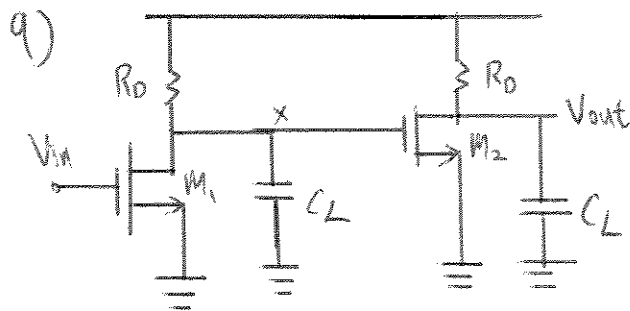For an ideal differentiator, gain at arbitrary high freq approaches infinity.





$\lambda = 0$, & neglect other caps.

DC gain: $\frac{V_x}{V_{in}} = -g_m R_D$, $\frac{V_{out}}{V_x} = -g_m R_D$

$$\frac{V_{out}}{V_{in}} = (g_m R_D)^2 \quad (\text{At DC})$$

2 poles at $\frac{1}{R_D C_L}$

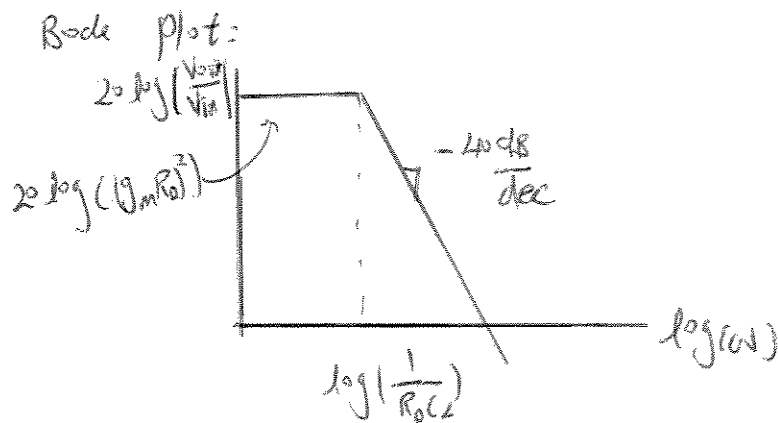

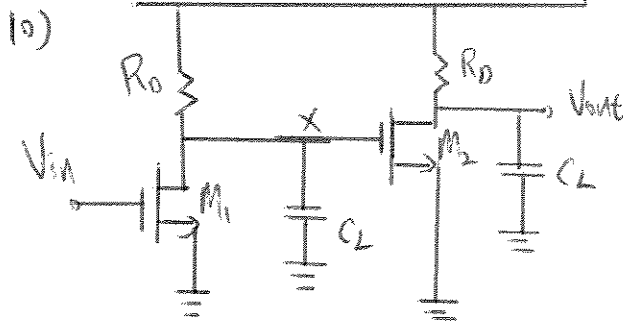

$$\frac{V_x(s)}{V_{in}} = -g_m \left(R_0 \parallel \frac{1}{C_L s} \right), \quad \frac{V_{out}(s)}{V_x} = -g_m \left(\frac{R_D}{R_D C_L s + 1} \right)$$

$$= -g_m \left(\frac{R_D}{R_D C_L s + 1} \right)$$

$$H(s) = \frac{V_x(s)}{V_{in}} \frac{V_{out}(s)}{V_x} = \left(\frac{g_m R_D}{R_D C_L s + 1} \right)^2$$

$$s \rightarrow j\omega, \quad H(j\omega) = \left(\frac{g_m R_D}{1 + R_D C_L j\omega} \right)^2$$

$$|H(j\omega)| = \frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2}$$

-3dB Bandwidth:


$$\frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} = \frac{(g_m R_D)^2}{\sqrt{2}}$$

$$\Rightarrow (R_D C_L \omega)^2 + 1 = \sqrt{2}$$

$$\Rightarrow \omega = \frac{\sqrt{\sqrt{2}-1}}{R_D C_L} = \frac{0.6436}{R_D C_L} \left(\frac{\text{rad}}{\text{s}} \right)$$

$$2\pi f = \frac{0.6436}{R_D C_L} \Rightarrow f = \frac{0.10243}{R_D C_L} \text{ (Hz)}$$

11)

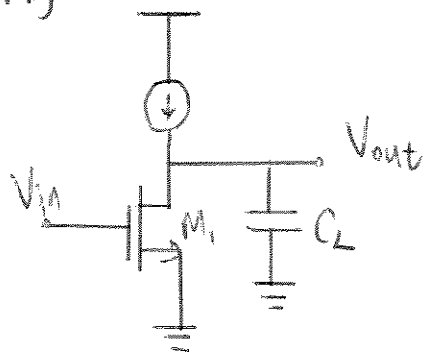

$$\lambda > 0$$

Since $\lambda > 0$, and we have an ideal current source, the impedance looking from out to ground is $r_o \parallel \frac{1}{C_L s}$


$$\text{So, } V_{out} = -g_m V_{in} \left(r_o \parallel \frac{1}{C_L s} \right)$$

$$H(s) = -g_m \left(\frac{r_o}{r_o C_L s + 1} \right), \quad |H(j\omega)| = \frac{g_m r_o}{\sqrt{(r_o C_L \omega)^2 + 1}}$$

$$\text{For } \lambda \rightarrow 0, r_o \rightarrow \infty \Rightarrow H(s) \rightarrow \frac{-g_m r_o}{r_o C_L s}$$

$H(s) = \frac{-g_m}{C_L s}$, A pole at origin, thus operating as an ideal integrator.

12)

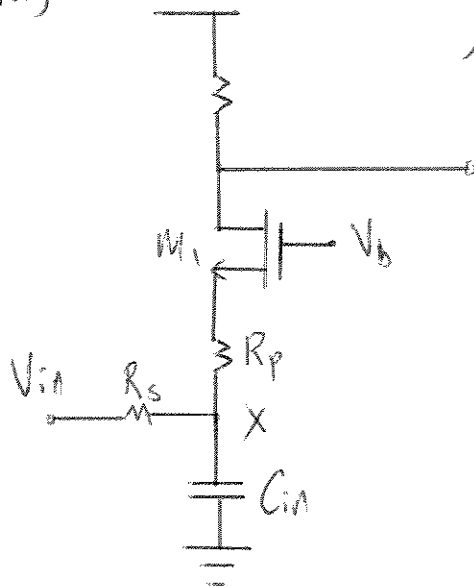


To find input pole,
let $V_{in} = 0$ and
find the equivalent
resistance and capacitance
from node X to
ground.

$$R_x = R_s \parallel \left(R_p + \frac{1}{g_{m_1}} \right), \quad C_x = C_{in}$$

$$\omega_{p.in} = \frac{1}{C_{in} \left[R_s \parallel \left(R_p + \frac{1}{g_m} \right) \right]}$$

$$\omega_{p.out} = \frac{1}{R_o C_L}$$

13)

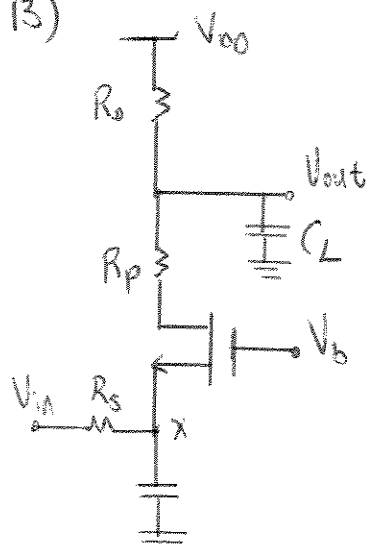

$\lambda = 0$, neglect all other caps.

$$R_x = R_s // \frac{1}{g_m}$$

$$C_x = C_{in}$$


$$R_{out} = R_D \quad (\text{Since } r_o = \infty)$$

$$C_{out} = C_L$$

$$\omega_{pin} = \frac{1}{(R_s // \frac{1}{g_m}) C_{in}}$$

$$\omega_{pout} = \frac{1}{R_D C_L}$$


14)

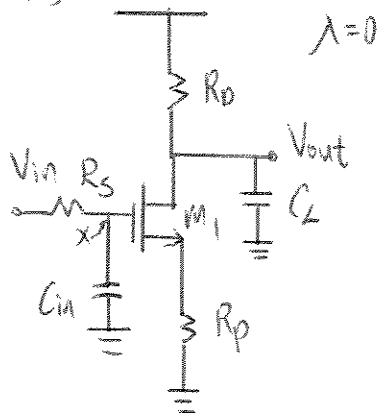

$$R_x = R_s, \quad R_{out} = R_0$$

$$C_x = C_{in}, \quad C_{out} = C_L$$
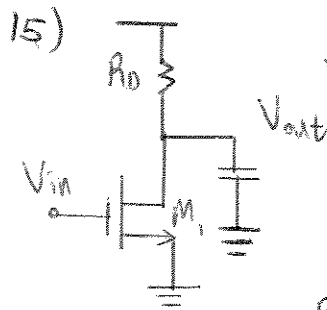
$$\omega_{pin} = \frac{1}{R_s C_{in}}, \quad \omega_{pout} = \frac{1}{R_0 C_L}$$



DC Gain: $g_m R_D = \frac{2 I_D R_D}{V_{eff}}$

Where $V_{eff} = V_{GS} - V_{th}$

Band Width: $\frac{1}{R_D C_L}$

Power Consumption: $V_{DD} I_D$


F.O.M. (11.5) = $\frac{\text{Gain} \times \text{Band Width}}{\text{Power Consumption}}$

$$= \frac{\left(\frac{2 I_D R_D}{V_{eff}} \right) \left(\frac{1}{R_D C_L} \right)}{V_{DD} I_D}$$

$$= \frac{2}{V_{eff} V_{DD} C_L}$$


For practical design, $V_{eff} > V_t$, thus bipolar has a larger F.O.M. than MOS.

16)

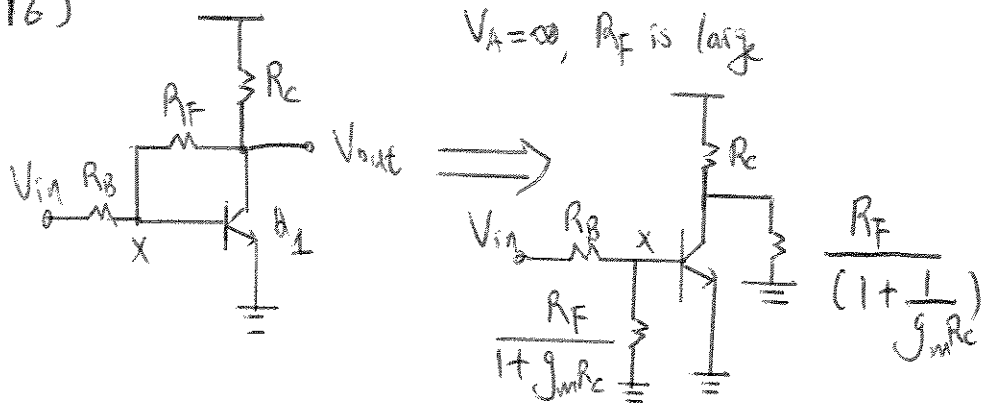

$$R_x = R_B \parallel \left(\frac{R_F}{1 + g_m R_C} \right), \quad R_{out} = R_C \parallel \left(\frac{R_F}{1 + \frac{1}{g_m R_C}} \right)$$

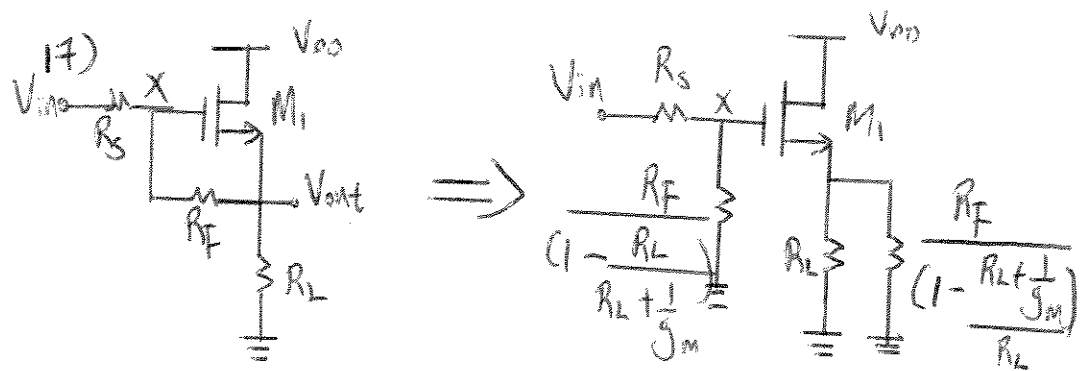
$$\frac{V_{out}}{V_{in}} = \frac{-R_{out}}{\frac{1}{g_m} + \frac{R_x}{\beta + 1}} = \frac{-R_C \parallel \left(\frac{R_F}{1 + 1/g_m R_C} \right)}{\frac{1}{g_m} + \frac{R_B \parallel (R_F / (1 + g_m R_C))}{\beta + 1}}$$



$$R_{out}: R_L \parallel \frac{R_F}{1 - \frac{R_L + \frac{1}{g_m}}{R_L}} = R_L \parallel \frac{R_F}{-\frac{1}{g_m R_L}}$$

$$R_{out}: R_L \parallel -R_F g_m R_L \quad (\text{note that } R_{out} \text{ may be negative})$$

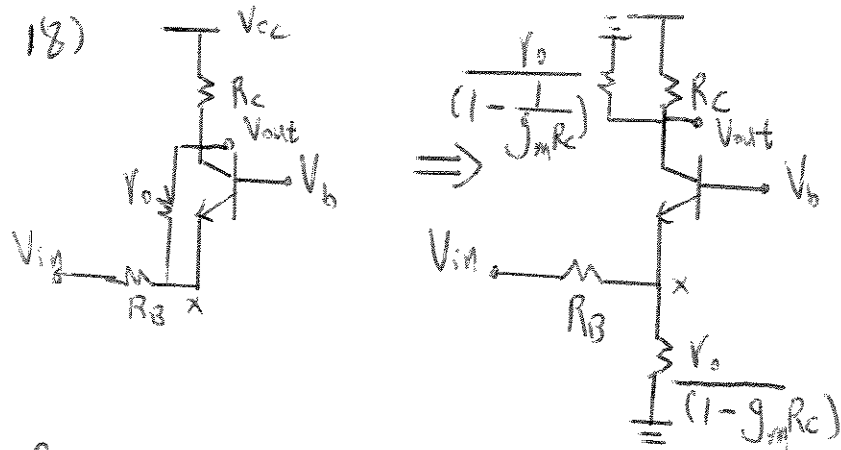
$$\frac{V_{out}}{V_{in}} = \frac{R_L \parallel -R_F g_m R_L}{R_L \parallel (-R_F R_L g_m) + \frac{1}{g_m}}$$




$$R_{out} = R_C \parallel \left(\frac{V_o}{1 - \frac{1}{g_m R_C}} \right)$$

$$R_x = R_B \parallel \left(\frac{V_o}{1 - g_m R_C} \right)$$
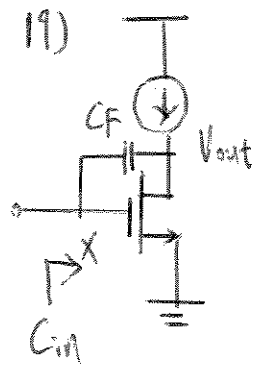
$$\frac{V_{out}}{V_{in}} = \frac{R_{out}}{R_x + \frac{1}{g_m}} = \frac{R_C \parallel \left(\frac{V_o}{1 - \frac{1}{g_m R_C}} \right)}{R_B \parallel \left(\frac{V_o}{1 - g_m R_C} \right) + \frac{1}{g_m}}$$



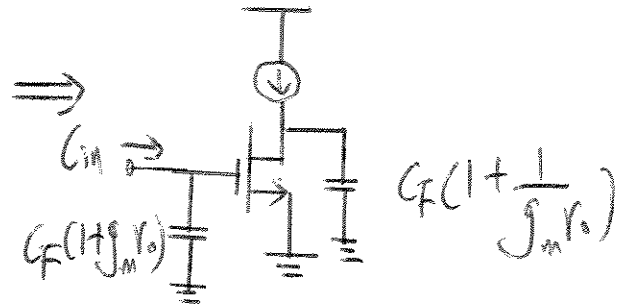
$$\lambda > 0, \text{ DC gain} = -g_m r_o$$



$$C_{in} = C_F(1 + g_m r_o), \text{ neglecting other caps.}$$

$$\text{As } \lambda \rightarrow 0, r_o \rightarrow \infty, \text{ DC gain} \rightarrow \infty,$$

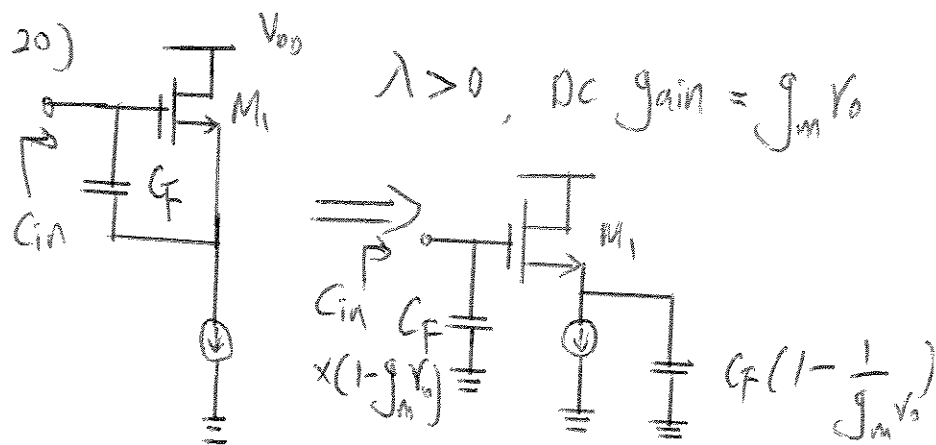
$$C_{in} \rightarrow \infty, \text{ this bandwidth will } \rightarrow 0.$$



$$C_{in} = C_F (1 - g_m r_o)$$


As $\lambda \rightarrow 0$, $r_o \rightarrow \infty$, $g_m r_o \rightarrow \infty$, $C_{in} = -\infty$

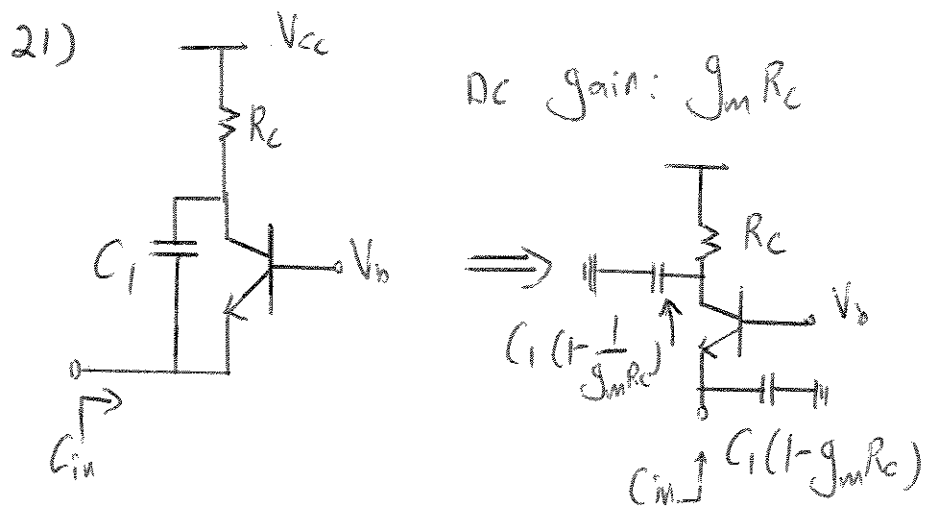When $C \rightarrow$ negative in value, we have inductive activity. So right here, we have an effective infinite inductor.




$$C_{in} = C_1 (1 - g_m R_c)$$

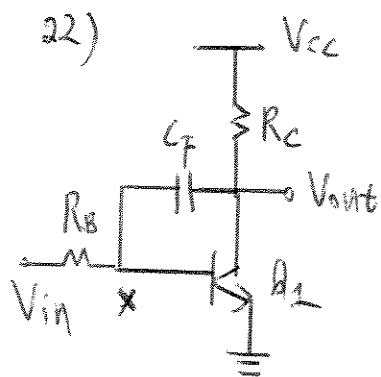If $g_m R_c$ is designed to be larger than 1, as it normally would, we will have inductive action.



DC gain (from x to out):
 $-g_m R_c$

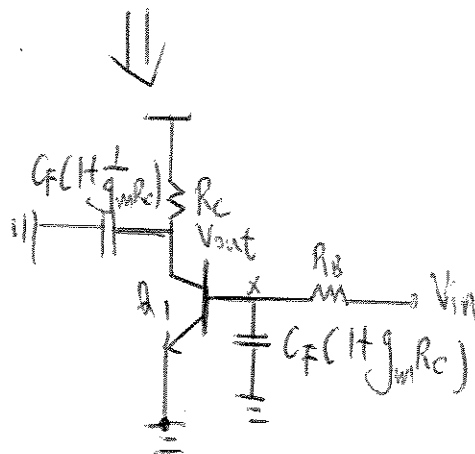

$$C_{in} = C_F (1 + g_m R_c)$$

$$R_{in} = R_B \parallel r_{\pi}$$

$$C_{out} = C_F (1 + \frac{1}{g_m R_c})$$


$$R_{out} = R_c$$

$$\omega_{p1} = \frac{1}{R_B \parallel r_{\pi} [C_F (1 + g_m R_c)]}$$


$$\omega_{pout} = \frac{1}{R_c C_F (1 + \frac{1}{g_m R_c})} \approx \frac{1}{R_c C_F}$$

$$(\text{if } g_m R_c \gg 1)$$

23)

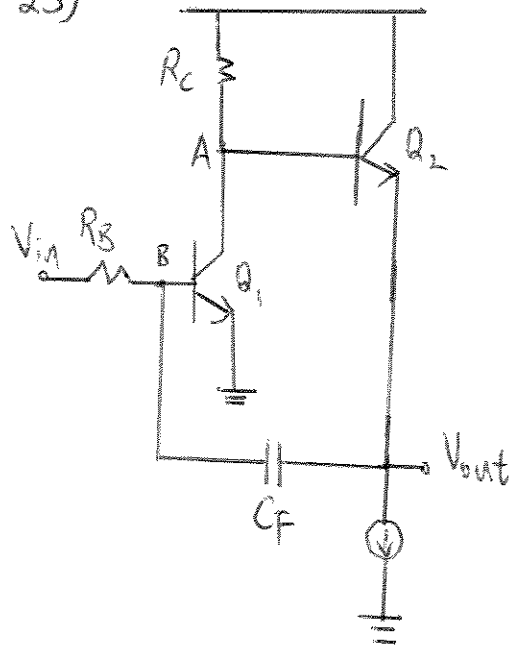

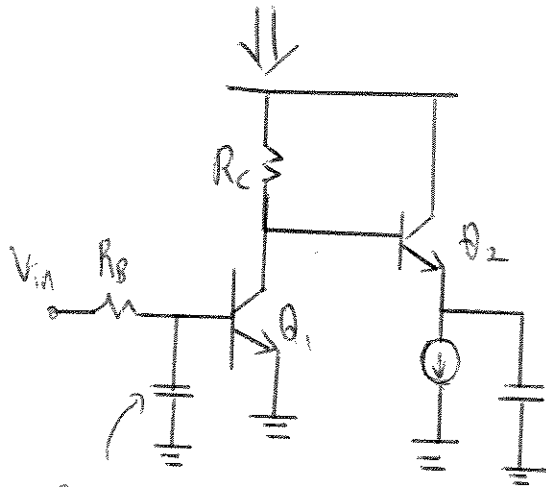The gain from B to A is $-g_m R_C$, from A to out is 1 (since we have an ideal current source). So the gain from B to out is $-g_m R_C$.



$$R_{in} = R_B \parallel r_{\pi}$$

$$C_{in} = C_F (1 + g_m R_C)$$


$$R_{out} = \frac{1}{g_m} + \frac{R_C}{\beta + 1}$$

$$C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$C_{out} = C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$\omega_{pin} = \frac{1}{R_B \parallel r_{\pi} [C_F (1 + g_m R_C)]}$$

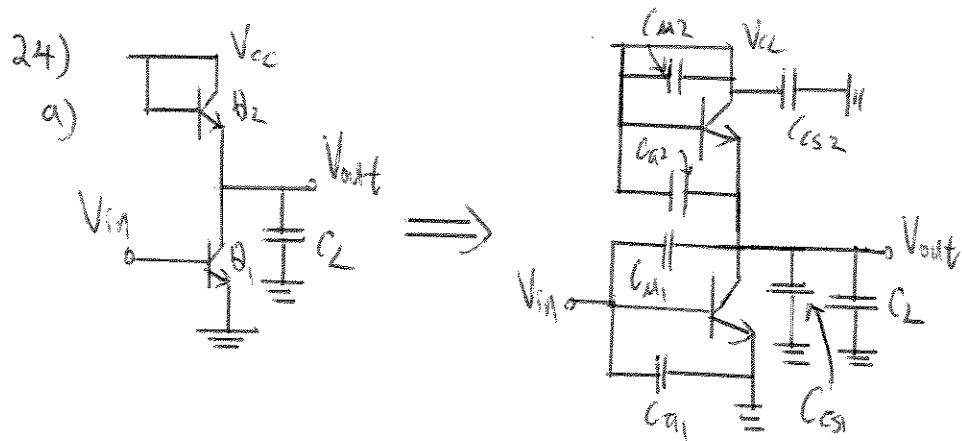
$$\omega_{pout} = \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F \left(1 + \frac{1}{g_m R_C}\right)} \approx \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F}, \quad (g_m R_C \gg 1)$$



$C_{\pi 2}$, C_{s1} , C_L are in parallel

$C_{\mu 2}$, C_{s2} are grounded on both ends.

(and technically in parallel as well)


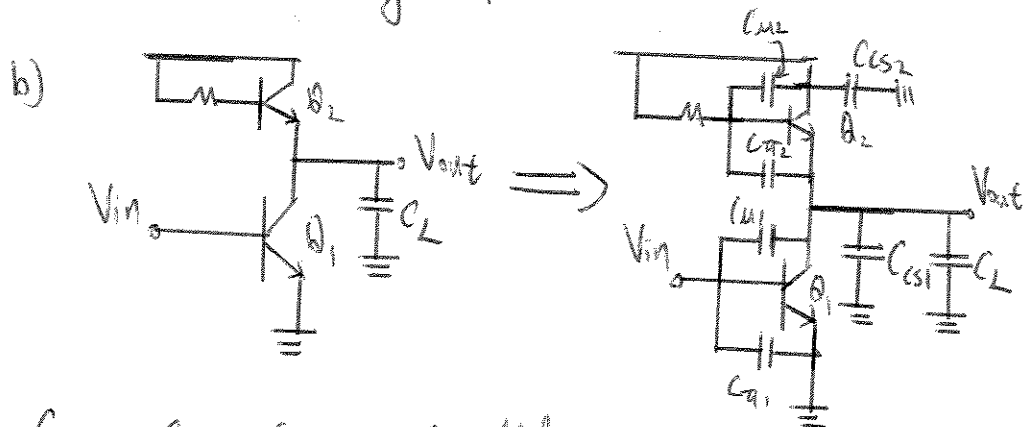


C_{s1} , C_L are in parallel


C_{s2} is grounded on both ends

24)


c)

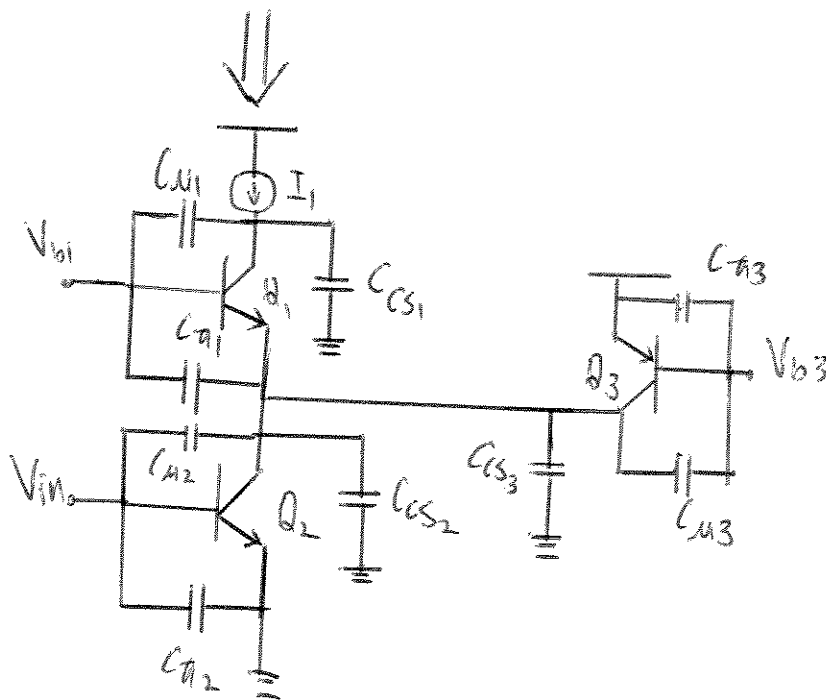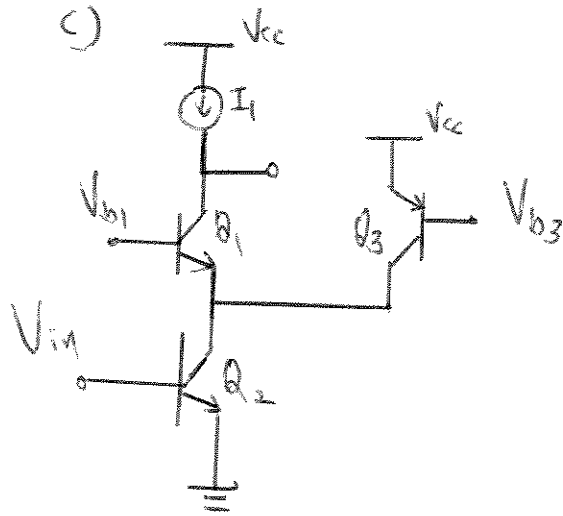

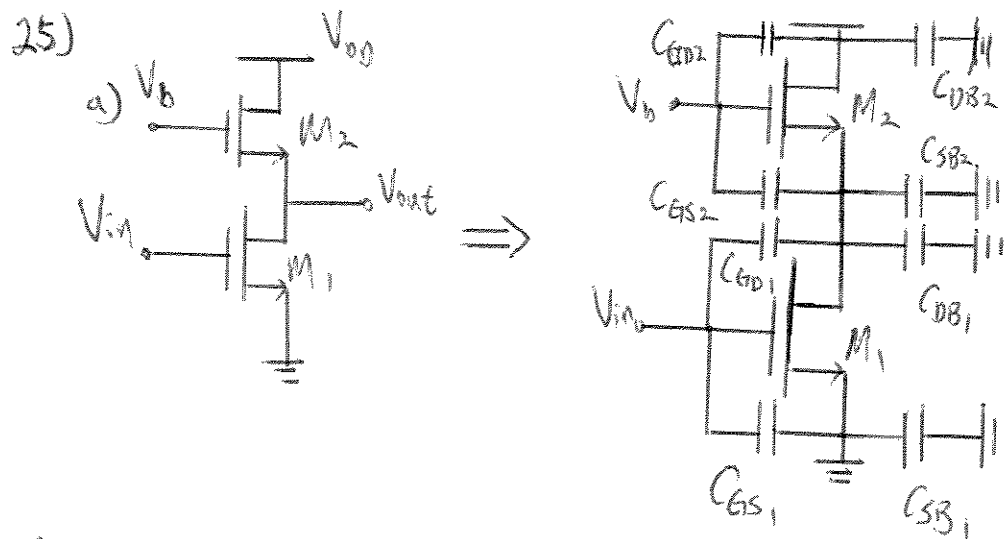$C_{\mu 1}$, C_{cs2} , C_{cs3} , $C_{\mu 3}$ are in parallel
 $C_{\mu 1}$, C_{cs1} are also in parallel
 $C_{\mu 3}$ is grounded on both ends




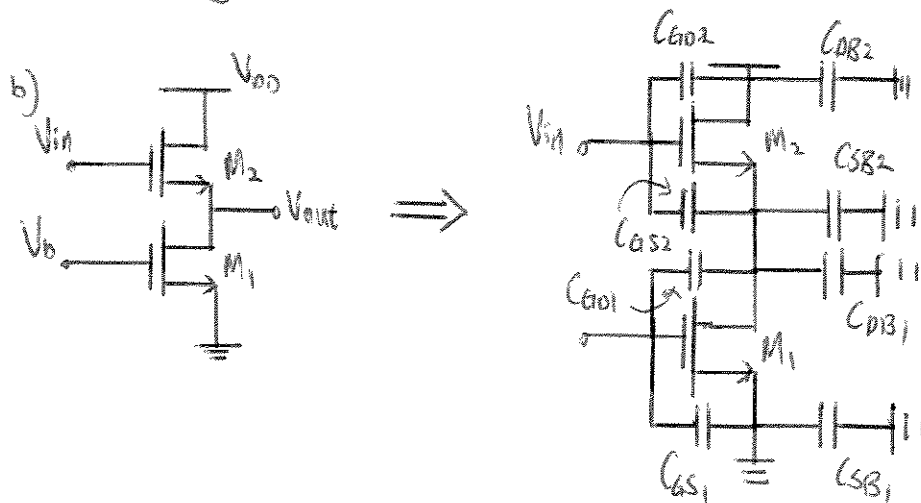C_{GS2} , C_{SB2} , C_{DB1} are in parallel
 C_{GD2} , C_{DB2} are in parallel and grounded on both ends
 C_{SB1} is grounded on both ends.



C_{GD1} , C_{DB1} , C_{SB2} are in parallel
 C_{GS1} , C_{SB1} are in parallel and grounded on both ends
 C_{DB2} is grounded on both ends.

25)

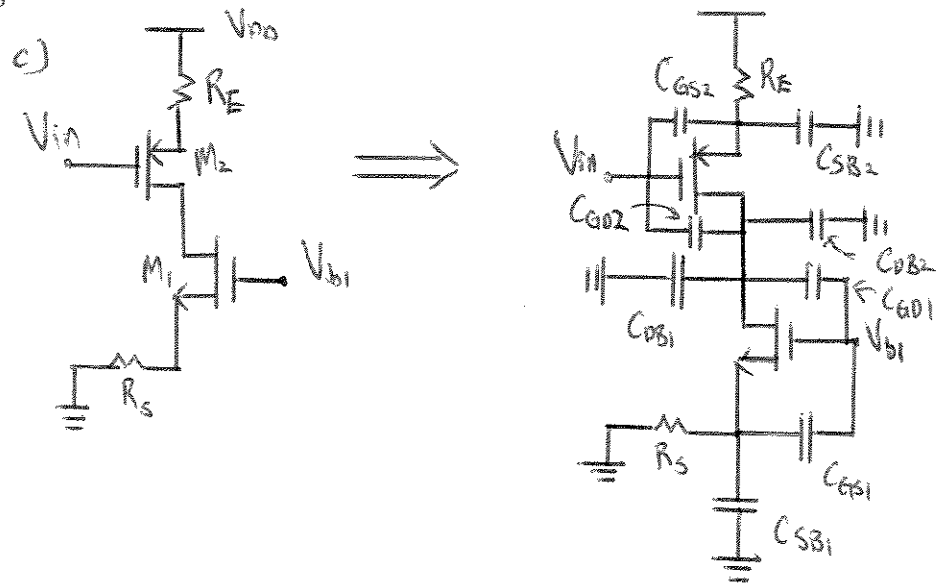


C_{DB2} , C_{G01} , C_{DB1} , are in parallel

C_{SB1} , C_{GS1} are also in parallel.

26)

Bipolar

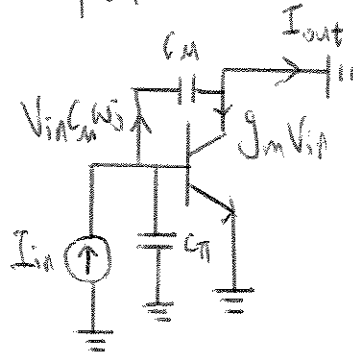


$$V_{in} = (I_{in}) \left(\frac{1}{[C_{\mu} + C_{\pi}] \omega j} \right) \quad \text{(Assuming we are at freq, and } V_A \text{ can be neglected)}$$

$$I_{out} = V_{in} C_{\mu} \omega j - g_m I_{in} \left(\frac{1}{[C_{\mu} + C_{\pi}] \omega j} \right)$$

$$\frac{I_{out}}{I_{in}} = \frac{C_{\mu} \omega j - g_m}{[C_{\mu} + C_{\pi}] \omega j} \Rightarrow \left| \frac{I_{out}}{I_{in}} \right| = \frac{\sqrt{(g_m)^2 + (C_{\mu} \omega)^2}}{[C_{\mu} + C_{\pi}] \omega_T} = 1$$
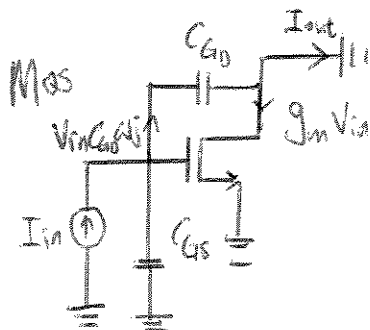
$$\omega_T^2 = \frac{g_m^2}{2 C_{\mu} C_{\pi} + C_{\pi}^2} \Rightarrow \omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2 C_{\mu} C_{\pi} + C_{\pi}^2}}$$



Similarly for MOS, with C_{μ} and C_{π} replaced by C_{gd} and C_{gs} respectively.

$$\omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2 C_{gd} C_{gs} + C_{gs}^2}}$$


27)

$$C_{\pi} = g_m \tau_F + C_{je}$$

$$2\pi f_T = \frac{g_m}{C_{\pi}} = \frac{g_m}{g_m \tau_F + C_{je}}$$

Assume C_{je} to be independent
of I_c .
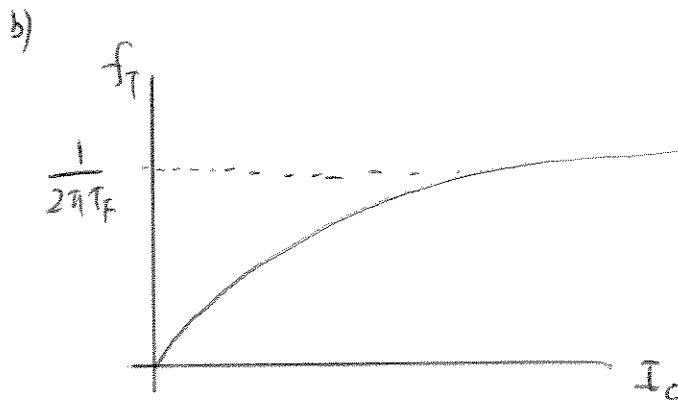
$$a) \quad 2\pi f_T = \frac{\frac{I_c}{V_T}}{\frac{I_c}{V_T} \tau_F + C_{je}} \Rightarrow f_T = \frac{I_c}{2\pi (I_c \tau_F + V_T C_{je})}$$



$$\text{As } I_c \rightarrow \infty, f_T \rightarrow \frac{1}{2\pi\tau_F}$$

28)

$$C_{gs} \approx \left(\frac{2}{3}\right) WL C_{ox}$$

$$2\pi f_T = \frac{g_m}{C_{gs}} = \frac{\frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})}{\frac{2}{3} WL C_{ox}}$$

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

29)

$$2\pi f_T = \frac{3}{2} \frac{2I_D}{WLC_{ox}} \frac{1}{(V_{GS} - V_{TH})}$$

Apparently, f_T decreases with the overdrive.

However, when we look closely, I_D is

actually proportional to $(V_{GS} - V_{TH})^2$ (In

saturation), so f_T is proportional to

$(V_{GS} - V_{TH})$.


30)

a) As $W \uparrow$, $(V_{GS} - V_{TH})$ has to \downarrow by

$\frac{1}{\sqrt{W}}$ in order to maintain I_0 constant

using equation $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \frac{1}{\sqrt{W}}$$

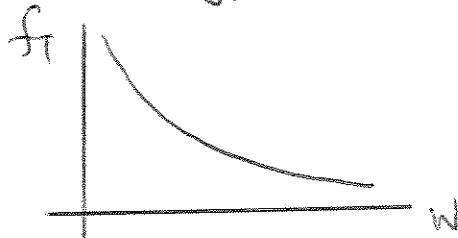

b) $I_0 \uparrow$, W constant it means $V_{GS} - V_{TH} \uparrow$

with $\sqrt{I_0}$. Using equation $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \sqrt{I_0}$$

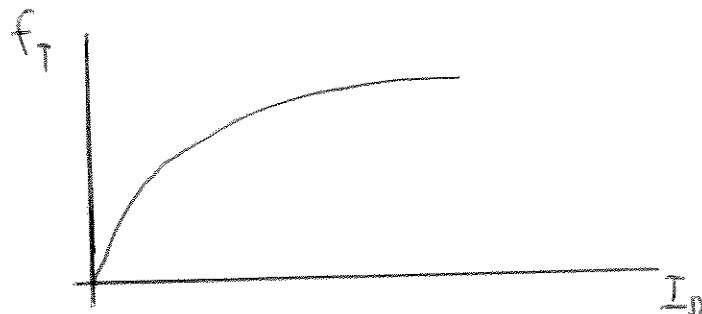

31)


Using equation $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$

a) $2\pi f_T \propto (V_{GS} - V_{TH})$

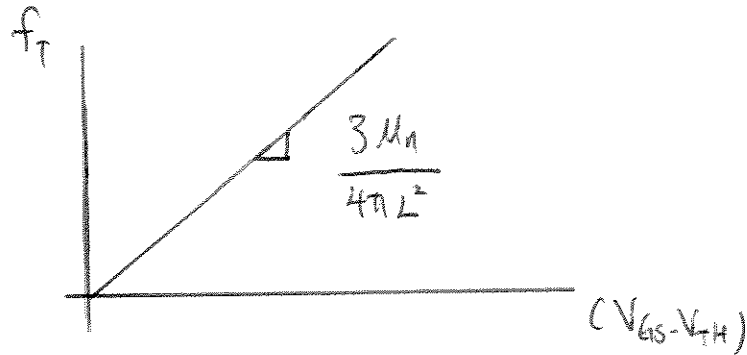

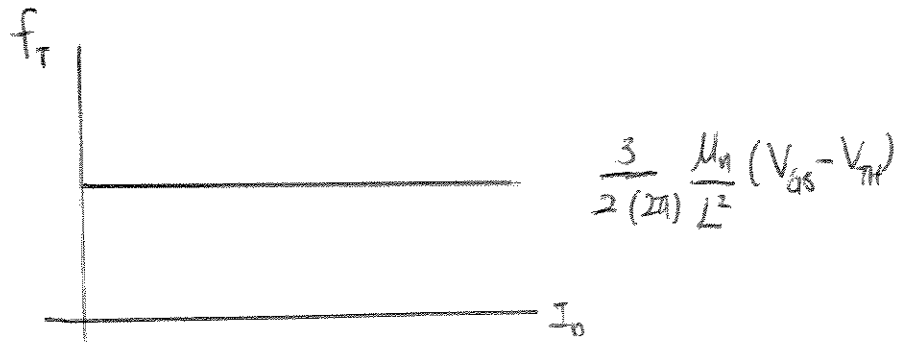b) Using equation $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$2\pi f_T = \text{constant for all } I_D$



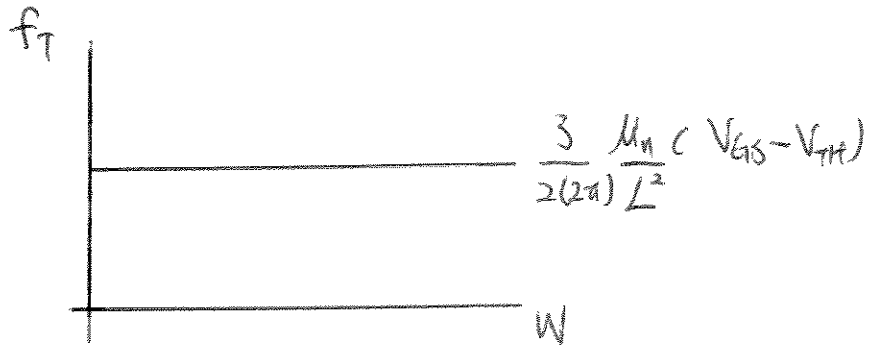32) a)


Using equation $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$

We know that $2\pi f_T$ is constant for all W .



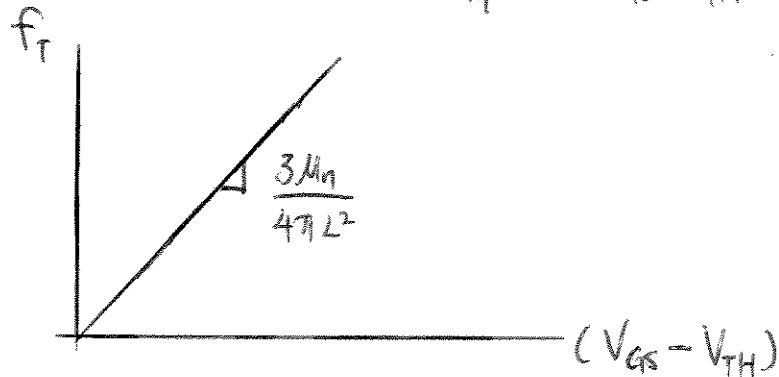b) Using equation $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$,

We know that $2\pi f_T \propto (V_{GS} - V_{TH})$.



33)

$$a) I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})^2$$

As $L \uparrow$, to maintain the same current and overdrive voltage, $W \uparrow$ as well.

So W also $2\times$.

$$b) \text{ Since } 2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH}), \text{ and}$$

L $2\times$ while $(V_{GS} - V_{TH})$ is constant,

$$f_T \downarrow \text{ by } \frac{3}{4} \text{ or } f_{T_{\text{new}}} = \frac{1}{4} f_{\text{old}}.$$

34)

$$a) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$

Constant I_D and $W \uparrow$ (L constant)

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T_{\text{new}}} = \frac{f_{T, \text{old}}}{2}$$

$$b) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$


Constant W and $I_D \downarrow$ (L constant)

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T_{\text{new}}} = \frac{f_{T, \text{old}}}{2}$$

35)


Bipolar CE Stage

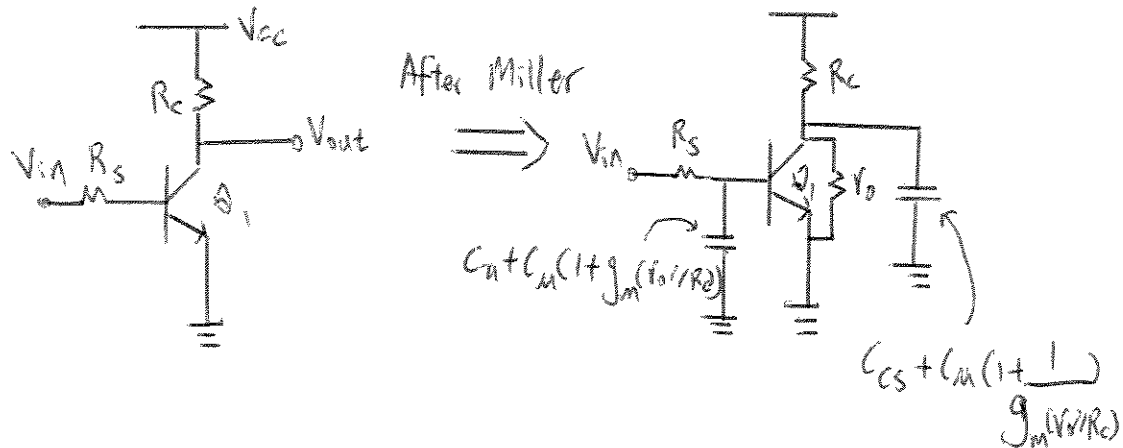

$$\omega_{pin} = \frac{1}{(R_s \parallel R_{in}) [C_{\pi} + C_{\mu}(1 + g_m(R_o \parallel R_c))]}$$

$$\omega_{pout} = \frac{1}{(R_o \parallel R_{out}) [C_{cs} + C_{\mu}(1 + 1/g_m(R_o \parallel R_c))]}$$


MOS CS Stage

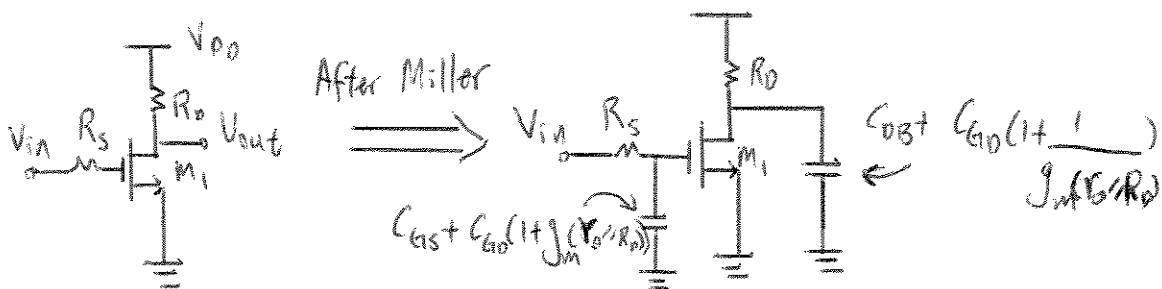

$$\omega_{pin} = \frac{1}{R_s [C_{gs} + C_{gd}(1 + g_m(R_o \parallel R_D))]}$$

$$\omega_{pout} = \frac{1}{(R_o \parallel R_{out}) [C_{DB} + C_{gd}(1 + 1/g_m(R_o \parallel R_D))]}$$

36)

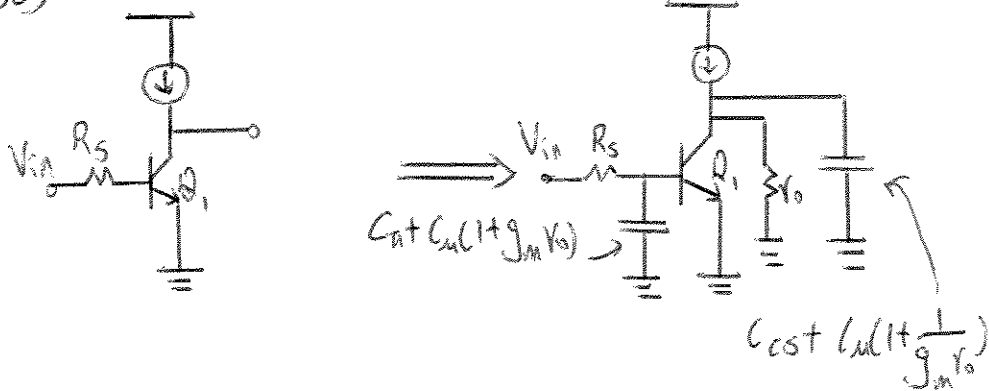


$$\omega_{pin} = \frac{1}{(R_s \parallel r_{\pi}) [C_{pi} + C_i(1 + g_m R_o)]}$$

$$\omega_{pout} = \frac{1}{R_o [C_{cs} + C_i(1 + 1/g_m R_o)]}$$

$$H(s) = \frac{DC \text{ gain}}{(1 + \frac{s}{\omega_{pin}})(1 + \frac{s}{\omega_{pout}})}$$
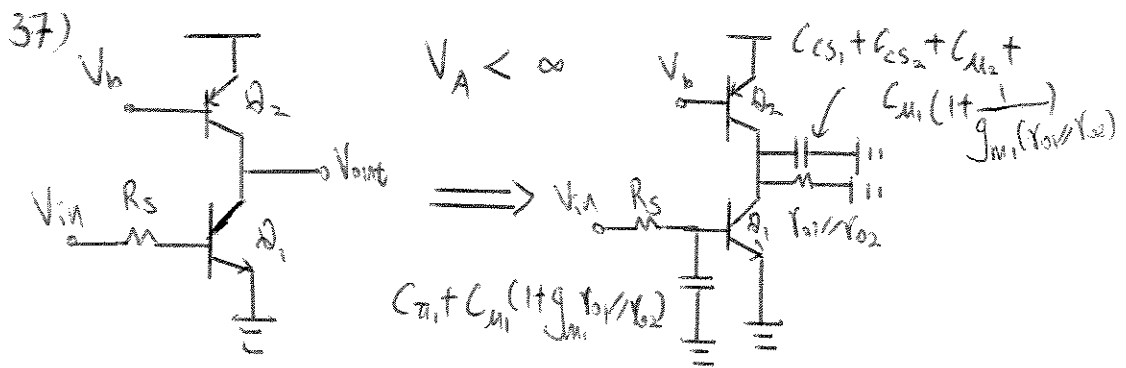
$$H(s) = \frac{g_m R_o (r_{\pi} / (r_{\pi} + R_s))}{(1 + \frac{s}{1 / (R_s \parallel r_{\pi}) [C_{pi} + C_i(1 + g_m R_o)]})(1 + \frac{s}{1 / (R_o [C_{cs} + C_i(1 + \frac{1}{g_m R_o})])})}$$



$$A_{pin} = \frac{1}{(R_s // r_{\pi_1}) [C_{\pi_1} + C_M (1 + g_{m_1} (r_{o_1} // r_{o_2}))]}$$


$$A_{pout} = \frac{1}{(r_{o_1} // r_{o_2}) [C_{CS_1} + C_{CS_2} + C_{M_2} + C_{M_1} (1 + 1/(g_{m_1} r_{o_1} // r_{o_2}))]}$$

$$g_{m_1} r_{o_1} \gg 1$$

$$H(s) = \frac{g_{m_1} (r_{o_1} // r_{o_2}) (r_{\pi_1} // r_{\pi_1} + R_s)}{(1 + R_s [C_{\pi_1} + C_M (g_{m_1} (r_{o_1} // r_{o_2})) s]) (1 + (r_{o_1} // r_{o_2}) [C_{CS_1} + C_{CS_2} + C_{M_2} + C_{M_1}] s)}$$


38)

a)

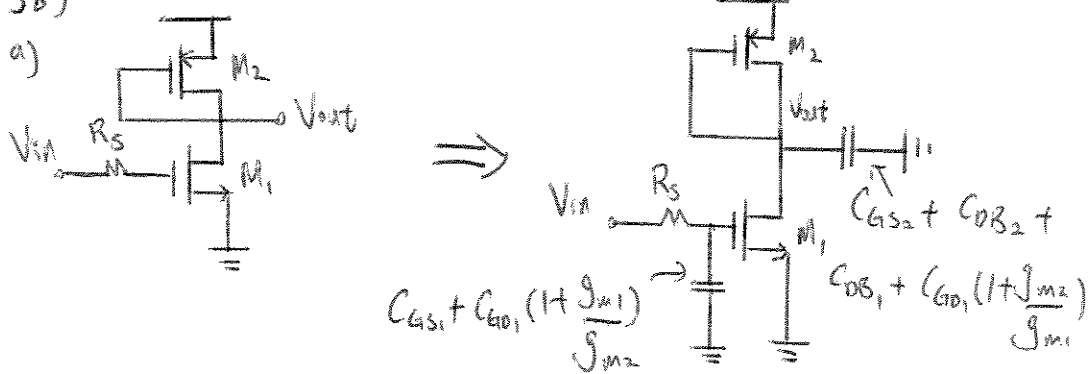

$$DC \text{ gain} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$
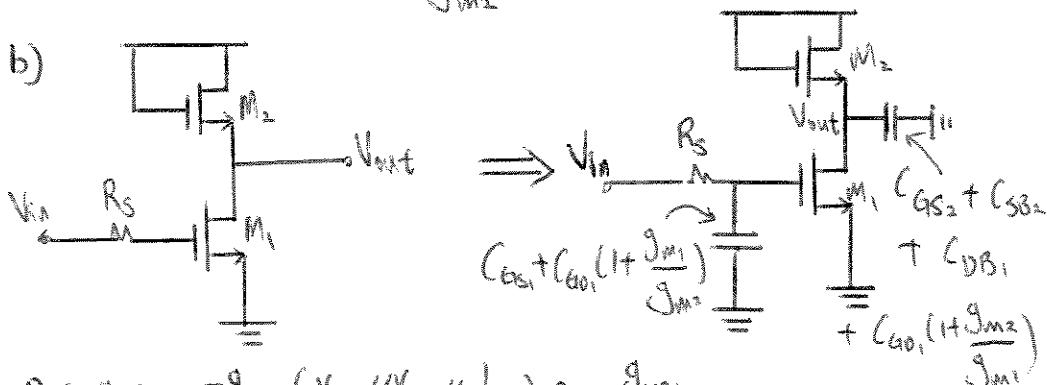
$$\omega_{pin} = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))} \quad \omega_{pout} = \frac{g_{m2}}{(C_{GS2} + C_{DB2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}}))}$$




$$DC \text{ gain} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{pin} = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{pout} = \frac{g_{m2}}{C_{SB2} + C_{GS2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}})}$$

38)

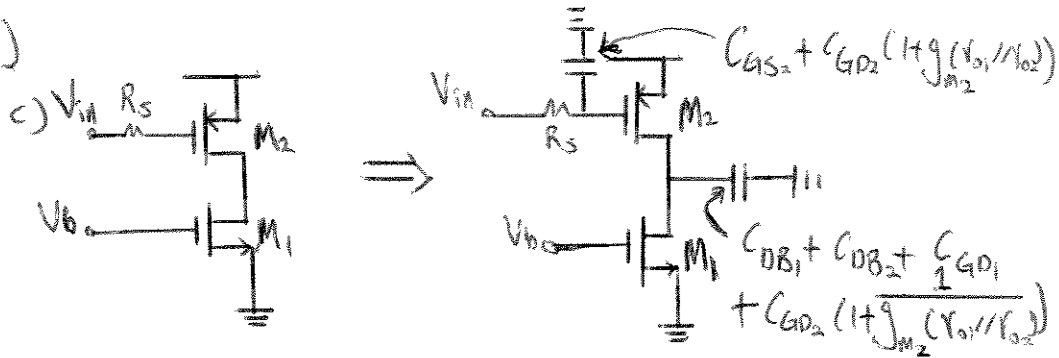

DC gain: $-g_{m2} (r_{o1} || r_{o2})$


$$\omega_{pin} = \frac{1}{R_s (C_{gs2} + C_{gd2} (1 + g_{m2} (r_{o1} || r_{o2})))}$$

$$\omega_{pout} = \frac{1}{(r_{o1} || r_{o2}) [C_{db1} + C_{db2} + C_{gd1} + C_{gd2} (1 + \frac{1}{g_{m2} (r_{o1} || r_{o2})})]}$$

$$\omega_{pout} \approx \frac{1}{(r_{o1} || r_{o2}) [C_{db1} + C_{db2} + C_{gd1} + C_{gd2}]}$$

Since $g_{m2} (r_{o1} || r_{o2}) \gg 1$

39)

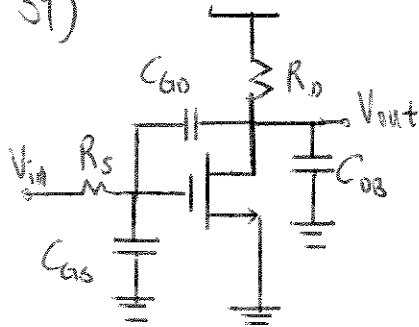


$$R_S = 200\Omega \quad C_{GS} = 50\text{fF}$$

$$R_D = 1\text{K}\Omega \quad C_{GD} = 10\text{fF}$$

$$I_D = 1\text{mA} \quad C_{DB} = 15\text{fF}$$

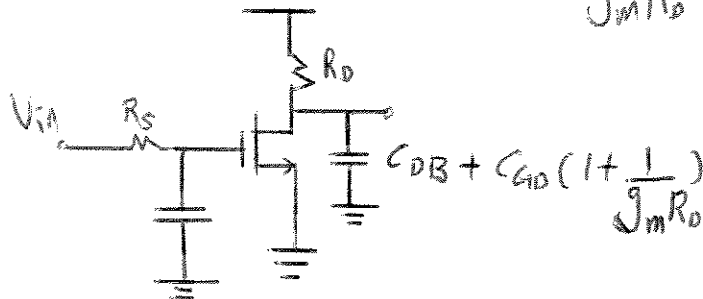a) Miller's approximation:

$$-g_m R_D = -\frac{(1)(2)(1)}{(0.2)} = -10$$



$$C_{GS} + (1 + g_m R_D) C_{GD}$$

$$\omega_{pin} = \frac{1}{R_S (C_{GS} + (1 + g_m R_D) C_{GD})} = \frac{1}{200 (50\text{fF} + (11)(10\text{fF}))} = 31.25\text{GHz}$$

$$\omega_{pout} = \frac{1}{R_D (C_{DB} + (1 + \frac{1}{10}) C_{GD})} = \frac{1}{1000 (15\text{fF} + (1.1)10\text{fF})} = 38.46\text{GHz}$$

39)

b) Equation
$$\frac{V_{out}(s)}{V_{thetv}} = \frac{(C_{xy}s - g_m)R_L}{as^2 + bs + 1}$$

$$a = R_{thetv} R_L (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out})$$

$$R_{thetv} = R_s, C_{in} = C_{gs}, C_{out} = C_{ob}, R_L = R_o, C_{xy} = C_{gd}$$

$$a = (200 \times 1000) [(50 \times 10^{-15})(10 \times 10^{-15}) + (15 \times 10^{-15})(10 \times 10^{-15}) + (50 \times 10^{-15})(15 \times 10^{-15})] = 2.8 \times 10^{-22}$$

$$b = (1 + g_m R_L) C_{xy} R_{thetv} + R_{thetv} C_{in} + R_L (C_{xy} + C_{out})$$

$$b = (1 + 10)(10 \times 10^{-15})(200) + (200)(50 \times 10^{-15}) + (1000)(10 \times 10^{-15}) + 1000(15 \times 10^{-15})$$

$$b = 5.7 \times 10^{-11}$$

$$\text{So denominator} = (2.8 \times 10^{-22} s^2 + 5.7 \times 10^{-11} s + 1)$$

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s = -1.93909 \times 10^{10}, -1.84181 \times 10^{11}$$

$$\omega_{p1} = 19.39 \text{ GHz}, \omega_{p2} = 184.2 \text{ GHz}$$

Which one is ω_{pin} , and which one is ω_{pout} ?

This can be seen from inspection, at output and high frequency C_{gd} starts to become a short and thus the output resistance collapses to $1/g_m$, and pushes the output pole out. Whereas at the input the pole location does not change too much because R_s is small and C_{gs} is large.

Therefore, we conclude that when solving the transfer function directly, the ω_{pin} is 19.39 GHz (on the same order as

39)

- b). that obtained from Miller's approximation), while ω_{pout} is pushed out significantly, 184.2 GHz (when compared to that obtained from Miller's approximation).

Miller Approximation

$$\omega_{\text{pin}} = 31.25 \text{ GHz}$$


$$\omega_{\text{pout}} = 38.46 \text{ GHz}$$

Transfer Function


$$\omega_{\text{pin}} = 19.39 \text{ GHz}$$

$$\omega_{\text{pout}} = 184.2 \text{ GHz}$$

40)

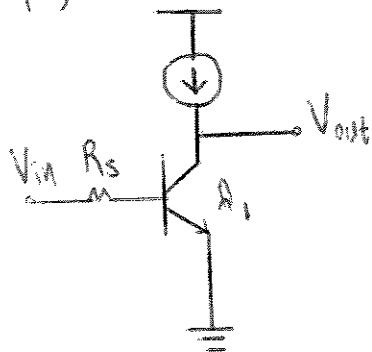

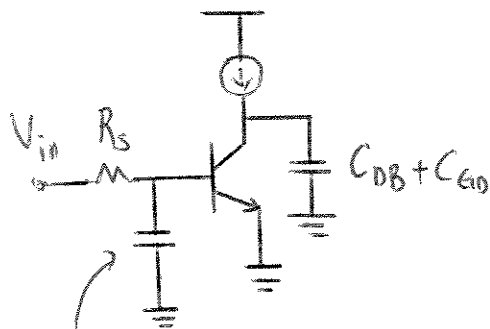a) Miller's Approximation: DC gain: $-\infty$



$C_{GS} + \infty$

$$\omega_{pin} = \frac{1}{R_S(\infty)} = 0, \quad \omega_{part} = \frac{1}{\infty(C_{DB} + C_{GD})} = 0$$

b) Transfer Function:

$$\frac{V_{out}}{V_{thev}}(s) = \frac{(C_{xy}s - g_m)R_L}{as^2 + bs + 1}$$

$$a = R_{Thev}R_L(C_{in}C_{xy} + C_{out}C_{xy} + C_{in}C_{out})$$

$$b = (1 + g_mR_L)C_{xy}R_{Thev} + R_{Thev}C_{in} + R_L(C_{xy} + C_{out})$$

40)

b) $R_L \rightarrow \infty$

$$\frac{V_{out}}{V_{thv}} = \frac{C_{xy} S - g_m}{S [R_{thv} (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}) S + g_m C_{xy} R_{thv} + (C_{xy} + C_{out})]}$$

So $\omega_{p1} = 0$

$$\omega_{p2} = \frac{(g_m C_{xy} R_{thv} + (C_{xy} + C_{out}))}{R_{thv} [C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}]}$$

$$\omega_{p2} = \frac{g_m C_u R_S / R_n + C_u + C_{cs}}{R_S / R_n [C_n C_u + C_{cs} C_u + C_n C_{cs}]}$$

$\omega_{p1} = \omega_{pin}, \quad \omega_{p2} = \omega_{pout}.$

Miller:

$\omega_{pin} = 0, \quad \omega_{pout} = 0$

Again, the output pole predicted by the transfer function is pushed out, and the input poles are similar. (In fact, they are the same this time.)

This shows one of the short-comings of Miller's approximation.

41) Dominant - Pole approximation:

$$\omega_{p1} = \frac{1}{(1 + g_m R_L) C_{xy} R_{Ther} + R_{Ther} C_{in} + R_L (C_{xy} + C_{out})}$$

$$\omega_{p1} = 0 \quad (\text{Since } R_L = \infty)$$

$$\omega_{p2} = \frac{(1 + g_m R_L) C_{xy} R_{Ther} + R_{Ther} C_{in} + R_L (C_{xy} + C_{out})}{R_{Ther} R_L (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out})}$$


Since $R_L = \infty$

$$\omega_{p2} = \frac{g_m C_{xy} R_{Ther} + C_{xy} + C_{out}}{R_{Ther} (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out})}$$

$$\omega_{p2} = \frac{g_m C_M R_S' R_\pi + C_M + C_{CS}}{R_S (C_\pi C_M + C_{CS} C_M + C_\pi C_{CS})}$$

Dominant - Pole approximation gives the same result as the transfer function method.

42)

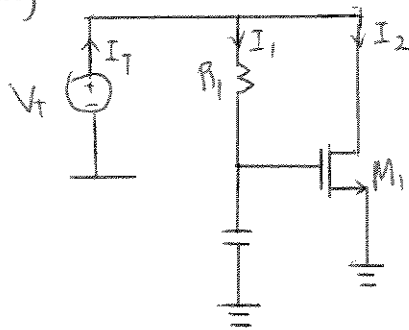

$\lambda=0$, and neglect other capacitances.

$$I_T = I_1 + I_2$$

$$I_1 = \frac{V_T}{(R_1 + \frac{1}{C_1 s})}, \quad I_2 = \frac{g_{m1} V_T}{C_1 R_1 s + 1}$$


$$I_T = \frac{C_1 s V_T}{C_1 R_1 s + 1} + \frac{g_{m1} V_T}{C_1 R_1 s + 1} \Rightarrow \frac{V_T}{I_T} = \frac{C_1 R_1 s + 1}{C_1 s + g_{m1}}$$

$$s \rightarrow j\omega \Rightarrow \frac{C_1 R_1 (j\omega) + 1}{C_1 j\omega + g_{m1}} = Z_T(j\omega)$$

$$|Z_T| = |Z_{in}| = \frac{\sqrt{(C_1 R_1 \omega)^2 + 1}}{\sqrt{C_1^2 \omega^2 + g_{m1}^2}} = \frac{\sqrt{C_1 R_1 \omega^2 + 1}}{g_{m1} \sqrt{\left(\frac{C_1 \omega}{g_{m1}}\right)^2 + 1}}$$



At $\omega = \frac{1}{C_1 R_1}$, we have a zero, at $\omega = \frac{g_{m1}}{C_1}$, we have a pole. If $R_1 > \frac{1}{g_{m1}}$, the zero $\frac{1}{C_1 R_1}$ is at a lower frequency than the pole, and the bode-plot for magnitude would look like the following.

$20 \log(Z_{in})$

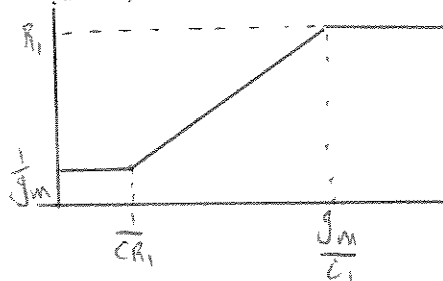

The bode-plot shows an impedance that increases with frequency, an inductive behavior.

43)

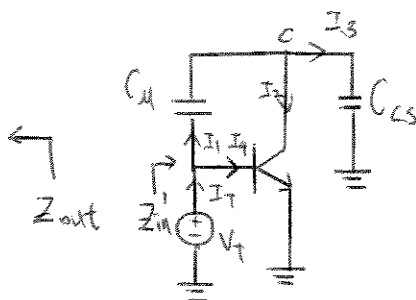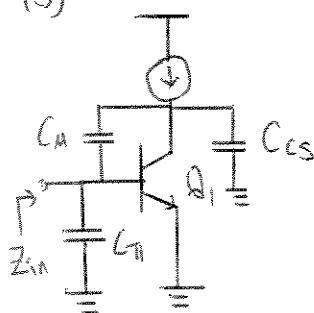

$$Z_{in} = Z_{in}' // \frac{1}{C_u s}, \quad I_T = I_1 + I_2 = C_u s V_{bc} + \frac{g_m V_T}{\beta}$$

$$V_{bc} = V_T - V_c, \quad V_c = (I_1 - g_m V_T) \frac{1}{C_{cs} s}$$

$$I_1 = \left[V_T - (I_1 - g_m V_T) \frac{1}{C_{cs} s} \right] C_u s$$

$$I_1 = V_T \left[C_u s + \frac{g_m C_u}{C_{cs}} \right] / \left(1 + \frac{C_u}{C_{cs}} \right)$$


$$I_T = V_T \left[C_u s + \frac{g_m C_u}{C_{cs}} \right] / \left(1 + \frac{C_u}{C_{cs}} \right) + \frac{g_m V_T}{\beta}$$

$$Z_{in}' = \frac{V_T}{I_T} = \frac{1}{\frac{g_m}{\beta} + \frac{C_u s}{\left(1 + \frac{C_u}{C_{cs}} \right)} + \frac{g_m \frac{C_u}{C_{cs}}}{\left(1 + \frac{C_u}{C_{cs}} \right)}}$$

$$Z_{in} = Z_{in}' // \frac{1}{C_u s} = r_{\pi} // \frac{1}{\frac{C_{cs} C_u s}{C_{cs} + C_u}} // \frac{1}{C_u s} // \frac{C_{cs} + C_u}{g_m C_u}$$

$$Z_{out} = \frac{1}{(C_u + C_{cs}) s}$$

44)

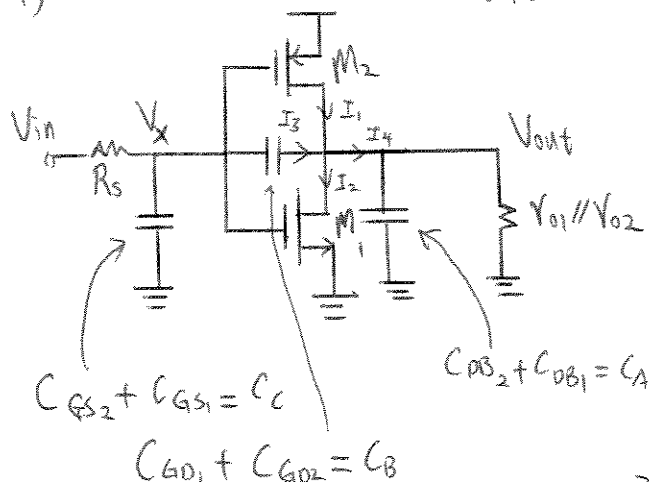 $\lambda > 0$ 

$$V_{out} = I_4 (Y_{01} // Y_{02} // \frac{1}{[C_{db2} + C_{db1}]s}) \quad \xrightarrow{Z_{out}}$$

$$I_4 = I_1 + I_3 - I_2$$

$$I_1 = (0 - V_x) g_{m2}$$

$$I_2 = V_x g_{m1}$$

$$I_3 = (V_x - V_{out}) (C_{gd1} + C_{gd2}) s$$

$$I_4 = -V_x g_{m2} + (V_x - V_{out}) C_b s - V_x g_{m1}$$

$$V_{out} = Z_{out} [-V_x (g_{m2} + g_{m1}) + (V_x - V_{out}) C_b s]$$

Writing a node equation at X.

$$\frac{V_x - V_{in}}{R_s} + V_x C_c s + (V_x - V_{out}) C_b s = 0$$

$$V_x = \frac{V_{out} C_b s + V_{in} / R_s}{(1/R_s + C_c s + C_b s)}$$

44)

Substitute everything and we get

$$V_{out} = Z_{out} \left[-(g_{m1} + g_{m2}) \left(\frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} \right) + \left(\frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} - V_{out} \right) C_B s \right]$$

Collect all the V_{out} 's on one-side and likewise for V_{in} 's,
we will get


$$\frac{V_{out}}{V_{in}} = \frac{Z_{out} (C_B s - (g_{m1} + g_{m2}))}{1/R_s + (C_c + C_B) s + Z_{out} C_B s (g_{m1} + g_{m2}) + Z_{out} C_B s \left(\frac{1}{R_s} + (C_c + C_B) s \right) - Z_{out} C_B^2 s^2}$$

$$\text{where } Z_{out} = Y_{o1} // Y_{o2} // \frac{1}{[C_{DB1} + C_{DB2}] s}$$

$$C_B = C_{GD1} + C_{GD2}$$

$$C_c = C_{GS1} + C_{GS2}$$

45)

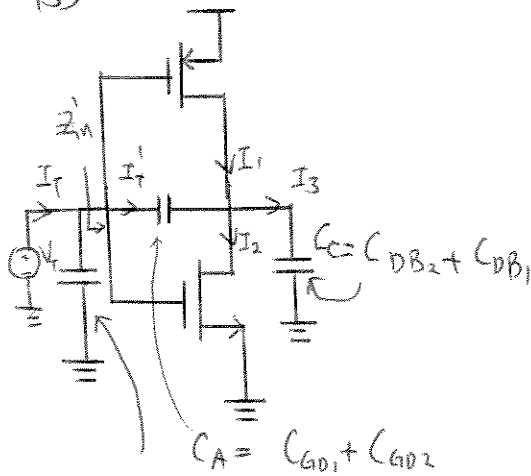

$$Z_{in} = \frac{V_T}{I_T} = \frac{1}{C_B} \parallel Z_{in}'$$

$$Z_{in}' = \frac{V_T}{I_T'}$$

$$C_B = C_{GS1} + C_{GS2}$$

$$I_T' = \left[V_T - \left(I_3 \frac{1}{C_{CS}} \right) \right] C_{AS}$$

$$I_3 = I_T' - V_T g_{m2} - g_{m1} V_T$$


$$\text{We get } \Rightarrow I_T' \left(1 + \frac{C_A}{C_C} \right) = V_T \left[C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C} \right]$$

$$Z_{in}' = \frac{V_T}{I_T'} = \frac{\left(1 + \frac{C_A}{C_C} \right)}{\left[C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C} \right]}$$

$$Z_{in} = \frac{1}{[C_{GS1} + C_{GS2}]s} \parallel \frac{\left(1 + \frac{C_{GD1} + C_{GD2}}{C_{DB1} + C_{DB2}} \right)}{\left[(C_{GD1} + C_{GD2})s + (g_{m1} + g_{m2}) \frac{C_{GD1} + C_{GD2}}{C_{DB2} + C_{DB1}} \right]}$$

46)

a)

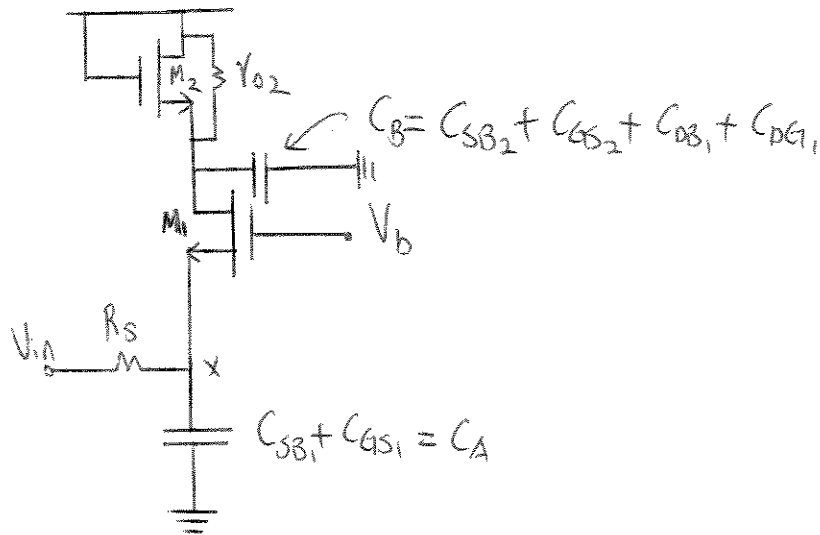

$$V_{out} = -(0 - V_x) g_{m1} \left[\frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right] = V_x g_{m1} \left[\frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]$$

Node equation at X, $\frac{V_x - V_{in}}{R_s} + V_x C_A s - g_m (0 - V_x) = 0$

$$V_x \left(\frac{1}{R_s} + C_A s + g_m \right) = \frac{V_{in}}{R_s} \Rightarrow V_x = \frac{V_{in}}{(1 + R_s C_A s + R_s g_m)}$$

substitute in V_x and solving for $V_{out}/V_{in} \Rightarrow$


$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} \left[\frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]}{(1 + R_s C_A s + R_s g_m)}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_s C_A s + R_s g_{m1})}$$

Where $C_B = C_{sb2} + C_{gs2} + C_{db1} + C_{db2}$

$C_A = C_{sb1} + C_{gs1}$

46)

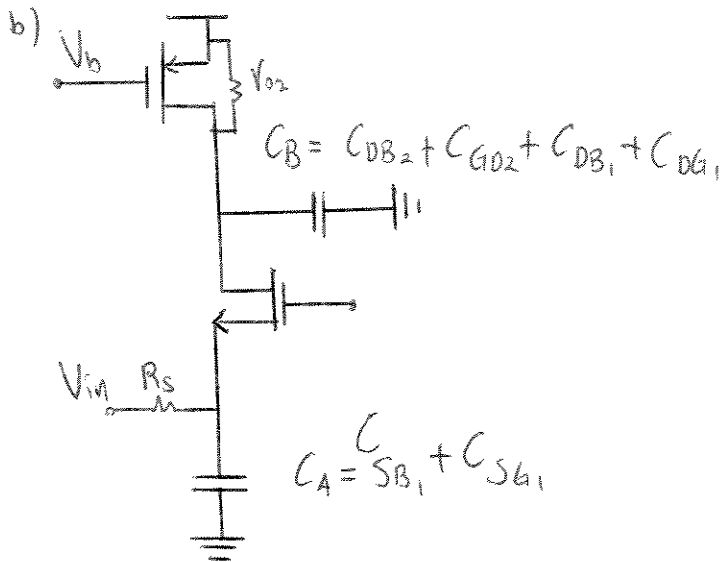

Similar to part a), with $\frac{1}{g_{m2}}$ replaced by V_{o2} ,
and different C_B .


$$\text{So } \frac{V_{out}}{V_{in}} = \frac{g_{m1} V_{o2}}{(C_B V_o s + 1)(1 + R_s C_A s + R_s g_{m1})}$$

Where $C_B = C_{DB2} + C_{GD2} + C_{DB1} + C_{DG1}$

$$C_A = C_{SB1} + C_{SG1}$$

46)

c)

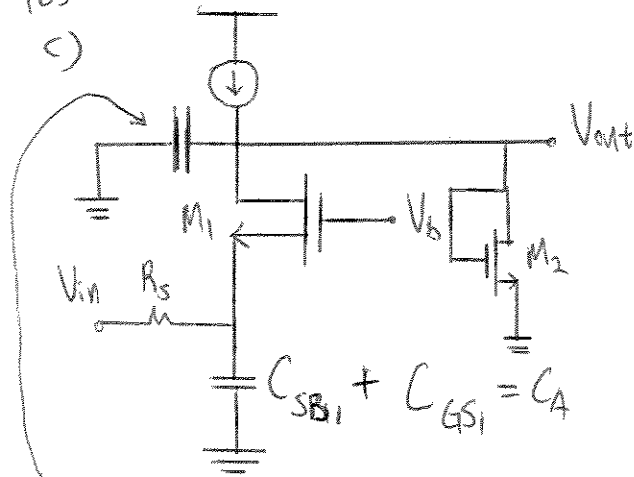

$$C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$$


AC-wise, this circuit is very similar to part a). Its transfer function is the same as part a), except for C_B .

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_S C_A s + R_S g_{m1})}$$

Where $C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$

$$C_A = C_{SB1} + C_{GS1}$$

47)

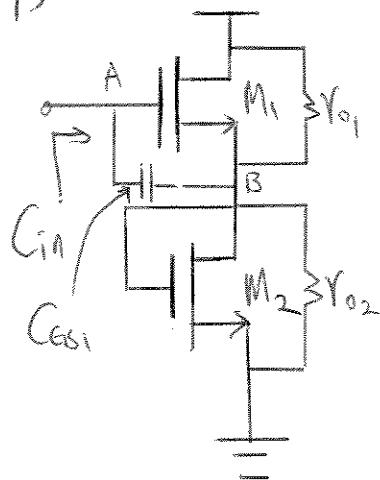

DC gain from A to B:

$$A_v = \frac{\frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2}}{\frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2} + \frac{1}{g_{m1}}}$$

$$A_v \approx \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}} = \frac{g_{m1}}{g_{m1} + g_{m2}}$$


$$\text{Since } g_{m1} r_{o1} \gg 1$$

Using Miller's Capacitance:

$$C_{in} = C_{gs1} (1 - A_v) = C_{gs1} \left(1 - \frac{g_{m1}}{g_{m1} + g_{m2}} \right)$$

$$C_{in} = C_{gs1} \left(\frac{g_{m2}}{g_{m2} + g_{m1}} \right)$$

48)

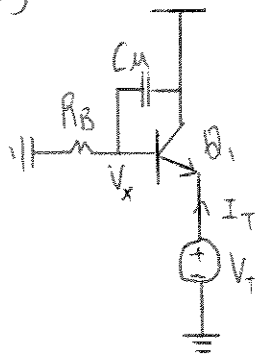

$$V_A = \infty$$

$$\frac{\beta}{\beta+1} \approx 1, \text{ if } \beta \gg 1$$

$$I_T = -(V_x - V_T) g_m \approx -(V_x - V_T) g_m$$

$$V_x = \frac{I_T}{\beta} \left(R_B \parallel \frac{1}{C_u s} \right)$$

$$I_T = \left(V_T - \frac{I_T}{\beta} \left(R_B \parallel \frac{1}{C_u s} \right) \right) g_m$$

$$I_T = g_m V_T - \frac{g_m}{\beta} \left(R_B \parallel \frac{1}{C_u s} \right) I_T$$


$$I_T \left(1 + \frac{g_m}{\beta} \left(R_B \parallel \frac{1}{C_u s} \right) \right) = g_m V_T$$


$$\frac{V_T}{I_T} = \frac{1}{g_m} + \frac{R_B \parallel \frac{1}{C_u s}}{\beta} = \frac{\beta C_u R_B (s + \frac{\beta + R_B g_m}{\beta C_u R_B})}{g_m \beta (1 + C_u R_B s)}$$

$$\text{Zero: } \frac{\beta + R_B g_m}{\beta C_u R_B}, \text{ Pole: } \frac{1}{C_u R_B}$$

$$\text{At DC, } |Z_{out}| = \frac{1}{g_m} + \frac{R_B}{\beta}$$

$$\text{At very high freq: } |Z_{out}| = \frac{1}{g_m}$$

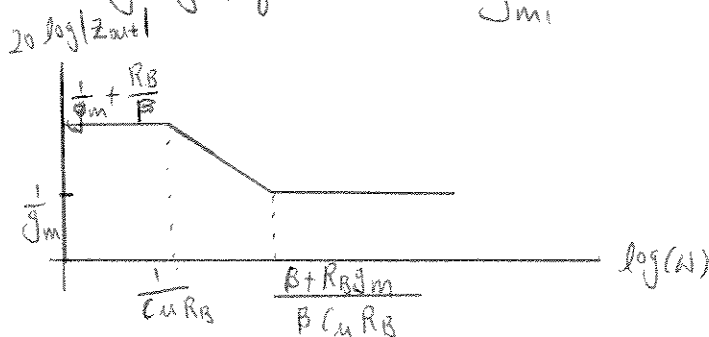

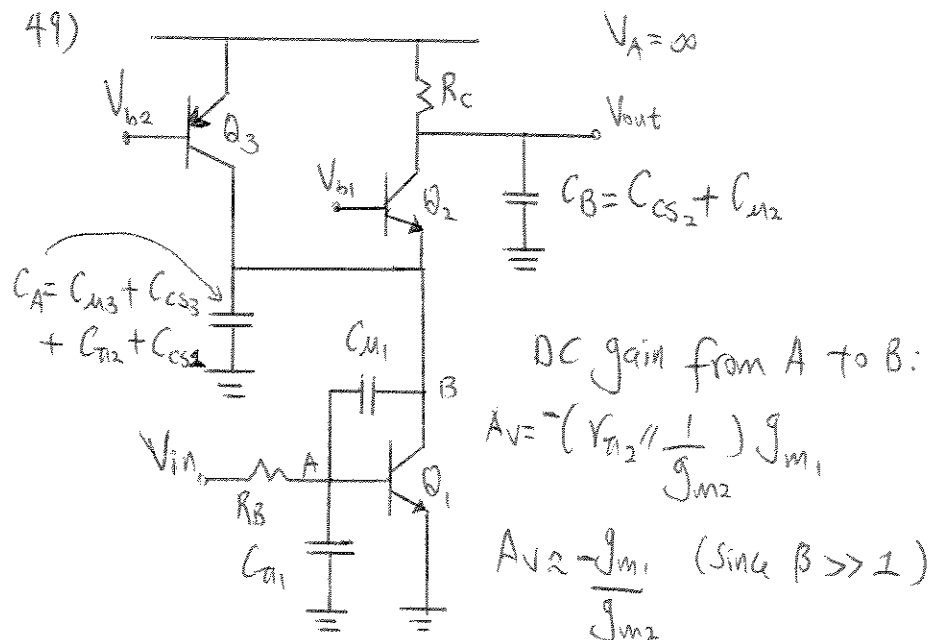

We have $I_{c2} = 0.25 I_{c1}$, $g_m = \frac{I_c}{V_T} \Rightarrow g_{m2} = 0.25 g_{m1}$

$A_v = -\frac{g_{m1}}{g_{m2}} = -4$. (If $I_{c2} = I_{c1}$, $A_v = -1$)

Applying Miller's Theorem: $C_{in} = C_{n1} + C_{n1}(1+4) = C_{n1} + 5C_{n1}$

$$C_B = C_A + C_u(1+\frac{1}{4}) = C_A + C_u(\frac{5}{4})$$


$\omega_{p1}(\omega_{pA}) = \frac{1}{(R_B \parallel r_n)[C_{n1} + 5C_{n1}]}$, $\omega_{pB} = \frac{0.25 g_{m1}}{[C_A + \frac{5}{4} C_{n1}]}$

$\omega_{pB} = \frac{g_{m2}}{[C_A + \frac{5}{4} C_{n1}]}$, $\omega_{pout} = \frac{1}{R_c [C_{cs2} + C_{n2}]}$

Where $C_A = C_{n3} + C_{cs3} + C_{n2} + C_{cs1}$.

Since the DC gain is increased, Miller effect is more significant.
(In magnitude)

50)

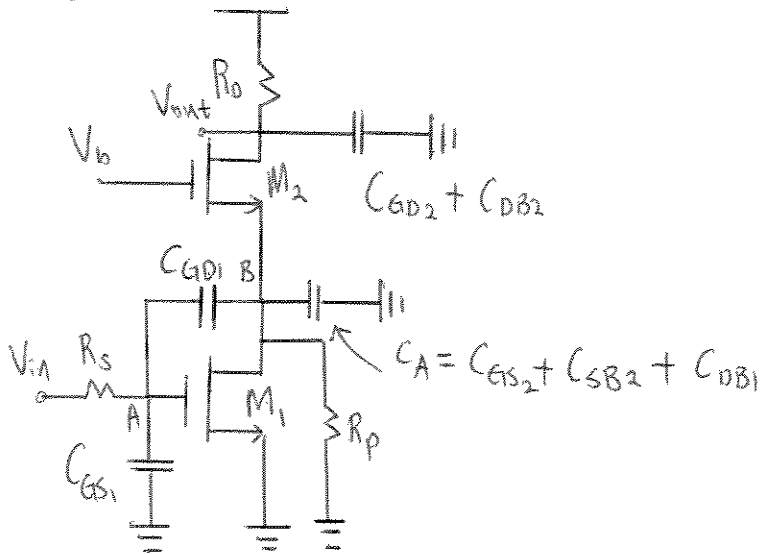

Dc gain from A to B is $-g_{m1}(R_p \parallel \frac{1}{g_{m2}})$


Applying Miller's Theorem:

$$W_{pin}(W_{PA}) = \frac{1}{R_s(C_{gs1} + C_{gd1}(1 + g_{m1}(R_p \parallel \frac{1}{g_{m2}}))}$$

$$\omega_{pB} = \frac{1}{R_p \parallel \frac{1}{g_{m2}} [C_{GS2} + C_{SB2} + C_{DB1} + C_{GD1} (1 + 1/g_{m1} (R_p \parallel \frac{1}{g_{m2}}))]}$$

$$W_{\text{pout}} = \frac{1}{R_o (C_{m2} + C_{pB2})}$$

51)

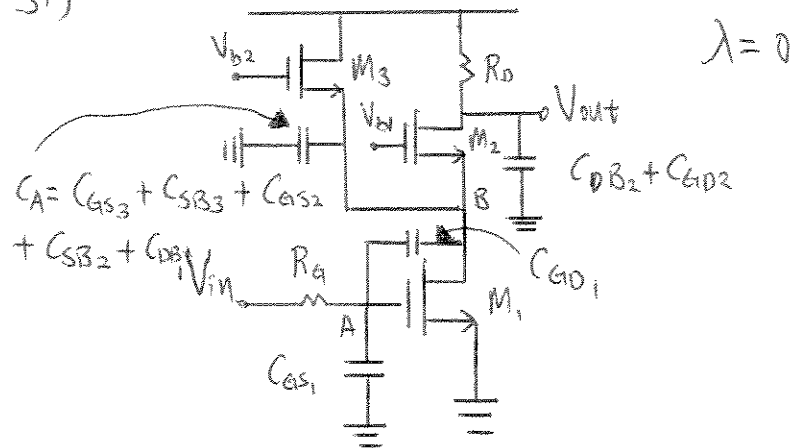

$$\text{DC gain from A to B: } -g_{m1} \left(\frac{1}{g_{m3}} \parallel \frac{1}{g_{m2}} \right) = -g_{m1} \left(\frac{1}{g_{m2} + g_{m3}} \right)$$

Applying Miller's Theorem:


$$\omega_{pi} (\omega_{pa}) = \frac{1}{R_A (C_{gs1} + C_{GD1} \left(\frac{g_{m1} + g_{m2} + g_{m3}}{g_{m2} + g_{m3}} \right))}$$

$$\omega_{pB} = \frac{g_{m3} + g_{m2}}{\left(C_A + C_{GD1} \left(\frac{g_{m1} + g_{m2} + g_{m3}}{g_{m1}} \right) \right)}$$

$$\omega_{pout} = \frac{1}{R_D (C_{DB2} + C_{GD2})}$$

$$\text{Where } C_A = C_{gs3} + C_{SB3} + C_{gs2} + C_{SB2} + C_{DB1}$$

52)

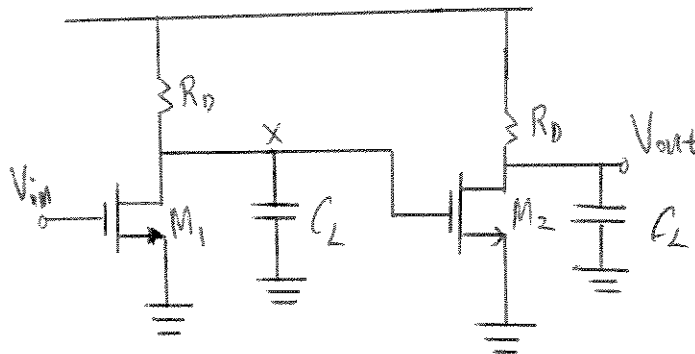

Bias Current = 1mA (each stage)

$$C_L = 50 \text{ fF}$$

$$\mu_n C_{ox} = 100 \mu\text{A/V}^2, A_v = 20, -3\text{dB: } 1\text{GHz}$$

$$\text{DC gain: } (g_m R_D)^2 = 20$$

$$-3\text{dB bandwidth: } 0.10243 / (R_D C_L) = 1\text{GHz}$$

$$\text{Since } C_L = 50 \text{ fF}, R_D = 2048.6 \Omega$$

$$(g_m R_D)^2 = 20 \Rightarrow g_m = 0.002183 = \frac{2I_D}{V_{eff}} \Rightarrow V_{eff} = 0.916\text{V}$$


$$V_{eff} = V_{GS} - V_{th} = 0.916\text{V}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{eff}) \Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{eff})} = 23.83$$

$$\text{So } R_D = 2.05\text{K}, C_L = 50\text{fF}$$

$$V_{GS} - V_{th} = 0.916\text{V}, W/L = 23.83$$

53)

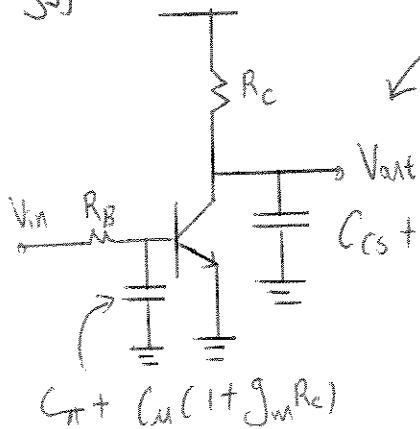

After apply Miller's theorem

$$\omega_{pin} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = (2\pi)(2\text{G})$$

$$I_c = 1\text{mA}, C_{\pi} = 2\text{pF},$$

$$C_u = 5\text{fF}, C_{cs} = 1\text{pF}$$

$$V_A = \infty$$

Low frequency Voltage gain:
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{\frac{1}{g_m} + \frac{R_B}{\beta + 1}}$$

$$\omega_{pin} = \frac{1}{(R_B // r_{\pi})(C_{\pi} + C_u(1 + g_m R_c))} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = \frac{1}{R_c [C_{cs} + (1 + 1/(g_m R_c))C_u]} = (2\pi)(2\text{G})$$

$$\Rightarrow g_m = 2\pi(2\text{G}) [g_m R_c C_{cs} + g_m R_c C_u + C_u]$$

$$\Rightarrow R_c = \left(\frac{g_m}{(2\pi)(2\text{G})} - C_u \right) / (g_m (C_{cs} + C_u))$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}, R_c = 5296.53 \Omega$$

53)

In order to maximize low frequency gain V_{out}/V_{in} , R_B should be as small as possible (restricted by the input pole location). So $R_B // r_{\pi} \approx R_B$.

$$\omega_{pin} \approx \frac{1}{R_B (C_{\pi} + C_{\mu} (1 + g_m R_c))} = (2\pi \times 50 \times 10^6)$$

$$g_m R_c = 204.446$$


$$R_B = \frac{1}{\omega_{pin} (C_{\pi} + C_{\mu} (1 + g_m R_c))} \approx 303.95 \Omega$$

So

$$R_B = 303.95 \Omega$$

$$R_c = 5296.53 \Omega$$

54)

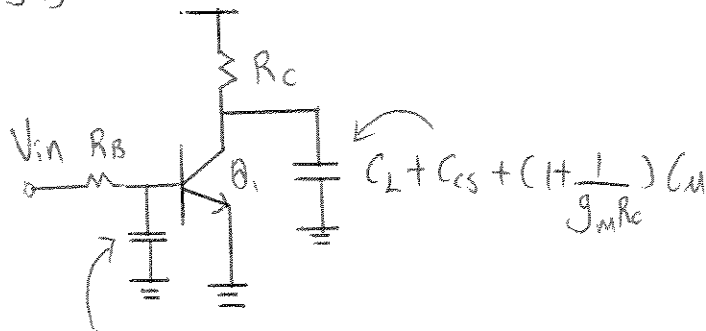

$$C_{\pi} + (1 + g_m R_c) C_{\mu}$$

Low freq Voltage gain:
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{1/g_m + \frac{R_B}{\beta + 1}}$$

$$\omega_{out} = \frac{1}{R_c [C_L + C_{cs} + (1 + \frac{1}{g_m R_c}) C_{\mu}]} = (2\pi)(2 \text{ GHz})$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}$$

$$g_m = (2\pi)(2 \text{ GHz}) [g_m R_c [C_L + C_{cs}] + g_m R_c (C_{\mu} + C_{\pi})]$$

$$R_c = \left[\frac{g_m}{(2\pi)(2 \text{ GHz})} - C_{\mu} \right] / (g_m [C_L + C_{cs} + C_{\mu}])$$

$$R_c = 2269.94 \Omega \approx 2.27 \text{ K}\Omega$$


Again, to maximize low freq gain, R_B should be as small as possible, so $R_B / V_T \approx R_B$

$$\omega_{in} \approx \frac{1}{R_B (C_{\pi} + C_{\mu} (1 + g_m R_c))} = (2\pi)(500 \times 10^6), g_m R_c = 87.62$$

$$R_B = 687.35 \Omega$$

So, $R_c = 2.27 \text{ K}\Omega, R_B = 687.35 \Omega$

55)

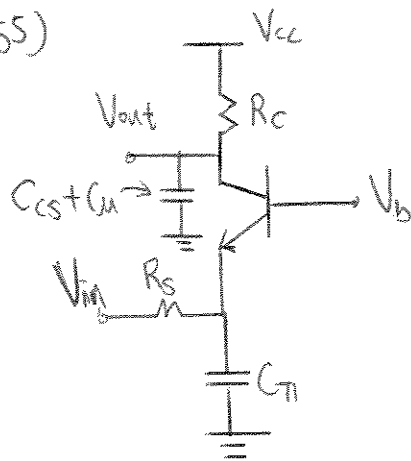

$$V_A = \infty, I_C = 1 \text{ mA}, R_S = 50 \Omega, \\ C_{\pi} = 20 \text{ fF}, C_{cs} = 20 \text{ fF}, C_u = 5 \text{ fF}$$

$$-3 \text{ dB bandwidth} = 10 \text{ GHz}$$

Since the output node sees a larger capacitance and resistance than the input, (R_C usually large for large gain), dominant pole and thus -3 dB bandwidth occurs at the output.


$$\omega_{\text{out}} = \frac{1}{R_C [C_u + C_{cs}]} = (2\pi)(10 \text{ GHz})$$

$$R_C = 636.62 \Omega, \quad \frac{1}{g_m} = \frac{25.9 \text{ mV}}{1 \text{ mA}}$$

$$\text{Maximum achievable gain} = \frac{R_C}{R_S + \frac{1}{g_m}} = 8.4$$

Here we have a tradeoff between gain and bandwidth.

56)

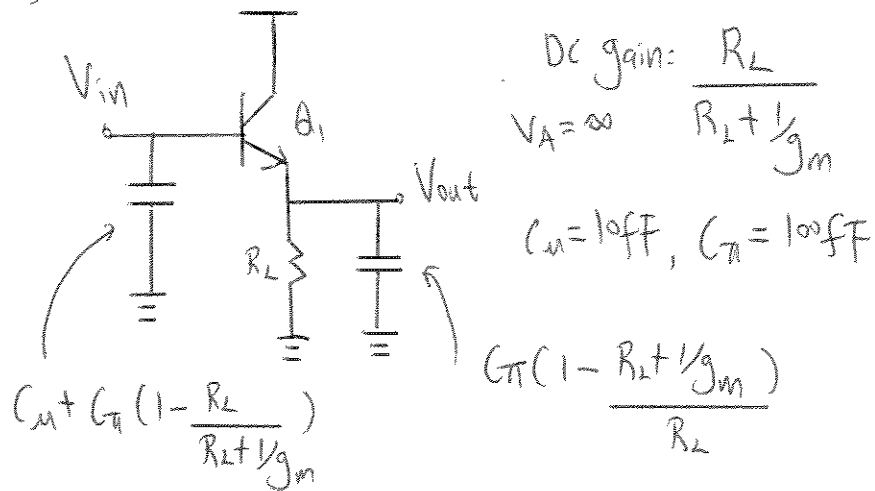

$$C_{in} < 50\text{fF} \Rightarrow C_n + C_{\pi} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50\text{fF}$$


$$10\text{fF} + 100\text{fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50\text{fF}$$

$$100\text{fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 40\text{fF}$$

$$\left(\frac{\frac{1}{g_m}}{R_L + 1/g_m}\right) < 0.4$$

$$R_L > \frac{3}{2g_m} = 38.85\Omega$$

57)

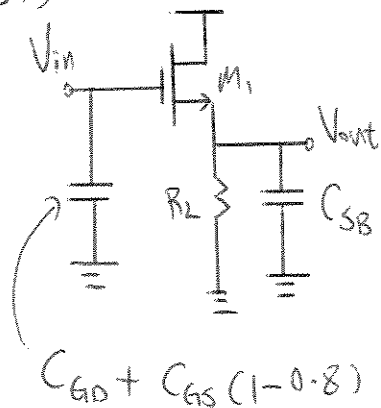

$$R_L = 100\Omega, \quad I_D = 1\text{mA}$$

$$A_V = \frac{V_{out}}{V_{in}} = 0.8 \quad \mu_n C_{ox} = 100\mu\text{A/V}^2$$

$$L = 0.18\mu\text{m}, \quad \lambda = 0, \quad C_{GD} \approx 0,$$

$$C_{SB} \approx 0, \quad C_{GS} = \left(\frac{2}{3}\right)WL C_{ox}$$

$$C_{ox} = 12\text{fF}/(\mu\text{m}^2)$$

$$C_{in} = C_{GD} + C_{GS} (0.2), \quad C_{in} = C_{GS} (0.2) = C_{in, \min}$$


$$A_V = \frac{R_L}{R_L + 1/g_m} = 0.8, \quad \frac{1}{g_m} = 25 = \frac{V_{eff}}{2I_D}$$

$$V_{eff} = 50\text{mV}, \quad I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 \Rightarrow W = 1440$$

$$C_{in, \min} = 0.2 C_{GS} = 0.2 \left(\frac{2}{3}\right)WL C_{ox} = 414.72\text{fF}$$

$$\text{or } C_{in, \min} = 0.415\text{pF}$$

58)

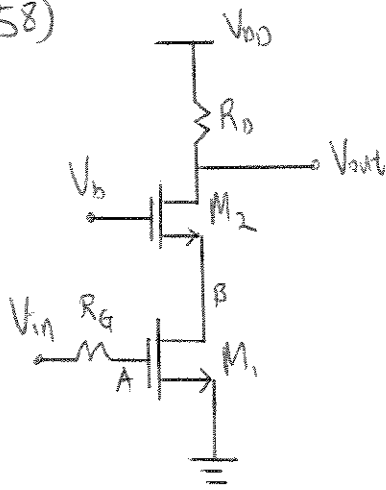

$$\omega_{pin} = 5 \text{ GHz}, \omega_{pout} = 10 \text{ GHz}$$

$$V_{eff} = 200 \text{ mV} (V_{GS} - V_{th}), I_D = 0.5 \text{ mA}$$

$$\lambda = 0, C_{GS} = (2/3) W L C_{ox}$$

$$L = 0.18 \mu\text{m}, \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$C_{GD} = W C_o, C_o = 0.2 \text{ fF}/\mu\text{m}$$

$$C_{ox} = 12 \text{ fF}/\mu\text{m}^2$$

$$\text{DC gain from A to B: } -\frac{g_{m1}}{g_{m2}} = 1$$

$$C_{in} = C_{GS} + C_{GD} (1 + g_{m1}/g_{m2}) = C_{GS} + 2 C_{GD}$$

$$I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 = 0.5 \text{ mA} \Rightarrow \frac{W}{L} = 250$$

$$L = 0.18 \mu\text{m}, W = 45 \mu\text{m}$$

$$\omega_{pin} = (2\pi)(5 \times 10^9) = \frac{1}{R_D \left[\frac{2}{3} (45)(0.18)(12 \text{ fF}/\mu\text{m}^2) + (0.2)(45)(2) \right]}$$

$$R_D = 384.43 \Omega$$

$$\omega_{pout} = \frac{1}{R_D [0.2 W]} = (10 \times 10^9)(2\pi), W = 45 \mu\text{m}$$

$$\Rightarrow R_D = 1.8 \text{ k}\Omega \quad (1768.4 \Omega \text{ exact value})$$

$$\text{Gain} = |g_m R_D| = \frac{2 I_D R_D}{V_{eff}} = 8.842$$

59)

$$W_2 = 4W_1, \quad V_{eff2} = \frac{V_{eff1}}{2} \quad (\text{To maintain the current constant})$$

$$V_{eff1} = 200 \text{ mV}, \quad V_{eff2} = 100 \text{ mV} \quad (\text{Assume } V_{eff1} \text{ is not changed})$$

$$\text{DC gain: } -\frac{g_{m1}}{g_{m2}} = -\frac{g_{m1}}{2g_{m1}} = -\frac{1}{2}$$

$$\omega_{pin} = \frac{1}{R_G \left[\frac{2}{3} W L (C_{ox} + 0.2) W \left(\frac{1}{2} \right) \right]} = (5 \times 10^9)(2\pi)$$

$$W = 45 \mu\text{m}$$

$$\Rightarrow R_G = 459.32 \Omega$$

$$R_D = \frac{1}{(10 \times 10^9)(2\pi)(0.2)(4)(45)} = 442.097 \Omega$$

$$\text{DC gain: } |g_{m1} R_D| = \frac{2I_D R_D}{V_{eff1}} = 2.2105$$