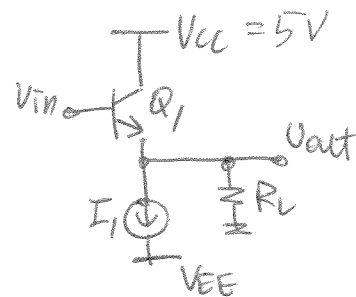


$$1. \quad A_v = \frac{g_{m1} R_L}{1 + g_{m1} R_L}$$

$$(a) \quad 0.8 = \frac{g_{m1} (85\Omega)}{1 + g_{m1} (85\Omega)}$$

$$\Rightarrow g_{m1} = 0.5 = \frac{I_{C1}}{V_T} = \frac{I_1}{V_T}$$

$$\therefore I_1 = 13 \text{ mA}$$



$$P_{\text{LOAD}} = 0.5 \text{ W}$$

$$R_L = 85\Omega$$

(Assume V_{out} biased at $V_{BE(ON)} \approx 800 \text{ mV}$)

(b) When $V_{in} = V_p = V_{CC}$, $V_{out} \approx V_{CC} - V_{BE(ON)1}$

$$I_{C1} = I_1 + \frac{V_{out}}{R_L} \Rightarrow I_{C1} = I_1 + \frac{5 - 0.8}{8} \approx 0.54 \text{ A}$$

$$\Rightarrow g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.54 \text{ A}}{0.026 \text{ V}} = 20.8 \text{ S}$$


$$\Rightarrow A_v \big|_{V_{in}=V_p} = \frac{g_{m1} R_L}{1 + g_{m1} R_L} = \frac{(20.8 \text{ S})(85\Omega)}{1 + (20.8 \text{ S})(85\Omega)} \approx 0.99$$

2.

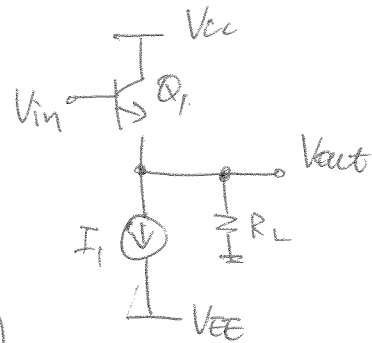(a) $I_1 = V_P / R_L$ $V_P \gg V_T$

$$A_V = \frac{I_C R_L}{I_C R_L + V_T}$$

$$= \frac{\frac{I_C}{I_1} V_P}{\frac{I_C}{I_1} V_P + V_T} = \frac{V_P}{V_P + V_T} \quad (\approx 1)$$



(b) When $V_{out} = V_P$, $I_{C1} = I_1 + \frac{V_{out}}{R_L} = \frac{V_P}{R_L} + \frac{V_P}{R_L}$
 $= \frac{2V_P}{R_L}$


$$\therefore A_V = \frac{\left(\frac{2V_P}{R_L}\right) R_L}{\left(\frac{2V_P}{R_L}\right) R_L + V_T} = \frac{2V_P}{2V_P + V_T} \quad \left(\approx \frac{2V_P}{2V_P} = 1\right)$$

$$\Delta A_V = \frac{\frac{2V_P}{2V_P + V_T} - \frac{V_P}{V_P + V_T}}{\frac{V_P}{V_P + V_T}} = \frac{V_T}{2V_P + V_T} \quad \left(\approx \frac{V_T}{V_P}\right)$$

3. $A_v = 0.7$ $R_L = 4\Omega$

Q_1 shuts off when:

$$I_1 = \frac{V_P}{R_L}$$

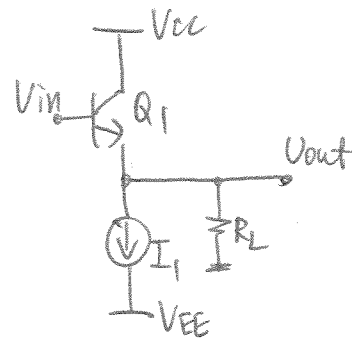

• Suppose $V_{out} = V_P \sin \omega t$. $(\omega = \frac{2\pi}{T})$

$$P_{R_L, AVG} = \frac{1}{T} \int_0^T \frac{(V_{out})^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_P^2 \sin^2 \omega t}{R_L} dt$$


$$\therefore \text{Largest power (average)} = \frac{1}{2} \left(\frac{I_1 R_L}{R_L} \right)^2 = \frac{1}{2} V_P^2 / R_L$$

$$A_v = 0.7 = \frac{g_{m1} R_L}{1 + g_{m1} R_L} \Rightarrow g_{m1} = \frac{A_v}{(1 - A_v) R_L} = \frac{0.7}{(1 - 0.7)(4)} = 0.58 \text{ S}$$

$$\Rightarrow I_{C1} (= I_1) = g_{m1} V_T = 0.015 \text{ A}$$

$$\therefore P_{AV, MAX} = \frac{1}{2} I_1^2 R_L = \frac{1}{2} (0.015 \text{ A})^2 (4\Omega) = 0.45 \text{ W}$$
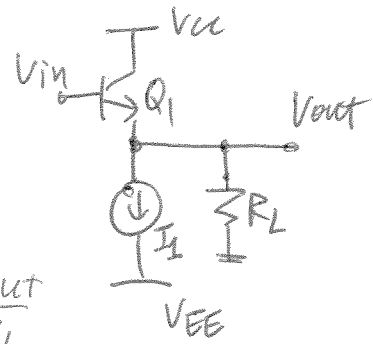
$$4. A_v = \frac{g_{m1} R_L}{1 + g_{m1} R_L} \quad (g_m = \frac{I_{C1}}{V_T})$$



- Q_1 shuts off when $I_1 = -\frac{V_{out}}{R_L}$
 $\Rightarrow V_p = I_1 \times R_L$

$$g_{m1} = \frac{A_v}{(1 - A_v) R_L} = \frac{I_{C1}}{V_T} \Rightarrow I_{C1} = \frac{V_T A_v}{R_L (1 - A_v)} (= I_1)$$

- Power delivered to R_L :

$$P_{R_L} = \frac{1}{T} \int_0^T \frac{V_{out}^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_p^2 \sin^2 \omega t}{R_L} dt$$

$$= \frac{1}{2} \frac{V_p^2}{R_L}$$

$$\therefore \text{Maximum power} = \frac{1}{2} \left(\frac{I_1 R_L}{R_L} \right)^2$$

$$= \frac{1}{2} \left[\frac{V_T A_v}{(1 - A_v)} \right]^2 \cdot \frac{1}{R_L}$$

5.

(a) By KCL,

$$I_1 = I_{S1} \cdot \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) + \frac{V_{cc} - V_{out}}{R_L}$$


$$\Rightarrow V_{in} = V_{out} + V_T \ln\left(\frac{I_1}{I_{S1}} - \frac{V_{cc} - V_{out}}{I_{S1} R_L}\right)$$

$$= 0 \quad (X) \text{—no solution}$$

$$\therefore V_{out} \approx 5 - I_1 R_L = 4.84 \text{ V}$$

(i.e. Q_1 is off.)

Assume $V_{cc} = 5 \text{ V}$

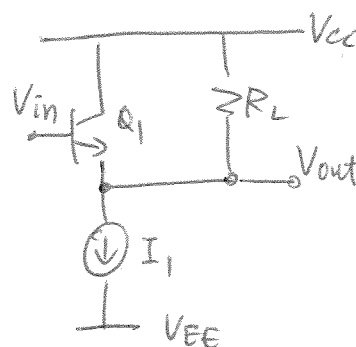

$$I_{S1} = 5 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \Omega$$

$$I_1 = 20 \text{ mA}$$

(b) $(0.01)I_1 = I_1 - \frac{V_{cc} - V_{out}}{R_L}$

$$\Rightarrow V_{out} = 4.84 \text{ V}$$

$$I_{C1} = (0.01)I_1 = I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right)$$

$$\Rightarrow V_{in} = V_{out} + V_T \ln\left(0.01 \frac{I_1}{I_{S1}}\right)$$

$$= 4.84 + (0.026) \ln\left(0.01 \frac{20 \text{ mA}}{5 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 5.59 \text{ V}$$

(exceeds V_{cc})

b.

(a) Calculate V_{BE} for

$$\underline{V_{in} = 1 \text{ V} :}$$

$$I_{C1} = I_1 + \frac{V_{out}}{R_L}$$

$$\Rightarrow I_{S1} \cdot \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) = I_1 + \frac{V_{out}}{R_L}$$

Solving for V_{out} gives:

$$V_{out} \approx 0.113 \text{ V}$$


$$\therefore V_{BE} \Big|_{V_{in}=1\text{V}} = V_{in} - V_{out} = 1 - 0.113 = 0.887 \text{ V}$$

$$\underline{V_{in} = -1 \text{ V} :}$$

$$I_{C1} = I_1 + \frac{-V_{out}}{R_L} \Rightarrow I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) = I_1 - \frac{V_{out}}{R_L}$$

Solving for V_{out} gives: $V_{out} \approx -1.95 \text{ V}$

$$\therefore V_{BE} \Big|_{V_{in}=-1\text{V}} = V_{in} - V_{out} = -1 - (-1.95\text{V}) = 0.95 \text{ V}$$

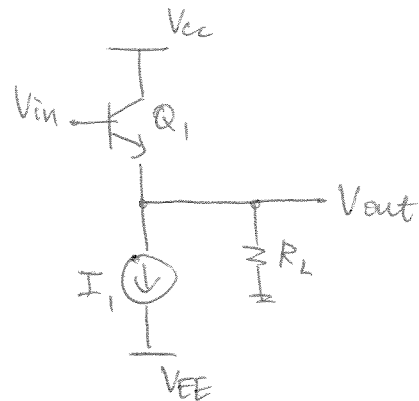


$$I_{S1} = 6 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \text{ k}\Omega$$

$$I_1 = 25 \text{ }\mu\text{A}$$

$$V_p = 1 \text{ V}$$

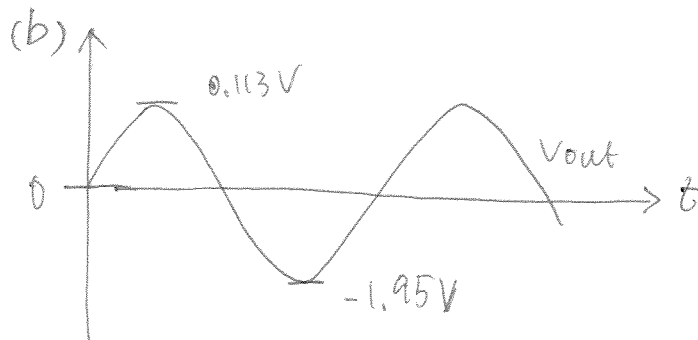

7. Determine V_p such that

$$V_{BE} \big|_{V_{in}=+V_p} - V_{BE} \big|_{V_{in}=-V_p} = 10 \text{ mV}$$

$$\Rightarrow (V_p^+ - V_{out,+}) - (V_p^- - V_{out,-}) = 10 \text{ mV}$$

$$I_S \exp\left(\frac{V_p^+ - V_{out,+}}{V_T}\right) = I_1 + \frac{V_{out,+}}{R_L} \quad \text{--- (1)}$$


$$I_S \exp\left(\frac{V_p^- - V_{out,-}}{V_T}\right) = I_1 - \frac{V_{out,-}}{R_L} \quad \text{--- (2)}$$

Iterate (1) & (2). This gives:

$$V_p \approx 0.7 \text{ V}$$

$$\Rightarrow \text{Nonlinearity} = \frac{10 \text{ mV}}{0.7 \times 2} \approx 0.007.$$

8.

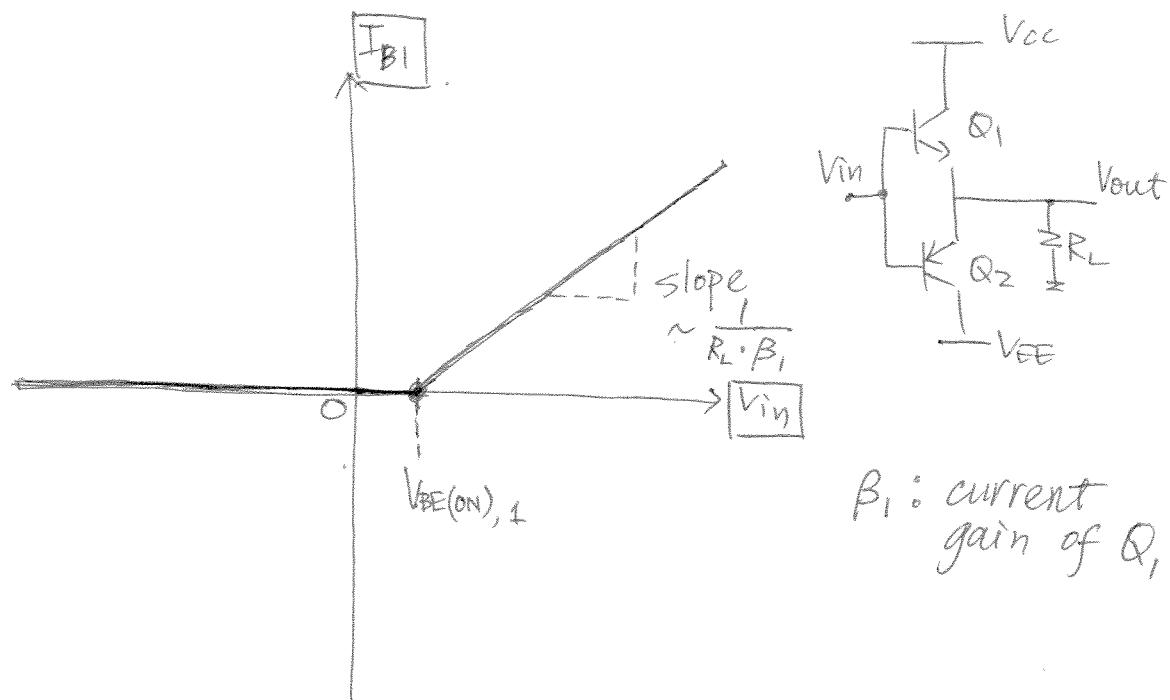

β_1 : current gain of Q_1

- Q_1 is on whenever $V_{in} \geq V_{BE(ON),1}$. In this region,

$$V_{out} = V_{in} - V_{BE(ON),1}$$


$$I_{C1} = \frac{V_{out}}{R_L}$$

$$\therefore I_{B1} = \frac{I_{C1}}{\beta} = \frac{V_{out}}{\beta R_L} = \frac{V_{in} - V_{BE(ON),1}}{\beta R_L}$$

9.

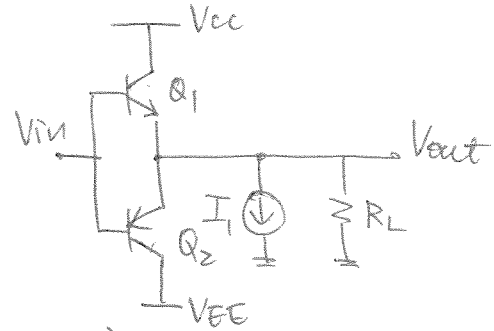(a) To guarantee Q_1 on,

- $V_{out} \approx V_{in} - V_{BE(ON)1}$
 $= -800 \text{ mV}$



$$\Rightarrow I_{C1} = I_1 + \frac{V_{out}}{R_L} \quad (Q_2 \text{ is off})$$

$$I_{S2} = 6 \cdot 10^{-17} \text{ A}$$

- $I_{C1} \geq 0 \Rightarrow I_1 + \frac{V_{out}}{R_L} \geq 0$

$$R_L = 8 \text{ k}\Omega$$

$$\Rightarrow I_1 + \frac{-800 \text{ mV}}{R_L} \geq 0$$

$$\therefore I_1 R_L \geq 800 \text{ mV} \quad \text{————— ①}$$

(b) When Q_2 turns on,

$$-\frac{V_{out}}{R_L} - I_1 = I_{C2}$$

$$\Rightarrow -\frac{V_{out}}{R_L} - \left(\frac{800 \text{ mV}}{R_L} \right) = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right)$$


$$\begin{aligned} \Rightarrow V_{out} &= -R_L I_{S2} \cdot \exp\left(\frac{V_{BE2}}{V_T}\right) - 0.8 \\ &= -(8 \text{ k}\Omega)(6 \cdot 10^{-17} \text{ A}) \exp\left(\frac{0.8}{0.026}\right) - 0.8 \\ &\approx -0.81 \text{ V} \end{aligned}$$

$$\therefore V_{in} = V_{out} - |V_{BE(ON)2}| = -0.81 - 0.8 = -1.61 \text{ V}$$

10. Consider two scenarios :

- In gain regions ($|V_{in}| \geq |V_{BE(on)}|$), V_{out} tracks V_{in} .
- In dead zone, both transistors shut off.

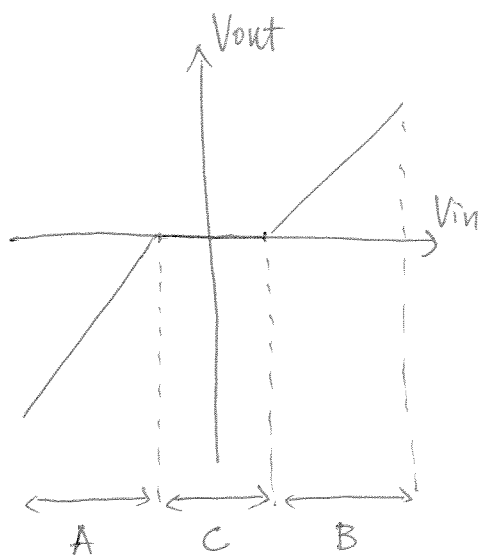In both cases, V_{out} has an important role. Current source I_1 affects the input/output characteristic by modulating V_{out} :



I/O characteristic of Push-pull stage.

Consider region A :

$$I_{C2} + I_1 = -\frac{V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE2}| = |V_{out} - V_{in}|$ stays relatively constant.

(Q_2 absorbs/sinks all the currents from I_1 in order to have the same $|V_{BE2}|$)

Consider region B :

$$I_{C1} = I_1 + \frac{V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE1}| = |V_{in} - V_{out}|$ stays relatively constant.

(Q_1 provides/sources current to I_1 in order to have $|V_{BE1}|$ constant.)

Consider region C: (Dead zone).

$$I_1 = -\frac{V_{out}}{R_L} \quad (\text{Both transistors off})$$



$$\therefore I_1 \uparrow \Rightarrow V_{out} \downarrow$$

$$I_1 \downarrow \Rightarrow V_{out} \uparrow$$

i.e. In the dead zone, V_{out} is predominantly controlled by I_1 . One can use this to control V_{out} and effectively shift the region of dead zone.

($\because V_{out}/v_{in=0} \neq 0$ anymore)

11.

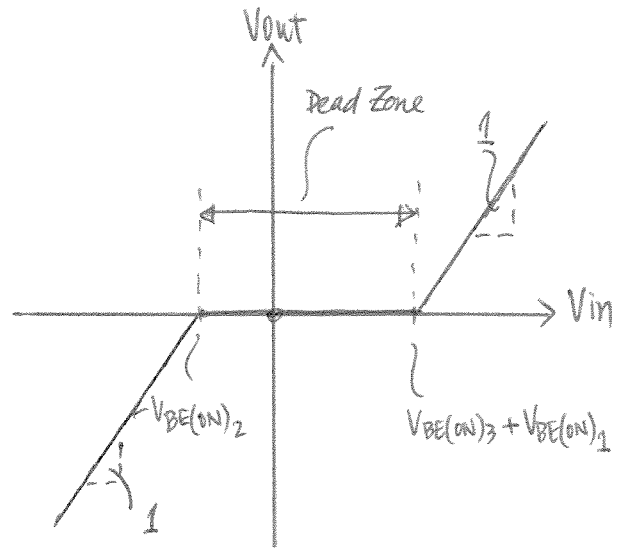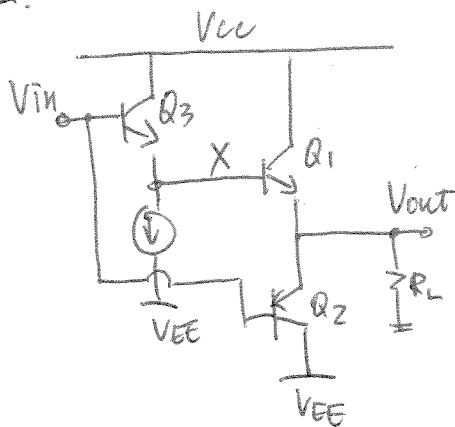



Analysis

Dead Zone

$$= |V_{BE(on)2}| + V_{BE(on)3} + V_{BE(on)1}$$

- $(0 < V_{in} < V_{BE(on)3} + V_{BE(on)1})$:
 Q_1 is OFF ($V_{in} < V_{BE(on)1}$)
 Q_2 is OFF (V_{BE2} reverse-biased) } $\Rightarrow V_{out} = 0$
- $(-|V_{BE(on)2}| < V_{in} < 0)$:
 Q_1, Q_2 OFF. } $V_{out} = 0$
- $(V_{BE(on)3} + V_{BE(on)1} < V_{in} < V_{cc})$
 Q_1 ON
 Q_2 OFF } $V_{out} = V_{in} - V_{BE(on)3} - V_{BE(on)1}$
- $(-|V_{EE}| < V_{in} < -|V_{BE(on)2}|)$
 Q_2 ON
 Q_1 OFF } $V_{out} = V_{in} + |V_{BE(on)2}|$

12.

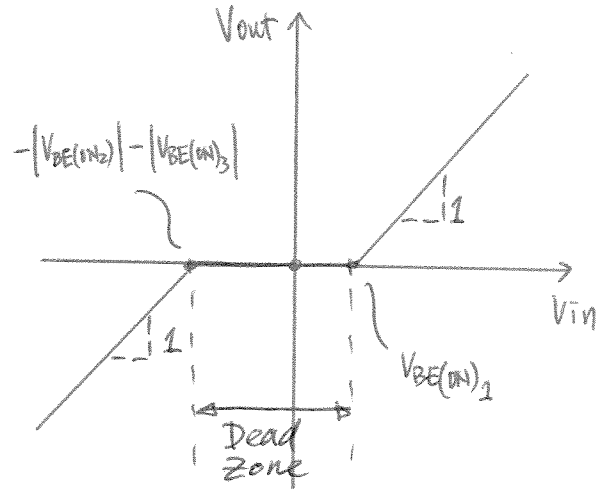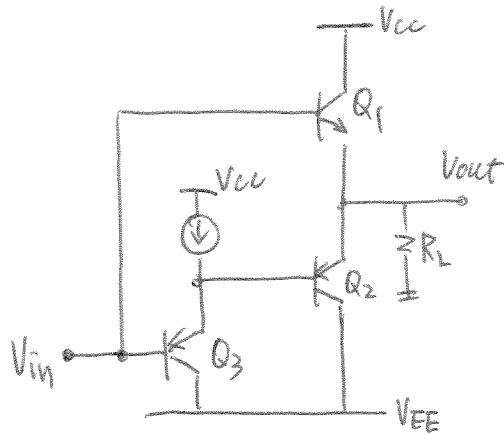

$$-V_{EE} < V_{in} < -(|V_{BE(ON)2}| + |V_{BE(ON)3}|) :$$

$$\Rightarrow \left. \begin{array}{l} Q_2, Q_3 \text{ ON} \\ Q_1 \text{ OFF} \end{array} \right\} V_{out} = V_{in} + |V_{BE(ON)3}| + |V_{BE(ON)2}|$$

$$-(|V_{BE(ON)2}| + |V_{BE(ON)3}|) < V_{in} < V_{BE(ON)1} :$$

$$\Rightarrow Q_1, Q_2 \text{ OFF} \Rightarrow V_{out} \cong 0$$

$$V_{BE(ON)1} < V_{in} < V_{cc} :$$

$$\Rightarrow \left. \begin{array}{l} Q_1 \text{ ON} \\ Q_2, Q_3 \text{ OFF} \end{array} \right\} V_{out} = V_{in} - V_{BE(ON)1}$$

$$\text{Dead Zone} = V_{BE(ON)1} + |V_{BE(ON)2}| + |V_{BE(ON)3}|$$

13.

(a)

$$-|V_{EE}| < V_{in} < -|V_{t,p}| :$$


$$\Rightarrow \left. \begin{array}{l} M_1 \text{ OFF} \\ M_2 \text{ ON} \\ \text{(saturation)} \end{array} \right\} V_{out} = V_{in} + V_{sg,2}$$

$$V_{cc} > V_{in} > V_{t,n} :$$

$$\Rightarrow \left. \begin{array}{l} M_1 \text{ ON} \\ M_2 \text{ OFF} \end{array} \right\} V_{out} = V_{in} - V_{gs,1}$$

$$-|V_{t,p}| < V_{in} < V_{t,n} :$$
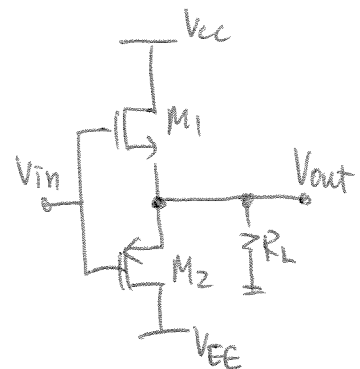
$$M_1, M_2 \text{ OFF} \Rightarrow V_{out} = 0$$




Ignore body effect.

$\Rightarrow M_1$ & M_2 can never on at the same time.

For MOS, $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (|V_{gs}| - |V_t|)^2$ — saturation region.

$$\Rightarrow M_1 \text{ ON: } \frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{t,n})^2, V_{out} > 0$$
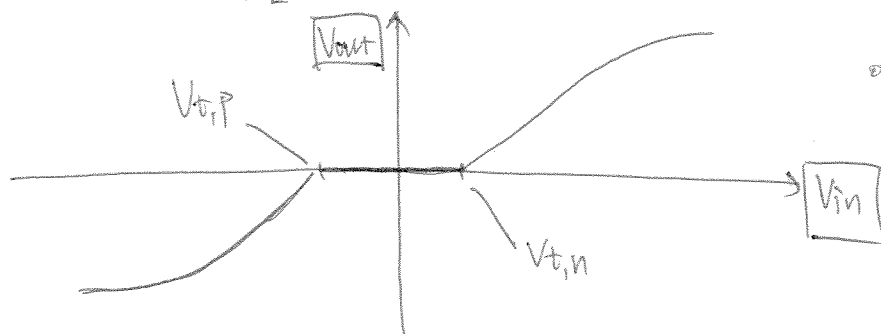
$$M_2 \text{ ON: } -\frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{out} - V_{in} - V_{t,p})^2, V_{out} < 0$$




• Solve for V_{out} in both cases.

(b) Outside dead zone

\Rightarrow either M_1 or M_2 is on.


• For positive inputs:

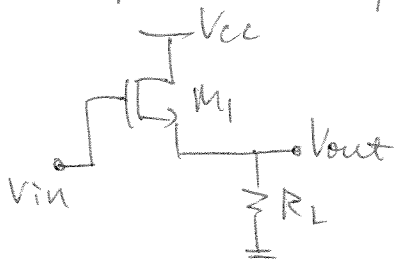

Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{1 + g_{m1} R_L}$$

• For negative inputs:


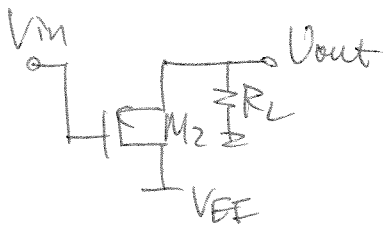


Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m2}}{1 + g_{m2} R_L}$$

14. Dead zone :



$$V_{out} \in [-|V_{BE(ON)_2}|, V_{BE(ON)_3} + V_{BE(ON)_1}]$$

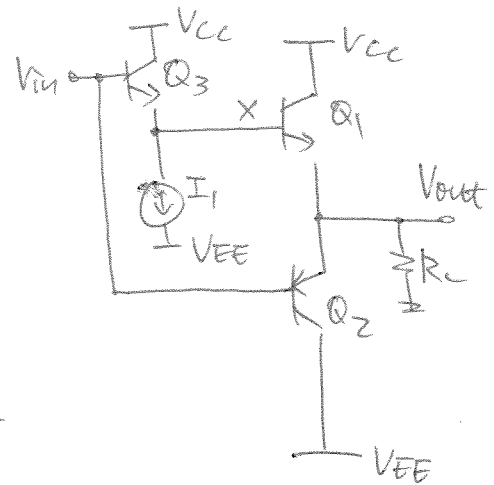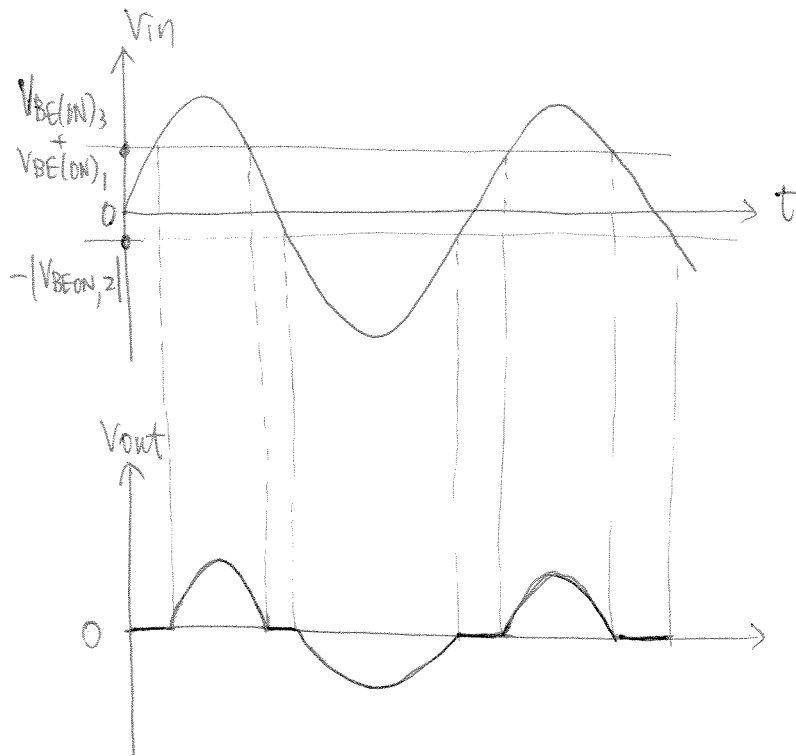



15.

Dead zone:


$$V_{out} \in [-(|V_{BE,ON,2}| + |V_{BE,ON,3}|), V_{BE,ON,1}]$$

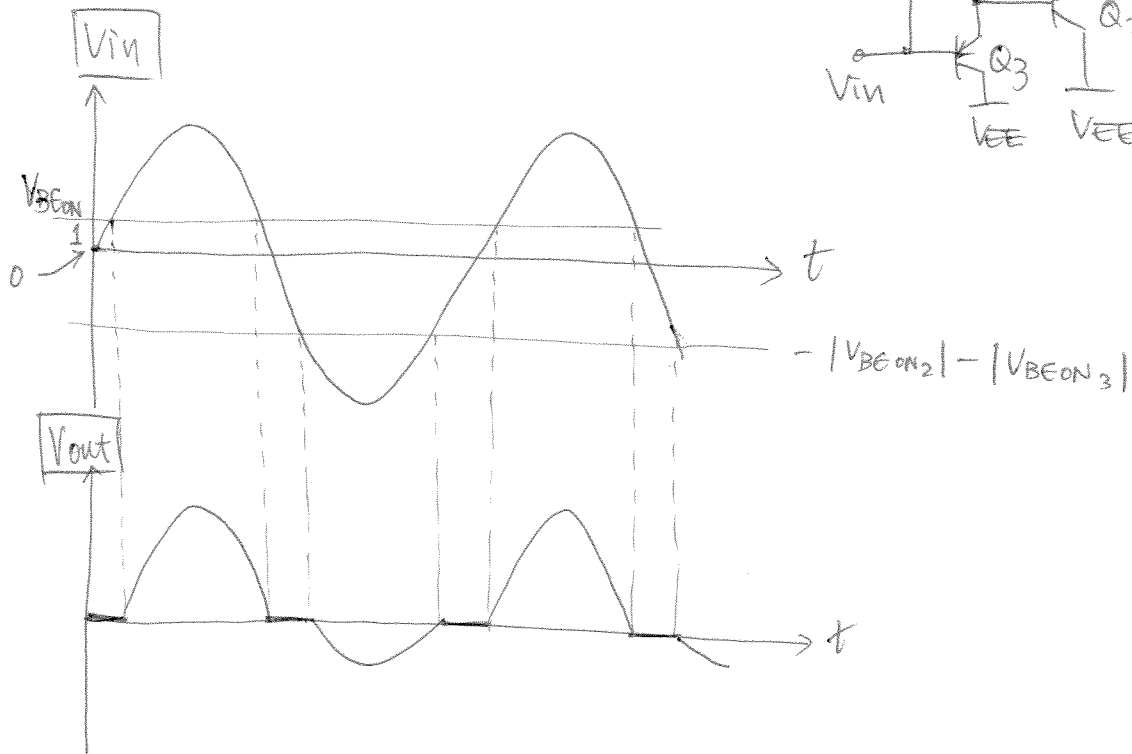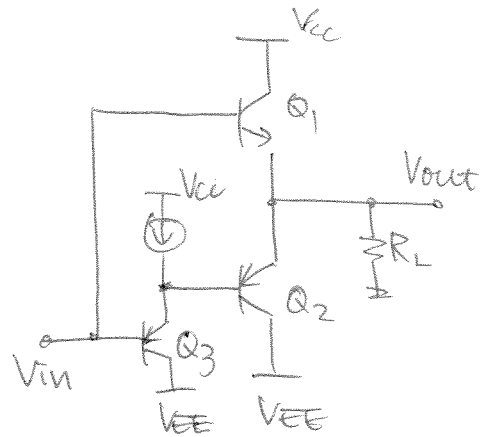

16.
(a)

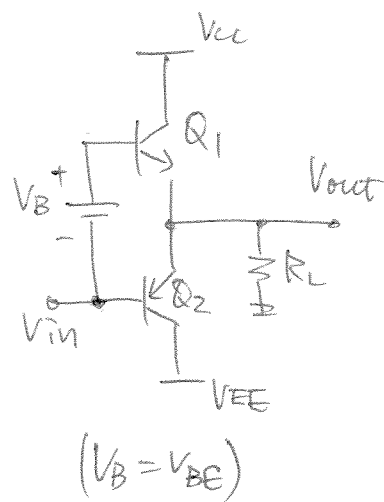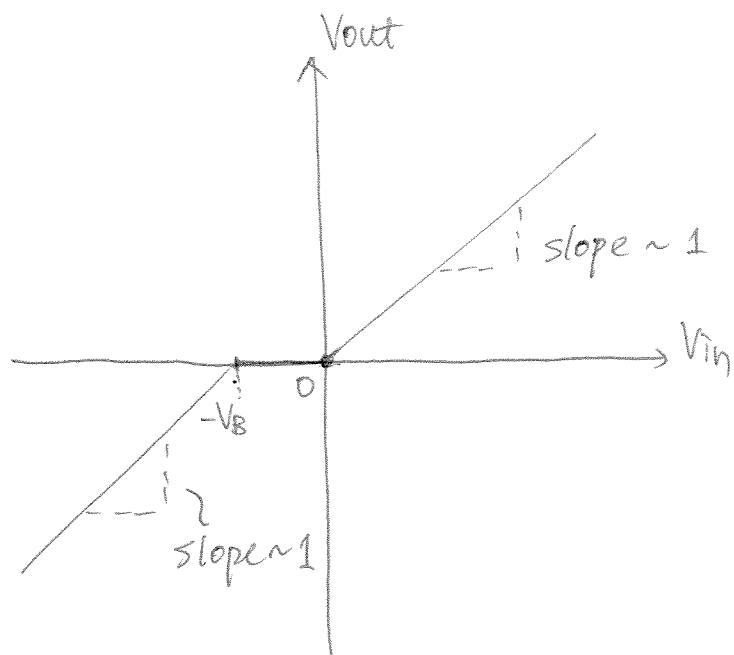

(b)

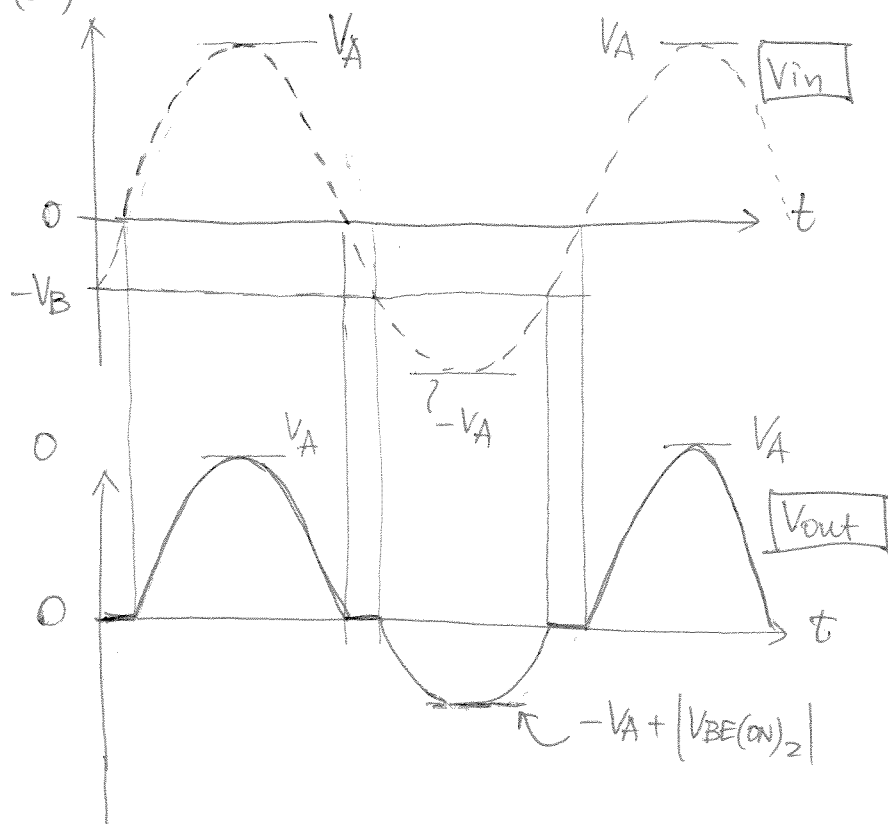

17.

• $V_{out} = 0$:

$$\Rightarrow I_{C1} = I_{C2} = I_{BIAS}$$

$$\Rightarrow I_{S1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = I_{S2} \exp\left(\frac{|V_{out} - V_{in}|}{V_T}\right)$$

$$\ln\left(\frac{I_{S1}}{I_{S2}}\right) + \frac{V_{in} + V_B - V_{out}}{V_T} = \frac{|V_{out} - V_{in}|}{V_T}$$

• For $V_{out} = 0$, $V_T = 0.026$ V :

$$\Rightarrow \ln\left(\frac{5}{8}\right) + \frac{V_{in} + V_B}{0.026} = +\frac{V_{in}}{0.026}$$


• Given $I_{C2} = 5$ mA

$$\Rightarrow I_{S2} \exp\left(\frac{-V_{in}}{0.026}\right) = 5 \text{ mA} \Rightarrow V_{in} = -0.83 \text{ V}$$

$$I_{C1} = I_{S1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = (5 \cdot 10^{-17} \text{ A}) \exp\left(\frac{-0.83 + V_B}{V_T}\right)$$

$$\Rightarrow V_B = 0.83 + 0.026 \ln\left(\frac{5 \text{ mA}}{5 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 1.67 \text{ V}$$

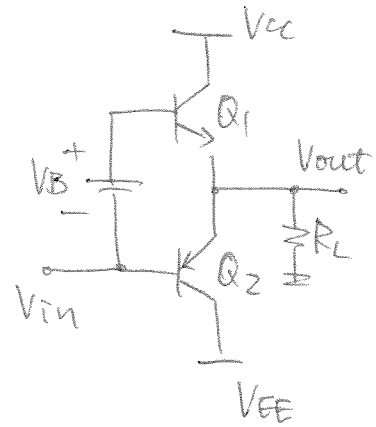

$$I_{S1} = 5 \cdot 10^{-17} \text{ A}$$



$$I_{S2} = 8 \cdot 10^{-17} \text{ A}$$

$$I_{BIAS} = 5 \text{ mA}$$

$$(V_{out} = 0)$$

18.

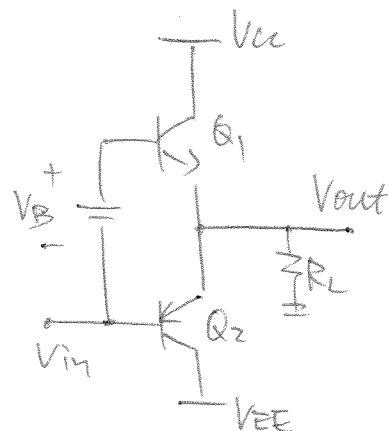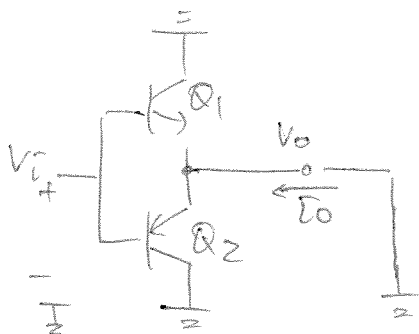(a) Equivalent circuit (small-signal) around $V_{out} = 0$:



$$V_{P_{in}} = 2V$$

$$R_L = 85\Omega$$

$$\begin{aligned} \bar{i}_o &= -g_{m1} V_i + (-V_i) g_{m2} \\ &= -(g_{m1} + g_{m2}) V_i \end{aligned}$$

$$\therefore G_m = \frac{\bar{i}_o}{V_i} = -(g_{m1} + g_{m2})$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{\bar{i}_o \times R_L}{V_i} = -(g_{m1} + g_{m2}) R_L$$

$$\begin{aligned} (b) \quad A_v &= -(g_{m1} + g_{m2}) R_L = -\left(\frac{I_{C1}}{V_T} + \frac{I_{C2}}{V_T}\right) R_L \\ &= -\left(\frac{5mA}{0.026V} + \frac{5mA}{0.026V}\right) (85\Omega) = -3.08 \end{aligned}$$



$$\Rightarrow |V_o|_P = |V_i A_v|_P = |(2V)(-3.08)| = 6.16V$$

(Assume V_{cc} is large enough)

$$(c) \quad I_{C1} = I_{C2} + \frac{V_{out}}{R_L}$$


$$\begin{aligned} I_{C1, peak} &= I_{C2} + \frac{V_P}{R_L} \\ &= 5mA + \frac{6.16V}{8.52} \\ &= 775mA \end{aligned}$$

19.

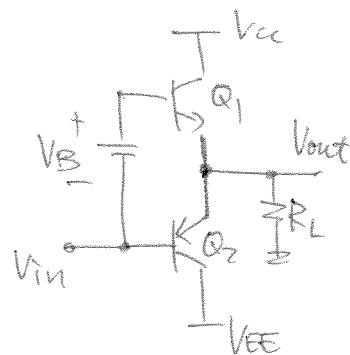
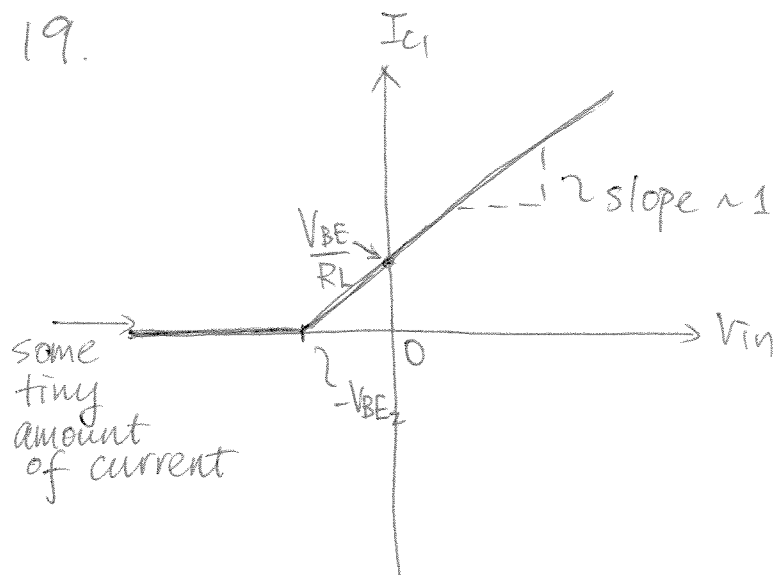


$$V_{out} = V_{in} + |V_{BE2}|$$
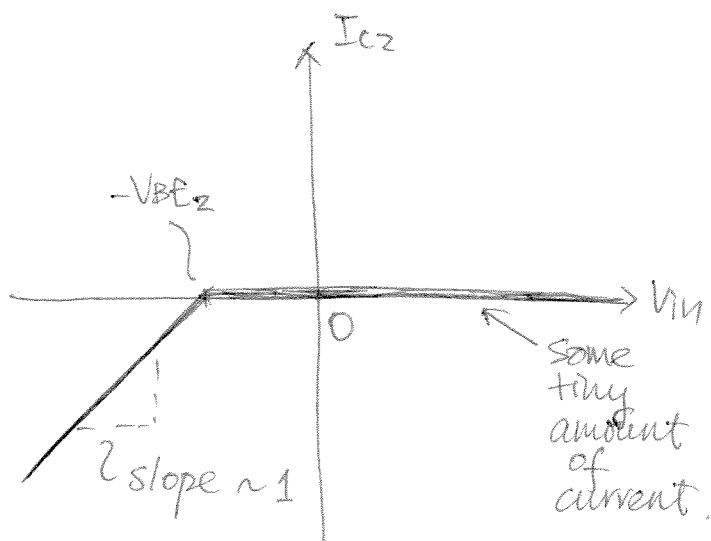
$$\Rightarrow I_{C1} = I_{C2} + \frac{V_{out}}{R_L}$$



20.

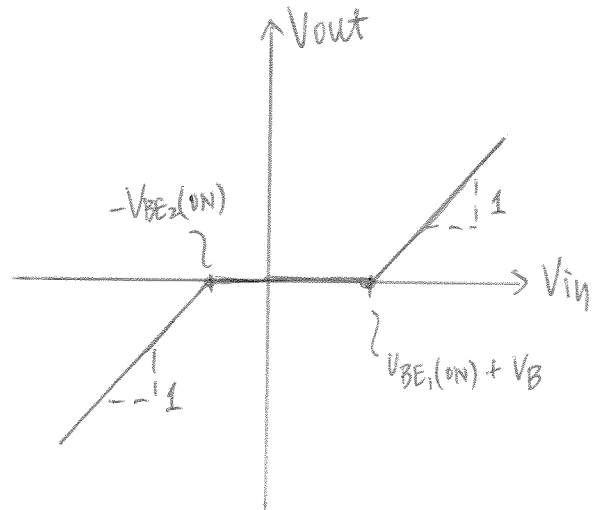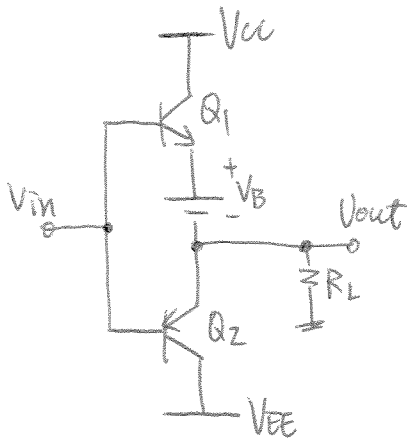

• To analyze such circuit, assume $V_{out} = 0$:

$$\Rightarrow -V_{BE2(ON)} < V_{in} < V_{BE1(ON)} + V_B$$

$$(V_{BE1(ON)} + V_B) < V_{in} \quad \therefore \quad V_{out} = V_{in} - V_{BE1(ON)} - V_B$$

$$V_{in} < -V_{BE2(ON)} \quad \therefore \quad V_{out} = V_{in} + |V_{BE2(ON)}|$$

$$21. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow V_T \left[\ln \frac{I_{C1}}{I_{S_{Q1}}} + \ln \frac{I_{C2}}{I_{S_{Q2}}} \right] = V_T \left[\ln \frac{I_{D1}}{I_{S_{D1}}} + \ln \frac{I_{D2}}{I_{S_{D2}}} \right]$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S_{Q1}} I_{S_{Q2}}} = \frac{I_{D1} I_{D2}}{I_{S_{D1}} I_{S_{D2}}}$$

$$\therefore \text{If } I_{S_{Q1}} I_{S_{Q2}} = I_{S_{D1}} I_{S_{D2}},$$

$$\text{then } I_{C1} I_{C2} = I_{D1} I_{D2}$$

$$22. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow V_T \ln\left(\frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}\right) = V_T \ln\left(\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}\right)$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{————— (1)}$$

$$I_1 = I_{D1} = I_{D2} = 1\text{mA}; \quad I_{S,Q} = 16 I_{S,D}$$

$$V_{out} = 0 \Rightarrow I_{C1} = I_{C2} \quad \text{————— (2)}$$

Substitute all into (1):

$$\frac{I_{C1} I_{C1}}{(16 I_{S,D})^2} = \frac{(1\text{mA})^2}{(I_{S,D})^2} \Rightarrow I_{C1} = I_{C2} = 16 \text{ mA}$$

$$23. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{_____} \quad (1)$$

$$I_{C1} = I_{C2} = 5 \text{ mA} \quad \text{_____} \quad (2)$$

$$I_{S,Q} = 8 I_{S,D} \quad \text{_____} \quad (3)$$

Substitute all into (1):

$$\frac{(5 \text{ mA})^2}{(8 I_{S,D})^2} = \frac{I_{D1} I_{D2}}{(I_{S,D})^2} \Rightarrow I_1 = I_D = 0.625 \text{ mA}$$

$$24. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{————— ①}$$

$$I_1 = I_D = 2 \text{ mA}$$

$$I_{S,Q1} = 8 I_{S,D1} \quad ; \quad I_{S,Q2} = 16 I_{S,D2}$$

Substitute all into ①:

$$\frac{I_{C1} I_{C2}}{(8 I_{S,D1})(16 I_{S,D2})} = \frac{(2 \text{ mA})^2}{I_{S,D1} I_{S,D2}}$$

$$\Rightarrow I_{C1} = I_{C2} \cong 22.6 \text{ mA}$$

$$25. V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{kT_Q}{q} \left[\ln \left(\frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} \right) \right] = \frac{kT_D}{q} \left[\ln \left(\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right) \right]$$

$$\text{Suppose } T_D = (T_Q + \Delta T) :$$

$$\Rightarrow T_Q \left[\ln \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} - \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right] = \Delta T \cdot \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}$$


$$\Rightarrow I_{C1} \cdot I_{C2} = I_{S,Q1} \cdot I_{S,Q2} \cdot \left(\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right)^{1 + \frac{\Delta T}{T_Q}}$$

$$\text{Typically, } \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} > 1$$

$$\Rightarrow \text{A } \Delta T \text{ introduces a factor } \left(\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right)^{\frac{\Delta T}{T_Q}} < 1,$$

implying that the $I_{C1} I_{C2}$ product drops corresponding to a change (positive) in temperature.


26. Small Signal:

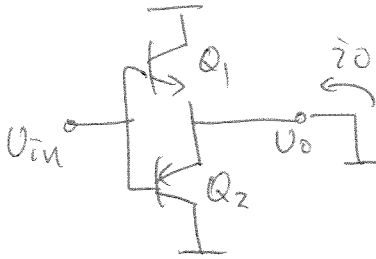

$$G_m = \frac{i_o}{v_{in}} = -(g_{m1} + g_{m2})$$

$$\Rightarrow \frac{v_o}{v_{in}} = \frac{i_o R_L}{v_{in}} = -(g_{m1} + g_{m2}) R_L$$

27. Small-signal:

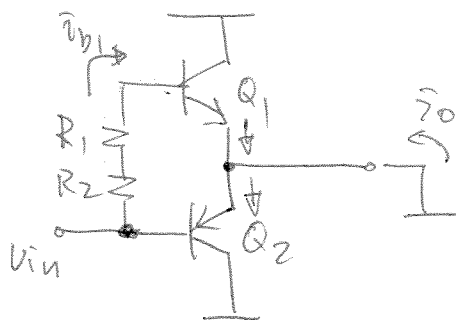

$$\bar{i}_o = -g_{m1} V_{be1} + g_{m2} |V_{be2}| \quad (\bar{i}_o = \bar{i}_{c2} - \bar{i}_{c1})$$

$$|V_{be2}| = V_{in}$$

$$V_{be1} = V_{in} - \bar{i}_{b1} (R_1 + R_2) = V_{in} - \frac{\bar{i}_{c1}}{\beta_1} (R_1 + R_2)$$

$$= V_{in} - \frac{\bar{i}_{c2} - \bar{i}_o}{\beta_1} (R_1 + R_2)$$

$$= V_{in} + \frac{g_{m2} V_{in} + \bar{i}_o}{\beta_1} (R_1 + R_2)$$


$$\therefore g_{m1} \left[V_{in} + \frac{g_{m2} V_{in} + \bar{i}_o}{\beta_1} (R_1 + R_2) \right] + \bar{i}_o = -g_{m2} V_{in}$$

Solving for $\frac{\bar{i}_o}{V_{in}}$ gives:

$$\bar{G}_m = \frac{\bar{i}_o}{V_{in}} = - \frac{\left[g_{m1} + \frac{g_{m1} g_{m2}}{\beta_1} (R_1 + R_2) + g_{m2} \right]}{1 + \frac{g_{m1} (R_1 + R_2)}{\beta_1}}$$

R_{out} :
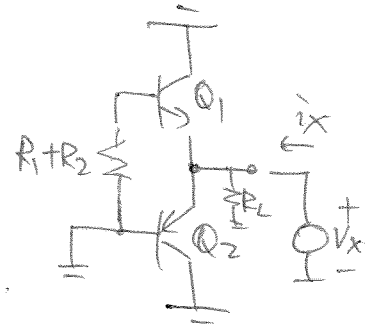
$$\frac{V_x}{i_x} = R_{out} = (r_{\pi_2} \parallel \frac{1}{g_{m_2}}) \parallel \left[(r_{\pi_1} + R_1 + R_2) \parallel \frac{1}{g_{m_1}} \right] \parallel R_L$$



$\therefore A_v = G_m R_{out}$

$$= - \left[\frac{g_{m_1} + \frac{g_{m_1} g_{m_2} (R_1 + R_2)}{\beta_1} + g_{m_2}}{1 + \frac{g_{m_1} (R_1 + R_2)}{\beta_1}} \right] \cdot \left\{ \left[r_{\pi_2} \parallel \frac{1}{g_{m_2}} \right] \parallel \left[(r_{\pi_1} + R_1 + R_2) \parallel \frac{1}{g_{m_1}} \right] \parallel R_L \right\}$$


28. Small signal gain
around $V_{out} = 0$:

$$A_v = +(g_{m1} + g_{m2}) R_L$$

$$0.8 = (I_{C1} + I_{C2}) \frac{R_L}{V_T}$$



If $I_{C1} = I_{C2} = I_{BIAS}$, then
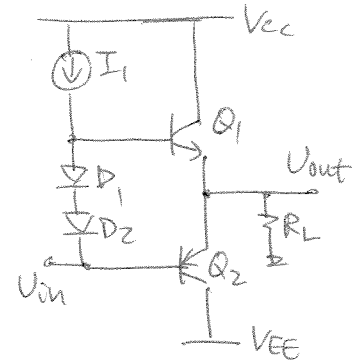
$$I_C = \frac{0.8}{2} \times \frac{V_T}{R_L} = 0.4 \frac{V_T}{R_L} = 0.01 \cdot R_L = 0.08 \text{ A}$$



$$R_L = 8 \Omega$$

29. Small-signal equivalent:

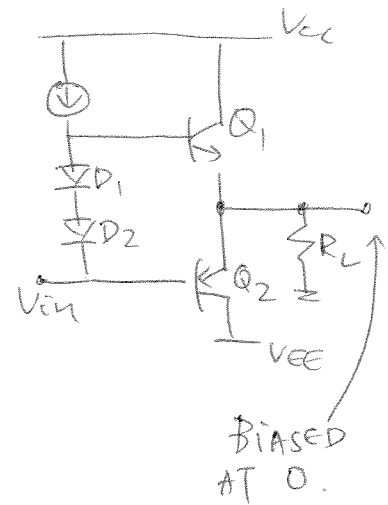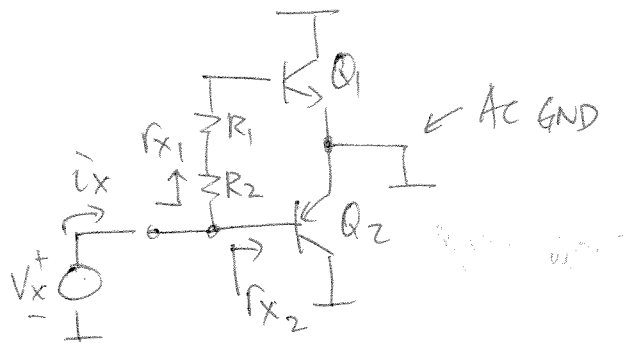

$$R_{in} = \frac{V_x}{I_x} = r_{x1} \parallel r_{x2}$$

$$= (R_1 + R_2 + r_{\pi 1}) \parallel r_{\pi 2}$$

• R_1 & R_2 can be neglected when $r_{\pi 1} \gg (R_1 + R_2)$


30. $I_{C1} = I_{C2} = 10 \text{ mA}$

$I_{C3} = I_{C4} = 1 \text{ mA}$


$\beta_1 = 40 \quad \beta_2 = 20$

$R_L = 8 \Omega$

$R_{D1} = R_{D2} = 0$

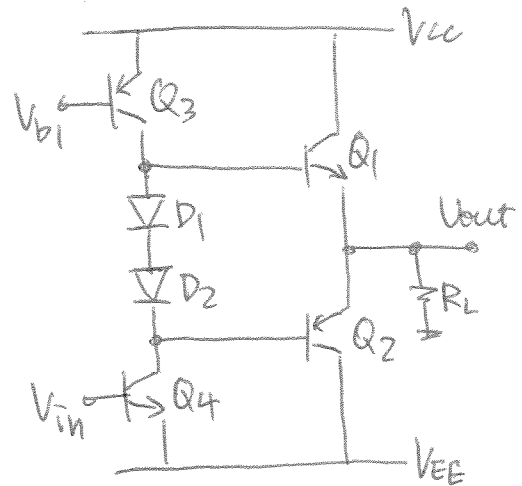

Small-signal

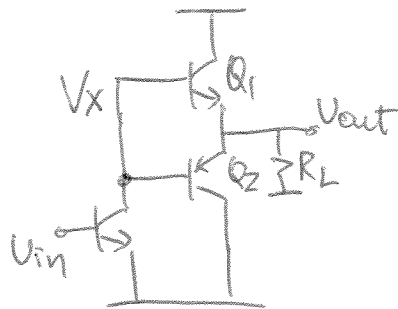

$$A_V = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$$

$$= -g_{m4} \left[(g_{m1} + g_{m2}) (r_{\pi 1} \parallel r_{\pi 2}) R_L + (r_{\pi 1} \parallel r_{\pi 2}) \right] \times \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$= -g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$\therefore A_V = - \frac{I_{C4}}{V_T} \left(\left(\frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} \right) \left(\frac{I_{C1}}{V_T} + \frac{I_{C2}}{V_T} \right) R_L \right)$$

$$= - \frac{1 \text{ mA}}{0.026} [35] \cdot \left(2 \times \frac{10 \text{ mA}}{V_T} \right) (8)$$

$$\approx -8.3$$

31.

$$\frac{V_{out}}{V_{in}} = -g_{m4} (\Gamma_{\pi_1} \parallel \Gamma_{\pi_2}) (g_{m_1} + g_{m_2}) R_L \quad (\Gamma_{\pi} = \frac{\beta}{g_m})$$

When $g_{m_1} \approx g_{m_2}$: $(\Rightarrow \Gamma_{\pi}$

$$\frac{V_{out}}{V_{in}} \hat{=} -g_{m4} R_L (2g_{m_1}) \left(\frac{\beta_1}{g_{m_1}} \parallel \frac{\beta_2}{g_{m_1}} \right)$$

$$= -g_{m4} R_L (2g_{m_1}) \left[\frac{1}{g_{m_1}} \cdot \frac{\beta_1 \beta_2}{\beta_1 + \beta_2} \right]$$

$$= - \frac{2\beta_1 \beta_2}{\beta_1 + \beta_2} g_{m4} R_L$$


32. From lecture, small-signal gain of the output stage is:

$$\left| \frac{V_{out}}{V_{in}} \right| = +g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$\approx +g_{m4} R_L \times \frac{2\beta_1 \beta_2}{\beta_1 + \beta_2}$$

$$\Rightarrow 4 = + \frac{I_{c4}}{V_T} (85\Omega) \times \frac{2(40)(20)}{40 + 20}$$
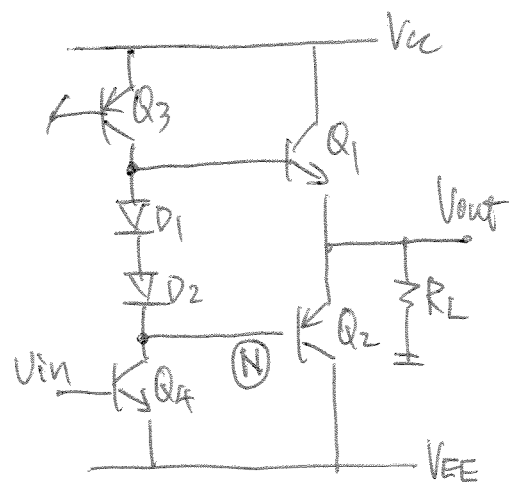
$$\begin{aligned} \Rightarrow I_{c4} &\approx I_{c3} \\ &= \frac{4 V_T}{(85\Omega)} \cdot \frac{40 + 20}{2(40)(20)} \\ &= 0.49 \text{ mA} \end{aligned}$$



$$A_V = \frac{V_{out}}{V_{in}} = 4$$

$$\beta_1 = 40$$

$$\beta_2 = 20$$

$$R_L = 85\Omega$$


33. From lecture,

$$\frac{v_x}{i_x} = \frac{1}{g_{m1} + g_{m2}} + \frac{r_{o3} \parallel r_{o4}}{(g_{m1} + g_{m2})(r_{\pi1} + r_{\pi2})}$$

If $g_{m1} \approx g_{m2} = g_m$:

$$\begin{aligned} \frac{v_x}{i_x} &\approx \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2g_m \left(\frac{\beta_1}{g_m} \parallel \frac{\beta_2}{g_m} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2g_m \left(\frac{1}{g_m} \frac{\beta_1 \beta_2}{\beta_1 + \beta_2} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2\beta_1 \beta_2} (\beta_1 + \beta_2) \end{aligned}$$

34.

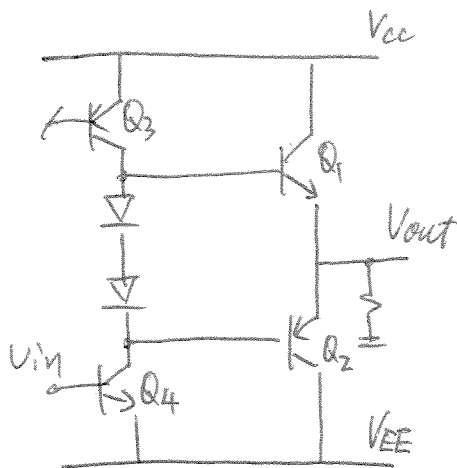


$$I_3 = I_4 = 1 \text{ mA}$$

$$I_1 = I_2 = 8 \text{ mA}$$


$$V_{A3} = 10 \text{ V}$$

$$V_{A4} = 15 \text{ V}$$

(a) Small-signal equivalent:

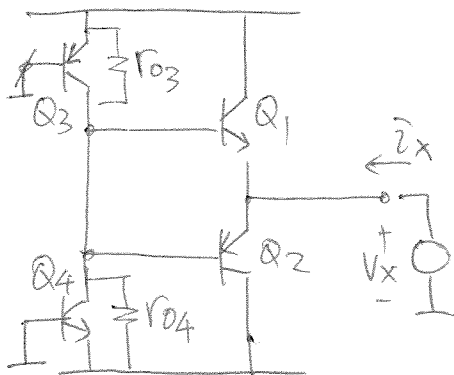

\Rightarrow

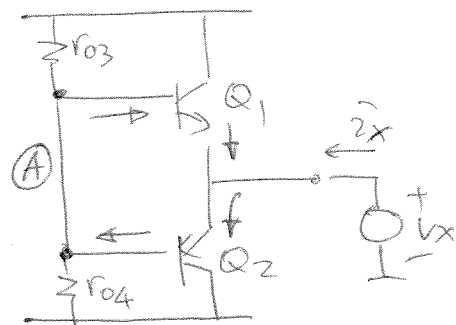

$$V_{eb} = V_x \frac{(r_{\pi 1} \parallel r_{\pi 2})}{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{o3} \parallel r_{o4})}$$

$$V_{be} = V_A - V_x$$

$$\bar{i}_x + \bar{i}_{c1} = \bar{i}_{c2} \Rightarrow \bar{i}_x = \bar{i}_{c2} - \bar{i}_{c1} = g_{m2} V_{eb} - g_{m1} V_{be}$$

$$\therefore \bar{i}_x = [g_{m2} + g_{m1}] V_x \frac{(r_{\pi 1} \parallel r_{\pi 2})}{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{o3} \parallel r_{o4})}$$

$$\Rightarrow \frac{V_x}{\bar{i}_x} = R_{out} = \frac{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{o3} \parallel r_{o4})}{[g_{m1} + g_{m2}] (r_{\pi 1} \parallel r_{\pi 2})}$$

$$r_{\pi 1} = \beta_1 \frac{V_T}{I_{C1}} = 130 \Omega$$

$$r_{\pi 2} = \beta_2 \frac{V_T}{I_{C2}} = 65 \Omega$$

$$r_{O3} = \frac{V_{A3}}{I_{C3}} = 10 \text{ k}\Omega$$

$$r_{O4} = \frac{V_{A4}}{I_{C4}} = 15 \text{ k}\Omega$$


$$g_{m1} = 0.31 \text{ S}$$

$$g_{m2} = 0.31 \text{ S}$$

$$\Rightarrow R_{out} = \frac{43.3 + 6000}{(0.62)(43.3)} \approx 6001 \Omega$$

$$(b) \text{ Effective } R_{out} = R_{out,a} \parallel 8 \Omega \approx 8 \Omega.$$
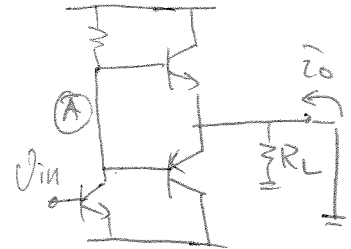
$$\begin{aligned} G_m &= \frac{i_o}{v_A} \cdot \frac{v_A}{v_{in}} \\ &= -g_{m4} (r_{\pi 1} \parallel r_{\pi 2} \parallel r_{O3}) \cdot (g_{m1} + g_{m2}) \end{aligned}$$



$$\begin{aligned} g_{m4} &= \frac{I_{C4}}{V_T} \\ &= 0.038 \text{ S} \end{aligned}$$

$$\therefore A_v = G_m R_{out}$$


$$= -g_{m4} (r_{\pi 1} \parallel r_{\pi 2} \parallel r_{O3}) (g_{m1} + g_{m2}) R_{out}$$

$$= -0.038 [130 \parallel 65 \parallel 10 \text{ k}] [0.62] (8)$$

$$\approx -8.1$$

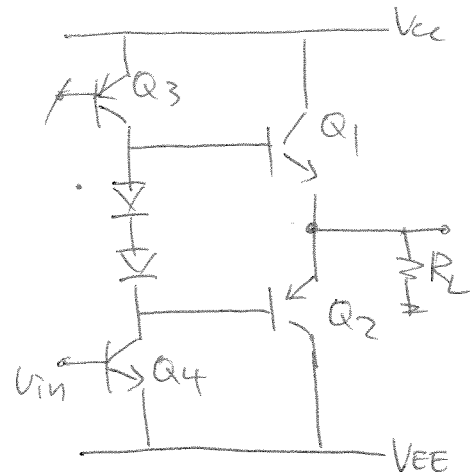35. Max current delivered
by $Q_1 = I_{C3} \beta_1 = 1 \text{ mA} \cdot 40$
 $= 40 \text{ mA}$. (Q_4 off)

Max current delivered
by $Q_2 = I_{C4} \cdot \beta_2$
 $= 1 \text{ mA} \cdot 20$
 $= 20 \text{ mA}$. (Q_3 off)



$$I_{C3} = I_{C4} = 1 \text{ mA}$$


$$\beta_1 = 40 \quad \beta_2 = 20$$

36. $P = 0.5 \text{ W}$ $R_L = 8 \Omega$
 $\beta_1 = 40$ $\beta_2 = 20$.

$$P_{AVG} = \frac{1}{2} \frac{V_p^2}{R_L} = 0.5$$

$$\Rightarrow V_p^2 = 2(0.5)R_L$$
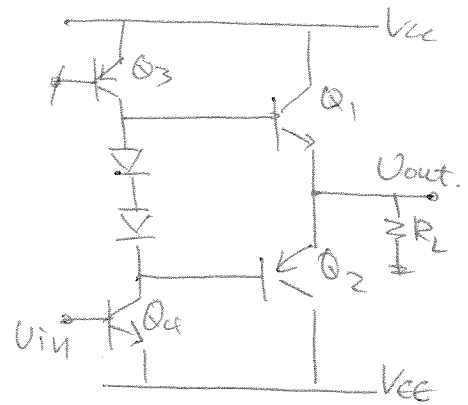
$$\Rightarrow V_p = \sqrt{R_L} = 2\sqrt{2}$$



At positive V_p , $I_{C1} = \frac{V_p}{R_L} = \frac{2\sqrt{2}}{8} = 0.35 \text{ A}$.

At negative V_p , $I_{C2} = \frac{V_p}{R_L} \Rightarrow I_{C2} = 0.35 \text{ A}$.

- At $+V_p$, all of I_{C3} supports the base current of Q_1

$$\Rightarrow I_{C3} = I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{0.35 \text{ A}}{40} = 8.75 \text{ mA}$$

- At $-V_p$, all of I_{C4} supports the base current of Q_2


$$\Rightarrow I_{C4} = I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{0.35 \text{ A}}{20} = 17.5 \text{ mA}$$

37. $P_{AVG} = 0.5 \text{ W}$ $R_L = 8 \Omega$

$V_{CC} = 5 \text{ V}$

$$\Rightarrow 0.5 \text{ W} = \frac{1}{2} \frac{V_p^2}{R_L}$$
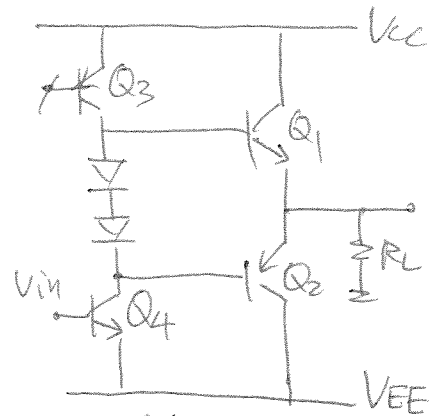
$$\Rightarrow V_p = 2\sqrt{2} \text{ V}$$



(Assume negligible currents at $V_{out} = 0$)

$$P_{Q_1} = \frac{1}{T} \int_0^{T/2} I_{C_1} V_{CE_1} dt$$

$$= \frac{1}{T} \int_0^{T/2} \left(\frac{V_p \sin \omega t}{R_L} \right) (V_{CC} - V_p \sin \omega t) dt$$

$$= \frac{1}{T} \int_0^{T/2} \left[\frac{V_{CC} V_p}{R_L} \sin \omega t - \frac{V_p^2}{2R_L} \right] dt$$

$$= \frac{V_p}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_p}{4} \right) = \frac{2\sqrt{2}}{8} \left(\frac{5}{\pi} - \frac{2\sqrt{2}}{4} \right)$$


$$\approx 0.31 \text{ W}$$

38. $P_{Q,MAX} = 0.75 W$

$R_L = 8 \Omega$

$V_{CC} = 5 V$

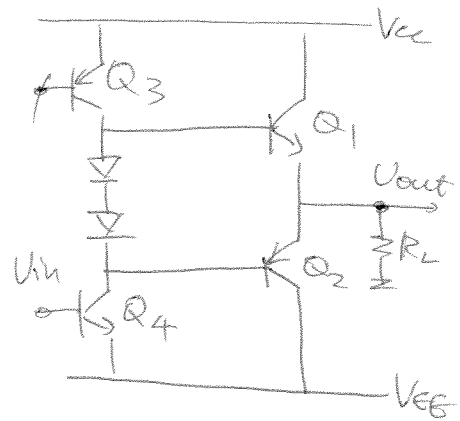- Out of all 4 transistors, Q_1 & Q_2 must sustain the most currents.



$$P_{Q_1,MAX}^{(INST)} = V_{CE} \times I_{C_1,MAX} = (V_{CC} - V_{out}) I_{C_1,MAX}$$

$$\begin{aligned} \Rightarrow P_{Q_1,MAX}^{(AVG)} &= \frac{1}{T} \int_0^{T/2} \frac{V_p \sin \omega t}{R_L} \cdot (V_{CC} - V_p \sin \omega t) dt \\ &= \frac{1}{T} \int_0^{T/2} \left(\frac{V_{CC} V_p}{R_L} \sin \omega t - \frac{V_p^2}{2R_L} \right) dt \\ &= \frac{V_p}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_p}{4} \right) \end{aligned}$$

$$\begin{aligned} \Rightarrow \frac{dP_Q}{dV_p} &= \frac{V_{CC}}{\pi R_L} - \frac{V_p}{2R_L} \\ &= 0 \quad \text{when} \quad V_p = \frac{2V_{CC}}{\pi} = 3.18 V \end{aligned}$$

$$P_Q|_{V_p = \frac{2V_{CC}}{\pi}} = 0.32 W$$

$$\therefore P_{R_L,MAX} = \frac{1}{2} \frac{V_p^2}{R_L} = 0.63 W$$

$$39. P_{Q1, \text{MAX}} = \left(\frac{V_{CC}}{\pi} - \frac{2V_{CC}}{4\pi} \right) \cdot \frac{2V_{CC}}{\pi R_L} \leq 0.75 \text{ W}$$

$$\Rightarrow V_{CC| \text{MAX}} = 7.7 \text{ V}$$


$$\Rightarrow V_{P, \text{MAX}} = \frac{2V_{CC \text{ MAX}}}{\pi} = 4.9 \text{ V}$$

$$\Rightarrow P_{R_L, \text{MAX}} = \frac{1}{2} \frac{V_{P \text{ MAX}}^2}{R_L} = 1.5 \text{ W}$$

$$\begin{aligned}
 40. \quad I_1 &= I_{C1} + I_{E2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{C2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{B1} \\
 &= \beta_1 I_{B1} + \frac{\beta_1 + 1}{\beta_1} I_{B1}
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow I_{B1} &= \frac{I_1}{\beta_1 + \frac{\beta_1 + 1}{\beta_1}} = \frac{0.005}{40 + \frac{41}{40}} \\
 &\approx 0.12 \text{ mA}
 \end{aligned}$$
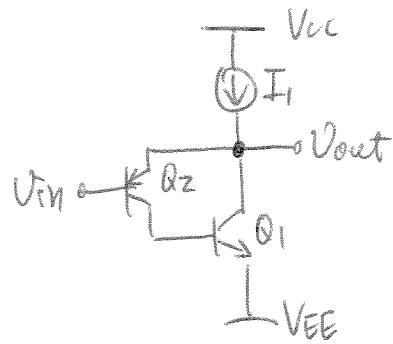
$$\Rightarrow I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{I_{B1}}{\beta_2} = 0.0024 \text{ mA}$$




$$\begin{aligned}
 I_1 &= 5 \text{ mA} \\
 \beta_1 &= 40 \\
 \beta_2 &= 50
 \end{aligned}$$

41. $V_{in} = 0.5 \text{ V}$
 $I_{S2} = 6 \cdot 10^{-17} \text{ A}$


$$I_{B1} = I_{C2} = 0.12 \text{ mA}$$

$$\Rightarrow I_{C2} = I_{S2} \cdot \exp\left(\frac{V_{out} - V_{in}}{V_T}\right)$$
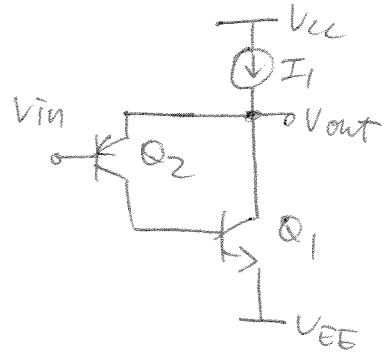
$$\begin{aligned} \therefore V_{out} &= V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right) + V_{in} \\ &= 0.026 \ln\left(\frac{0.12 \text{ mA}}{6 \cdot 10^{-17} \text{ A}}\right) + 0.5 \\ &\approx 1.24 \text{ V} \end{aligned}$$



42.

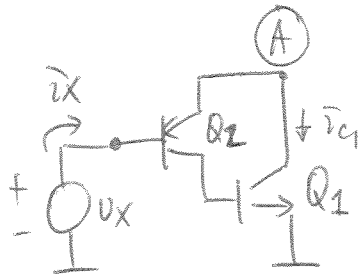

$$\bar{u}_2 = \bar{v}_x \beta_2$$

$$\bar{u}_1 = -g_{m2} \bar{v}_{eb2} = \bar{v}_{e2} = \bar{v}_{c2} + \bar{v}_{b2} = \bar{v}_x (\beta_2 + 1)$$


$$\bar{v}_{eb2} = \bar{v}_A - \bar{v}_x$$

$$\text{where } \bar{v}_A = \bar{v}_x - \bar{v}_x r_{\pi 2}$$

$$\therefore \bar{v}_{b1} = -g_{m2} (\bar{v}_x \cdot r_{\pi 2})$$

$$\bar{v}_{c1} = \bar{v}_{b1} + \bar{v}_{b1} \beta_1 = -g_m \bar{v}_x \cdot r_{\pi 2} (1 + \beta_1)$$
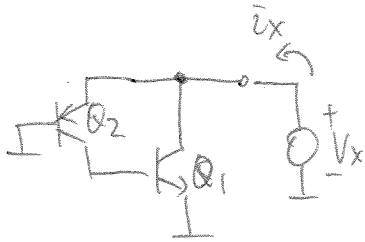
$$\Rightarrow \frac{\bar{v}_x}{\bar{i}_x} \rightarrow \infty \quad (R_{in})$$



$$\bar{v}_x = \bar{v}_{e2} + \bar{v}_{c1}$$

$$= \bar{v}_{e2} + \bar{v}_{b1} \beta_1$$

$$= \bar{v}_{e2} + \bar{v}_{c2} \beta_1$$

$$= \bar{v}_{c2} + \bar{v}_{b2} + \bar{v}_{c2} \beta_1$$

$$= \bar{v}_{c2} (1 + \beta_1 + \frac{1}{\beta_1})$$

$$= \bar{v}_x g_{m2} (1 + \beta_1 + \frac{1}{\beta_1})$$

$$\Rightarrow R_{out} = \frac{\bar{v}_x}{\bar{i}_x} = \frac{1}{g_{m2} (1 + \beta_1 + \frac{1}{\beta_1})}$$

$$= 0.005 \Omega$$

$$g_{m2} = \frac{I_{B2} \beta_2}{V_T}$$

$$= 4.6 \text{ S}$$

43. $R_{out} = 1 \Omega$.

$\beta_1 = 40 \quad \beta_2 = 50$.

$$R_{out} = 1 = \frac{1}{g_{m2} (1 + \beta_1 + \frac{1}{\beta_1})}$$

$$\Rightarrow g_{m2} = 0.024 \text{ S} = \frac{I_{B2} \beta_2}{V_T}$$

$$\Rightarrow I_{B2} = 0.012 \text{ mA}$$


$$I_1 = I_{C1} + I_{E2} = I_{B1} \beta_1 + (I_{C2} + I_{B2})$$

$$= I_{C2} \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= I_{B2} \beta_2 \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= 0.012 [50 \times 40 + 50 + 1]$$

$$= 25.6 \text{ mA}$$

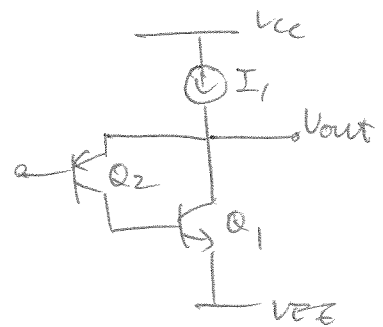


44. $V_p = 0.5V$
 $R_L = 8\Omega$

$$P_{R_L} = \frac{V_p^2}{2R_L} = \frac{0.25}{16} = 0.0156 \text{ W}$$

$$P_I = -I \times V_{EE} = 0.14 \text{ W}$$

$$P_{Q_1} = I_1 \left(V_{CC} - \frac{V_p}{2} \right) = 0.1225 \text{ W}$$
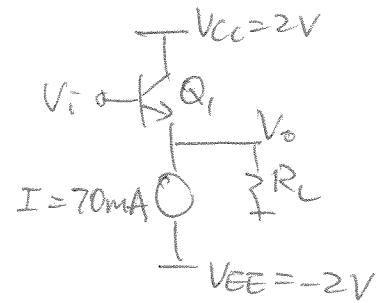
$$\therefore \eta = \frac{P_{R_L}}{P_{R_L} + P_I + P_{Q_1}} = \frac{0.0156}{0.2781} = 5.6\%$$



$$45. P_{R_L} = \frac{V_P^2}{2R_L} = \frac{(V_{CC} - V_{BE})^2}{2R_L}$$

$$P_{Q_1} = I_1 \left(V_{CC} - \frac{V_{CC} - V_{BE}}{2} \right)$$

$$P_I = +I_1 |V_{EE}|$$

• Assume

$$|V_{CC}| = |V_{EE}|,$$

$$I_1 = V_P / R_L = \frac{V_{CC} - V_{BE}}{R_L}$$

$$\begin{aligned} \therefore \eta &= \frac{P_{R_L}}{P_{R_L} + P_{Q_1} + P_I} = \frac{\frac{(V_{CC} - V_{BE})^2}{2R_L}}{\frac{(V_{CC} - V_{BE})^2}{2R_L} + I_1 \left[V_{CC} - \frac{V_{CC} - V_{BE}}{2} + |V_{EE}| \right]} \\ &= \frac{\frac{1}{2R_L}}{\frac{1}{2R_L} + \frac{3V_{CC} - V_{BE}}{2R_L(V_{CC} - V_{BE})}} \\ &= \frac{1}{1 + \frac{3V_{CC} - V_{BE}}{V_{CC} - V_{BE}}} \approx \frac{V_{CC} - V_{BE}}{3V_{CC} - V_{BE}} \end{aligned}$$

$$46. \eta = \frac{\frac{V_P^2}{2R_L}}{\frac{V_P^2}{2R_L} + \frac{2V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)}$$

$$= \frac{\pi}{4} \frac{V_P}{V_{CC}}$$

$$\Rightarrow \eta|_{V_P=V_{CC}-V_{BE}} = \frac{\pi}{4} - \frac{\pi}{4} \cdot \frac{V_{BE}}{V_{CC}}$$

$$\begin{aligned}
 47. \quad \eta &= \frac{\frac{(V_p/2)^2}{2R_L}}{\frac{(V_p/2)^2}{2R_L} + \frac{2(V_p/2)}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_p/2}{4} \right)} \\
 &= \frac{V_p^2/8R_L}{\frac{V_p^2}{8R_L} + \frac{V_p}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_p}{8} \right)} = \frac{1/8R_L}{1/8R_L + \frac{1}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{1}{8} \right)} \\
 &= \frac{1}{1 + \left(\frac{8V_{CC}}{V_p\pi} - 1 \right)} = \frac{\pi}{8} \frac{V_p}{V_{CC}} \approx 39\%.
 \end{aligned}$$

$$48. \quad V_{CC} = 3V \quad P_{R_L} = 0.2W \quad R_L = 8\Omega.$$

$$P_{R_L} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = \sqrt{2P_{R_L} \times R_L} = 1.8V$$

$$\therefore \eta = \frac{P_{R_L}}{P_{R_L} + \frac{2V_p}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_p}{4} \right)} = \frac{0.2}{0.2 + \frac{3.6}{8} \left(\frac{3}{\pi} - \frac{1.8}{4} \right)}$$

$$\approx 18\%.$$


49. Power = 1 W
 $R_L = 8\Omega$

$$P_{LOAD} = \frac{1}{2} \frac{V_P^2}{R_L} = 1W$$

$$\Rightarrow V_P = 4V \Rightarrow I_1 = \frac{V_P}{R_L} = 0.5mA$$

(Note: the problem does not specify small-signal voltage gain, so choose $V_P = I_1 R_L$)
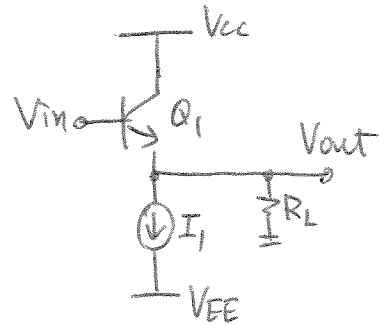
$$\begin{aligned} P_{Q_1} (\text{power rating}) &= I_1 (V_{CC}) \\ &= (0.5mA)(5V) \\ &= 2.5mW \end{aligned}$$



50. $A_v = 0.8$
 $R_L = 4 \Omega$


$$A_v = \frac{R_L}{R_L + \frac{1}{g_{m_1}}} = \frac{4}{4 + \frac{0.026}{I_{C_1}}} = 0.8$$

$$\Rightarrow I_{C_1} = 26 \text{ mA}$$

$$\therefore I_1 = I_{C_1} = 26 \text{ mA} \quad (V_{out} \text{ biased at } 0 \text{ V.})$$

$$\begin{aligned} \text{Max Output Swing} &= I_1 R_L \\ &\approx (26 \text{ mA})(8 \Omega) \\ &= 0.208 \text{ V} \end{aligned}$$
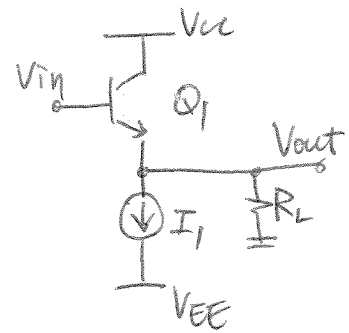
$$\begin{aligned} P_{Q_1} (\text{power rating}) &= I_1 V_{CC} (V_p = 0) \\ &= (26 \text{ mA})(5 \text{ V}) = 130 \text{ mW} \end{aligned}$$




51. $A_v = 0.6$
 $R_L = 8 \Omega$
 $r_{D1} = r_{D2} = 0$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_{m1}}} = \frac{(8\Omega)}{(8\Omega) + \frac{0.026V}{I_{Q1}}}$$

$$= 0.6$$
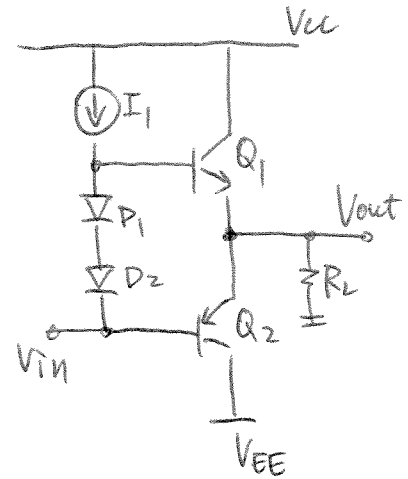
$$\Rightarrow I_{Q1} = I_{Q2} = 4.8 \text{ mA}$$



(V_{out} biased at $0V$.)

52. Power = 1 W (to load)

$$R_L = 8\Omega$$

$$|V_{BE}| \approx 0.8 \text{ V}$$

$$\beta_1 = 40$$

$$P_L = \frac{1}{2} \frac{V_p^2}{R_L} = 1 \text{ W}$$


$$\Rightarrow V_p = 4 \text{ V}$$

\therefore Min allowable supply = $V_p + |V_{BE}| = 4.8 \text{ V}$
voltage

• At $+V_p$, all of I_1 goes to base of Q_1

$$\Rightarrow I_1 = I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{V_p}{R_L} \cdot \frac{1}{\beta_1} \quad (Q_2 \text{ off})$$
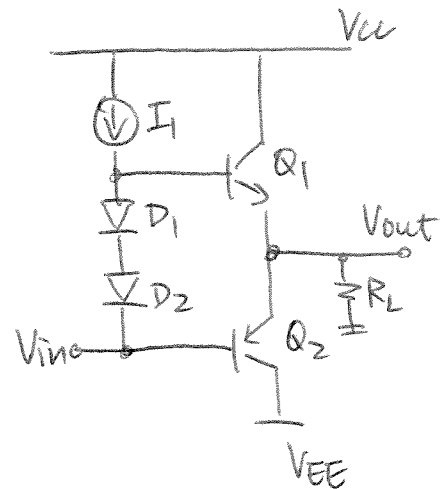
$$= \frac{4}{8} \cdot \frac{1}{40} = \frac{1}{80} = 12.5 \text{ mA}$$



53. $P_{Q, \text{MAX}} = 2 \text{ W}$
 $R_L = 8 \Omega$.


For this circuit,

$$P_{\text{AVG}, \text{MAX}} = \frac{V_{cc}^2}{\pi^2 R_L} \quad \left(V_p = \frac{2V_{cc}}{\pi} \right)$$

$$= 2 \text{ W}$$

$$\Rightarrow V_{cc}|_{\text{MAX}} = 12.6 \text{ V} \Rightarrow V_p|_{\text{MAX}} = \frac{2 \cdot 12.6}{\pi} = 8.02 \text{ V}$$
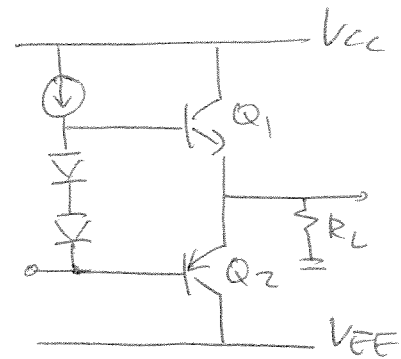
$$\therefore P_{R_L \text{ MAX}} = \frac{V_{p \text{ MAX}}^2}{2R_L} = \frac{(8.02)^2}{2 \cdot 8} = 4.02 \text{ W}$$



54. For this circuit,

$$P_{Q,MAX} = 2W$$

$$R_L = 4\Omega$$

$$P_{AVG,MAX} = \frac{V_{CC}^2}{2R_L} \quad \left(V_p = \frac{2V_{CC}}{\pi} \right)$$

$$\Rightarrow V_{CC,MAX} = \sqrt{\frac{\pi^2 R_L P_{Q,MAX}}{1}} = 8.9 V$$

$$\Rightarrow V_{p,MAX} = \frac{2V_{CC,MAX}}{\pi} = 5.6 V$$

$$\therefore P_{R_L,MAX} = \frac{V_{p,MAX}^2}{2R_L} = \frac{32}{2(4)} = 4W$$

$$55. \quad A_v = 4 \quad R_L = 8\Omega \quad I_{C1} \approx I_{C2}$$

$$\beta_1 = 40 \quad \beta_2 = 20$$

Suppose we want 1st-stage (CE amplifier) to have gain = 5 \Rightarrow 2nd stage gain = 0.8.

$$\Rightarrow 0.8 = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$0.8 = \frac{8}{8 + \frac{1}{2g_{m1}}} \Rightarrow g_{m1} = 5' \Rightarrow I_{C1} = I_{C2} = 6.5 \text{ mA}$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = \frac{40(0.026)}{6.5 \text{ mA}} \parallel \frac{20(0.026)}{6.5 \text{ mA}} \approx 133\Omega$$

$$\bullet \quad A_v = 4 = g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$= \frac{I_{C4}}{V_T} (133) (0.5) 8$$

$$\Rightarrow I_{C4} = I_{C3} = \frac{4 V_T}{8 (133) (0.5)} = 0.195 \text{ mA}$$

Max I_{Q1} when all of I_{C3}/I_{C4} supports base current of Q_1

$$\Rightarrow I_{Q1, \text{MAX}} = I_{C4} = 0.195 \text{ mA}$$

56. $A_v = 4$ $R_L = 4 \Omega$ $I_{C1} \approx I_{C2}$
 $\beta_1 = 40$ $\beta_2 = 20$

1st stage gain = 5 (CE amplifier)

2nd " " = 0.8

$$0.8 = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} = \frac{4}{4 + \frac{1}{2g_{m1}}}$$

$$\Rightarrow g_{m1} = 0.5 \text{ S} \Rightarrow I_{C1} = I_{C2} = 13 \text{ mA}$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = 80 \parallel 40 = 26.7 \Omega$$


$$\begin{aligned} A_v = 4 &= g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L \\ &= \frac{I_{C4}}{V_T} (26.7) (1) (4) \end{aligned}$$

$$\Rightarrow I_{C4} = I_{E3} = \frac{4 V_T}{(26.7)(1)(4)} = 0.974 \text{ mA}$$

• Max I_{Q1} ($I_{Q1, \text{MAX}}$) when $I_{C4} = I_{Q, \text{MAX}} = 0.974 \text{ mA}$.

• For a reduction of 2x the R_L , we have to provide $\sim 5x$ current to base of Q_1 . ($\frac{0.974}{0.195} \approx 5$)

57. $P_{RL} = 2W$ $\beta_1 = 40$
 $R_L = 8\Omega$ $\beta_2 = 20$
 $|V_{BE}| = 0.8V$

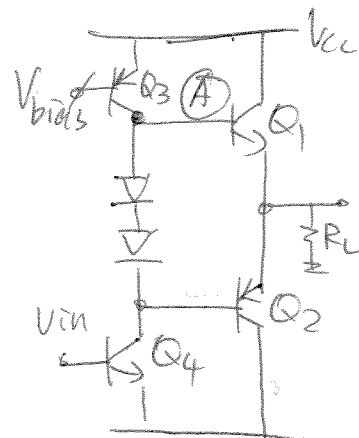

(a) $P_{RL} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p \approx 5.6V$

• At $+V_p$, $V_A = V_p + |V_{BE}|$.

• For Q_3 in active region, $V_A \leq V_{bias}$

$$\Rightarrow V_{CC} \geq V_{bias} + |V_{BE}| = V_p + 2|V_{BE}|$$

$$\geq 5.6 + 1.6 = 7.2V.$$

(b) $I_p = \frac{V_p}{R_L} = 0.7A. (= I_{E1}), (= I_{E2})$

$$\Rightarrow I_{B1} = \frac{I_{E1}}{1 + \beta_1} = 17mA.$$

\therefore We bias Q_3 & Q_4 with $I_C = 17mA$.

$$\begin{aligned}
 (c) \quad P_{AV} &= \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right) \\
 &= \frac{5.6}{8} \left(\frac{5}{\pi} - \frac{5.6}{4} \right) = 3.66 \text{ W}
 \end{aligned}$$

$$(d) \quad P_{I_{Q3}} = 2V_{CC} \times I_{Q3} = 10 \times 17 \text{ mA} = 170 \text{ mW}$$

$$P_{AV, Q_1} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right) = 3.66 \text{ W}$$

$$P_{R_L} = 2 \text{ W}$$

$$\Rightarrow \eta = \frac{P_{R_L}}{P_{I_{Q3}} + 2 \cdot P_{AV, Q_1} + P_{R_L}}$$

$$= \frac{2}{170 \text{ m} + 3.66 \times 2 + 2} = 0.21 = 21\%$$

58.


(a) $A_v = 5$ $R_L = 4\Omega$ $\beta_1 = 40$ $\beta_2 = 20$.

Assume $I_{C1} \approx I_{C2}$.

$$\frac{V_{out}}{V_{in}} = \frac{R_L}{(g_{m1} + g_{m2})^{-1} + R_L} = 0.8$$

$$\Rightarrow 2g_{m1}^{-1} = 1 \Rightarrow I_{C1} = 2V_T$$

$$= 0.052 \text{ A.}$$

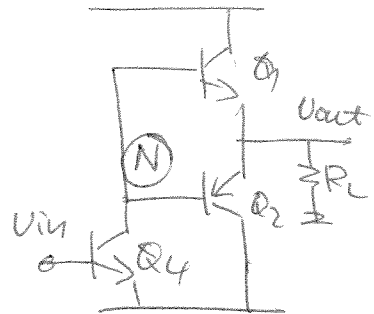

$$\Rightarrow \frac{V_{out}}{V_{in}} = +g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L = 5$$

Assume $g_{m1} \approx g_{m2}$:

$$\Rightarrow I_{C4} = V_T \frac{5}{(r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L}$$

$$= V_T \times \frac{5}{(r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} \times 2) R_L}$$

$$= 0.026 \frac{5}{(6.7\Omega) (2 \times 2 \times 4)}$$

$$\approx 1.2 \text{ mA.}$$

$$\Rightarrow \text{Max } I \text{ by } Q_1 = \beta_1 \times I_{C4} = 48 \text{ mA}$$

$$\Rightarrow P_{R_L} = \frac{1}{2} I^2 R_L = 24 \times 4 \text{ mW} = 96 \text{ mW, BELOW requirement!}$$

$$(b) \quad P = 5 \text{ W} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = 6.3 \text{ V}$$

$$\Rightarrow I_p = \frac{V_p}{R_L} = 1.6 \text{ A}$$

$$\Rightarrow I_{B2, \text{MAX}} = \frac{I_p}{\beta_2} = \frac{1.6}{20} = 79 \text{ mA}$$

$\Rightarrow I_{C2}$ must equal 79 mA to allow max output swing V_p

$$\Rightarrow g_{m4} = \frac{I_{C4}}{V_T} = 3.04 \text{ S}$$

Suppose 2nd stage gain = 0.8 ($I_{C1} = I_{C2}$)

$$\Rightarrow \frac{v_{out}}{v_{in}} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \Rightarrow g_{m1} = 0.5 \text{ S}$$

$$\Rightarrow I_{C1} = I_{C2} = 13 \text{ mA}$$

$$= 0.8$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = 26.7 \Omega$$

$$\therefore \frac{v_{out}}{v_{in}} = -(3.04)(26.7 \Omega)(0.5 + 0.5)4$$

$$= -324 !! \text{ (Huge! Impractical)}$$

• Even when the 2nd stage gets close to 1, we still need huge gain from first stage.