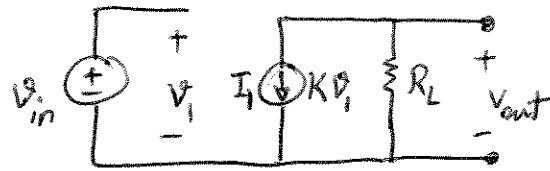


chapter 4

4.1



$$K = 20 \text{ mA/V}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = 15 \quad v_{in} = v_1$$


$$v_{out} = -I_1 R_L = -K R_L v_{in}$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = -K R_L \Rightarrow \left| \frac{v_{out}}{v_{in}} \right| = K R_L$$

$$\Rightarrow K R_L = 15 \Rightarrow R_L = \frac{15}{20 \text{ mA/V}} = 750 \Omega$$

$$\boxed{R_L = 750 \Omega}$$

4.2

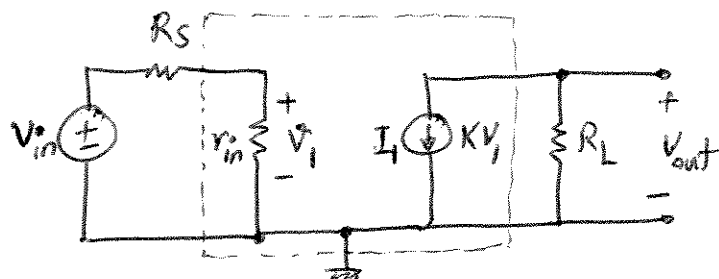

$$\frac{V_{out}^*}{V_{in}^*} = ?$$

$$V_1 = \frac{r_{in}}{r_{in} + R_S} V_{in}^*$$

$$I_1 = K V_1$$

$$V_{out}^* = -R_L I_1$$

$$\left. \begin{array}{l} V_1 = \frac{r_{in}}{r_{in} + R_S} V_{in}^* \\ I_1 = K V_1 \\ V_{out}^* = -R_L I_1 \end{array} \right\} \Rightarrow V_{out}^* = -K R_L \frac{r_{in}}{r_{in} + R_S} V_{in}^*$$

$$\Rightarrow A_V = \frac{V_{out}^*}{V_{in}^*} = -K R_L \frac{r_{in}}{r_{in} + R_S}$$

4.3 From solution for problem 4.2,

$$a > 0$$


$$b > 0$$

$$x \geq 0$$

$$A_v = -K R_L \frac{r_{in}}{r_{in} + R_S}$$

$$\frac{r_{in} = a/x}{K = bx} \rightarrow A_v = -bx R_L \frac{a/x}{a/x + R_S} = -b R_L \frac{a}{\frac{a}{x} + R_S}$$
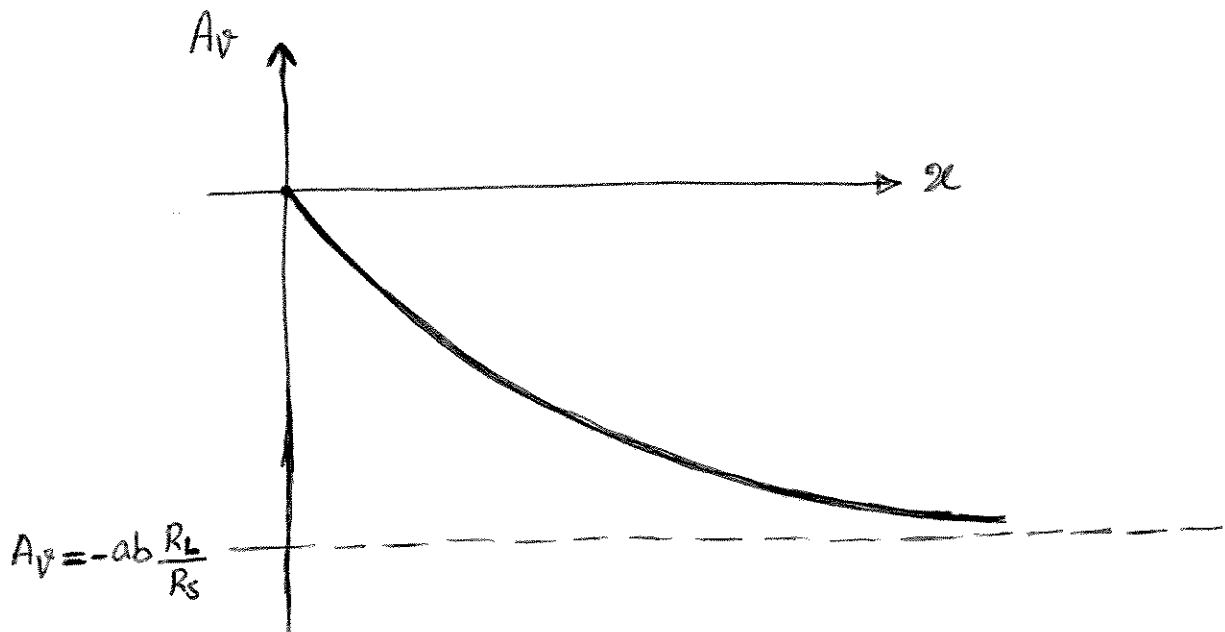
$$\Rightarrow A_v = -b R_L \left(\frac{x}{1 + \frac{R_S}{a} x} \right)$$




4.4) From equation (4.8) page 136,

$$I_C = \frac{A_E q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE}}{V_T}} \quad W_B \equiv \text{width of the Base}$$

if $W_B \uparrow 2 \Rightarrow I_C \downarrow 2$

Collector current decreases by a factor of two

4.5

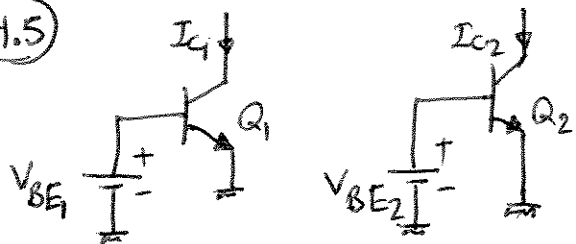

$$V_T = 26 \text{ mV}$$

$$I_{C1} = I_{C2}$$

$$V_{BE1} - V_{BE2} = 20 \text{ mV}$$

$$I_C = \frac{A_E q D_n n_i^2}{N_E W_B} \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \quad \text{equation (4.8) page 136}$$

$$\Rightarrow I_C \approx \frac{A_E q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE}}{V_T}} \quad A_E \equiv \text{Cross Section}$$

if $I_{C1} = I_{C2}$

$$\Rightarrow \cancel{A_{E1}} \frac{q D_n n_i^2}{\cancel{N_E W_B}} e^{\frac{V_{BE1}}{V_T}} = \cancel{A_{E2}} \frac{q D_n n_i^2}{\cancel{N_E W_B}} e^{\frac{V_{BE2}}{V_T}}$$

$$\Rightarrow \frac{A_{E2}}{A_{E1}} = \frac{e^{V_{BE1}/V_T}}{e^{V_{BE2}/V_T}}$$

$$\Rightarrow \frac{A_{E2}}{A_{E1}} = e^{(V_{BE1} - V_{BE2})/V_T} = e^{\frac{20 \text{ mV}}{26 \text{ mV}}}$$

$$\Rightarrow \boxed{\frac{A_{E2}}{A_{E1}} = e^{\frac{20}{26}} \approx 2.16}$$

$$\textcircled{6a} \quad I_x = 1^{\text{mA}} \Rightarrow I_{Q_1} = I_{Q_2} = 0.5^{\text{mA}}$$

$$I_{Q_1} = I_{S_1} e^{\frac{V_{BE1}}{V_T}} \Rightarrow 5 \times 10^{-4} = 3 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}}$$

$$\Rightarrow V_B = 26^{\text{mV}} \ln\left(\frac{5}{3} \times 10^{12}\right) \Rightarrow$$

$$\boxed{V_B \approx 731.7^{\text{mV}}}$$

$$\textcircled{6b} \quad I_y = I_{S_3} e^{\frac{V_B}{V_T}}$$

$$\Rightarrow I_{S_3} = I_y e^{-\frac{V_B}{V_T}} = 2.5 \times 10^{-3} \times e^{-\frac{V_B}{26 \text{ mV}}} = 2.5 \times 10^{-3} \times \frac{1}{\frac{5}{3} \times 10^{12}}$$

$$\Rightarrow \boxed{I_{S_3} = 1.5 \times 10^{-15} \text{ A}}$$

$$(7a) \quad I_x = I_1 + I_2$$

$$\Rightarrow I_x = I_{s1} e^{\frac{V_B}{V_T}} + I_{s2} e^{\frac{V_B}{V_T}} \Rightarrow I_x = (I_{s1} + I_{s2}) e^{\frac{V_B}{V_T}}$$

$$\Rightarrow V_B = V_T \ln \left(\frac{I_x}{I_{s1} + I_{s2}} \right) \xrightarrow{I_{s1} = 2I_{s2}} \boxed{V_B = V_T \ln \left(\frac{I_x}{\frac{3}{2} I_{s1}} \right)}$$

$$V_B = 26 \times 10^{-3} \ln \left(\frac{1.2 \times 10^{-3}}{\frac{3}{2} \times 5 \times 10^{-16}} \right) \Rightarrow \boxed{V_B \approx 730.6 \text{ mV}}$$

$$(7b) \quad \text{Transistors at the edge of the active mode} \Rightarrow V_C = V_B$$

applying KVL, we have:

$$V_{CC} = R_C I_x + V_B \Rightarrow \boxed{R_C = \frac{V_{CC} - V_B}{I_x}}$$

$$\Rightarrow R_C = \frac{2.5 - 0.73}{1.2 \times 10^{-3}}$$

$$\Rightarrow \boxed{R_C \approx 1475 \, \Omega}$$

⑧a Same as 7a,

$$V_B \approx 730.6 \text{ mV}$$

⑧b According to 7b,

$$R_C = \frac{V_{CC} - V_B}{I_X} = \frac{1.5 - 0.73}{1.2 \times 10^{-3}}$$

$$\Rightarrow R_C \approx 642 \, \Omega$$

④ Q_1 is at the edge of the active region $\Rightarrow V_C = V_B$


applying KVL, we have:

$$V_{CC} = R_C I_C + V_C$$

$$\xRightarrow{V_C = V_B} V_{CC} = R_C I_C + V_B$$

$$\Rightarrow V_{CC} = R_C I_S e^{\frac{V_B}{V_T}} + V_B$$
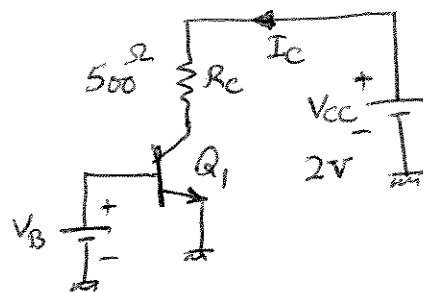
$$\Rightarrow 500 \Omega \times 5 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}} + V_B = 2 \text{ V}$$



Using numerical methods or simply, trial & error:



$$\boxed{V_B \approx 760 \text{ mV}}$$

⑩ Q_1 at the edge of saturation $\Rightarrow V_C = V_B$

Hence: $V_{CC} = R_C I_C + V_B$

$$\Rightarrow V_{CC} = R_C I_S e^{\frac{V_B}{V_T}} + V_B$$

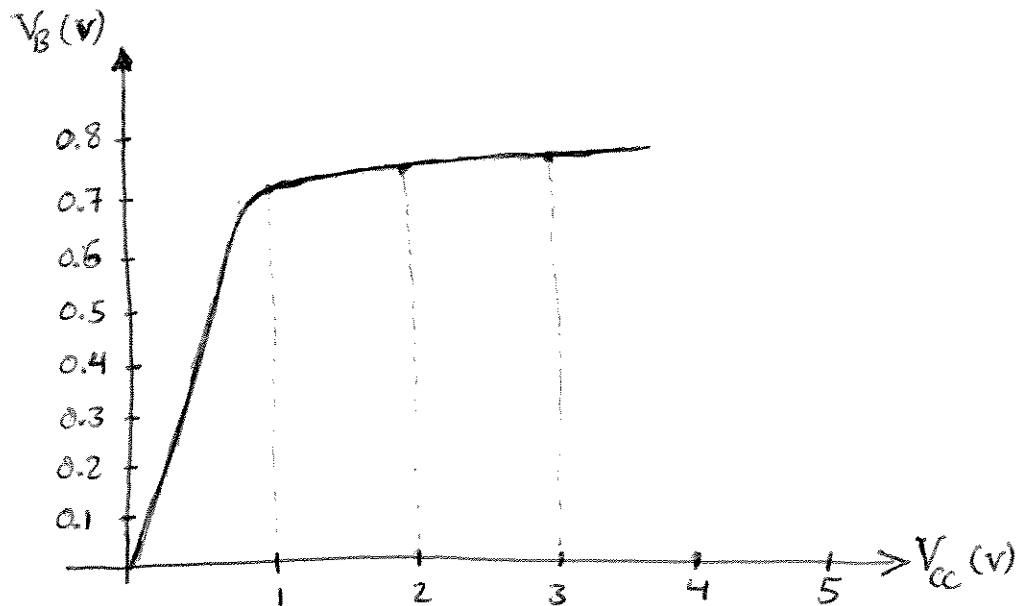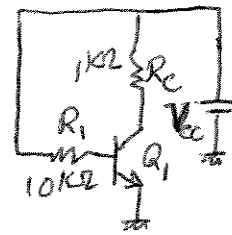$I_S = 3 \times 10^{-16} \text{ A}$ \rightarrow $V_{CC} = 3 \times 10^{-13} e^{\frac{V_B}{V_T}} + V_B$ $\xrightarrow[\text{with } V_{CC} = 2\text{V}]{}$ $V_B \approx 755 \text{ mV}$



⑪ Assuming $I_E \approx I_C$, we can write:

$$\text{Applying KVL: } 1.5V = V_{BE} + V_X \text{ where } V_X = 1^{k\Omega} \times I_E$$


$$\text{Hence: } 1.5 = V_{BE} + 1^{k\Omega} \times I_C$$

$$\Rightarrow 1.5 = V_{BE} + 1^{k\Omega} \times I_S e^{\frac{V_{BE}}{V_T}}$$

$$\frac{I_S = 6 \times 10^{-16} A}{V_T = 26 mV} \quad 1.5 = V_{BE} + 6 \times 10^{-13} e^{\frac{V_{BE}}{26 mV}} \Rightarrow \boxed{V_{BE} \approx 724.5 mV}$$

$$V_X = 1.5 - V_{BE} \Rightarrow \boxed{V_X \approx 775.5 mV}$$

(12)

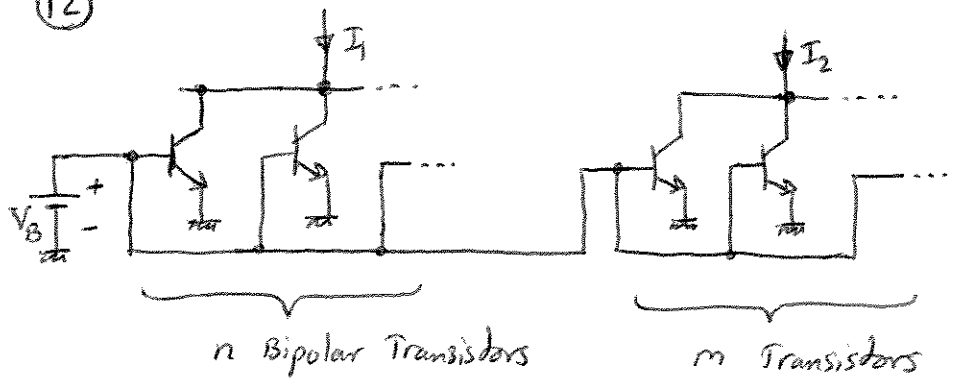

$$\left. \begin{aligned} I_1 &= n I_C = n I_S e^{\frac{V_B}{V_T}} \\ I_2 &= m I_C = m I_S e^{\frac{V_B}{V_T}} \end{aligned} \right\} \Rightarrow \frac{I_1}{I_2} = \frac{n}{m}$$

$$\Rightarrow \frac{n}{m} = \frac{1 \text{ mA}}{1.5 \text{ mA}} = \frac{2}{3} \quad \xrightarrow{\text{choose}} \quad \boxed{\begin{matrix} n=2 \\ m=3 \end{matrix}}$$

$$I_1 = n I_C = n I_S e^{\frac{V_B}{V_T}}$$

$$\Rightarrow I_1 = n \times 3 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}} = 1 \text{ mA} \quad n=2 \quad \Rightarrow \quad \boxed{V_B \approx 750 \text{ mV}}$$

⑬ Using the same technique as in ^{problem} 12, we have:

$$\frac{n_1}{I_1} = \frac{n_2}{I_2} = \frac{n_3}{I_3}$$

$$\Rightarrow \frac{n_1}{0.2} = \frac{n_2}{0.3} = \frac{n_3}{0.45} \Rightarrow \boxed{\frac{n_1}{4} = \frac{n_2}{6} = \frac{n_3}{9}}$$

$$\text{So let's choose } \begin{cases} n_1 = 4 \\ n_2 = 6 \\ n_3 = 9 \end{cases}$$


Hence,

$$I_1 = n_1 I_s e^{\frac{V_B}{V_T}} \Rightarrow 0.2 \times 10^{-3} = 4 \times 3 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}}$$

$$\Rightarrow \boxed{V_B \approx 672 \text{ mV}}$$

⑭ From KVL,

$$V_B = R_1 I_B + V_{BEQ_1}$$

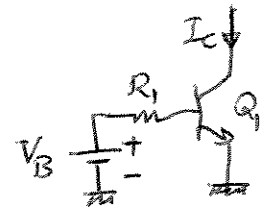

$$I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{100} \Rightarrow \boxed{I_B = 10^{-5} \text{ A}}$$

$$V_{BEQ_1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \times 10^{-3} \ln\left(\frac{10^{-3}}{7 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{BEQ_1} \simeq 727.7 \text{ mV}}$$

Therefore,

$$V_B = R_1 I_B + V_{BEQ_1}$$

$$\simeq 10 \times 10^{-5} \text{ A} + 728 \times 10^{-3}$$

$$\Rightarrow V_B \simeq 0.1 + 0.728 \Rightarrow \boxed{V_B \simeq 0.828 \text{ V}}$$

⑤ According to the solution for problem 14, we have:

$$\text{Applying KVL: } V_B = R_B I_B + V_{BE}$$

$$\Rightarrow V_B = R_B \frac{I_C}{\beta} + V_T \ln\left(\frac{I_C}{I_S}\right)$$


$$\Rightarrow 0.8 = 10^4 \times \frac{I_C}{100} + 26 \times 10^{-3} \ln\left(\frac{I_C}{7 \times 10^{-16}}\right)$$

$$\Rightarrow 0.8 = 100 I_C + 26 \times 10^{-3} \ln\left(\frac{I_C}{7 \times 10^{-16}}\right)$$

using trial & error or numerical methods,

$$\boxed{I_C \approx 7.85 \times 10^{-4} \text{ A} = 785 \mu\text{A}}$$
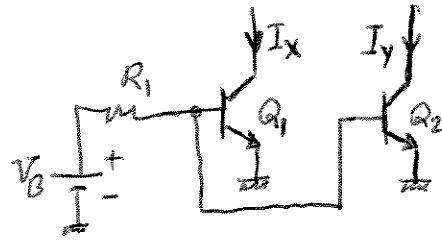
$$\textcircled{16} \begin{cases} I_x = I_{S1} \exp\left(\frac{V_{BE1}}{V_T}\right) \\ I_y = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right) \\ V_{BE1} = V_{BE2} = V_{BE} \end{cases}$$



$$\Rightarrow \frac{I_x}{I_y} = \frac{I_{S1}}{I_{S2}} = \frac{2I_{S2}}{I_{S2}} \Rightarrow \boxed{\frac{I_x}{I_y} = 2} \quad \begin{cases} I_x = \beta_1 I_{B1} \\ I_y = \beta_2 I_{B2} \\ \beta_1 = \beta_2 \end{cases}$$

$$\Rightarrow \boxed{\frac{I_{B1}}{I_{B2}} = \frac{I_x}{I_y} = 2}$$

Applying KVL:

$$V_B = R_1 (I_{B1} + I_{B2}) + V_{BE}$$

$$V_{BE} = V_{BE1} = V_T \ln\left(\frac{I_x}{I_{S1}}\right) = 26 \text{ mV} \ln\left(\frac{1 \text{ mA}}{4 \times 10^{-16}}\right) \approx 742 \text{ mV}$$

$$I_{B1} = \frac{I_x}{\beta} \xrightarrow{\beta=100} I_{B1} = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}$$

$$\frac{I_{B1}}{I_{B2}} = 2 \longrightarrow I_{B2} = \frac{I_{B1}}{2} = \frac{10 \mu\text{A}}{2} \Rightarrow I_{B2} = 5 \mu\text{A}$$

$$\text{Hence: } V_B = 5 \times 10^3 \Omega \times (10 \mu\text{A} + 5 \mu\text{A}) + 0.742 \text{ V}$$

$$= 0.075 + 0.742 \Rightarrow \boxed{V_B \approx 0.817 \text{ V}}$$

⑪ Applying KVL :

$$V_B = R_1 (I_{B_1} + I_{B_2}) + V_{BE} \xrightarrow{\beta_1 = \beta_2 = \beta} \frac{R_1}{\beta} (I_{C_1} + I_{C_2}) + V_{BE}$$

$$\Rightarrow V_B = \frac{R_1}{\beta} (I_{S_1} + I_{S_2}) \exp\left(\frac{V_{BE}}{V_T}\right) + V_{BE}$$

$$\beta=100 \Rightarrow 0.8^V = \frac{5000^{\Omega}}{100} (3 \times 10^{-16} + 5 \times 10^{-16}) \exp\left(\frac{V_{BE}}{26^{mV}}\right) + V_{BE}$$

$$\Rightarrow 0.8^V = 4 \times 10^{-14} \cdot \exp\left(\frac{V_{BE}}{26^{mV}}\right) + V_{BE}$$

Numerical methods or Trial & error $\Rightarrow \boxed{V_{BE} \approx 732^{mV}}$

$$I_x = I_{S_1} \exp\left(\frac{V_{BE}}{V_T}\right) = 3 \times 10^{-16} \left[\exp\left(\frac{732}{26}\right) \right] \Rightarrow \boxed{I_x \approx 506 \mu A}$$

$$I_y = I_{S_2} \exp\left(\frac{V_{BE}}{V_T}\right) = 5 \times 10^{-16} \exp\left(\frac{732}{26}\right) \Rightarrow \boxed{I_y \approx 843 \mu A}$$

⑮ Since Transistor is in Forward active region,


No change across V_{BE}



No change in I_B



No change in I_C

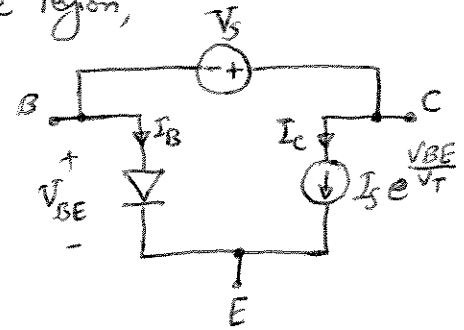

$$(19) \quad g_m = \frac{I_c}{V_T}$$

$$\Rightarrow g_m = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_T} \Rightarrow \boxed{V_{BE} = V_T \ln\left(\frac{g_m V_T}{I_S}\right)}$$

$$\begin{array}{l} I_S = 6 \times 10^{-16} \text{ A} \\ g_m = \frac{1}{13 \Omega} \end{array} \rightarrow V_{BE} = 26 \text{ mV} \cdot \ln\left(\frac{\frac{1}{13 \Omega} \times 26 \times 10^{-3}}{6 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{BE} \approx 750 \text{ mV}}$$

$$\textcircled{20} \quad g_m = \frac{I_C}{V_T}$$

$$\Delta g_m = \frac{\Delta I_C}{V_T} = \frac{1}{V_T} \Delta \left(I_S e^{\frac{V_{BE}}{V_T}} \right) \approx \frac{I_S}{V_T^2} e^{\frac{V_{BE}}{V_T}} \Delta V_{BE}$$

$$\Rightarrow \boxed{\Delta g_m \approx \frac{I_C}{V_T^2} \Delta V_{BE}}$$


$$\Rightarrow \Delta g_m \approx \frac{g_m}{V_T} \Delta V_{BE}$$

$$\Rightarrow \boxed{\frac{\Delta g_m}{g_m} \approx \frac{1}{V_T} \Delta V_{BE}}$$

$$\left. \frac{\Delta g_m}{g_m} \right|_{I_C=1\text{mA}}^{\text{max}} 0.1 \Rightarrow \Delta V_{BE_{\text{max}}} = 0.1 V_T$$

$$\Rightarrow \boxed{\Delta V_{BE} \leq 2.6 \text{ mV}}$$

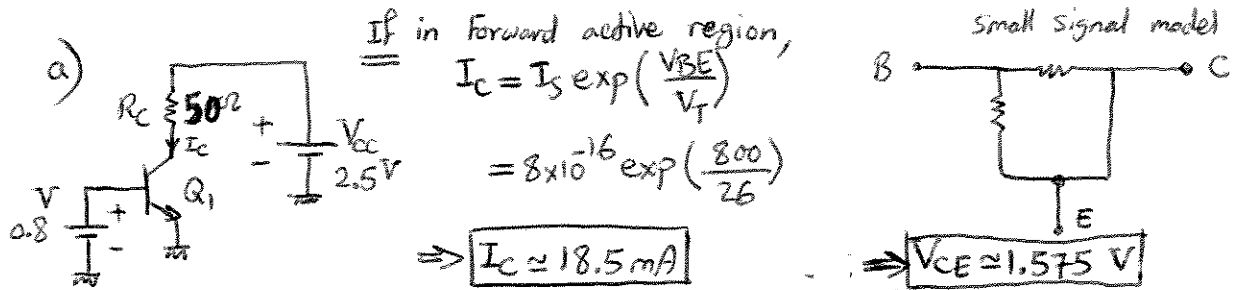
② $V_A = \infty \Rightarrow r_o = \infty$, $I_S = 8 \times 10^{-16} \text{ A}$, $\beta = 100$



Hence Transistor should be in Forward Active



$$I_{CQ} = \frac{V_{CC} - V_{CE}}{R_C} = \frac{2.5 - 1.575}{50} = \frac{0.925}{50} \Rightarrow I_C \approx 18.5 \text{ mA}$$

which matches with I_C

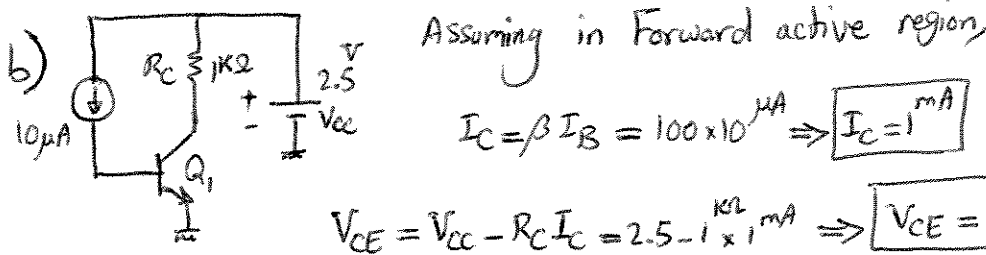

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m = \frac{1}{26} \text{ S}^{-1}$$
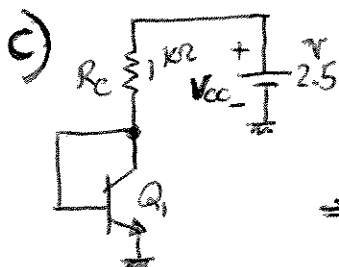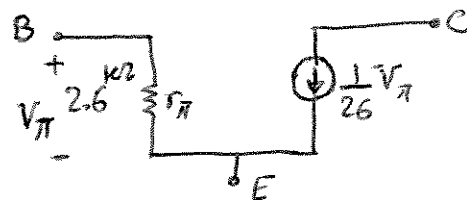
$$r_\pi = \frac{\beta}{g_m} = \frac{100}{1/26} \Rightarrow r_\pi \approx 2600 \Omega$$




Applying KVL,

$$V_{CC} \approx R_C I_C + V_{BE}$$


$$\Rightarrow 2.5 \text{ V} \approx 1 \text{ k} \times I_C + V_{BE}$$

$$\Rightarrow 2.5 \text{ V} \approx 8 \times 10^{-13} \cdot \exp\left(\frac{V_{BE}}{V_T}\right) + V_{BE} \Rightarrow V_{BE} \approx 739 \text{ mV}$$
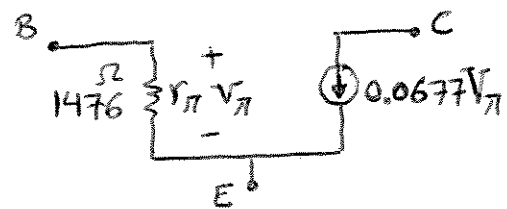
$$g_m = \frac{I_C}{V_T} = \frac{V_{CC} - V_{BE}}{R_C V_T} \Rightarrow g_m = \frac{2.5 - 0.739}{1 \text{ k} \times 0.026} \Rightarrow g_m \approx 67.7 \text{ mS}, I_C \approx 1.76 \text{ mA}$$



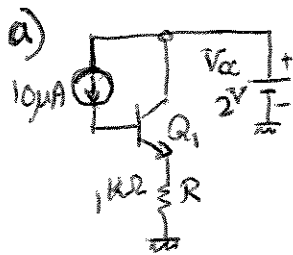
② $V_A = \infty \Rightarrow r_o = \infty$, $I_S = 8 \times 10^{-16} \text{ A}$, $\beta = 100$



$$I_C = \beta I_B = 100 \times 10^{-5} \text{ A} \Rightarrow \boxed{I_C = 1 \text{ mA}}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \text{ mV} \times \ln\left(\frac{10^{-3}}{8 \times 10^{-16}}\right)$$

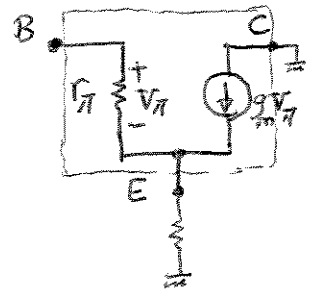
$$\Rightarrow \boxed{V_{BE} \approx 724 \text{ mV}}$$



$$V_{CE} = V_{CC} - R I_E \approx V_{CC} - R I_C = 2 - 1 \text{ k}\Omega \times 1 \text{ mA} \Rightarrow \boxed{V_{CE} = 1 \text{ V}}$$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} \Rightarrow \boxed{g_m = \frac{1}{26 \Omega}}$$

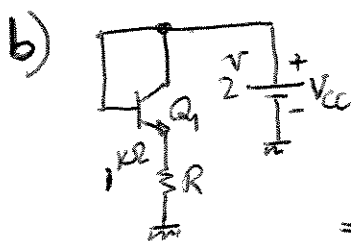
$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{\frac{1}{26}} \Rightarrow \boxed{r_{\pi} = 2.6 \text{ k}\Omega}$$



Applying KVL,

$$V_{CC} = V_{BE} + R I_E$$
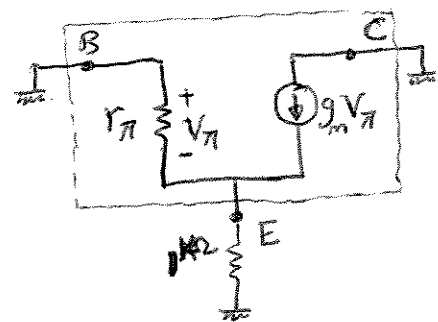
$$\Rightarrow V_{CC} \approx V_{BE} + R I_C$$



$$\Rightarrow V_{CC} \approx V_{BE} + R I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$\Rightarrow 2 \text{ V} \approx V_{BE} + 8 \times 10^{-13} \exp\left(\frac{V_{BE}}{26 \text{ mV}}\right) \Rightarrow \boxed{V_{BE} \approx 730 \text{ mV}}$$

$$\boxed{V_{CE} = V_{BE} = 730 \text{ mV}}$$


$$I_C = 8 \times 10^{-16} \exp\left(\frac{730}{26}\right) \Rightarrow \boxed{I_C \approx 1.2 \text{ mA}}$$

$$g_m = \frac{I_C}{V_T} = \frac{1.2 \text{ mA}}{26 \text{ mV}} \Rightarrow \boxed{g_m \approx 46 \text{ mS}}$$

$$r_{\pi} = \frac{\beta}{g_m} \xrightarrow{\beta=100} \boxed{r_{\pi} \approx 2167 \Omega}$$

22) Continued...

c)

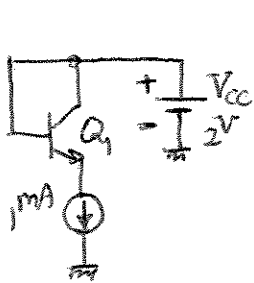

$$I_C \approx I_E = 1 \text{ mA}$$


$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 26 \text{ mV} \ln \left(\frac{1 \text{ mA}}{8 \times 10^{-16}} \right)$$

$$\Rightarrow V_{BE} \approx 724 \text{ mV}$$


$$V_{CE} = V_{BE} = 724 \text{ mV}$$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m = \frac{1}{26 \Omega}$$
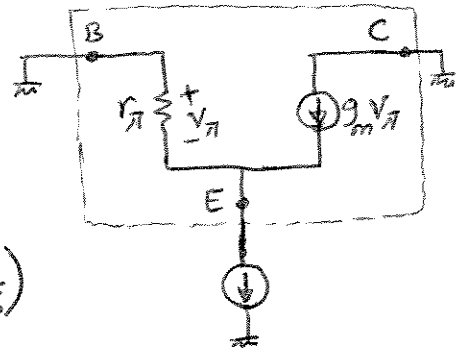
$$r_\pi = \frac{\beta}{g_m} = \frac{100}{\frac{1}{26}} \Rightarrow r_\pi \approx 2.6 \text{ k}\Omega$$



d)

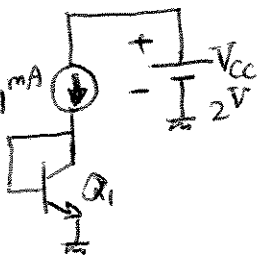


As in part c, we have,

$$I_C \approx 1 \text{ mA}$$

$$V_{CE} \approx 724 \text{ mV}$$

$$g_m = \frac{1}{26 \Omega}$$


$$r_\pi = 2.6 \text{ k}\Omega$$

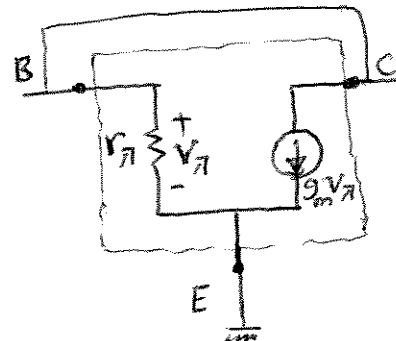

$$(23) \quad I_C = I_S \exp\left(\frac{V_{BE}}{nV_T}\right) \quad I_C = \beta I_B$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{1}{nV_T} I_S \exp\left(\frac{V_{BE}}{nV_T}\right) = \frac{I_C}{nV_T}$$

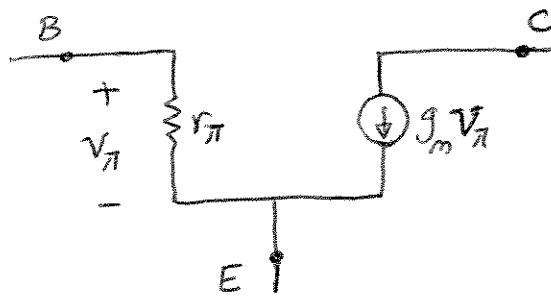
$$r_\pi = \frac{\partial V_{BE}}{\partial I_B} = \frac{\partial V_{BE}}{\frac{1}{\beta} \partial I_C} = \frac{\beta}{g_m} = \frac{n\beta V_T}{I_C}$$



$$(24) \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right), \quad I_C = \alpha I_B^2 \Rightarrow \frac{\partial I_B}{\partial I_C} = \frac{1}{2\sqrt{\alpha I_C}}$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) = \boxed{\frac{I_C}{V_T}}$$
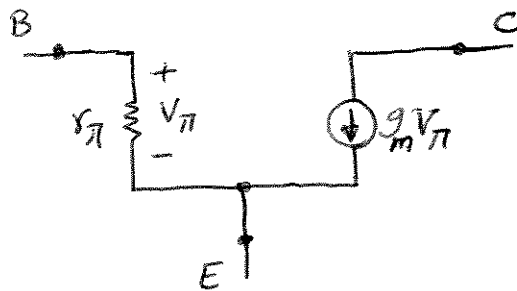
$$r_\pi = \frac{\partial V_{BE}}{\partial I_B} = \frac{\partial V_{BE}}{\frac{1}{2\sqrt{\alpha I_C}} \partial I_C} = \frac{2\sqrt{\alpha I_C}}{g_m} = \frac{2\sqrt{\alpha I_C}}{\frac{I_C}{V_T}} = \boxed{2V_T \sqrt{\frac{\alpha}{I_C}}}$$



$$(25) \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] \quad V_{BE} \text{ is Constant}$$

$$\Delta I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} \Delta V_{CE}$$

$$\Rightarrow \frac{\Delta I_C}{I_C} = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} \cdot \Delta V_{CE}}{I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]} = \frac{\Delta V_{CE}}{V_A + V_{CE}}$$

$$\frac{\Delta I_C}{I_{C_{min}}} < 0.05 \Rightarrow \frac{\Delta V_{CE}}{V_A + V_{CE_{min}}} < 0.05$$

$$\Rightarrow 20 \Delta V_{CE} < V_A + V_{CE_{min}}$$

$$\left. \begin{array}{l} \Delta V_{CE} = 2V \\ V_{CE_{min}} = 1V \end{array} \right\} \Rightarrow 40 < V_A + 1 \Rightarrow \boxed{V_A > 39V}$$

26

$$a) I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = 5 \times 10^{-17} \exp\left(\frac{800 \text{ mV}}{26 \text{ mV}}\right) \approx \boxed{1.15 \text{ mA}}$$

$$V_X = V_{CC} - R_C I_C = 2.5 \text{ V} - 1 \text{ k}\Omega \times 1.15 \text{ mA}$$

$$\boxed{V_X = 1.35 \text{ V}}$$

Transistor is in Forward Active Region

$$b) I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

$$\Rightarrow I_C = 5 \times 10^{-17} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5 \text{ V}}\right] \quad \text{equation 1}$$

$$\text{Also we know: } V_X = V_{CC} - R_C I_C \Rightarrow I_C = \frac{V_{CC} - V_X}{R_C} \quad \text{equation 2}$$

$$\text{equations 1, 2} \Rightarrow \frac{V_{CC} - V_X}{R_C} = 5 \times 10^{-17} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5}\right]$$


$$\Rightarrow V_X + 5 \times 10^{-14} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5}\right] = 2.5$$

$$\Rightarrow 1.2306 V_X \approx 1.347$$

$$\Rightarrow \boxed{V_X \approx 1.095 \text{ V}} \quad \text{equation 1} \Rightarrow \boxed{I_C \approx 1.406 \text{ mA}}$$

Transistor is in Forward Active Region

(27)

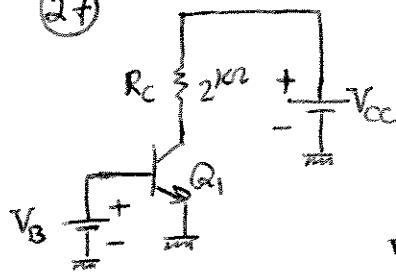

$$I_S = 1 \times 10^{-17} \text{ A} \quad V_A = 5 \text{ V}$$

Applying KVL:

$$V_{CC} = R_C I_C + V_{CE}$$

$$\Rightarrow V_{CC} = R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] + V_{CE}$$

$$\xrightarrow{V_{BE} \text{ Constant}} \Delta V_{CC} = \left[R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} + 1 \right] \cdot \Delta V_{CE} \quad \text{equation 1}$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left[1 + \frac{V_{CE}}{V_A}\right] \Rightarrow \Delta I_C = I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A} \Delta V_{CE}$$

$$\Rightarrow \Delta V_{CE} = \frac{1}{I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}} \cdot \Delta I_C \quad \text{equation 2}$$


$$\text{equations 1, 2} \Rightarrow \Delta I_C = \frac{I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}}{1 + R_C I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}} \cdot \Delta V_{CC}$$

$$\Rightarrow \Delta I_C = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_A + R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right)} \cdot \Delta V_{CC} = \frac{1}{r_o + R_C} \cdot \Delta V_{CC}$$

Could also be obtained using small signal model

$$\Rightarrow \Delta I_C = \frac{2.31 \times 10^{-4}}{5 + 0.4613} \times 0.5 \Rightarrow \Delta I_C \approx 0.021 \text{ mA}$$

(28)

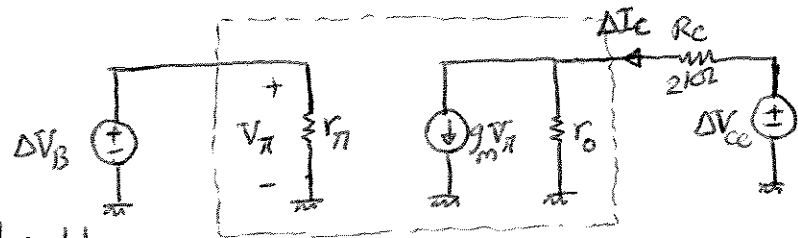

We use small signal model,

Assuming that the required ΔV_B is small enough.

Applying Superposition,

$$\Delta I_C = \left(\frac{1}{r_o + R_C} \right) \Delta V_{CC} + \left(\frac{g_m r_o}{r_o + R_C} \right) \Delta V_B$$

$$\Delta I_C = 0 \Rightarrow \boxed{\Delta V_B = - \frac{1}{g_m r_o} \Delta V_{CC}}$$


$$\Delta V_B = - \frac{1}{\frac{I_C}{V_T} \cdot \frac{V_A}{I_C}} \Delta V_{CC} \Rightarrow \Delta V_B = - \frac{V_T}{V_A} \Delta V_{CC}$$

$$\Rightarrow \Delta V_B = - \frac{26 \times 10^{-3}}{5} \times (3 - 2.5)$$

$$\Rightarrow \boxed{\Delta V_B = -2.6 \text{ mV}}$$

which is small enough

for small signal model

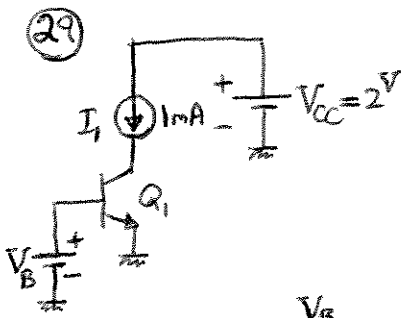

$$I_S = 3 \times 10^{-17} \text{ A}$$

$$a) I_C = I_S e^{\frac{V_B}{V_T}} \Rightarrow V_B = V_T \ln\left(\frac{I_C}{I_S}\right) = 26^{\text{mV}} \ln\left(\frac{10^{-3}}{3 \times 10^{-17}}\right)$$

$$\Rightarrow \boxed{V_B \approx 809.6 \text{ mV}}$$

$$b) I_C = I_S e^{\frac{V_B}{V_T}} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$10^{-3} = 3 \times 10^{-17} e^{\frac{V_B}{V_T}} \left(1 + \frac{1.5}{5}\right) \Rightarrow e^{\frac{V_B}{V_T}} = \frac{10^{14}}{3.9}$$

$$\Rightarrow V_B = 26^{\text{mV}} \ln\left(\frac{10^{14}}{3.9}\right) \Rightarrow \boxed{V_B \approx 802.8 \text{ mV}}$$

$$\textcircled{30} \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

$$r_o^{-1} = \frac{dI_C}{dV_{CE}} = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \cdot \frac{1}{V_A} \approx \frac{I_C}{V_A} \Rightarrow r_o \approx \frac{V_A}{I_C}$$


$$r_o > 10^4 \Omega \Rightarrow \frac{V_A}{I_C} > 10^4 \Omega$$

$$\Rightarrow V_A > 10^4 \Omega \times 2^{mA}$$

$$\Rightarrow \boxed{V_A > 20V}$$

③ $I_S = 5 \times 10^{-16} \text{ A}$, $V_A = 8 \text{ V}$
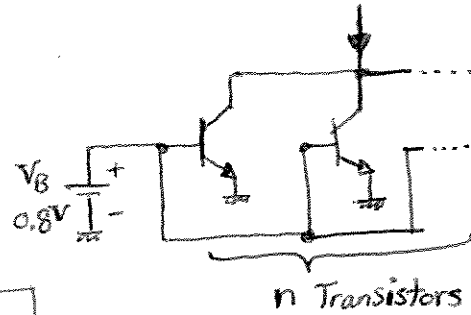
$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$




$$g_{m_{Total}} = \frac{I_{C_{Total}}}{V_T} \approx \frac{n I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_T}$$

$$\Rightarrow g_{m_{Total}} \approx \frac{n \times 5 \times 10^{-16} \exp\left(\frac{800}{26}\right)}{26 \text{ mV}} \Rightarrow g_{m_{Total}} \approx 0.4435 n$$


$$r_o^{-1} = \frac{\partial I_{C_{Total}}}{\partial V_{CE}} = \frac{\partial}{\partial V_{CE}} \left[n I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] \right]$$

$$\Rightarrow r_o = \frac{V_A}{n I_S \exp\left(\frac{V_{BE}}{V_T}\right)}$$
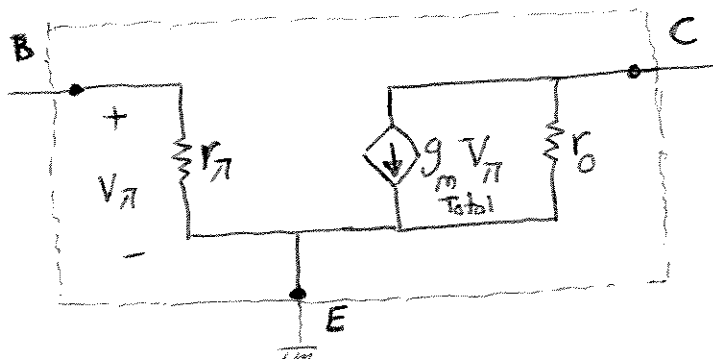
$$r_{\pi} = \frac{\beta}{g_{m_{Total}}} \approx \frac{\beta=100}{0.4435 n} \approx \frac{225.5}{n}$$



32

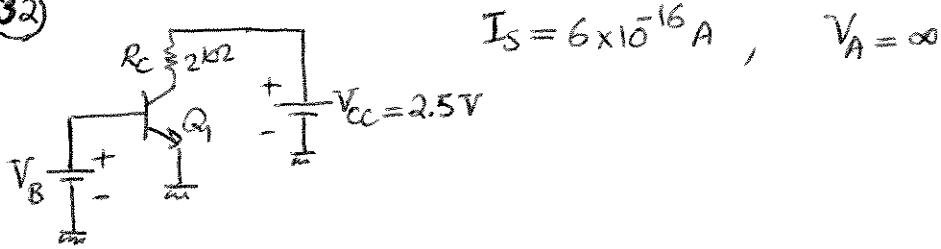

a) Q_1 at the edge of the active region $\Rightarrow V_{CE} = V_{BE}$

applying KVL, $V_{CC} = R_C I_C + V_{CE}$

at the edge $\Rightarrow V_{CC} = R_C I_C + V_{BE} \Rightarrow R_C I_S e^{\frac{V_{BE}}{V_T}} + V_{BE} = V_{CC}$

$\Rightarrow 2k\Omega \times 6 \times 10^{-16} A e^{\frac{V_B}{26mV}} + V_B = 2.5 \Rightarrow \boxed{V_B \approx 728.5mV}$

b) Applying KVL, $V_{CC} = R_C I_C + V_{CE}$


Soft Saturation $\Rightarrow V_{CE} = V_{BE} - 0.2V$

$\Rightarrow V_{CC} = R_C I_C + V_{BE} - 0.2V$

$\Rightarrow 2k\Omega \times 6 \times 10^{-16} A e^{\frac{V_B}{26mV}} + V_B = 2.7V$

$\Rightarrow \boxed{V_B \approx 731.5mV}$ So V_B Can increase by 3mV

(33)

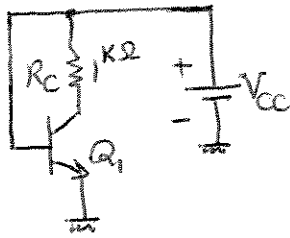

$$I_S = 7 \times 10^{-16} \text{ A}, \quad V_A = \infty$$

$$\Downarrow$$

$$r_o = \infty$$

Applying KVL,

$$V_{CC} = R_C I_C + V_{CE} \xrightarrow{V_{CE} = V_{BE} - 0.2 \text{ V}} R_C I_C + V_{BE} - 0.2 \text{ V} = V_{CC}$$

$$\Rightarrow R_C I_S e^{\frac{V_{BE}}{V_T}} + V_{BE} - 0.2 \text{ V} = V_{CC}$$


$$\xRightarrow{V_{BE} = V_{CC}} R_C I_S e^{\frac{V_{CC}}{V_T}} + V_{CC} - 0.2 = V_{CC}$$

$$\Rightarrow R_C I_S e^{\frac{V_{CC}}{V_T}} = 0.2 \text{ V}$$

$$\Rightarrow 1 \text{ k}\Omega \times 7 \times 10^{-16} e^{\frac{V_{CC}}{26 \text{ mV}}} = 0.2 \text{ V}$$

$$\Rightarrow \boxed{V_{CC} \approx 686 \text{ mV}}$$

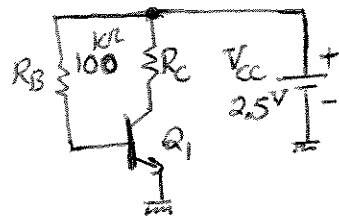(34) $I_S = 2 \times 10^{-17} \text{ A}$, $V_A = \infty$ $\beta = 100$



$$\begin{cases} V_{CC} = R_C I_C + V_{CE}, & V_{CE} = V_{BE} - 0.2 \text{ V} \\ V_{CC} = R_B I_B + V_{BE} \Rightarrow V_{CC} = R_B \frac{I_C}{\beta} + V_{BE} \end{cases}$$

$$R_B \frac{I_C}{\beta} + V_{BE} = V_{CC} \Rightarrow \frac{R_B}{\beta} I_S e^{\frac{V_{BE}}{V_T}} + V_{BE} = V_{CC}$$

$$\Rightarrow \frac{100}{100} \times 2 \times 10^{-17} e^{\frac{V_{BE}}{26 \text{ mV}}} + V_{BE} = 2.5 \text{ V}$$

$$\Rightarrow \boxed{V_{BE} \approx 833.5 \text{ mV}}$$

Soft Saturation $\Rightarrow V_{CE} = V_{BE} - 0.2 \text{ V} \Rightarrow \boxed{V_{CE} = 692.5 \text{ mV}}$

$$V_{CC} = R_C I_C + V_{CE} \Rightarrow R_C = \frac{V_{CC} - V_{CE}}{I_C}$$


$$\Rightarrow R_C = \frac{V_{CC} - V_{CE}}{I_S \exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{2.5 - 0.6925}{2 \times 10^{-17} \exp\left(\frac{892.5}{26}\right)}$$

$$\Rightarrow \boxed{R_C \approx 112 \Omega}$$

③⑤ $I_S = 5 \times 10^{-16} \text{ A}$, $V_A = \infty \Rightarrow r_o = \infty$

Soft Saturation $\Rightarrow V_{BC} = 200 \text{ mV}$
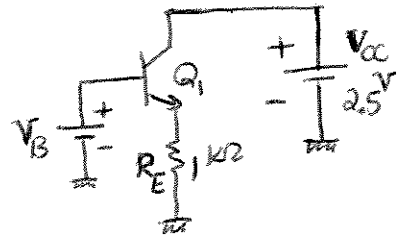
$$\Rightarrow V_B = V_C + 0.2 \text{ V} \Rightarrow \boxed{V_B = 2.7 \text{ V}}$$



Applying KVL $\Rightarrow V_B = V_{BE} + R_E I_E \xrightarrow{I_E \approx I_C} V_B = V_{BE} + R_E I_C$

$$\Rightarrow V_{BE} + 1 \text{ k}\Omega \times I_S e^{\frac{V_{BE}}{V_T}} = 2.7 \text{ V}$$


$$\Rightarrow V_{BE} + 5 \times 10^{-13} e^{\frac{V_{BE}}{V_T}} = 2.7 \text{ V} \Rightarrow \boxed{V_{BE} \approx 754 \text{ mV}}$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} = 5 \times 10^{-16} e^{\frac{0.754}{0.026}} \Rightarrow \boxed{I_C \approx 2 \text{ mA}}$$

$$\textcircled{36} \quad \beta = 100, \quad V_A = \infty \Rightarrow r_o = \infty$$

$$V_{BC} = 0.2 \text{ V} \Rightarrow R_p I_C = 0.2 \text{ V}$$
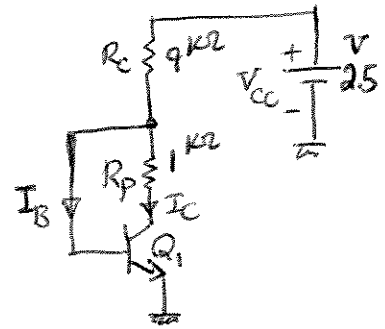
$$\Rightarrow \boxed{I_C = \frac{0.2 \text{ V}}{R_p}}$$



$$V_{BE} = V_{CC} - R_C (I_B + I_C)$$

$$\stackrel{\beta=100}{\Rightarrow} V_{BE} = V_{CC} - \frac{\beta+1}{\beta} R_C I_C \Rightarrow \boxed{V_{BE} = V_{CC} - \frac{\beta+1}{\beta} \frac{R_C \times 0.2}{R_p}}$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow I_S = I_C \exp\left(-\frac{V_{BE}}{V_T}\right)$$

$$\Rightarrow \boxed{I_S = \frac{0.2}{R_p} \exp\left[\frac{0.2}{V_T} \cdot \frac{\beta+1}{\beta} \cdot \frac{R_C}{R_p} - \frac{V_{CC}}{V_T}\right]}$$

$$\stackrel{\beta=100}{\Rightarrow} \boxed{I_S \approx \frac{0.2}{R_p} \exp\left[\frac{0.2}{V_T} \frac{R_C}{R_p} - \frac{V_{CC}}{V_T}\right]}$$

$$\Rightarrow \boxed{I_S \approx 4.06 \times 10^{-16} \text{ A}}$$


$$\textcircled{37} \quad I_{S_1} = 3I_{S_2} = 6 \times 10^{-16} \text{ A}$$

$$I_1 = I_{S_1} \exp\left(\frac{V_{EB_1}}{V_T}\right) = 6 \times 10^{-16} \exp\left(\frac{300}{26}\right) \Rightarrow \underline{I_1 \approx 6.155 \times 10^{-11} \text{ A}}$$

$$I_2 = I_{S_2} \exp\left(\frac{V_{EB_2}}{V_T}\right) = 2 \times 10^{-16} \exp\left(\frac{820}{26}\right) \Rightarrow \underline{I_2 \approx 10 \text{ mA}}$$

$$I_X = I_1 + I_2 \Rightarrow \boxed{I_X \approx 10 \text{ mA}}$$

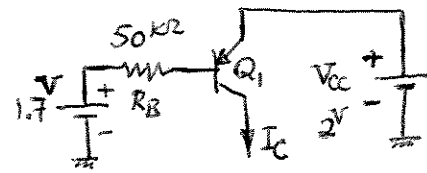38) $I_S = 2 \times 10^{-17} \text{ A}$ $\beta = 100$



Applying KVL,

$$V_{CC} = V_{EB} + R_B I_B + 1.7 \text{ V}$$

$$\Rightarrow 2 \text{ V} = V_{EB} + R_B \frac{I_C}{\beta} + 1.7 \text{ V}$$

$$\Rightarrow 0.3 \text{ V} = V_{EB} + \frac{50 \text{ k}\Omega}{100} I_C$$

$$\Rightarrow 0.3 \text{ V} = V_{EB} + 500 \times I_S e^{\frac{V_{EB}}{V_T}}$$


$$\Rightarrow 0.3 \text{ V} = V_{EB} + 10^{-14} e^{\frac{V_{EB}}{26 \text{ mV}}} \Rightarrow \boxed{V_{EB} \approx 0.3 \text{ V}}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow I_C = 2 \times 10^{-17} e^{\frac{300}{26}}$$

$$\Rightarrow \boxed{I_C \approx 2.05 \times 10^{-12} \text{ A}}$$

③⑨ $I_C = 3 \text{ mA}$, $\beta = 100$, $R_B = 23 \text{ k}\Omega$

Applying KVL,

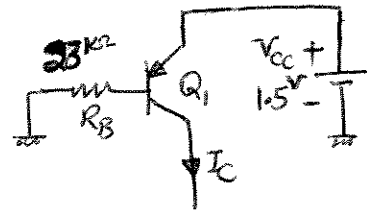

$$V_{CC} = V_{EB} + R_B I_B \Rightarrow V_{CC} = V_{EB} + R_B \frac{I_C}{\beta}$$

$$\Rightarrow -I_C \frac{R_B}{\beta} + V_{CC} = V_{EB}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}}$$

$$\Rightarrow I_S = I_C e^{\frac{-V_{EB}}{V_T}}$$


$$\Rightarrow I_S = I_C e^{\frac{1}{V_T} \left(\frac{R_B I_C}{\beta} - V_{CC} \right)}$$

$$\Rightarrow I_S \approx 8.85 \times 10^{-17} \text{ A}$$

④ At the edge of active $\Rightarrow V_{BC} = 0$

$$I_C = \frac{V_B - V_{BC}}{R_C} = \frac{V_B}{R_C}$$
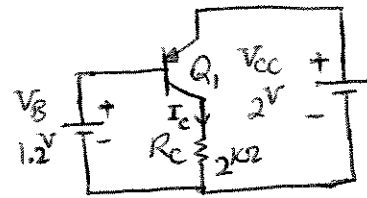
$$\Rightarrow I_C = \frac{1.2V}{2k\Omega} \Rightarrow \boxed{I_C \approx 0.6 \text{ mA}}$$




$$I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right) \Rightarrow I_S = I_C \exp\left(-\frac{V_{EB}}{V_T}\right)$$

$$\Rightarrow I_S = 0.6 \times 10^{-3} \exp\left(-\frac{800}{26}\right)$$

$$\Rightarrow \boxed{I_S \approx 2.6 \times 10^{-17} \text{ A}}$$

④ $I_S = 8 \times 10^{-16} \text{ A}$

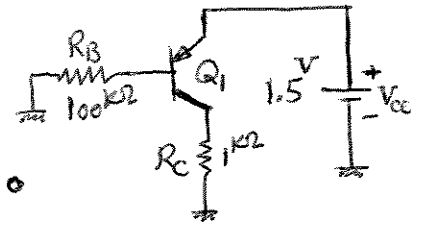

At the edge of the active mode $\Rightarrow V_{BC} = 0$

$$\Rightarrow V_{EB} = V_{EC}$$

Applying KVL,

$$V_{CC} = V_{EC} + R_C I_C \xrightarrow{V_{EB} = V_{EC}} V_{CC} = V_{EB} + R_C I_C$$

$$\Rightarrow V_{EB} + R_C I_S e^{\frac{V_{EB}}{V_T}} = V_{CC}$$

$$\Rightarrow V_{EB} + 8 \times 10^{-13} e^{\frac{V_{EB}}{26 \text{ mV}}} = 1.5 \Rightarrow \boxed{V_{EB} \approx 718 \text{ mV}}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow \boxed{I_C \approx 0.788 \text{ mA}}$$


Applying KVL,

$$V_{BC} = 0 \Rightarrow V_B = V_C \Rightarrow R_B I_B = R_C I_C$$

$$\Rightarrow R_B \frac{I_C}{\beta} = R_C I_C \Rightarrow \boxed{\beta = \frac{R_B}{R_C}}$$

$$\Rightarrow \beta = \frac{100 \text{ k}\Omega}{1 \text{ k}\Omega} \Rightarrow \boxed{\beta = 100}$$

④② $I_S = 3 \times 10^{-17} \text{ A}$

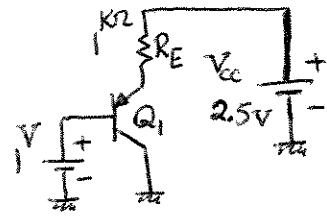

Applying KVL,

$$V_{CC} = R_E I_E + V_{EB} + 1 \text{ V} \quad \xrightarrow{I_E = I_C} \quad V_{CC} = R_E I_C + V_{EB} + 1 \text{ V}$$

$$\Rightarrow 2.5 = 1 \text{ k}\Omega \times 3 \times 10^{-17} e^{\frac{V_{EB}}{26 \text{ mV}}} + V_{EB} + 1 \text{ V}$$

$$\Rightarrow V_{EB} + 3 \times 10^{-14} e^{\frac{V_{EB}}{26 \text{ mV}}} = 1.5 \text{ V}$$

$$\Rightarrow \boxed{V_{EB} \approx 800.5 \text{ mV}}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} = 3 \times 10^{-17} e^{\frac{800.5}{26}} \Rightarrow \boxed{I_C \approx 0.705 \text{ mA}}$$

$$(43) I_S = 3 \times 10^{-17} \text{ A}, \beta = 100, V_A = \infty \Rightarrow \boxed{r_o = \infty}$$


$$a) V_{EB} = 2.5 - 1.7 = 0.8 \text{ V}$$

$$I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right) = 3 \times 10^{-17} \exp\left(\frac{800}{26}\right) \Rightarrow \boxed{I_C \approx 0.692 \text{ mA}}$$

$$V_{EC} = V_{CC} - R_C I_C = 2.5 - 1 \times 0.692 \Rightarrow \boxed{V_{EC} \approx 1.808 \text{ V}}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.692 \text{ mA}}{26 \text{ mV}} \Rightarrow \boxed{g_m \approx 26.6 \text{ mS}}$$
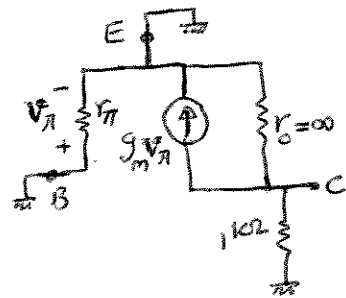
$$r_\pi = \frac{\beta}{g_m} = \frac{100}{26.6 \times 10^{-3}} \Rightarrow \boxed{r_\pi \approx 3.76 \text{ k}\Omega}$$




$$b) V_{EB} = V_T \ln\left(\frac{I_C}{I_S}\right) \Rightarrow V_{EB} = V_T \ln\left(\frac{\beta I_B}{I_S}\right)$$

$$\Rightarrow V_{EB} = 26 \text{ mV} \times \ln\left(\frac{100 \times 20 \times 10^{-6}}{3 \times 10^{-17}}\right)$$

$$\Rightarrow \boxed{V_{EB} \approx 827.6 \text{ mV}}$$
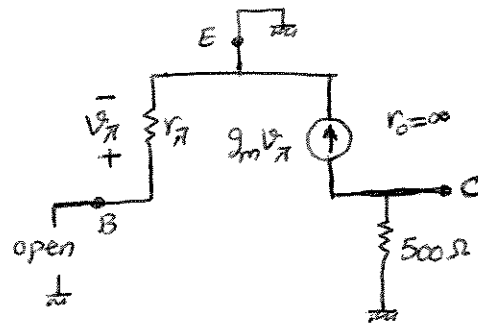
$$I_C = \beta I_B \Rightarrow \boxed{I_C = 2 \text{ mA}}$$



$$V_{EC} = V_{CC} - R_C I_C = 2.5 - 0.5 \times 2 \Rightarrow \boxed{V_{EC} = 1.5 \text{ V}}$$

$$g_m = \frac{I_C}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow \boxed{g_m \approx 77 \text{ mS}}$$

$$r_\pi = \frac{\beta}{g_m} \Rightarrow \boxed{r_\pi \approx 1.3 \text{ k}\Omega}$$

④③ Continued

c) Applying KVL,

$$V_{ce} = V_{EB} + (I_C + I_B) \times 2^{k\Omega} \simeq V_{EB} + 2^{k\Omega} \times I_C$$


$$\Rightarrow V_{EB} + 2^{k\Omega} \times I_S e^{\frac{V_{EB}}{V_T}} = V_{CC}$$

$$\Rightarrow V_{EB} + 6 \times 10^{-14} e^{\frac{V_{EB}}{26mV}} = 2.5V \Rightarrow \boxed{V_{EB} \simeq 805mV}$$

$$I_C = \frac{V_{CC} - V_{EB}}{R} = \frac{2.5 - 0.805}{2^{k\Omega}} \Rightarrow \boxed{I_C \simeq 847.5\mu A}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.8475 \times 10^{-3}}{0.026} \Rightarrow \boxed{g_m \simeq 32.6 mS}$$
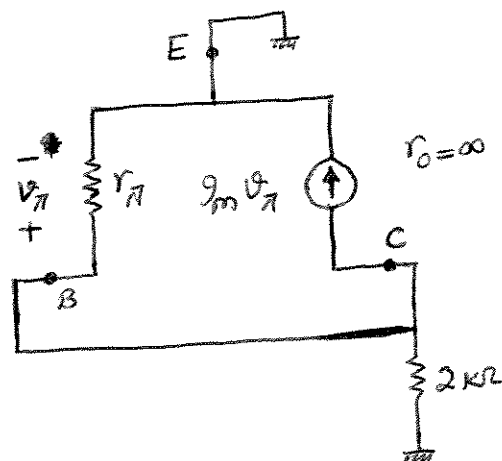
$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{32.6 \times 10^{-3}} \Rightarrow \boxed{r_{\pi} \simeq 3068 \Omega}$$




44) $I_S = 3 \times 10^{-17} \text{ A}$, $\beta = 100$, $V_A = \infty \Rightarrow r_o = \infty$

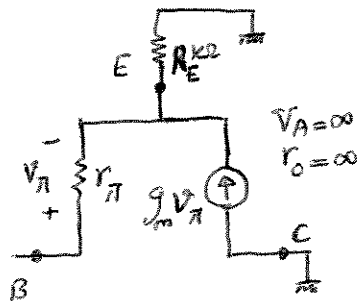a) Applying KVL,

$$V_{CC} = R_E I_E + V_{EC} \xrightarrow{I_E \approx I_C} V_{EC} = V_{CC} - R_E I_C \quad \boxed{I_C = \beta I_B = 0.2 \text{ mA}}$$

$$\Rightarrow \boxed{V_{EC} = V_{CC} - \beta R_E I_B} \xrightarrow[\substack{R_E = 2 \text{ k}\Omega \\ V_{CC} = 2.5 \text{ V}}]{I_B = 2 \mu\text{A}} \boxed{V_{EC} = 2.1 \text{ V}}$$



Transistor is in
Forward Active Region

b) Applying KVL,


$$V_{CC} = R_E I_E + V_{EB} \Rightarrow V_{CC} = R_E I_C + V_{EB}$$

$$\Rightarrow 2.5 = 5 \text{ k}\Omega \times 3 \times 10^{-17} e^{V_{EB}/V_T} + V_{EB}$$

$$\Rightarrow \boxed{V_{EB} \approx 781.9 \text{ mV}}$$

Forward
Active
Region

From Circuit
 $V_{EC} = V_{EB}$

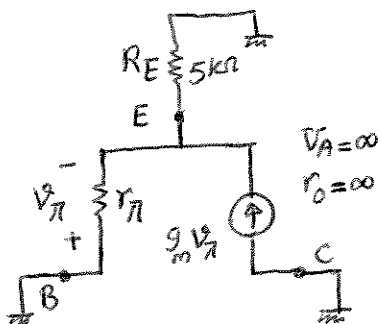

$$g_m = \frac{I_C}{V_T} = \frac{3 \times 10^{-17} e^{\frac{781.9}{26}}}{0.026} \Rightarrow \boxed{g_m \approx 0.0133 \text{ S}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.0133} \Rightarrow \boxed{r_{\pi} \approx 7538 \Omega}$$

④ Continued.....


c) $I_E = 0.5 \text{ mA} \Rightarrow I_C \approx 0.5 \text{ mA}$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow 0.5 \text{ mA} = 3 \times 10^{-17} e^{\frac{V_{EB}}{26 \text{ mV}}} \Rightarrow V_{EB} \approx 741.6 \text{ mV}$$

In the given circuit: $V_{EC} = V_{EB}$

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m \approx 19.2 \text{ mS}$$

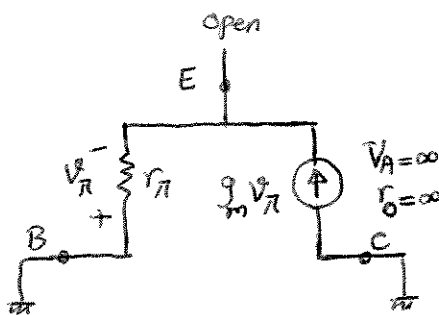
$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.0192} \Rightarrow r_\pi \approx 5.2 \text{ k}\Omega$$



Forward Active Region

45) $I_S = 5 \times 10^{-17} \text{ A}$

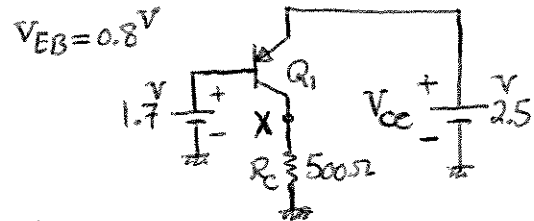a) $V_A = \infty \Rightarrow r_o = \infty$



$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow I_C = 5 \times 10^{-17} e^{\frac{0.8}{0.026}} \Rightarrow \boxed{I_C = 1.15 \text{ mA}}$$

$$V_X = R_C I_C = 0.5 \times 1.15 \text{ mA} \Rightarrow \boxed{V_X = 0.58 \text{ V}}$$

b) $V_A = 6 \text{ V}$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{EC}}{V_A} \right), \quad V_{EC} = V_{CC} - R_C I_C$$

$$\Rightarrow I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CC} - R_C I_C}{V_A} \right)$$

$$\Rightarrow I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CC}}{V_A} \right) - \frac{I_S R_C}{V_A} e^{\frac{V_{BE}}{V_T}} I_C$$

$$\Rightarrow \boxed{I_C = \frac{I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CC}}{V_A} \right)}{1 + \frac{I_S R_C}{V_A} e^{\frac{V_{BE}}{V_T}}} = \frac{5 \times 10^{-17} e^{\frac{0.8}{0.026}} \left(1 + \frac{2.5}{6} \right)}{1 + \frac{5 \times 10^{-17} \times 0.5}{6} e^{\frac{0.8}{0.026}}}}$$

$$\Rightarrow \boxed{I_C = 1.49 \text{ mA}} \quad V_X = R_C I_C = 500 \times 1.49 \times 10^{-3} \Rightarrow \boxed{V_X = 0.745 \text{ V}}$$

$$(46) \quad r_o = 60 \text{ k}\Omega, \quad I_C = 2 \text{ mA}$$

$$r_o = \frac{V_A}{I_C} \Rightarrow 60 \times 10^3 \Omega = \frac{V_A}{2 \times 10^{-3} \text{ A}} \Rightarrow \boxed{V_A = 120 \text{ V}}$$

$$(47) \quad r_o = 60 \text{ k}\Omega, \quad I_C = 1 \text{ mA}$$

$$r_o = \frac{V_A}{I_C} \Rightarrow \boxed{V_A = r_o \cdot I_C} \Rightarrow \underline{V_A \propto I_C}$$


$$\Rightarrow V_A = 60 \text{ k}\Omega \times 1 \text{ mA}$$

$$\Rightarrow \boxed{V_A = 60 \text{ V}}$$

V_A is half the value in ^{problem} 46 as V_A is proportional to I_C .

48) $V_A = 5\text{V}$

a) At the edge of active mode

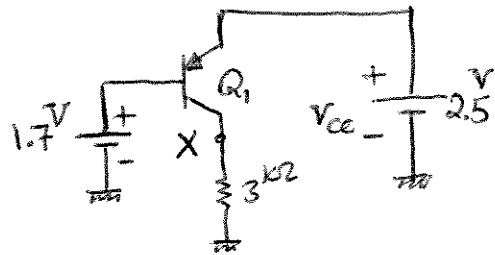

$$\Rightarrow V_X = V_B = 1.7\text{V}$$

$$I_C = \frac{V_X}{R_C} = \frac{1.7\text{V}}{3\text{k}\Omega} \Rightarrow I_C \approx 0.567\text{mA}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \left(1 + \frac{V_{EC}}{V_A}\right) \Rightarrow I_S = \frac{I_C e^{-\frac{V_{EB}}{V_T}}}{1 + \frac{V_{EC}}{V_A}}$$

$$I_S = \frac{0.567 \times 10^{-3} e^{-\frac{800}{26}}}{1 + \frac{2.5-1.7}{5}} \Rightarrow I_S \approx 2.118 \times 10^{-17}\text{A}$$

b) $V_A = \infty$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow I_S = I_C e^{-\frac{V_{EB}}{V_T}}$$

$$I_S = 0.567 \times 10^{-3} e^{-\frac{800}{26}} \Rightarrow I_S \approx 2.457 \times 10^{-17}\text{A}$$


I_S increases

④ The direction of currents in large-signal model shows how currents would flow when the PNP transistor is properly DC biased.

The direction of currents in small-signal model shows how the AC currents flow when AC voltage across Base-Emitter increases.

⑤ $I_S = 6 \times 10^{-16} \text{ A}$, $V_A = 5 \text{ V}$, $I_1 = 2 \text{ mA}$

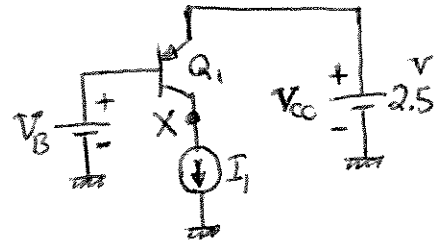a) $I_C = I_S e^{\frac{V_{EB}}{V_T}} \left(1 + \frac{V_{EC}}{V_A} \right)$



$\Rightarrow V_{EB} = V_T \ln \left(\frac{I_C}{I_S \left(1 + \frac{V_{EC}}{V_A} \right)} \right)$

$V_{EC} = V_{CC} - V_X$
 $V_{EB} = V_{CC} - V_B$

$V_B = V_{CC} - V_T \ln \left(\frac{I_C}{I_S \left(1 + \frac{V_{CC} - V_X}{V_A} \right)} \right)$

$\Rightarrow V_B = 2.5 - 0.026 \ln \left(\frac{2 \times 10^{-3}}{6 \times 10^{-16} \left(1 + \frac{2.5 - 1}{5} \right)} \right) \Rightarrow V_B \approx 1.757 \text{ V}$

b) $I_C = I_S e^{\frac{V_{EB}}{V_T}} \left(1 + \frac{V_{EC}}{V_A} \right) \Rightarrow 1 + \frac{V_{EC}}{V_A} = \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}}$

$V_{EC} = V_{CC} - V_X$
 $V_{EB} = V_{CC} - V_B$

$V_X = V_{CC} - V_A \left(\frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} - 1 \right)$

$\Delta V_X \approx \frac{dV_X}{dV_{EB}} \Delta V_{EB} \Rightarrow \Delta V_X \approx \frac{V_A}{V_T} \cdot \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} \Delta V_{EB}$


$\Delta V_{EB} = -\Delta V_B$

$\Delta V_X \approx -\frac{V_A}{V_T} \cdot \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} \Delta V_B$

$\Rightarrow \Delta V_X \approx -\frac{5}{0.026} \times \frac{2 \times 10^{-3}}{6 \times 10^{-16}} \exp \left(-\frac{2.5 - 1.757}{0.026} \right) \times 0.1 \times 10^{-3} \Rightarrow \Delta V_X \approx -24.9 \text{ mV}$

50) Continued

c)

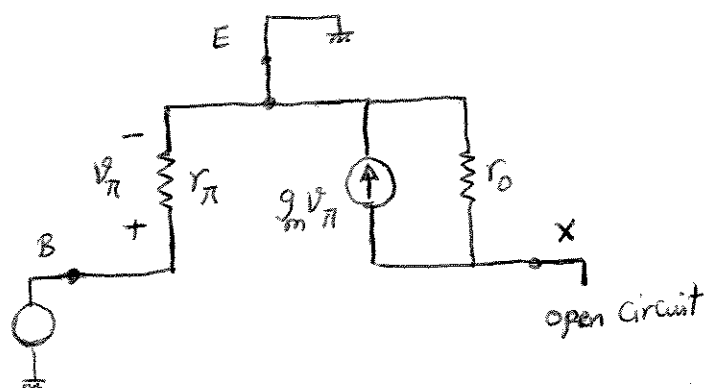


$$r_O = \frac{V_A}{I_C} = \frac{5V}{2mA} \Rightarrow \boxed{r_O \approx 2.5 k\Omega}$$

$$g_m = \frac{I_C}{V_T} = \frac{2mA}{0.026V} \Rightarrow \boxed{g_m \approx 76.9 mS}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{\frac{2}{26}} \Rightarrow \boxed{r_\pi \approx 1.3 k\Omega}$$

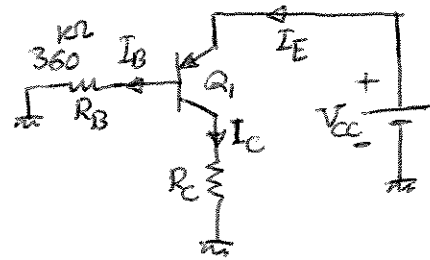⑤ $\beta = 100, V_A = \infty \Rightarrow r_o = \infty$
 $R_B = 360 \text{ k}\Omega$



a) given: $V_C = V_B + 0.2 \text{ V}$

$$\Rightarrow R_C I_C = R_B I_B + 0.2 \text{ V}$$

$$\Rightarrow R_C I_C = R_B \frac{I_C}{\beta} + 0.2 \text{ V} \Rightarrow \boxed{I_C = \frac{0.2 \text{ V}}{R_C - \frac{R_B}{\beta}}} \Rightarrow \boxed{I_C = 0.5 \text{ mA}}$$

$$I_C = I_S e^{+\frac{V_{EB}}{V_T}} \Rightarrow I_S = I_C e^{-\frac{V_{EB}}{V_T}} \Rightarrow I_S = I_C e^{-\frac{(V_{CC} - R_B I_B)}{V_T}}$$

$$\Rightarrow \boxed{I_S = \left(\frac{0.2}{R_C - \frac{R_B}{\beta}} \right) \exp \left[-\frac{1}{V_T} \left(V_{CC} - R_B \times \frac{0.2 \text{ V}}{\beta \left(R_C - \frac{R_B}{\beta} \right)} \right) \right]}$$

$$\Rightarrow \boxed{I_S \approx 10^{-15} \text{ A} = 1 \text{ fA}}$$

b) $g_m = \frac{I_C}{V_T}$

$$\Rightarrow \boxed{g_m = \frac{0.2 \text{ V}}{V_T \left(R_C - \frac{R_B}{\beta} \right)}} \Rightarrow \boxed{g_m \approx 19.23 \text{ mS}}$$

⑤2 $I_S = 5 \times 10^{-16} \text{ A}$, $\beta = 100$, $V_A = \infty \Rightarrow r_o = \infty$

a) $V_{EB} = 0 \Rightarrow Q_1 \text{ is off} \quad I_C = 0$

b) $I_B = 0 \Rightarrow Q_1 \text{ is off}$

c) Applying KVL: $V_{CC} = V_{EB} + 1 \text{ k}\Omega \times I_C$

$$\Rightarrow V_{EB} + 1 \text{ k}\Omega \times I_S e^{\frac{V_{EB}}{V_T}} \approx V_{CC} \Rightarrow V_{EB} + 5 \times 10^{-13} e^{\frac{V_{EB}}{26 \text{ mV}}} \approx 2.5 \text{ V}$$

$$\Rightarrow \boxed{V_{EB} \approx 751 \text{ mV}} \quad I_C = 5 \times 10^{-16} e^{\frac{0.751}{0.026}} \Rightarrow \boxed{I_C \approx 1.8 \text{ mA}}$$

With this current, Transistor is saturated. Note $V_B < V_C$
Always

d) $V_{BC} = 0 \Rightarrow$ Transistor is at the edge of saturation

e) $I_C \approx 0.5 \text{ mA} \Rightarrow V_{EB} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \text{ mV} \ln\left(\frac{0.5 \text{ mA}}{5 \times 10^{-16}}\right)$

$$\Rightarrow \boxed{V_{EB} \approx 718 \text{ mV}}$$

$$V_{\text{Collector}} = 500 \Omega \times I_C \Rightarrow \boxed{V_C = 0.25 \text{ V}}$$

As $V_B = 0$, $V_C = 0.25 \text{ V} \Rightarrow$ Transistor is soft saturated


53) $I_{S1} = 3I_{S2} = 5 \times 10^{-16} \text{ A}$, $\beta_1 = 100$, $\beta_2 = 50$, $V_A = \infty \Rightarrow r_o = \infty$

a) $V_{B2} = 0 \xrightarrow{\text{BC } Q_2 \text{ Forward Bias by } 200 \text{ mV max}} V_{C2} = 0.2 \text{ V max}$

$$\Rightarrow I_{C2 \text{ max}} = \frac{V_{C2 \text{ max}}}{R_C} = \frac{0.2 \text{ V}}{500 \Omega}$$

$$\Rightarrow \boxed{I_{C2 \text{ max}} = 0.4 \text{ mA}}$$

As shown
 $I_{C1} = I_{C2}$

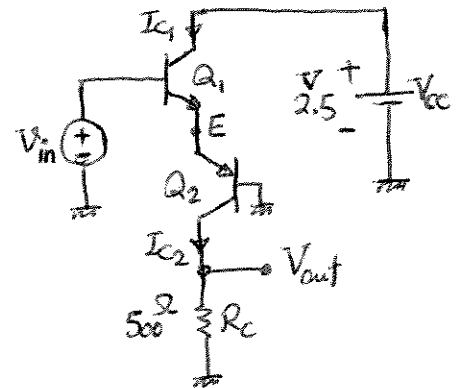

$$V_{in \text{ max}} = V_{BE1 \text{ max}} + V_{EB2 \text{ max}} = V_T \ln \frac{I_{C1 \text{ max}}}{I_{S1}} + V_T \ln \frac{I_{C2 \text{ max}}}{I_{S2}}$$

$$\Rightarrow V_{in \text{ max}} = 26 \text{ mV} \cdot \left[\ln \frac{0.4 \times 10^{-3}}{5 \times 10^{-16}} + \ln \frac{0.4 \times 10^{-3}}{\frac{5}{3} \times 10^{-16}} \right] \Rightarrow \boxed{V_{in \text{ max}} = 1.454 \text{ V}}$$

b) $g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.4 \text{ mA}}{26 \text{ mV}}$


$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.4 \text{ mA}}{26 \text{ mV}}$$

$$\Rightarrow \boxed{g_{m1} = g_{m2} \approx 15.4 \text{ mS}}$$

$$r_{\pi1} = \frac{\beta_1}{g_{m1}} = \frac{100}{\frac{0.4}{26}} \Rightarrow \boxed{r_{\pi1} = 6.5 \text{ k}\Omega}$$

$$r_{\pi2} = \frac{\beta_2}{g_{m2}} = \frac{50}{\frac{0.4}{26}} \Rightarrow \boxed{r_{\pi2} = 3.25 \text{ k}\Omega}$$

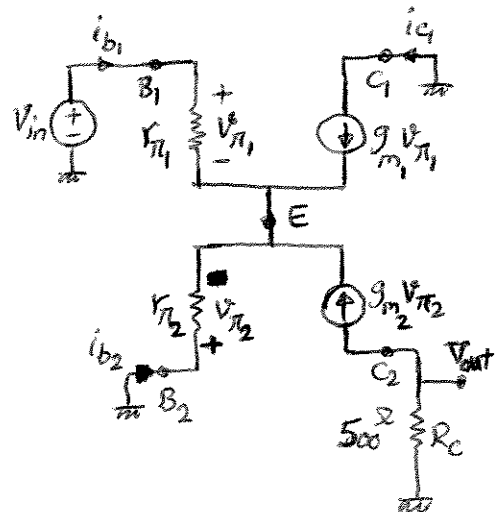
$$V_A = \infty \Rightarrow \boxed{r_o = \infty}$$



⑤4 $I_{S1} = 3I_{S2} = 5 \times 10^{-16} \text{ A}$, $\beta_1 = 100$, $\beta_2 = 50$, $V_A = \infty$

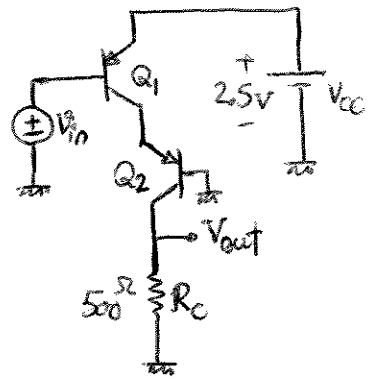a) $V_{B2} = \phi$ $\xrightarrow[\text{Forward biased by } 200 \text{ mV}]{Q_2 \text{ Base-Collector}}$ $V_{C2} = 0.2 \text{ V}$

$$\Rightarrow I_{C2_{\max}} = \frac{V_{C2_{\max}}}{R_C} = \frac{0.2 \text{ V}}{500 \Omega} \Rightarrow \boxed{I_{C2_{\max}} = 0.4 \text{ mA}}$$



As shown: $I_{C1} \approx I_{C2}$ (Note: $I_{C1} = I_{E2} = \frac{\beta_2 + 1}{\beta_2} I_{C2}$ precisely)

$$I_{C1} \approx I_{S1} e^{\frac{V_{EB1}}{V_T}} \Rightarrow V_{EB1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) \Rightarrow V_{CC} - V_{in} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$$


$$\Rightarrow \boxed{V_{in} = V_{CC} - V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)} \Rightarrow V_{in} = 2.5 - 0.026 \ln\left(\frac{4 \times 10^{-4}}{5 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{in} = 1.787 \text{ V}} \quad \text{This is minimum acceptable } V_{in}$$

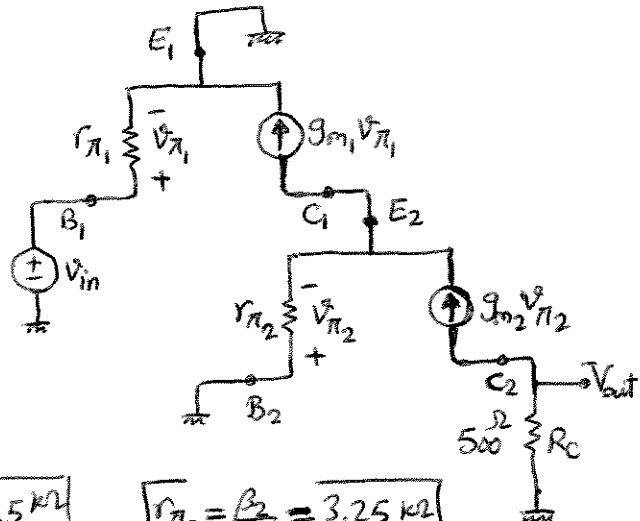b) $g_{m1} = \frac{I_{C1}}{V_T} \approx \frac{0.4 \text{ mA}}{26 \text{ mV}}$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.4 \text{ mA}}{26 \text{ mV}}$$

$$\Rightarrow \boxed{g_{m1} = g_{m2} \approx 15.4 \text{ mS}}$$



$$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{100}{\frac{0.4}{26}} \Rightarrow \boxed{r_{\pi 1} = 6.5 \text{ k}\Omega}$$


$$\boxed{r_{\pi 2} = \frac{\beta_2}{g_{m2}} = 3.25 \text{ k}\Omega}$$

$$V_{EB2} = V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right) = 26 \text{ mV} \ln\left(\frac{0.4 \times 10^{-3}}{5 \times 10^{-16}}\right) \Rightarrow \boxed{V_{EB2} \approx 741 \text{ mV}} \Rightarrow \boxed{V_{EC1} \approx 1.759 \text{ V}}$$

Q_1 in active mode

⑤ $I_{S1} = 3I_{S2} = 5 \times 10^{-16} \text{ A}$, $\beta_1 = 100$, $\beta_2 = 50$, $V_A = \infty$

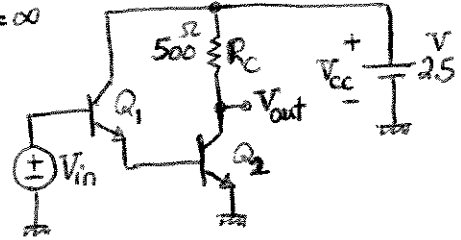a) Q_2 is softly saturated $\Rightarrow V_{BC2} = 0.2 \text{ V}$



$$V_{BC2} = 0.2 \text{ V} \Rightarrow V_{B2} - V_{C2} = 0.2 \text{ V} \Rightarrow V_{BE2} - (V_{CC} - R_C I_{C2}) = 0.2 \text{ V}$$

$$\Rightarrow V_{BE2} + R_C I_{S2} e^{\frac{V_{BE2}}{V_T}} = V_{CC} + 0.2$$

$$\Rightarrow V_{BE2} + 500 \times \frac{5}{3} \times 10^{-16} e^{\frac{V_{BE2}}{V_T}} = 2.5 + 0.2 \Rightarrow \boxed{V_{BE2} \approx 800 \text{ mV}}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) \quad I_{C2} = I_{S2} e^{\frac{V_{BE2}}{V_T}} = \frac{5}{3} \times 10^{-16} e^{\frac{800}{26}} \Rightarrow \boxed{I_{C2} \approx 3.8 \text{ mA}}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C2}/\beta_2}{I_{S1}}\right) = 26 \text{ mV} \ln\left(\frac{3.8 \times 10^{-3}}{50 \times 5 \times 10^{-16}}\right) \Rightarrow \boxed{V_{BE1} \approx 669.4 \text{ mV}}$$

$$V_{in} = V_{BE1} + V_{BE2} \Rightarrow \boxed{V_{in} \approx 1.469 \text{ V}} \quad \text{Maximum allowable value for } V_{in}$$

b)


$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{I_{C2}/\beta_2}{V_T} = \frac{3.8 \text{ mA}}{26 \text{ mV}}$$

$$\Rightarrow \boxed{g_{m1} \approx 2.9 \text{ mS}}$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{3.8 \text{ mA}}{26 \text{ mV}} \Rightarrow \boxed{g_{m2} \approx 146 \text{ mS}}$$

$$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{100}{2.9 \times 10^{-3}} \Rightarrow \boxed{r_{\pi 1} \approx 3421 \Omega}$$
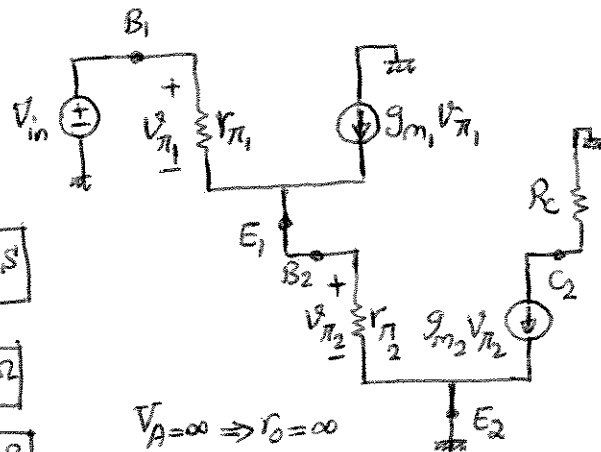
$$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{50}{146 \times 10^{-3}} \Rightarrow \boxed{r_{\pi 2} \approx 342 \Omega}$$



$$V_A = \infty \Rightarrow r_o = \infty$$

56) $I_{S1} = 2I_{S2} = 6 \times 10^{-17} \text{ A}$, $\beta_1 = 80$, $\beta_2 = 100$


a) $I_{C2} = 2 \text{ mA}$

$$V_{EB2} = V_T \ln \frac{I_{C2}}{I_{S2}} = 26 \text{ mV} \ln \left(\frac{2 \times 10^{-3}}{3 \times 10^{-17}} \right) \approx 827.6 \text{ mV}$$

$$V_{BE1} = V_T \ln \frac{I_{C1}}{I_{S1}} = 26 \text{ mV} \ln \left(\frac{2 \times 10^{-3}}{6 \times 10^{-17}} \right) \approx 689.9 \text{ mV}$$

$$V_{in} = V_{CC} - R_C I_{C2} - V_{EB2} + V_{BE1} = 2.5 - 0.5 \times 2 - 0.8276 + 0.6899$$
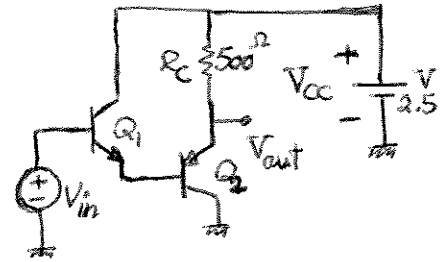
$$\Rightarrow V_{in} \approx 1.362 \text{ V}$$



b) $g_{m2} = \frac{I_{C2}}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_{m2} \approx 76.9 \text{ mS}$

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_{m1} \approx 76.9 \text{ mS}$$

$$r_{\pi1} = \frac{\beta_1}{g_{m1}} = \frac{80}{\frac{1}{1300}}$$

$$\Rightarrow r_{\pi1} = 104 \text{ k}\Omega$$

$$r_{\pi2} = \frac{\beta_2}{g_{m2}} = \frac{100}{\frac{2}{26}} \Rightarrow r_{\pi2} = 1300 \Omega$$

$$V_A = \infty \Rightarrow r_o = \infty$$

