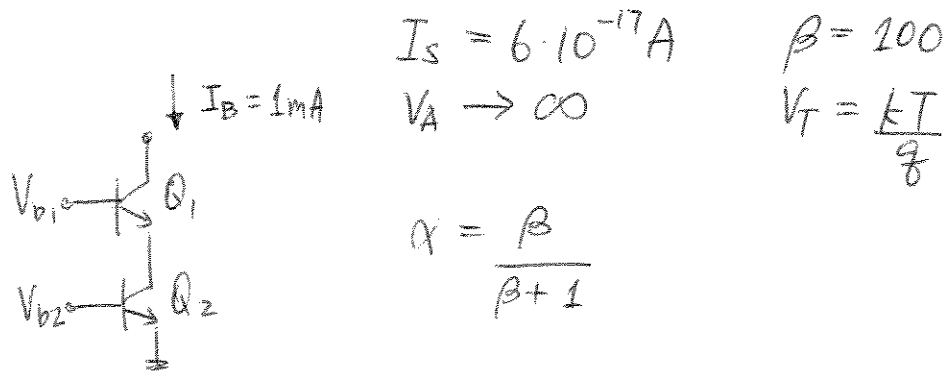


1.



$$(a) \quad V_{b2} = V_T \ln \left(\frac{I_B / \alpha^2}{I_S} \right) = (0.026 \text{ V}) \ln \left(\frac{1.02 \text{ mA}}{6 \cdot 10^{-17} \text{ A}} \right)$$

$$\approx 0.792 \text{ V}$$

(b) From the configuration,


$$V_{b1} = V_{CE2} + V_{BE1} = (V_{BE2} - 300 \text{ mV}) + V_{BE1}$$

$$V_{BE1} = V_T \ln \left(\frac{I_B}{I_S} \right) = (0.026 \text{ V}) \ln \left(\frac{1 \text{ mA}}{6 \cdot 10^{-17} \text{ A}} \right)$$

$$\approx 0.792 \text{ V}$$

$$\therefore V_{b1} = (0.792 - 0.3) + 0.79 = 1.28 \text{ V}$$

2.

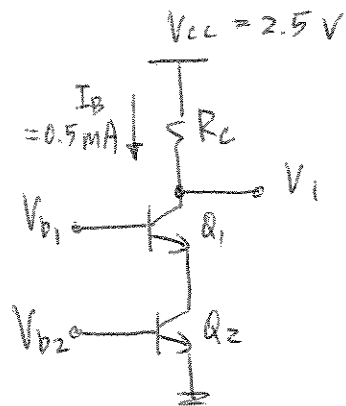

$$(a) \quad V_{b2} = V_{BE2} = V_T \ln \left(\frac{I_B / \alpha^2}{I_s} \right) = (0.026 \text{ V}) \ln \left(\frac{0.51 \text{ mA}}{6 \cdot 10^{-17} \text{ A}} \right) \\ \approx 0.774 \text{ V}$$

$$V_{BE1} = V_{b1} - V_{c2} = V_{b1} - (V_{b2} - 300 \text{ mV})$$


$$\Rightarrow V_{b1} = V_{BE1} + V_{b2} - 0.3 \text{ V} \\ = (0.026 \text{ V}) \ln \left(\frac{0.5 \text{ mA}}{6 \cdot 10^{-17} \text{ A}} \right) + (0.774 \text{ V}) - (0.3 \text{ V}) \\ \approx 1.25 \text{ V}$$

$$(b) \quad V_1 = V_{b1} - 0.3 \text{ V} = 0.95 \text{ V}$$

$$\therefore R_c = \frac{V_{cc} - V_1}{I_B} = \frac{(2.5 - 0.95) \text{ V}}{0.5 \text{ mA}} \approx 3.1 \text{ k}\Omega$$

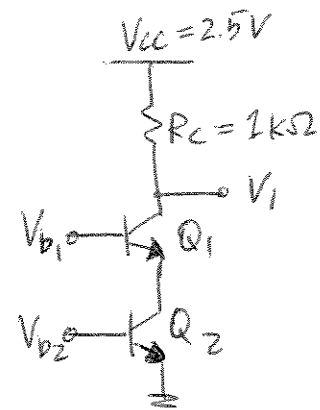3. From previous experience,
assume both V_{BE1} &
 $V_{BE2} = 0.8 \text{ V}$

$$\begin{aligned}\Rightarrow V_1 &= V_{CE1} + V_{CE2} \\ &= (V_{BE1} - 200\text{mV}) + (V_{BE2} - 200\text{mV}) \\ &= 1.2 \text{ V}\end{aligned}$$




* By KCL, maximum bias current

$$\approx \frac{V_{CC} - V_1}{R_C} = \frac{(2.5 - 1.2) \text{ V}}{1 \text{ k}\Omega} = 1.3 \text{ mA}.$$

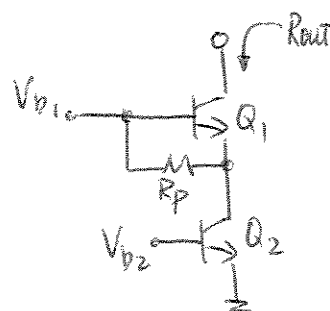
4. (a) R_p appears in parallel with $r_{\pi 1}$

$$\therefore R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{\pi 1} \parallel R_p)]r_{o1} + (r_{o2} \parallel r_{\pi 1} \parallel R_p)$$



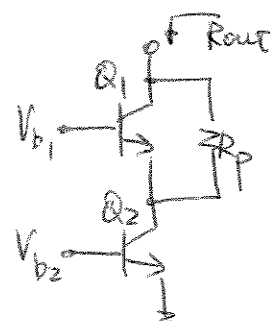
(b) R_p appears in parallel with r_{o1}

$$\therefore R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{\pi 1})](r_{o1} \parallel R_p) + (r_{o2} \parallel r_{\pi 1})$$



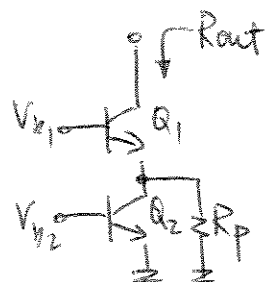
(c) R_p appears in parallel with r_{o2}

$$\therefore R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{\pi 1} \parallel R_p)]r_{o1} + (r_{o2} \parallel r_{\pi 1} \parallel R_p)$$




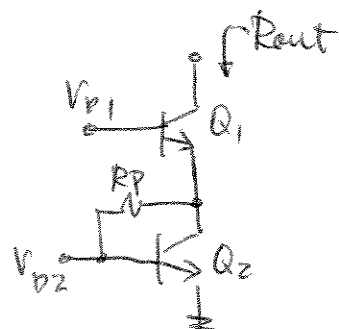(d) R_p appears in parallel with r_{o2} (in small-signal) $\therefore V_{b2}$ is AC GND.

$$\therefore R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{\pi 1} \parallel R_p)]r_{o1} + (r_{o2} \parallel r_{\pi 1} \parallel R_p)$$



5.

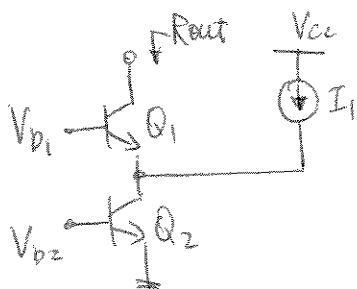

$$I_1 = 0.5 \text{ mA}$$

$$I_{C1} = 0.5 \text{ mA}$$

$$I_{C2} = 1 \text{ mA}$$

$$= 2 I_{C1}$$

$$\beta = 100 \quad V_A = 5 \text{ V}$$

$$R_{out} = g_{m1} r_{o1} (r_{o2} \parallel r_{\pi 1})$$


$$= \frac{I_{C1}}{V_T} \cdot \frac{V_A}{I_{C1}} \cdot \frac{V_{A2}/I_{C2} \cdot \beta V_T/I_{C1}}{V_{A2}/I_{C2} + \beta V_T/I_{C1}}$$

$$= \frac{V_A}{V_T} \cdot \frac{\frac{V_{A2}/2}{I_{C1}} \cdot \beta V_T/I_{C1}}{\frac{V_{A2}/2}{I_{C1}} + \beta V_T/I_{C1}} \approx \frac{1}{I_{C1}} \cdot \frac{V_A}{V_T} \cdot \frac{\beta V_A V_T}{V_A + 2\beta V_T}$$

$$= \frac{1}{0.5 \text{ mA}} \cdot \frac{5 \text{ V}}{0.026 \text{ V}} \cdot \frac{100(5 \text{ V})(0.026 \text{ V})}{(5 \text{ V}) + 2(100)(0.026 \text{ V})}$$


$$\therefore R_{out} \approx 490 \text{ k}\Omega$$

6.

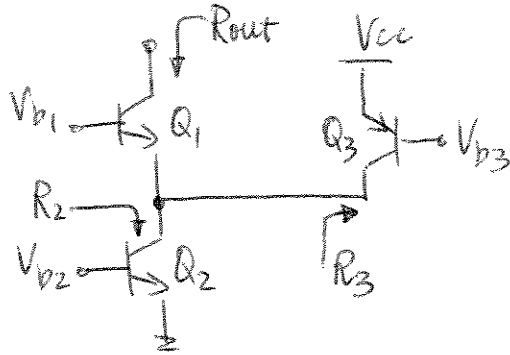

$$R_3 = r_{o3} \quad (V_{cc} \text{ \& } V_{b3} \text{ are AC GND})$$

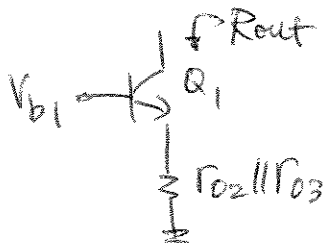
$$R_2 = r_{o2} \quad (V_{b2} \text{ is AC GND})$$



$$\therefore R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{o3} \parallel r_{\pi 1})]r_{o1} + (r_{o2} \parallel r_{o3} \parallel r_{\pi 1})$$

$$\approx g_{m1}r_{o1}(r_{o2} \parallel r_{o3} \parallel r_{\pi 1})$$

7.

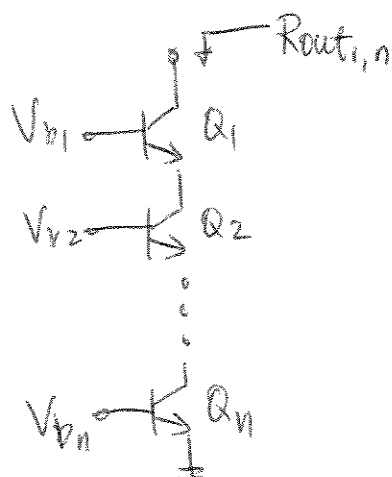

Suppose $R_{out i,j}$ is the output impedance of the cascode circuit with BJTs $Q_i, Q_{i+1}, Q_{i+2}, \dots, Q_{j-1}, Q_j$.

$$\begin{aligned}
 R_{out n-1,n} &= [1 + g_{m_{n-1}}(r_{on} \parallel r_{\pi_{n-1}})]r_{on-1} + (r_{on} \parallel r_{\pi_{n-1}}) \\
 &\approx g_{m_{n-1}}(r_{on} \parallel r_{\pi_{n-1}})r_{on-1} \approx g_{m_{n-1}}r_{\pi_{n-1}}r_{on-1} \\
 &= \beta r_o \quad (\text{usually, } r_{\pi} \ll r_o)
 \end{aligned}$$

$$\begin{aligned}
 R_{out n-2,n} &= [1 + g_{m_{n-2}}(\beta r_o \parallel r_{\pi_{n-2}})]r_o + (\beta r_o \parallel r_{\pi_{n-2}}) \\
 &\approx g_{m_{n-2}}\beta r_o r_o + r_{\pi_{n-2}} \approx \beta r_o
 \end{aligned}$$


This means that $R_{out} \approx \beta r_o$ even if an extra BJT is employed in the cascode configuration.

$$\text{i.e. } R_{out, \text{max}} \approx \beta r_o$$

$$8. (a) R_2 = (r_{\pi_2} \parallel r_{\pi_1})$$

$$\therefore R_{out} = [1 + g_{m_1} R_2] r_{o_1} + R_2$$
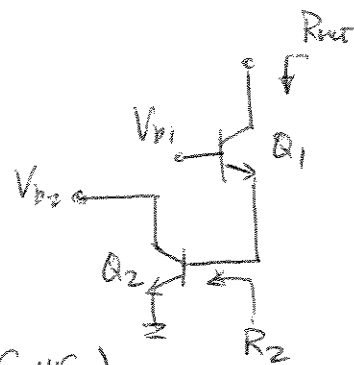
$$= [1 + g_{m_1} (r_{\pi_1} \parallel r_{\pi_2})] r_{o_1} + (r_{\pi_1} \parallel r_{\pi_2})$$



$$(b) \text{ In part (a), } I_{c_2} = \beta I_{c_1} (= I_{B_2})$$

$$\therefore R_{out(a)} = \left[1 + g_{m_1} \left(\frac{\beta V_T}{I_{c_1}} \parallel \frac{V_T}{I_{c_1}} \right) \right] r_{o_1} + (r_{\pi_1} \parallel r_{\pi_2})$$

$$\approx \left(1 + g_{m_1} \frac{V_T}{I_{c_1}} \right) r_{o_1} + \frac{V_T}{I_{c_1}}$$

$$= 2r_{o_1} + V_T/I_{c_1}$$

$$\begin{aligned} R_{out, \text{cascode}} &= [1 + g_{m_1} (r_{o_2} \parallel r_{\pi_1})] r_{o_1} + (r_{o_2} \parallel r_{\pi_1}) \\ &\approx [1 + g_{m_1} r_{\pi_1}] r_{o_1} + r_{\pi_1} \\ &\approx \beta r_{o_1} + r_{\pi_1} = \beta r_{o_1} + V_A/I_{c_1} \end{aligned}$$

Compare term-by-term:


$$\left. \begin{aligned} 2r_{o_1} &\ll \beta r_{o_1} \\ V_T &\ll V_A \end{aligned} \right\} \Rightarrow R_{out(a)} \ll R_{out, \text{cascode}}$$

i.e. using (a) reduces the effect of having a cascode configuration.

$$9. \quad R_{out} = \frac{1}{I_C} \cdot \frac{V_A}{V_T} \cdot \frac{\beta V_A V_T}{V_A + \beta V_T}$$

$$\approx \frac{1}{I_C} \cdot \frac{V_A}{V_T} \cdot \frac{\beta V_A V_T}{V_A} = \beta \frac{V_A}{I_C} = \beta r_o = R_{out, max}$$

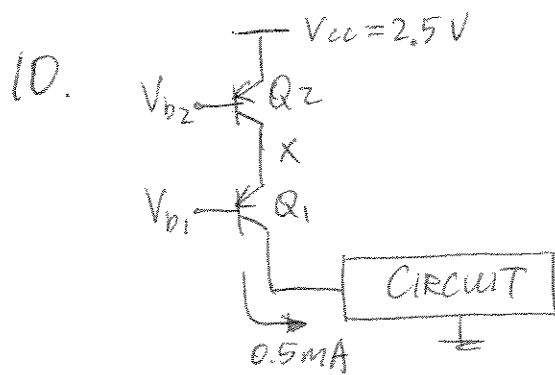This means that $R_{out, max}$ is often achieved with 2-BJT cascode.



$$I_S = 10^{-16} \text{ A} \quad \beta = 100$$

$$I_{\text{BIAS}} = 0.5 \text{ mA}$$

(a) $I_{\text{BIAS}} \approx I_{C2} = 0.5 \text{ mA}$


$$\begin{aligned} \therefore V_{b2} &= V_{cc} - |V_{be2}| \\ &= V_{cc} - V_T \ln \left(\frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \\ &= (2.5 \text{ V}) - (0.026 \text{ V}) \ln \left(\frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \approx 1.74 \text{ V} \end{aligned}$$

(b) $|V_{cb2}| = V_X - V_{b2} = 200 \text{ mV}$
 $\Rightarrow V_{c2} = V_{b2} + |V_{cb2}| = 1.94 \text{ V}$


$$\begin{aligned} \therefore V_{b1} &= V_{c2} - |V_{be1}| = V_{c2} - V_T \ln \left(\frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \\ &= (1.94 \text{ V}) - (0.026 \text{ V}) \ln \left(\frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \approx 1.18 \text{ V} \end{aligned}$$

\Rightarrow Maximum allowable $V_{b1} = 1.18 \text{ V}$

11. (a)

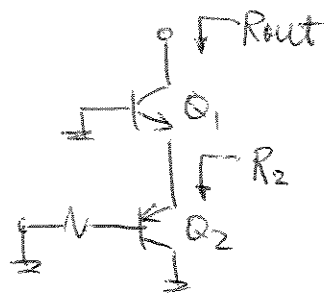

(Ac-small signal)

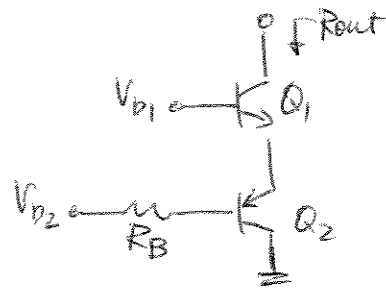


Looking into emitter of Q_2 ,

$$R_2 = \frac{1}{\left(\frac{\beta+1}{R_B + r_{\pi 2}} + \frac{1}{r_{o2}} \right)}$$

$$\Rightarrow R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})] r_{o1} + (R_2 \parallel r_{\pi 1})$$


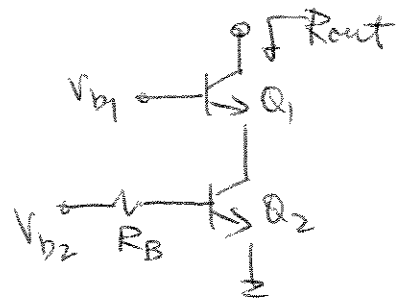
(b) R_B does not affect Q_2 in small-signal R_{out} :

$$\therefore R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{\pi 1})] r_{o1} + (r_{o2} \parallel r_{\pi 1})$$



This is a cascode stage.

(c) Use small-signal analysis:

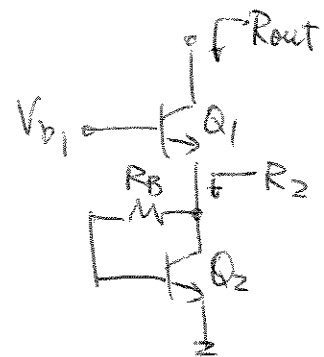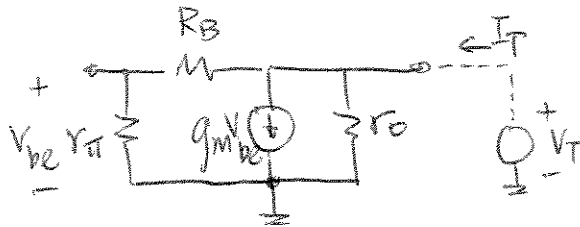


$$\text{By KCL, } I_T = \frac{V_T}{R_B + r_{\pi 2}} + g_{m2} \frac{V_T r_{\pi 2}}{r_{\pi 2} + R_B} + \frac{V_T}{r_{o2}}$$

$$\Rightarrow R_2 = \frac{V_T}{I_T} = \frac{1}{\left(\frac{\beta+1}{R_B + r_{\pi 2}} + \frac{1}{r_{o2}} \right)} \approx \frac{1}{\beta / (R_B + r_{\pi 2}) + 1/r_{o2}}$$

$$\therefore R_{out} = [1 + g_{m1} (R_2 \parallel r_{\pi 1})] r_{o1} + (R_2 \parallel r_{\pi 1})$$

$$\approx g_{m1} r_{o1} (R_2 \parallel r_{\pi 1})$$

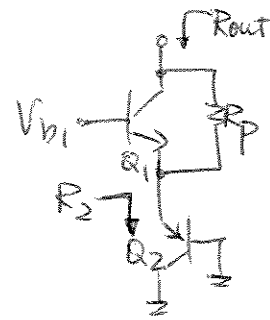(d) R_p appears in parallel with r_{o1} .



$$R_2 = r_{o2} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$\approx r_{o2} \parallel \frac{r_{\pi 2}}{\beta} \parallel r_{\pi 2}$$


$$\approx r_{o2} \parallel (r_{\pi 2}/\beta) \approx r_{\pi 2}/\beta$$

$$\therefore R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})](r_{o1} \parallel R_p) + (R_2 \parallel r_{\pi 1})$$

$$\approx g_{m1}(r_{o1} \parallel R_p)(r_{\pi 1} \parallel R_2)$$

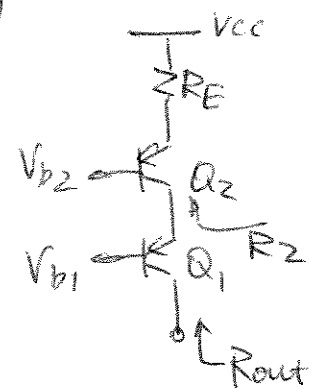(e) $R_2 = [1 + g_{m2}(R_E \parallel r_{\pi 2})]r_{o2} + (R_E \parallel r_{\pi 2})$

$$\approx g_{m2}(R_E \parallel r_{\pi 2})r_{o2}$$



$$\therefore R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})]r_{o1} + (R_2 \parallel r_{\pi 1})$$

$$\approx g_{m1}(R_2 \parallel r_{\pi 1})r_{o1}$$

$$= g_{m1} [g_{m2} r_{o2} (R_E \parallel r_{\pi 2}) \parallel r_{\pi 1}] r_{o1}$$


This is a cascode stage.

(f) $R_2 = r_{o2}$

$$\therefore R_{out} = [1 + g_{m1}(R_2 \parallel r_{\pi 1})] r_{o1} + (R_2 \parallel r_{\pi 1})$$

$$\approx g_{m1} r_{o1} (R_2 \parallel r_{\pi 1})$$

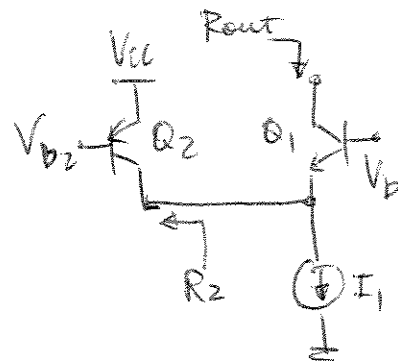
$$= g_{m1} r_{o1} (r_{\pi 1} \parallel r_{o2})$$



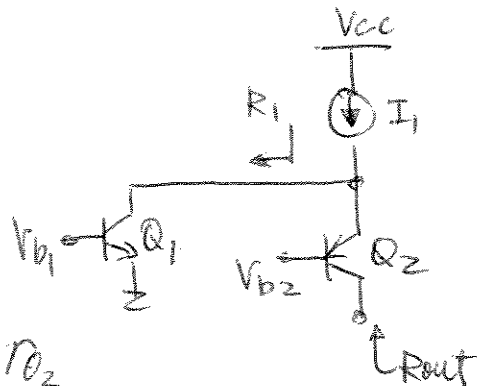
(g) $R_1 = r_{o1}$
(output impedance of a common-emitter.)

$$\therefore R_{out} = [1 + g_{m2}(R_1 \parallel r_{\pi 2})] r_{o2} + (R_1 \parallel r_{\pi 2})$$

$$\approx g_{m2} r_{o2} (r_{o1} \parallel r_{\pi 2})$$



12.

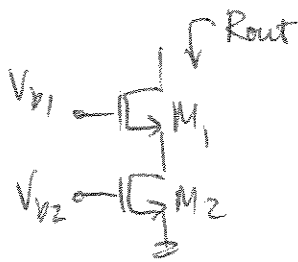

$$I_D = 0.5 \text{ mA} \quad R_{out} \geq 50 \text{ k}\Omega$$

$$\mu_n C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2} \quad \frac{W}{L} = \frac{20}{0.18}$$

Calculate max λ .

Assume M_1 & M_2 in saturation.


$$\begin{aligned} \Rightarrow R_{out} &\approx g_{m1} r_{o1} r_{o2} \\ &= \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \times \frac{1}{\lambda I_D} \times \frac{1}{\lambda I_D} \geq 50 \text{ k}\Omega. \end{aligned}$$

(All quantities are known).

Solve for λ :

$$\lambda_{\max} \approx 0.51 \text{ V}^{-1}$$

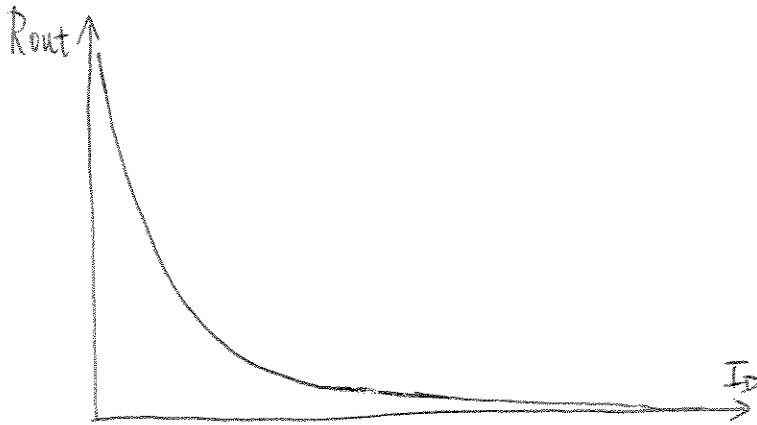
$$\begin{aligned}
 13. (a) \quad R_{out} &= g_{m1} r_{o1} r_{o2} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \cdot \frac{1}{\lambda I_D} \cdot \frac{1}{\lambda I_D} \\
 &= 2 \mu_n C_{ox} (W/L) \cdot (I_D)^{-3/2}
 \end{aligned}$$



$$\begin{aligned}
 (b) \quad R_{out} (BJT) &\propto I_B^{-1} \\
 R_{out} (MOS) &\propto I_D^{-3/2}
 \end{aligned}$$

\therefore MOS cascode is a stronger function of I in terms of R_{out} .

14.

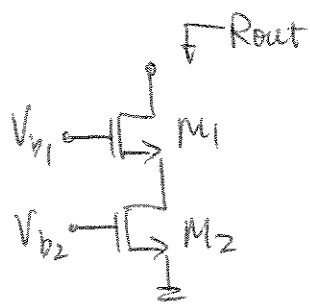

$$\left(\frac{W}{L}\right)_1 = 30/0.18 \quad \left(\frac{W}{L}\right)_2 = 20/0.18$$

$$I_{BIAS} = 0.5 \text{ mA}$$

$$\mu_n C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2} \quad V_{TH} = 0.4 \text{ V}$$

$$(a) \quad I_{D2} = I_{BIAS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH})^2$$

$$\begin{aligned} \Rightarrow V_{b2} &= \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} + V_{TH} \\ &= \sqrt{\frac{2 (0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{\text{V}^2}) (20/0.18)}} + 0.4 \text{ V} \approx 0.7 \text{ V} \end{aligned}$$

M_2 operates in saturation as long as

$$V_{GS2} - V_{TH} \leq V_{DS2} \Rightarrow V_{DS2} \geq 0.3 \text{ V.}$$

Observe that $V_{GS1} = V_{b1} - V_{DS2}$

$$I_{D1} = I_{BIAS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{b1} - V_{DS2} - V_{TH})^2$$

$$\Rightarrow V_{b1} \geq \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + 0.4 \text{ V} + 0.3 \text{ V}$$


$$= \sqrt{\frac{2 (0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{\text{V}^2}) (30/0.18)}} + 0.7 \text{ V} \approx 0.95 \text{ V.}$$

\therefore Minimum $V_{b1} = 0.95 \text{ V.}$

$$(b) \quad R_{out} = (1 + g_{m1} r_{o2}) r_{o1} + r_{o2}$$

$$\begin{aligned}
 &= \left(1 + \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L} \right)_1 I_{BIAS}} \cdot \frac{1}{\lambda I_{BIAS}} \right) \cdot \frac{1}{\lambda I_{BIAS}} + \frac{1}{\lambda I_{BIAS}} \\
 &= \left[1 + \sqrt{2 \left(100 \frac{\mu A}{V^2} \right) \left(\frac{30}{0.18} \right) (0.5 \text{ mA})} \cdot \frac{1}{(0.1)(0.5 \text{ m})} \right] \cdot \frac{1}{(0.1)(0.5 \text{ m})} \\
 &\quad + \frac{1}{(0.1)(0.5 \text{ mA})} \\
 &\approx 1.67 \text{ M}\Omega
 \end{aligned}$$

15.

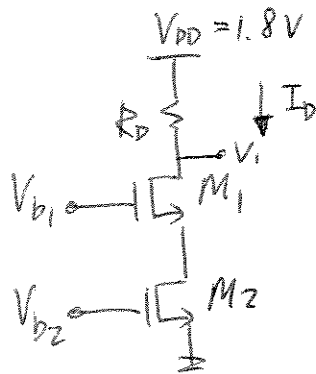

$$\left(\frac{W}{L}\right)_1 = \frac{20}{0.18} \quad \left(\frac{W}{L}\right)_2 = \frac{40}{0.18}$$

$$\mu_n C_{ox} = 100 \frac{\mu A}{V^2} \quad V_{TH} = 0.4 V$$

$$I_D = 1 mA \quad R_D = 500 \Omega$$

(a) Both M_1 & M_2 must stay in saturation.

$$\Rightarrow V_i = 1.8 - I_D R_D = 1.8 - (1mA)(500\Omega) = 1.3 V$$

Want this value equal to that which makes M_1 operates at the edge of saturation.



$$\therefore V_{b1} = V_i + V_{TH} = 1.3 + 0.4 = 1.7 V$$

$$(b) \quad I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \cdot [(V_{b1} - V_x) - V_{TH}]^2 = 1 mA$$

$$\begin{aligned} \Rightarrow V_x &= V_{b1} - V_{TH} - \sqrt{\frac{2 I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \\ &= (1.7 V) - (0.4 V) - \sqrt{\frac{2(1mA)}{(100 \mu A/V^2)(20/0.18)}} \end{aligned}$$

$$\approx 1.276 V$$



1b. (a) First compute R_x :

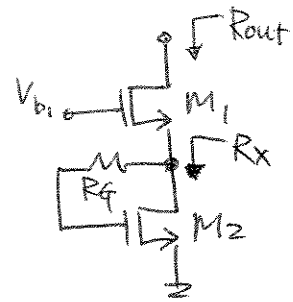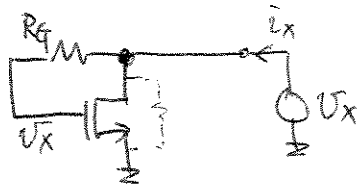

$$I_x = g_{m2}v_x + v_x/r_{o2} \Rightarrow R_x = v_x/i_x = \frac{1}{g_{m2} + 1/r_{o2}}$$


$$\therefore R_{out} = g_{m1}r_{o1}R_x = \frac{g_{m1}r_{o1}}{g_{m2} + 1/r_{o2}}$$

(b) Equivalent circuit:

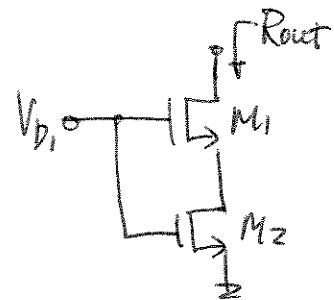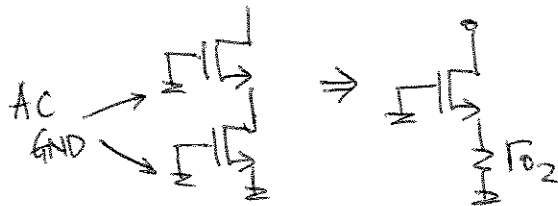

$$\therefore R_{out} = g_{m1}r_{o1}r_{o2}$$

(c) Equivalent Circuit:

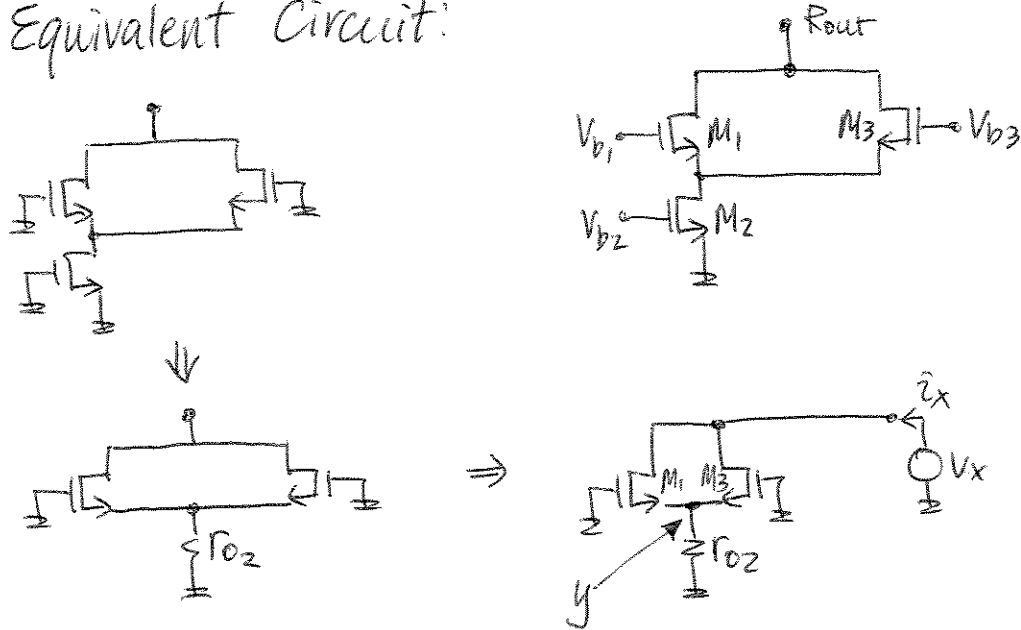

By KCL, $V_y = i_x \cdot r_{o2}$ ①

$$i_x = g_{m1}(-V_y) + g_{m3}(-V_y) + (V_x - V_y)\left(\frac{1}{r_{o1}} + \frac{1}{r_{o3}}\right)$$
②



Substitute ① into ② and re-arrange:

$$R_{out} = \frac{V_x}{i_x} = (r_{o1} \parallel r_{o3}) + r_{o2}(r_{o1} \parallel r_{o3})(g_{m1} + g_{m3}) + r_{o2}$$

$$\approx r_{o2}(r_{o1} \parallel r_{o3})(g_{m1} + g_{m3})$$

(Intuitively this makes sense because we have 2 NMOSs in parallel — $\ominus = g_m v_{gs}$ adds up, and r_o 's are splitting total current, i_x . This is as if an equivalent NMOS replacing M_1 & M_3 with $g_m = (g_{m1} + g_{m3})$ & $r_o = (r_{o1} \parallel r_{o3})$.)

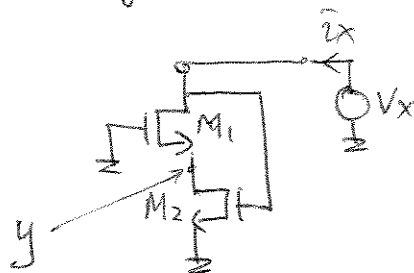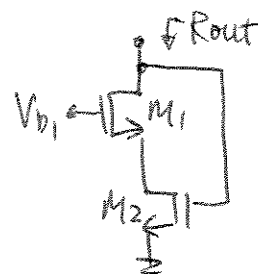(d) Examine the equivalent circuit with a test voltage:



By observation, i_x must flow through both M_1 & M_2 .

$$\text{By KCL, } \bar{i}_x = g_{m2} V_x + V_y / r_{o2}$$


$$\bar{i}_x = g_{m1} (-V_y) + (V_x - V_y) / r_{o1}$$

Substitute ① into ② and re-arrange:

$$R_{out} = \frac{V_x}{\bar{i}_x} = \frac{g_{m1} r_{o2} + \frac{r_{o2}}{r_{o1}} + 1}{g_{m1} g_{m2} r_{o2} + (g_{m2} r_{o2} + 1) \left(\frac{1}{r_{o1}} \right)}$$

$$\approx \frac{r_{o2} \left(g_{m1} + \frac{1}{r_{o1}} \right)}{g_{m2} r_{o2} \left(g_{m1} + \frac{1}{r_{o1}} \right)} \approx \frac{1}{g_{m2}}$$

17.

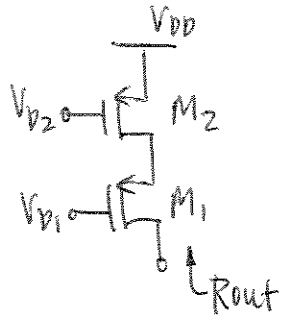

$$I_{BIAS} = 0.5 \text{ mA}$$

$$R_{out} = 40 \text{ k}\Omega$$

$$\mu_p C_{ox} = 50 \text{ } \mu\text{A/V}^2$$

$$\lambda = 0.2 \text{ V}^{-1}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$

$$R_{out} = 40 \text{ k}\Omega = (g_{m1} r_{o2} + 1) r_{o1} + r_{o2}$$


$$\Rightarrow g_{m1} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_{BIAS}} = \left(\frac{R_{out} - r_{o2}}{r_{o1}} - 1\right) \cdot \frac{1}{r_{o2}}$$

$$\therefore \left(\frac{W}{L}\right)_1 = \left[\left(\frac{R_{out} - r_{o2}}{r_{o1}} - 1\right) \frac{1}{r_{o2}} \right]^2 \cdot \frac{1}{2 \mu_p C_{ox} I_{BIAS}}$$

$$= \left\{ \left[\frac{(40 \text{ k}\Omega) - [0.2 \times 0.5 \text{ m}]}{[0.2 \times 0.5 \text{ m}]^{-1}} - 1 \right] \cdot [0.2 \cdot 0.5 \text{ m}] \right\}^2 \cdot \frac{1}{2 (50 \frac{\mu\text{A}}{\text{V}^2}) (0.5 \text{ mA})}$$

$$\approx 0.8$$

18.

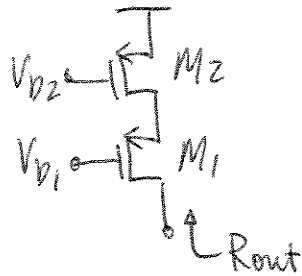


$$R_{out} = g_{m1} r_{o1} r_{o2} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_D} \cdot \frac{1}{\lambda I_D} \cdot \frac{1}{\lambda I_D}$$

If W_1 & W_2 increase by N times and L_1, L_2 , and I_D remain unchanged:


$$\begin{aligned} R_{out}(\text{new}) &= \sqrt{2\mu_p C_{ox} \left(\frac{NW}{L}\right) I_D} \cdot \left(\frac{1}{\lambda I_D}\right)^2 \\ &= \sqrt{N} \sqrt{2\mu_p C_{ox} \frac{W}{L} I_D} \left(\frac{1}{\lambda I_D}\right)^2 = \sqrt{N} R_{out} \end{aligned}$$

$\therefore R_{out}$ is increased by \sqrt{N} times.

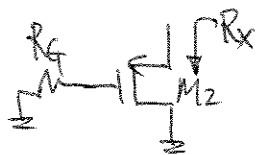19. (a) R_x is the input impedance of a common-gate configuration:



"Looking into" the source of M_2 ,

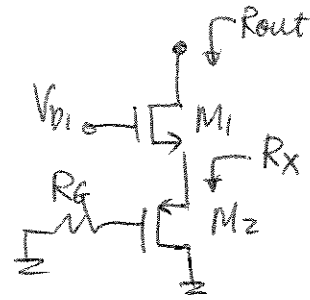


$$R_x = \frac{1}{g_{m2}} \parallel r_{o2}$$

$$\therefore R_{out} = g_{m1} r_{o1} R_x = g_{m1} r_{o1} \left(\frac{1}{g_{m2}} \parallel r_{o2} \right)$$

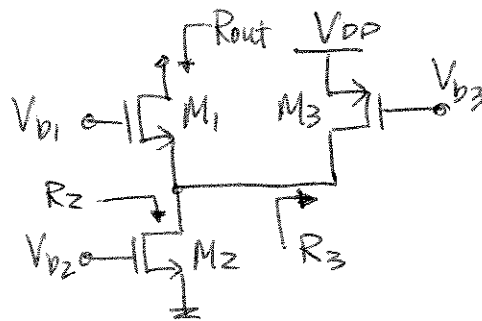(b) From observation,
 $\rightarrow R_3 = r_{o3}$ ($\because V_{sg} = 0$ in AC)

$\rightarrow R_2 = r_{o2}$ ($\because V_{sg} = 0$ in AC)




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 \parallel R_3) = g_{m1} r_{o1} (r_{o2} \parallel r_{o3})$$

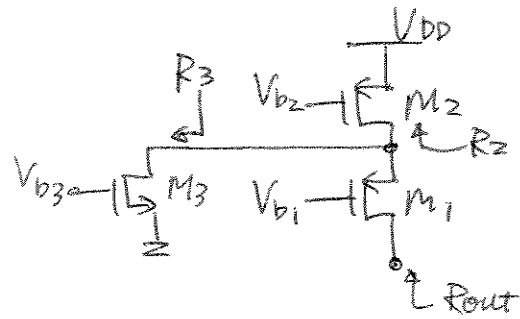(c) By observation,

$$R_2 = r_{o2} \quad (V_s = V_G = AC \text{ GND})$$

$$R_3 = r_{o3} \quad (V_s = V_G = AC \text{ GND})$$




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 || R_3) = g_{m1} r_{o1} (r_{o2} || r_{o3})$$



(d) $R_x = g_{m2} r_{o2} r_{o3}$

$$\Rightarrow R_{out} = g_{m1} r_{o1} R_x$$

$$= g_{m1} g_{m2} r_{o1} r_{o2} r_{o3}$$

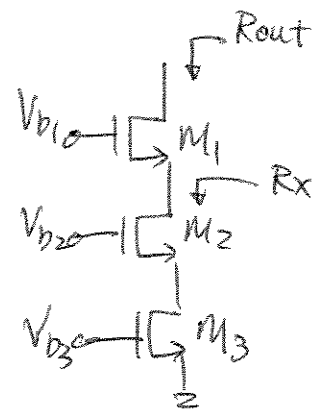

20.(a) Equivalent circuit :

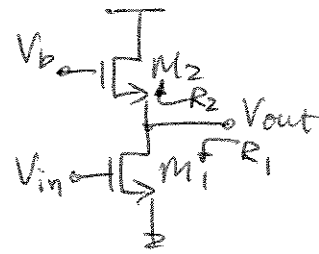
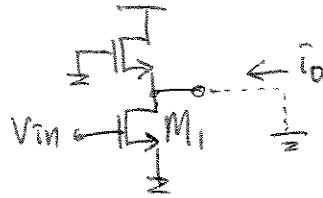


$$\bar{i}_o = G_m V_{in} \Rightarrow G_m = \frac{\bar{i}_o}{V_{in}} = g_{m1}$$

$$R_1 = r_{o1} ; R_2 = 1/g_{m2}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} (r_{o1} \parallel 1/g_{m2})$$

(b) Equivalent circuit :

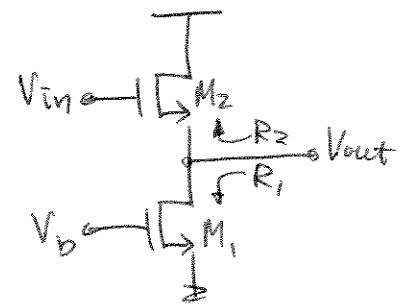
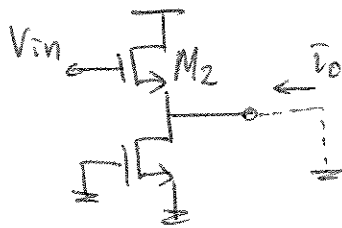


$$-\bar{i}_o = g_{m2} V_{in} \Rightarrow G_m = \frac{\bar{i}_o}{V_{in}} = -g_{m2}$$

$$R_1 = r_{o1} ; R_2 = 1/g_{m2}$$

$$\therefore A_v = -G_m R_{out} = g_{m2} (r_{o1} \parallel 1/g_{m2})$$

(c) Equivalent circuit:

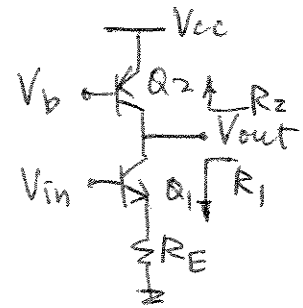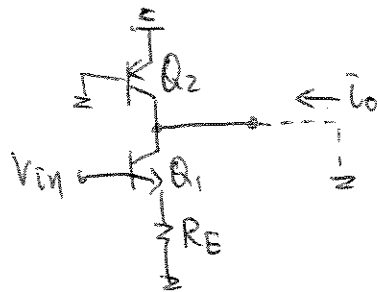

With output node shorted, this is a common-emitter stage with degeneration.

$$\Rightarrow G_m = \frac{g_{m1}}{g_{m1}(R_E \parallel r_{o1}) + 1}$$



$$R_1 = [1 + g_{m1}(R_E \parallel r_{\pi1})] r_{o1} + (R_E \parallel r_{\pi1})$$

$$R_2 = r_{o2}$$

$$\Rightarrow R_{out} = R_1 \parallel R_2$$

$$\therefore A_v = -G_m R_{out} = - \frac{g_{m1} (\{ [1 + g_{m1}(R_E \parallel r_{\pi1})] r_{o1} + (R_E \parallel r_{\pi1}) \} \parallel r_{o2})}{g_{m1}(R_E \parallel r_{o1}) + 1}$$

(d) Equivalent circuit:

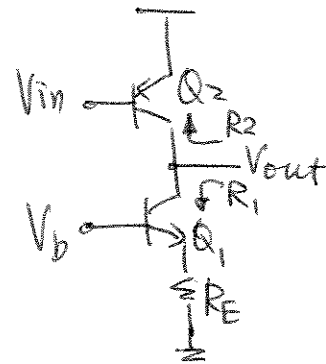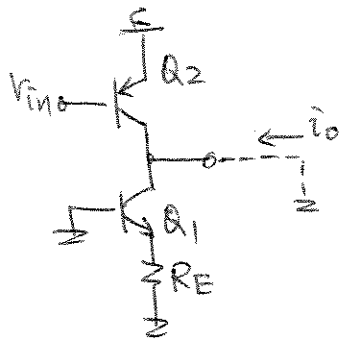

With output shorted to AC GND, circuit becomes a simple common-emitter stage:

$$\Rightarrow G_m = g_{m2}$$



$$R_1 = [1 + g_{m1}(R_E \parallel r_{\pi 1})]r_{o1} + (R_E \parallel r_{\pi 1})$$

$$R_2 = r_{o2}$$

$$\Rightarrow R_{out} = R_1 \parallel R_2$$

$$\therefore A_v = -G_m R_{out} = -g_{m2} \left(\{ [1 + g_{m1}(R_E \parallel r_{\pi 1})]r_{o1} + (R_E \parallel r_{\pi 1}) \} \parallel r_{o2} \right)$$

(e) Equivalent circuit:

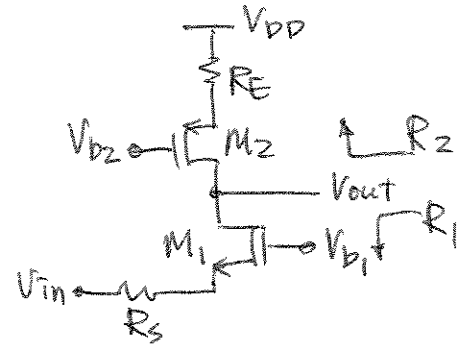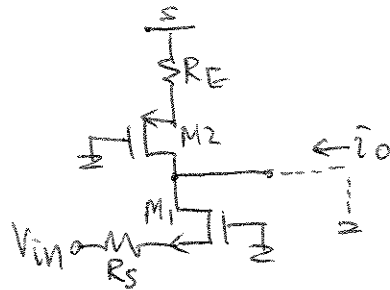

Observing that \bar{i}_o must flow through M_1 only:

$$\bar{i}_o = g_{m1} \overbrace{-(V_{in} + \bar{i}_o R_S)}^{\text{gate voltage of } M_1}$$

$$\Rightarrow G_m = \frac{\bar{i}_o}{V_{in}} = \frac{-g_{m1}}{1 + g_{m1} R_S}$$

$$R_1 = (1 + g_{m1} R_S) r_{o1} + R_S$$



$$R_2 = (1 + g_{m2} R_E) r_{o2} + R_E$$

$$R_{out} = R_1 \parallel R_2$$

$$\therefore A_v = -G_m R_{out}$$

$$= \frac{g_{m1}}{1 + g_{m1} R_S} \left\{ [(1 + g_{m1} R_S) r_{o1} + R_S] \parallel [(1 + g_{m2} R_E) r_{o2} + R_E] \right\}$$

(f) Equivalent circuit:

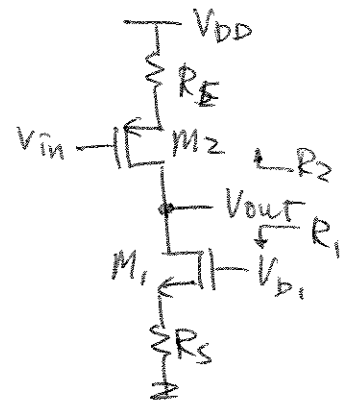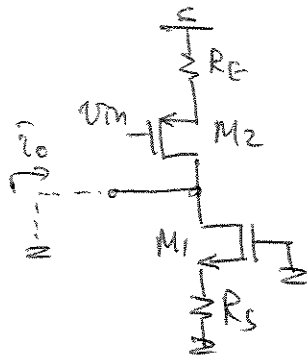

This is a common-source stage with degeneration:

$$\Rightarrow G_m = \frac{g_{m2}}{1 + g_{m2} R_E}$$


$$R_1 = (1 + g_{m1} R_S) r_{o1} + R_S$$

$$R_2 = (1 + g_{m2} R_E) r_{o2} + R_E$$

$$\therefore A_v = -G_m (R_1 \parallel R_2)$$


$$= \frac{g_{m2}}{1 + g_{m2} R_E} \left\{ [(1 + g_{m1} R_S) r_{o1} + R_S] \parallel [(1 + g_{m2} R_E) r_{o2} + R_E] \right\}$$

(g) Equivalent circuit:

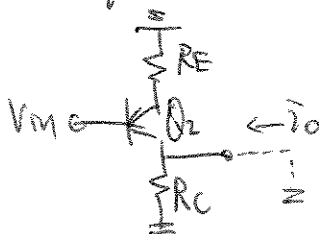

$$\Rightarrow G_m = \frac{g_{m2}}{1 + g_{m2} (R_E \parallel r_{\pi 2})}$$
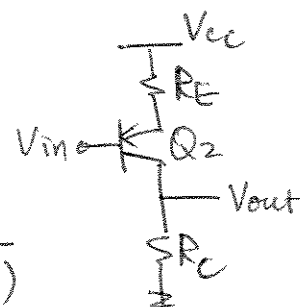
$$R_{out} = \left\{ [1 + g_{m2} (R_E \parallel r_{\pi 2})] r_{o2} + (R_E \parallel r_{\pi 2}) \right\} \parallel R_C$$




$$\Rightarrow A_v = -G_m R_{out} = \frac{g_{m2} R_{out}}{1 + g_{m2} (R_E \parallel r_{\pi 2})}$$

$$\begin{aligned}
 21. \quad A_v &= -g_{m1} r_{o1} g_{m1} (r_{o1} \parallel r_{\pi 2}) \\
 &= -\frac{I_{c1}}{V_T} \cdot \frac{V_{A1}}{I_{c1}} \cdot \frac{I_{c1}}{V_T} \cdot \frac{1}{\frac{I_{c1}}{V_{A1}} + \frac{I_{c2}}{\beta V_T}}
 \end{aligned}$$

Since $I_{c1} \approx I_{c2}$,

$$A_v \approx -\frac{V_{A1}/V_T^2}{\frac{1}{V_{A1}} + \frac{1}{\beta V_T}} = -\frac{\beta V_A^2}{V_T(V_A + \beta V_T)}$$

22.

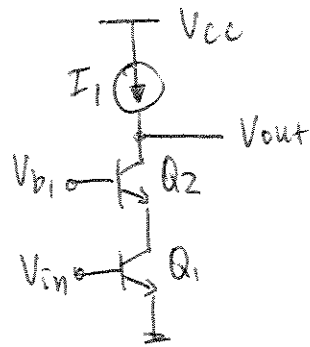

$$A_v = 500$$


$$I_1 = 1 \text{ mA}$$

$$\beta_1 = \beta_2 = 100$$

Determine minimum $V_{A1} = V_{A2}$.

Using small-signal analysis,
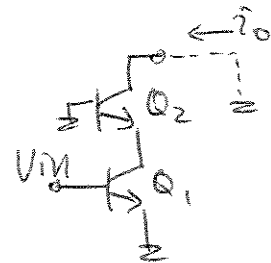
$$G_m = \frac{i_o}{v_{in}} = g_{m1} \left(\frac{\beta + 1}{\beta} \right) = \frac{I_1}{V_T} \left(\frac{\beta + 1}{\beta} \right)$$



$$R_{out} = [1 + g_{m2}(r_{o1} \parallel r_{\pi 2})]r_{o2} + (r_{o1} \parallel r_{\pi 2})$$

$$\approx g_{m2}(r_{o1} \parallel r_{\pi 2})r_{o2} = \frac{\beta V_A^2}{I_C(V_A + \beta V_T)}$$

$$\Rightarrow A_v = -G_m R_{out}$$

$$= -\frac{I_1}{V_T} \left(\frac{\beta + 1}{\beta} \right) \cdot \frac{\beta V_A^2}{I_C(V_A + \beta V_T)} = 500$$

\Rightarrow All values are given. V_A is solved using the quadratic formula:

$$\therefore V_A \approx 0.65 \text{ V}$$


23. (a) Even though R_{out} is independent of where V_{in} is applied, G_m changes:



The circuit is a common-emitter with degeneration, which always has $G_m \leq G_m$ of common-emitter stage without degeneration.

Alternatively, this circuit has less gain because it only has one amplifier stage.


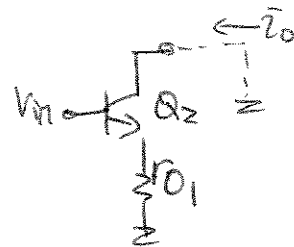
$$(b) \quad G_m = \frac{\bar{i}_o}{V_{in}} = \frac{g_{m2}}{1 + g_{m2}(r_{o1} \parallel r_{o2})}$$



$$R_{out} = [1 + g_{m2}(r_{o1} \parallel r_{\pi 2})] r_{o2} + r_{o1}$$

$$\Rightarrow A_v = -G_m R_{out} = \frac{g_{m2} \{ [1 + g_{m2}(r_{o1} \parallel r_{\pi 2})] [r_{o2} + r_{o1}] \}}{1 + g_{m2}(r_{o1} \parallel r_{o2})}$$

24. Equivalent circuit:

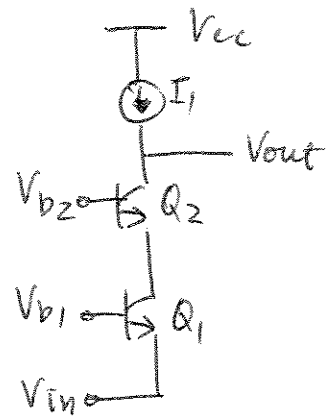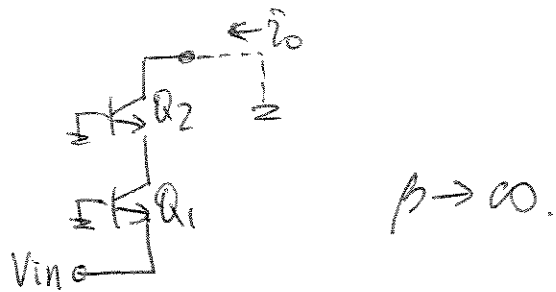


$$G_m = \frac{\bar{i}_o}{V_{in}} \approx -g_{m1}$$

$$R_{out} = [1 + g_{m2}(r_{o1} \parallel r_{\pi 2})] r_o + (r_{o1} \parallel r_{\pi 2})$$

$$\Rightarrow A_v = -G_m R_{out} = g_{m1} [\{1 + g_{m2}(r_{o1} \parallel r_{\pi 2})\} r_{o2} + (r_{o1} \parallel r_{\pi 2})]$$


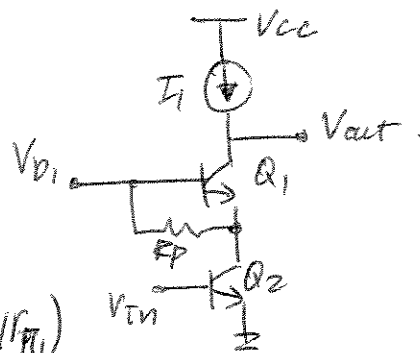
25. (a) From lecture,
we know that
the voltage gain of
a BJT cascode
circuit $\approx -g_{m2} r_{o2} g_{m1} (r_{o2} \parallel r_{\pi 1})$



This circuit resembles such, and the
only difference is that $r_{\pi 1}$ now
becomes $(r_{\pi 1} \parallel R_p)$

$$\therefore A_v \approx -g_{m2}^2 r_{o2} (r_{o2} \parallel r_{\pi 1} \parallel R_p)$$

(b) Equivalent circuit:

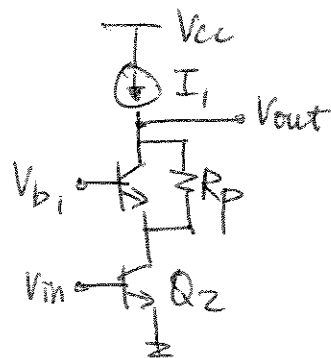
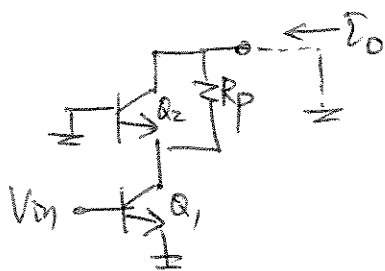


$$G_m = \frac{i_o}{V_{in}} = \frac{\beta+1}{\beta} g_{m1} \approx g_{m1}$$

$$R_{out} = [1 + g_{m2} (r_{o1} \parallel r_{\pi 2})] (r_{o2} \parallel R_p) + (r_{o1} \parallel r_{\pi 2})$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} \{ [1 + g_{m2} (r_{o1} \parallel r_{\pi 2})] (r_{o2} \parallel R_p) + (r_{o1} \parallel r_{\pi 2}) \}$$

(c) Equivalent circuit:

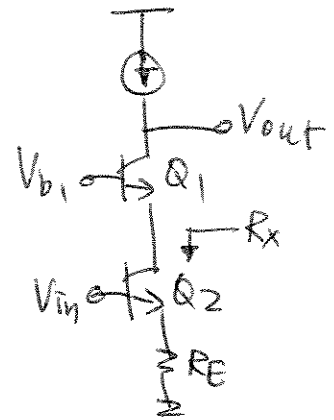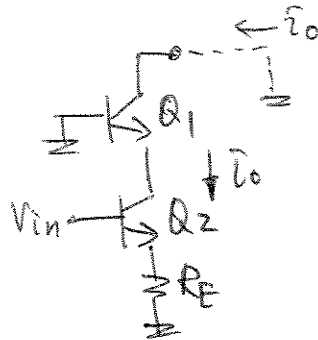



$$G_m = \frac{\bar{i}_o}{V_{in}} = \frac{g_{m2}}{1 + g_{m2}R_E} \quad (\text{small-signal analysis})$$

$$\begin{aligned} R_{out} &= (1 + g_{m1}R_x)R_{01} + R_x \\ &= [1 + g_{m1}[(1 + g_{m2}R_E)R_{02} + R_E]]R_{01} \\ &\quad + [(1 + g_{m2}R_E)R_{02} + R_E] \end{aligned}$$

$$\therefore A_v = -G_m R_{out}$$

$$= \frac{g_{m2}}{1 + g_{m2}R_E} \{ [1 + g_{m1}[(1 + g_{m2}R_E)R_{02} + R_E]]R_{01} + [(1 + g_{m2}R_E)R_{02} + R_E] \}$$

(d) Equivalent circuit:

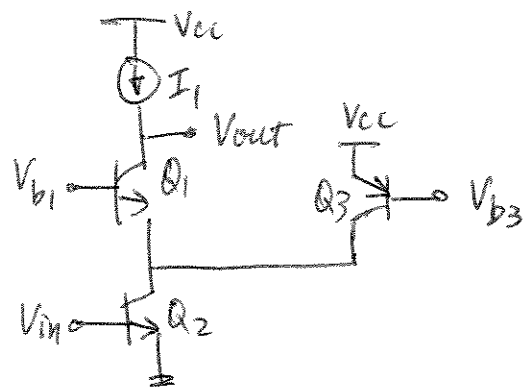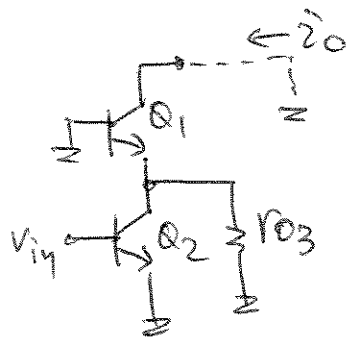

This resembles the BJT cascode topology, only now r_{o2} becomes $(r_{o2} || r_{o3})$


$$\Rightarrow A_v \approx -g_{m2}^2 (r_{o2} || r_{o3}) (r_{o2} || r_{o3} || r_{\pi 1})$$

$$Zb. A_v = -g_{m1} \left\{ \underbrace{[g_{m2} r_{o2} (r_{o1} \parallel r_{\pi2})]}_{R_{on}} \parallel \underbrace{[g_{m3} r_{o3} (r_{o4} \parallel r_{\pi3})]}_{R_{op}} \right\} V_{b3}$$

$$R_{on} = \frac{(V_{AN}/V_T)}{\left(\frac{1}{V_{AN}} + \frac{1}{\beta_n V_T}\right) I_C}$$

$$R_{op} = \frac{(V_{AP}/V_T)}{\left(\frac{1}{V_{AP}} + \frac{1}{\beta_p V_T}\right) I_C}$$

$$g_{m1} = \frac{I_C}{V_T}$$


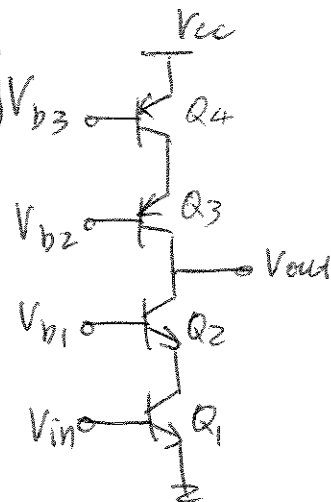


$$\therefore A_v = \frac{-(I_C/V_T)}{\frac{\left(\frac{1}{V_{AN}} + \frac{1}{\beta_n V_T}\right) I_C}{V_{AN}/V_T} + \frac{\left(\frac{1}{V_{AP}} + \frac{1}{\beta_p V_T}\right) I_C}{V_{AP}/V_T}}$$

$$= \frac{V_{AN} \cdot V_{AP}}{V_T^2 \left(\frac{V_{AP}}{V_{AN}} + \frac{V_{AP}}{\beta_n V_T} + \frac{V_{AN}}{V_{AP}} + \frac{V_{AN}}{\beta_p V_T} \right)}$$

$\therefore A_v$ is independent of bias current, I_C .

27. Equivalent circuit.

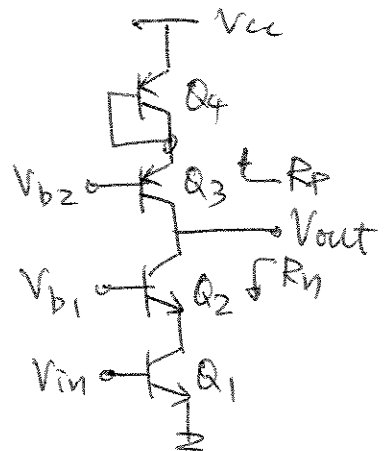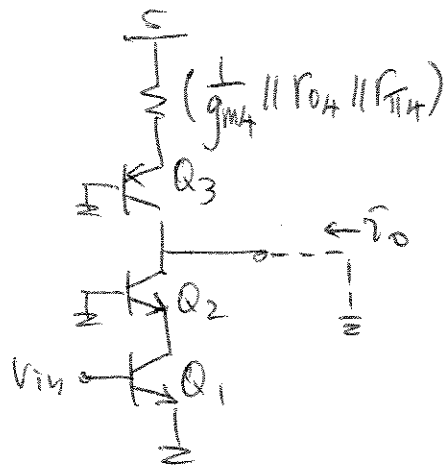

$$G_m = g_{m1} = \frac{\bar{i}_o}{v_{in}} = \frac{\bar{i}_{e1}}{v_{in}}$$


$$R_{out} = R_p \parallel R_n$$

$$R_p = [1 + g_{m3} (\frac{1}{g_{m4}} \parallel r_{o4} \parallel r_{\pi4} \parallel r_{\pi3})] r_{o3} + [\frac{1}{g_{m4}} \parallel r_{o4} \parallel r_{\pi4} \parallel r_{\pi3}]$$

$$R_n = [1 + g_{m2} (r_{o1} \parallel r_{\pi2})] r_{o2} + (r_{o1} \parallel r_{\pi2})$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} (R_p \parallel R_n)$$


$$\begin{aligned}
 28. |A_v| &= \frac{g_{m1} r_{o1} g_{m2} r_{o2}}{\sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_D} \cdot \frac{1}{\lambda I_D} \cdot \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_D} \cdot \frac{1}{\lambda I_D}} \\
 &= \frac{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2}{\lambda^2 I_D}
 \end{aligned}$$

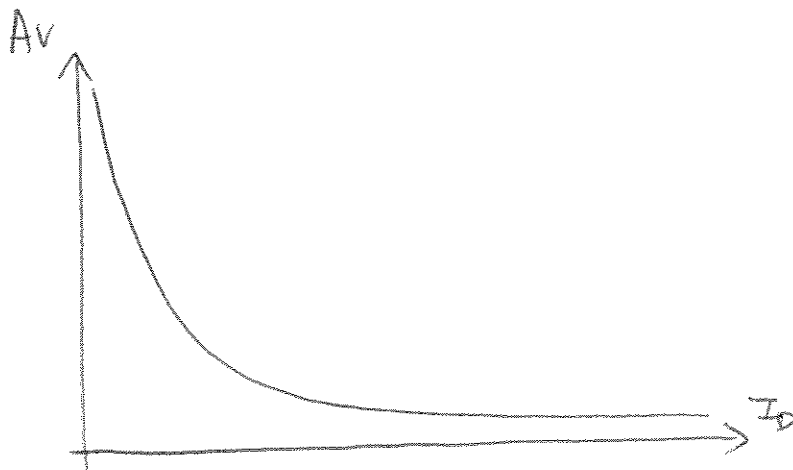


29. $|A_v| = 200$

$\mu_n C_{ox} = 100 \frac{\mu A}{V^2}$ $\lambda = 0.1 V^{-1}$

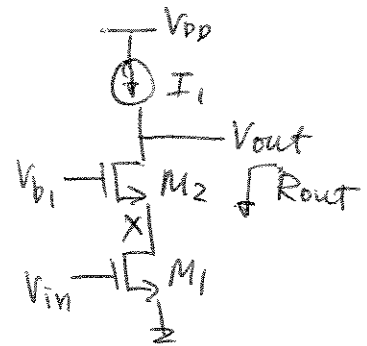Determine $(\frac{W}{L})_1 = (\frac{W}{L})_2$



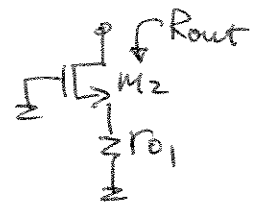$R_{out} = (1 + g_{m2} r_{o1}) r_{o2} + r_{o1}$



$G_m \cong g_{m1}$ (short-circuit current flows through both M_1 & M_2)

$|A_v| = G_m R_{out} = g_{m1} [(1 + g_{m2} r_{o1}) r_{o2} + r_{o1}]$

$\approx g_{m1} g_{m2} r_{o1} r_{o2} = (g_m r_o)^2 = 200$

($\because (\frac{W}{L})_1 = (\frac{W}{L})_2$ and $I_{D1} = I_{D2}$)

$(g_m r_o)^2 = \left(\frac{2 I_D}{V_{GS} - V_{TH}} \cdot \frac{1}{\lambda I_D} \right)^2 = 200$


$\Rightarrow V_{GS} - V_{TH} = \left(\sqrt{200} \cdot \lambda / 2 \right)^{-1} = \left[\sqrt{200} \cdot (0.05 V^{-1}) \right]^{-1}$
 $\approx 1.41 V$

$$\Rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2$$

$$\therefore \left(\frac{W}{L} \right) = \frac{2 I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2}$$

$$= \frac{2(1 \text{ mA})}{100 \frac{\mu\text{A}}{\text{V}^2} (1.4 \text{ V})^2} \approx 10$$

30.

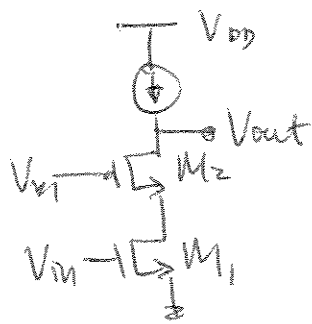

$$\left(\frac{W}{L}\right)_{1, \text{new}} = N \left(\frac{W}{L}\right)_1$$

$$\left(\frac{W}{L}\right)_{2, \text{new}} = N \left(\frac{W}{L}\right)_2$$

$$\lambda_{n,1} = \lambda_{n,2}$$

$$A_{v, \text{new}} \approx -g_{m1} g_{m2} r_{o1} r_{o2}$$


$$= -\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{1, \text{new}} I_D} \cdot \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{2, \text{new}} I_D} \cdot \frac{1}{\lambda_{I_D}} \cdot \frac{1}{\lambda_{I_D}}$$

$$= -\sqrt{N} \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_D} \cdot \sqrt{N} \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_D} \cdot \frac{1}{\lambda_{I_D}} \cdot \frac{1}{\lambda_{I_D}}$$

$$= -N (g_{m1} g_{m2} r_{o1} r_{o2}) = -N \cdot A_{v, \text{old}}.$$

Gain is N times of original value:

31.

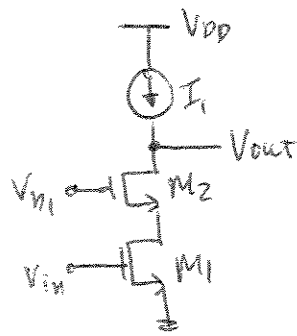

$$\left(\frac{W}{L}\right)_{1, \text{new}} = \frac{1}{N} \left(\frac{W}{L}\right)_1$$

$$\left(\frac{W}{L}\right)_{2, \text{new}} = \frac{1}{N} \left(\frac{W}{L}\right)_2$$

Assume $\lambda_{n,1} = \lambda_{n,2}$

$$A_{v, \text{new}} \approx -g_{m1} (g_{m2} (r_{o1} r_{o2}))$$


$$= -\sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_{1, \text{new}} I_{D1}} \cdot \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_{2, \text{new}} I_{D2}} \cdot \left(\frac{1}{\lambda I_{D1}}\right)^2$$

$$= -\sqrt{\frac{1}{N} \cdot 2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} \cdot \sqrt{\frac{1}{N} \cdot 2 \mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}} \cdot \left(\frac{1}{\lambda I_{D1}}\right)^2$$

$$= -\frac{1}{N} g_{m1} g_{m2} r_{o1} r_{o2} = -\frac{1}{N} (A_{v, \text{old}})$$

Gain is $1/N$ of original value.

32.

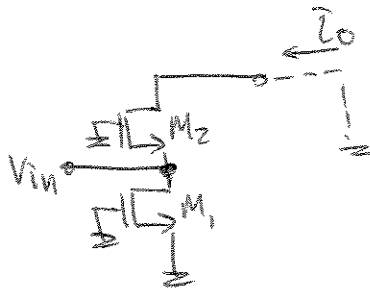


By KCL,

$$\frac{\bar{i}_o}{V_{in}} = -\left(g_{m2} + \frac{1}{r_{o1} \parallel r_{o2}}\right) = G_m$$

$$R_n = r_{o2}$$


$$R_p \approx g_{m3} r_{o3} r_{o4}$$
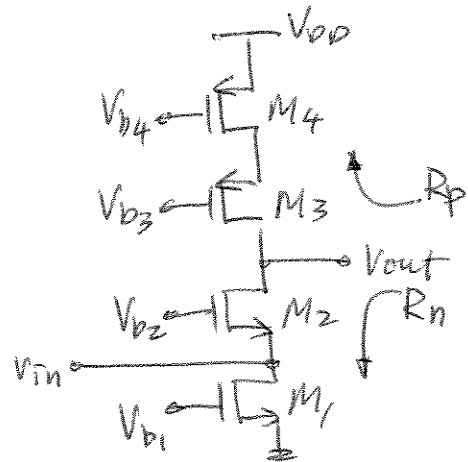
$$\therefore A_v = -G_m (R_n \parallel R_p) = \left(g_m + \frac{1}{r_{o1} \parallel r_{o2}}\right) (r_{o2} \parallel g_{m3} r_{o3} r_{o4})$$



33. $(\frac{W}{L}) = 20/0.18$
 $\mu_n C_{ox} = 100 \mu A/V^2$
 $\mu_p C_{ox} = 50 \mu A/V^2$
 $\lambda_n = 0.1 V^{-1} \quad \lambda_p = 0.15 V^{-1}$

Calculate I_{BIAS} such as
 $A_v = 500$.

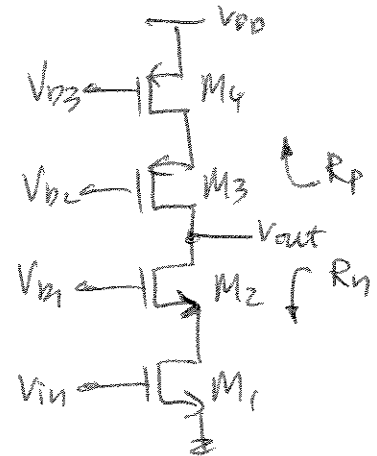



The cascode circuit has gain
 $\approx -g_{m1} \cdot [g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}]$

$$\Rightarrow 500 = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \left(\frac{\sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)}}{(\lambda_n)^2 I_D^{3/2}} \parallel \frac{\sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)}}{(\lambda_p)^2 I_D^{3/2}} \right)$$

All quantities are known. Solving I_D gives:

$$I_D = I_{BIAS} \approx 1.06 \text{ mA.}$$

34(a) Equivalent circuit:

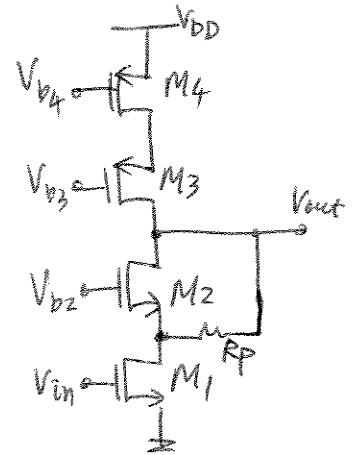
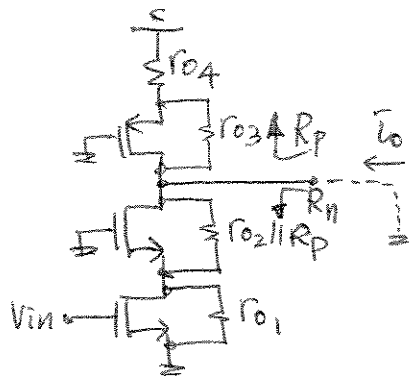


$$G_m = \frac{i_o}{v_{in}} \approx g_{m1} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} (r_{o2} \parallel R_p) r_{o1}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} (r_{o2} \parallel R_p) r_{o1}]$$

(b) Equivalent circuit

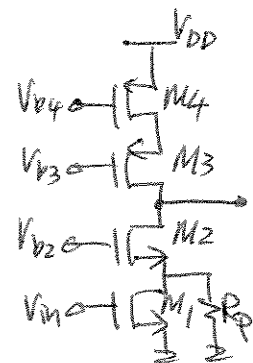
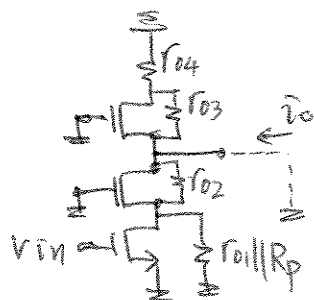


$$G_m = i_o / v_{in} \approx g_{m1} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} (r_{o1} \parallel R_p) r_{o2}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} (r_{o1} \parallel R_p) r_{o2}]$$

(c) Equivalent circuit:

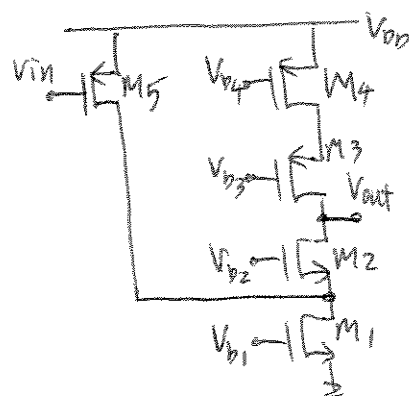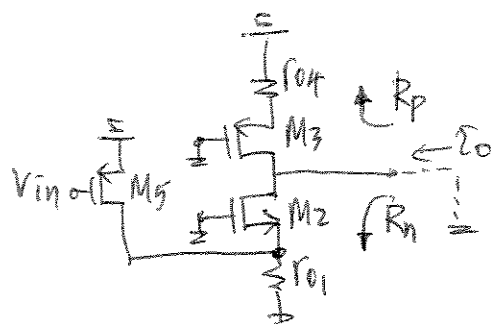

(Realize that r_{o1} & r_{o5} are in parallel.)



$$G_m = \frac{i_o}{v_{in}} \approx -g_{m5} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4}$$

$$R_n = g_{m2} r_{o2} (r_{o1} \parallel r_{o5})$$

$$\therefore A_v = -G_m R_{out} = g_{m5} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} r_{o2} (r_{o1} \parallel r_{o5})]$$

(d) Equivalent circuit:

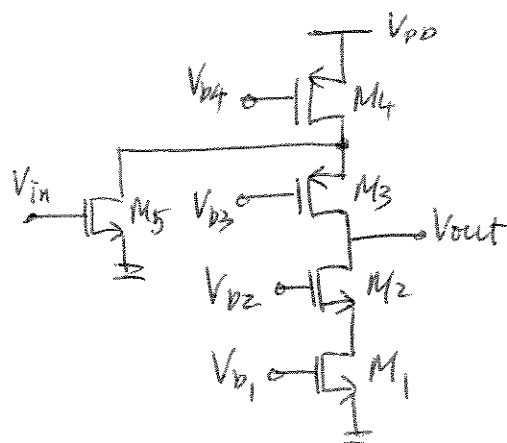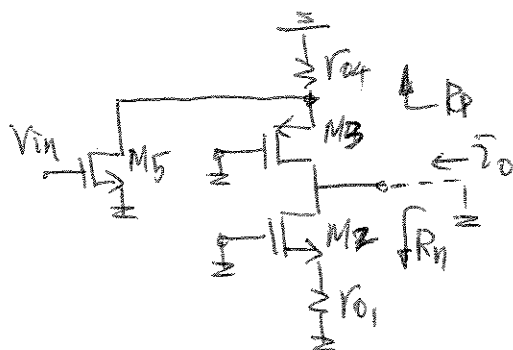

$$G_m = \frac{i_o}{v_{in}} \approx g_{m5}$$

$$R_p = g_{m3} r_{o3} (r_{o4} \parallel r_{o5})$$

$$R_n = g_{m2} r_{o2} r_{o1}$$

$$\therefore A_v = -G_m R_{out} = g_{m5} [g_{m3} r_{o3} (r_{o4} \parallel r_{o5}) \parallel g_{m2} r_{o2} r_{o1}]$$

$$35. \quad \frac{R_2}{R_1 + R_2} V_{CC} = V_T \ln \left(\frac{I_1}{I_S} \right)$$

$$\Rightarrow I_1 = I_S \cdot \exp \left[\frac{V_{CC}}{V_T} \cdot \frac{R_2}{R_1 + R_2} \right]$$

$$\begin{aligned} \frac{\partial I_1}{\partial V_{CC}} &= \frac{I_S}{V_T} \cdot \frac{R_2}{R_1 + R_2} \cdot \exp \left[\frac{V_{CC}}{V_T} \cdot \frac{R_2}{R_1 + R_2} \right] \\ &= \frac{I_1}{V_T} \cdot \frac{R_2}{R_1 + R_2} = g_m \left(\frac{R_2}{R_1 + R_2} \right) \end{aligned}$$

Intuitively, we know that an exponential relationship exists between I_C & V_{BE} . Its transconductance is also a function (linear) of I_C . Since V_{BE} comes from a voltage divider (which is also linear), we expect a linear relationship between I_C & V_{CC} .

$$36. \quad I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$

$$\frac{\partial I_1}{\partial V_{DD}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot 2 \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right) \cdot \frac{R_2}{R_1 + R_2}$$

$$= \mu_n C_{ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{R_2 \cdot V_{DD} - V_{TH}}{R_1 + R_2} \right)$$

$$= g_m \cdot \frac{R_2}{R_1 + R_2}$$


Intuitively, the voltage divider gives a linear relationship between V_{DD} & V_{GS1} . Since g_m of MOS is linearly proportional to $(V_{GS1} - V_{TH})$, we expect the same relationship between V_{DD} & $\frac{\partial I_1}{\partial V_{DD}}$.

$$37. \quad I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$

$$\frac{\partial I_1}{\partial V_{TH}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot 2 \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right) \cdot (-1)$$

$$= - \mu_n C_{ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)$$

38.

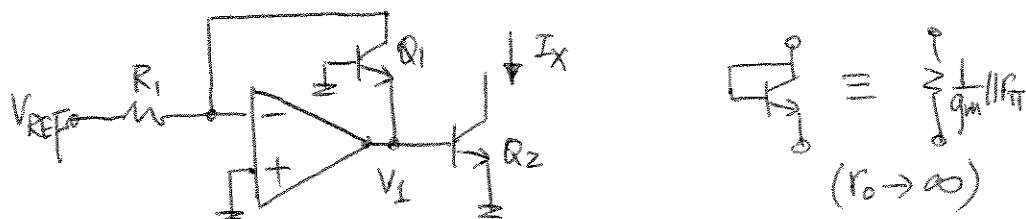


This is a negative feedback circuit.

The inverting input (-) of the op-amp is virtual ground. (\because of feedback) in DC. $\Rightarrow Q_1$ becomes diode-connected.

$$\Rightarrow \frac{V_{REF}}{R_1} = \frac{0 - V_1}{\left(\frac{1}{g_{m1}} \parallel r_{\pi 1}\right)} \Rightarrow V_1 = -\frac{V_{REF} \left(\frac{1}{g_{m1}} \parallel r_{\pi 1}\right)}{R_1} < 0$$

This implies $V_{BE2} < 0 \Rightarrow I_X = 0!$

39.

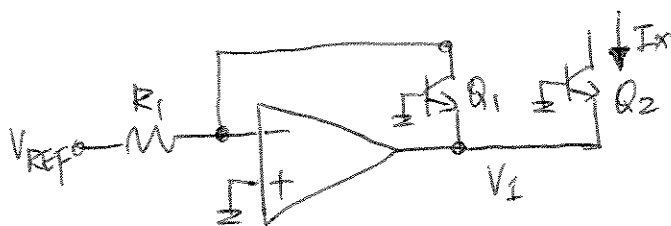


This is a negative feedback circuit.

The inverting input (-) is virtual ground, as a result. Q_1 then becomes diode-connected, and its resistance $= (\frac{1}{g_{m1}} \parallel r_{\pi1})$, assuming $r_o \rightarrow \infty$.

$$\Rightarrow \frac{V_{REF}}{R_1} = \frac{-V_1}{(\frac{1}{g_{m1}} \parallel r_{\pi1})} \Rightarrow V_1 = -\frac{V_{REF} (\frac{1}{g_{m1}} \parallel r_{\pi1})}{R_1}$$


$$\Rightarrow V_{BE1} = V_{BE2} = -V_1$$

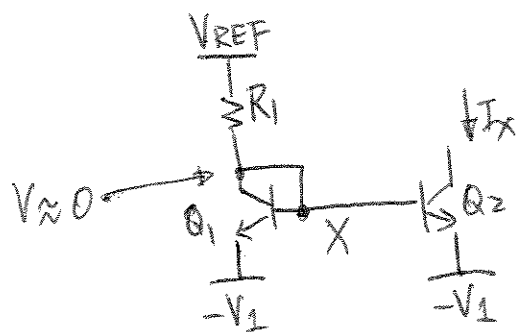This circuit will work if the negative supply voltage of the op-amp allows value of $-V_1$ or lower.



- An equivalent circuit, (without op-amp). The op-amp guarantees a stable voltage at node X. (i.e. inverting input.)

40.

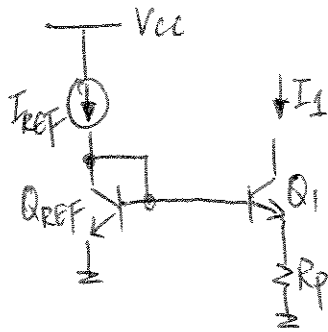

$$Q_{REF} = Q_1$$

$$\beta \rightarrow \infty.$$

$$I_1 = \frac{I_{REF}}{2}$$


By KVL, $V_{BE,REF} = V_{BE1} + I_1 R_P$

$$\Rightarrow V_T \ln\left(\frac{I_{REF}}{I_{S,REF}}\right) = V_T \ln\left(\frac{I_{REF}/2}{I_{S,1}}\right) + \frac{I_{REF} R_P}{2}$$

$$V_T \ln(2) = \frac{I_{REF} R_P}{2}$$

$$R_P = 2 \cdot \ln(2) \cdot (V_T / I_{REF})$$

41.

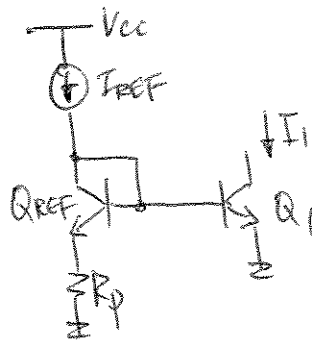

$$Q_{REF} = Q_1$$

$$\beta \rightarrow \infty$$


By KVL, $V_{BE,REF} + I_{REF} R_P = V_{BE,1}$

$$\Rightarrow V_T \ln \left(\frac{I_{REF}}{I_{S,REF}} \right) + I_{REF} R_P = V_T \ln \left(\frac{2 I_{REF}}{I_{S,1}} \right)$$

$$I_{REF} R_P = V_T \ln(2)$$


$$R_P = \frac{V_T}{I_{REF}} \ln(2)$$


42.

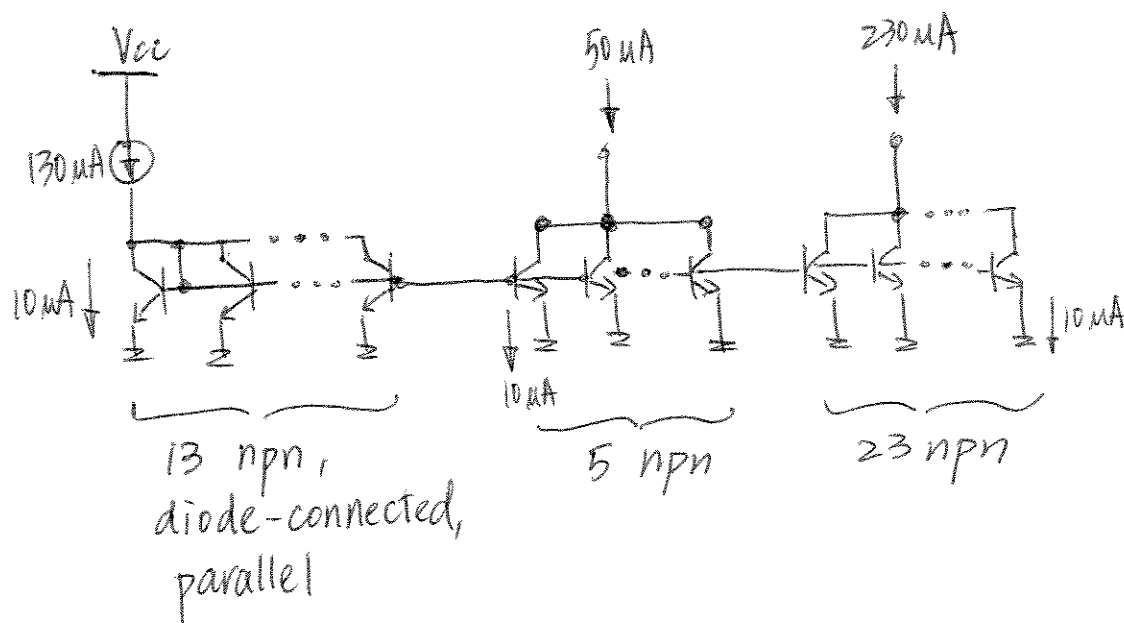

All the bases are the same node.

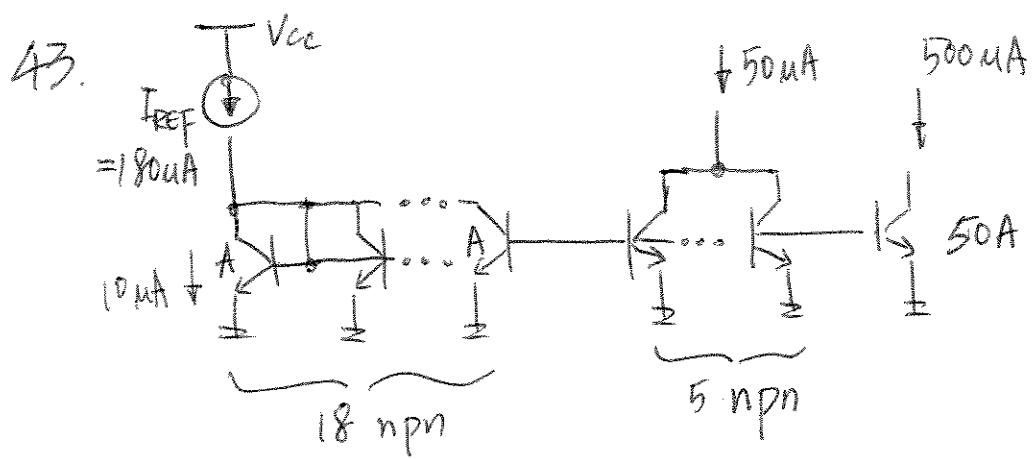If the area of BJT is flexible, the 5-npn group can be replaced by one BJT that is 5 times as big in area. Similar concept applies to 23-npn grouping.



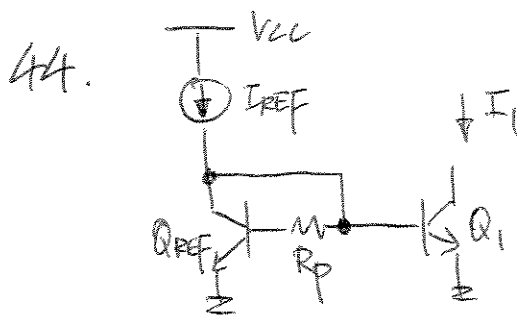

$$Q_{REF} = Q_1$$

I_1 10% larger. ($I_1 = 1.1 I_{C,REF}$)
Solve for R_P .

By KVL,

$$V_{BE,REF} + \frac{I_{C,REF} \cdot R_P}{\beta} = V_{BE_1}$$

$$\Rightarrow V_T \ln\left(\frac{I_1}{I_S}\right) - V_T \ln\left(\frac{I_{C,REF}}{I_S}\right) = \frac{I_{C,REF}}{\beta} \cdot R_P$$

$$V_T \ln\left(\frac{I_1}{I_{C,REF}}\right) = \frac{I_{C,REF}}{\beta} \cdot R_P$$


$$\Rightarrow V_T \ln(1.1) = \frac{I_{C,REF}}{\beta} R_P \quad \Rightarrow I_{C,REF} = \frac{\beta V_T \ln(1.1)}{R_P}$$

By KCL, $I_{REF} = I_{C,REF} + I_{C,REF}/\beta + I_1/\beta$

$$= \frac{\beta}{R_P} V_T \ln(1.1) \cdot \left(1 + \frac{1}{\beta}\right) + \frac{I_1}{\beta}$$

$$\therefore R_P = \frac{(\beta + 1) V_T \ln(1.1)}{I_{REF} - I_1/\beta}$$

45.

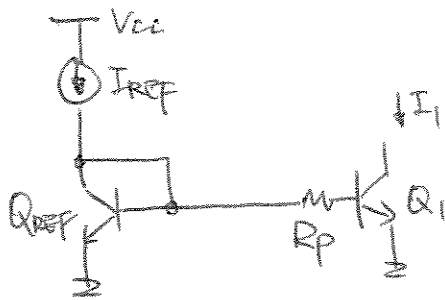

$$I_1 = 0.9 I_{C, REF}$$

By KVL, $V_{BE, REF} = \frac{I_1}{\beta} R_P + V_{BE, 1}$

$$\Rightarrow V_T \ln\left(\frac{I_{B, REF}}{I_1}\right) = \frac{I_1}{\beta} R_P$$

$$V_T \ln\left(\frac{1}{0.9}\right) = 0.9 I_{C, REF} \frac{R_P}{\beta}$$

$$\Rightarrow I_{C, REF} = \frac{\beta}{0.9 R_P} V_T \ln\left(\frac{1}{0.9}\right)$$


By KCL,

$$I_{REF} = I_{C, REF} + I_{C, REF}/\beta + I_1/\beta$$

$$\therefore I_{REF} - \frac{I_1}{\beta} = \frac{\beta}{0.9 R_P} V_T \ln\left(\frac{1}{0.9}\right) \left(1 + \frac{1}{\beta}\right)$$

$$\Rightarrow R_P = \frac{(\beta + 1) V_T \ln(10/9)}{0.9 (I_{REF} - I_1/\beta)}$$

4b (a)

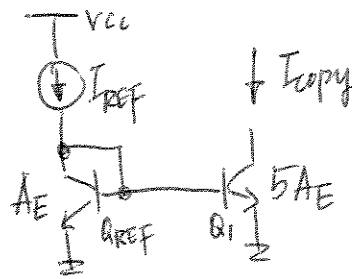

Q_1 has I_s 5 times
as that of Q_{REF}


$$\Rightarrow I_{C_{REF}} = I_{COPY} / 5$$

By KCL,

$$\begin{aligned} I_{REF} &= I_{C_{REF}} + \frac{I_{C_{REF}}}{\beta} + \frac{I_{COPY}}{\beta} \\ &= \frac{I_{COPY}}{5} \left(1 + \frac{1}{\beta} \right) + \frac{I_{COPY}}{\beta} \end{aligned}$$

$$\therefore I_{COPY} = I_{REF} \left(\frac{5\beta}{\beta+6} \right)$$
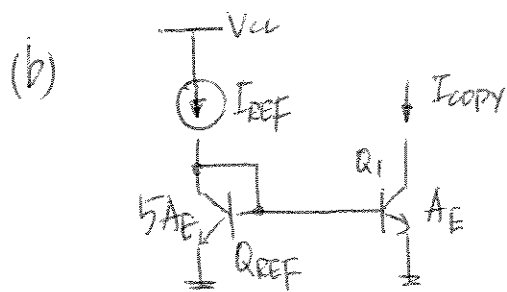
$$\therefore \text{error} = \frac{I_{COPY}}{I_{REF}} = \frac{5\beta}{\beta+6}$$




Q_1 & Q_{REF} have the same V_{BE} , but area of Q_{REF} is 5 times larger

$$\Rightarrow I_{C, REF} = 5 \cdot I_{COPY}$$

By KCL,

$$\begin{aligned} I_{REF} &= I_{C, REF} + \frac{I_{C, REF}}{\beta} + \frac{I_{COPY}}{\beta} \\ &= I_{COPY} \cdot 5 + \left(1 + \frac{1}{\beta}\right) + I_{COPY} \left(\frac{1}{\beta}\right) \end{aligned}$$
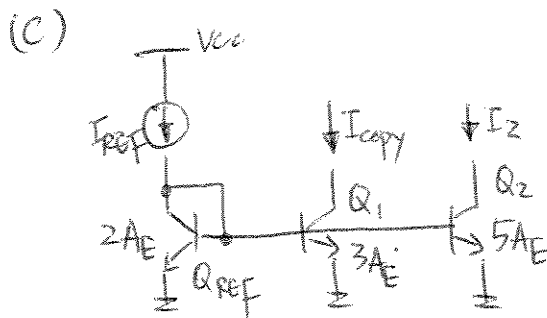
$$\therefore I_{COPY} = I_{REF} \left(\frac{\beta}{5\beta + 6} \right)$$



Q_1 & Q_{REF} have identical V_{BE} , but area of Q_1 is 1.5 times larger.


$$\Rightarrow 3 I_{C, REF} = 2 I_{COPY}$$

By KCL,

$$\begin{aligned} I_{REF} &= I_{C, REF} + \frac{I_{C, REF}}{\beta} + \frac{I_{COPY}}{\beta} + \frac{I_2}{\beta} \\ &= I_{COPY} \left(\frac{2}{3} \right) \left[\left(1 + \frac{1}{\beta}\right) + \frac{1}{\beta} + \frac{5}{3} \left(\frac{1}{\beta}\right) \right] \end{aligned}$$

$$\Rightarrow I_{COPY} = \frac{9\beta}{6\beta + 22} I_{REF}$$

47.

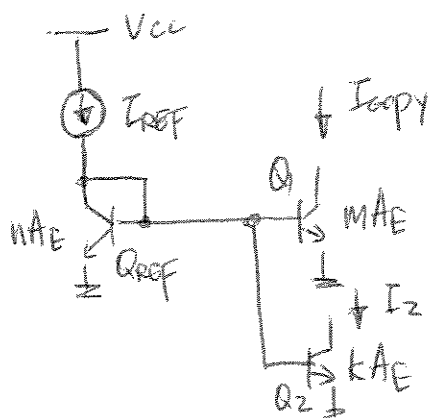


By observing the areas of the BJTs,

$$I_{C,REF} = \left(\frac{n}{m}\right) I_{COPY} = \left(\frac{n}{k}\right) I_2$$

By KCL, $I_{C,REF} = I_{REF} - \frac{I_{C,REF}}{\beta} - \frac{I_{COPY}}{\beta} - \frac{I_2}{\beta}$

$$\Rightarrow \frac{n}{m} I_{COPY} = I_{REF} - \frac{\left(\frac{n}{m}\right) I_{COPY}}{\beta} - \frac{I_{COPY}}{\beta} - \frac{\left(\frac{k}{m}\right) I_{COPY}}{\beta}$$
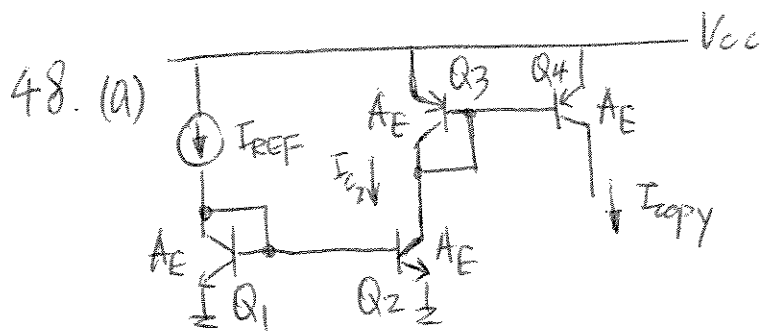
$$\therefore I_{COPY} = I_{REF} \left[\frac{\beta m}{(\beta + 1)n + k + m} \right]$$



$$V_{BE1} = V_{BE2} \\ \Rightarrow I_{C1} = I_{C2}$$


$$V_{BE3} = V_{BE4} \\ \Rightarrow I_{C3} = I_{C4}$$

First compute $I_{C1,2}$:

$$I_{C1} = I_{REF} - \frac{I_{C1}}{\beta} - \frac{I_{C2}}{\beta} \Rightarrow I_{C2} = \frac{\beta}{\beta+2} \cdot I_{REF}$$

View I_{C2} as the " I_{REF} " for the Q_3 - Q_4 current mirror and apply the equation derived.
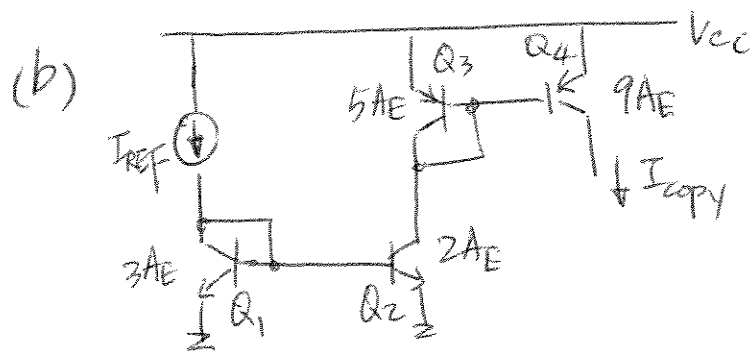
$$\Rightarrow I_{COPY} = \frac{\beta}{\beta+2} \left[\frac{\beta}{\beta+2} \cdot I_{REF} \right] = I_{REF} \left(\frac{\beta}{\beta+2} \right)^2$$



$$V_{BE1} = V_{BE2} \because$$

$$\Rightarrow I_{C1} = \frac{3}{2} I_{C2}$$

$$V_{BE3} = V_{BE4} \because$$

$$\Rightarrow I_{copy} = \frac{9}{5} I_{C3}$$

- By KCL,

$$I_{REF} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta}$$

$$\Rightarrow I_{C2} = \frac{2\beta}{3\beta+5} I_{REF} \quad \textcircled{1}$$

- By KCL,


$$I_{C2} = I_{C3} + \frac{I_{C3}}{\beta} + \frac{I_{copy}}{\beta}$$

$$\Rightarrow I_{copy} = \frac{9\beta}{5\beta+14} I_{C2}$$

Substitute $\textcircled{1}$ into I_{copy} :

$$\therefore I_{copy} = \frac{9\beta}{5\beta+14} \cdot \frac{2\beta}{3\beta+5} \cdot I_{REF}$$

49.

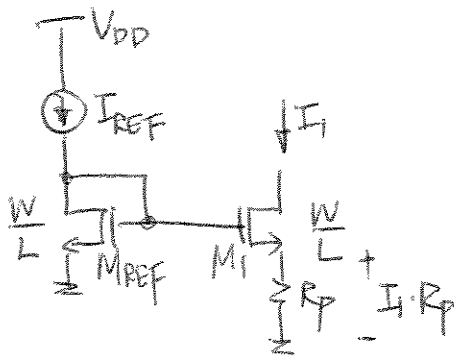

Determine R_P such that $I_1 = \frac{I_{REF}}{2}$.

First calculate $V_{GS, REF}$:

$$V_{GS, REF} = \sqrt{\frac{2 I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH} \quad \text{--- ①}$$

Assuming M_1 in saturation:


$$I_1 = \frac{I_{REF}}{2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{GS_1} - V_{TH}]^2$$

$$\Rightarrow \frac{I_{REF}}{2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{GS, REF} - \frac{I_{REF}}{2} R_P - V_{TH}]^2$$

Rearrange, substitute ① into equation above and solve for R_P :

$$\therefore R_P = \frac{2(\sqrt{2} - 1)}{\sqrt{I_{REF} \cdot \mu_n C_{ox} \frac{W}{L}}}$$

50.

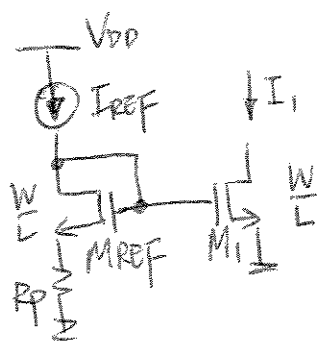

Determine R_P such that $I_1 = 2I_{REF}$.

First calculate V_{GS1} :

$$V_{GS1} = \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} = 2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} \quad \text{--- (1)}$$

Assuming I_1 is in saturation:

$$\begin{aligned} I_{REF} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS, REF} - V_{TH})^2 \\ &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) [V_{GS1} - I_{REF} R_P - V_{TH}]^2 \end{aligned}$$


Substitute (1) into I_{REF} :

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} - I_{REF} R_P \right]^2 \quad \text{--- (2)}$$

$$\text{Solve for } R_P: \quad R_P = \frac{(2 - \sqrt{2})}{\sqrt{I_{REF}} \cdot \mu_n C_{ox} \left(\frac{W}{L}\right)}$$

From (2), we find that R_P is independent of any change in V_{TH} , ΔV !!

51.

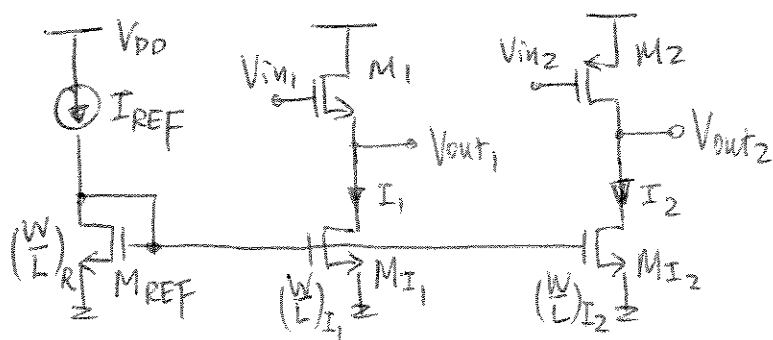


This figure implies that $V_{GS, REF} = V_{GS, I_1} = V_{GS, I_2}$.
 Assuming all devices operate in saturation, with $(V_{GS} - V_{TH})$ fixed, $I_D \propto (\frac{W}{L})$

$$\Rightarrow \text{we have } (\frac{W}{L})_R = 1 (\frac{W}{L})$$

$$(\frac{W}{L})_{I_1} = 4 (\frac{W}{L})$$

$$(\frac{W}{L})_{I_2} = 10 (\frac{W}{L})$$

52. (a)

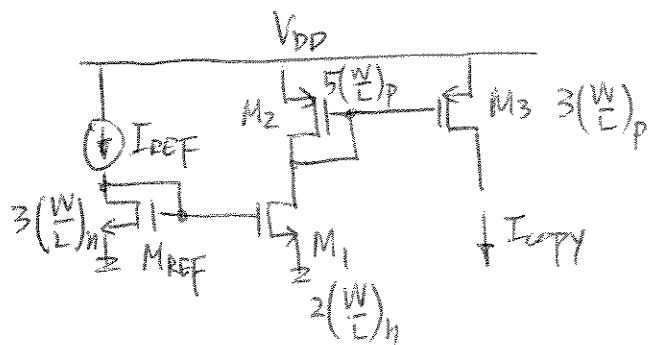


$$V_{GS, REF} = V_{GS, 1} : \Rightarrow I_{D, 1} = \frac{2}{3} I_{REF}$$

$$V_{GS, 2} = V_{GS, 3} : \Rightarrow I_{COPY} = \frac{3}{5} I_{D, 2} = \frac{3}{5} I_{D, 1}$$

$$= \frac{3}{5} \cdot \left(\frac{2}{3} I_{REF} \right) = \frac{2}{5} I_{REF}$$

(b)

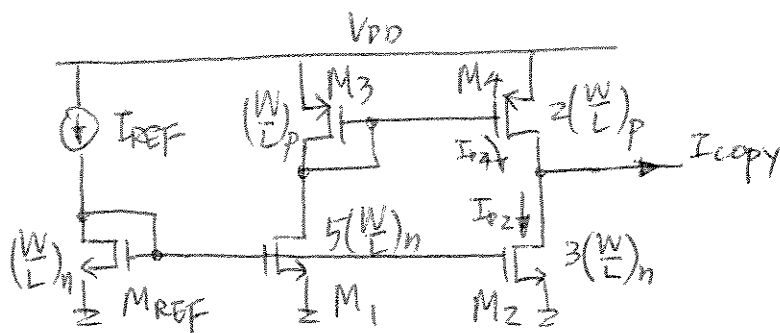


$$V_{GS, REF} = V_{GS, 1} : I_{D, 1} = 5 I_{REF}$$

$$V_{GS, 3} = V_{GS, 4} : I_{D, 4} = 2 I_{D, 3} = 2 I_{D, 1} = 10 I_{REF}$$

$$V_{GS, REF} = V_{GS, 2} : I_{D, 2} = 3 I_{REF}$$

$$\therefore I_{COPY} = I_{D, 4} - I_{D, 2} = 7 I_{REF}$$

53.

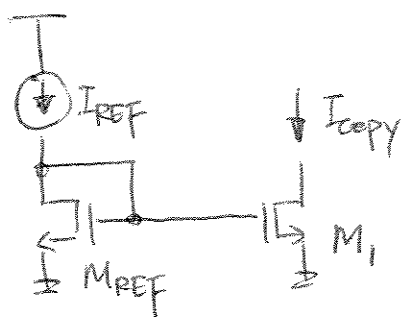

$$V_{GS, REF} = V_{GS, 1} = V_{GS}$$

$$\lambda \neq 0$$

$$(a) \quad I_{REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS})$$



$$I_{COPY} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS, 1})$$

$$\text{For } I_{REF} = I_{COPY} \Rightarrow V_{DS, 1} = V_{GS}$$

$$(b) \quad \frac{I_{REF}}{I_{COPY}} = \frac{1 + \lambda V_{GS}}{1 + \lambda (V_{GS} - V_{TH})}$$

$$\Rightarrow I_{COPY} = I_{REF} \left(1 - \frac{\lambda V_{TH}}{1 + \lambda V_{GS}} \right)$$

54.

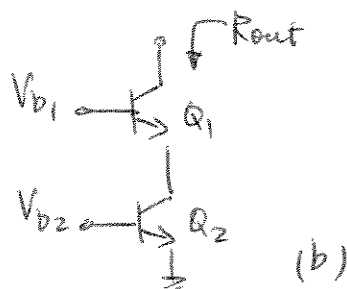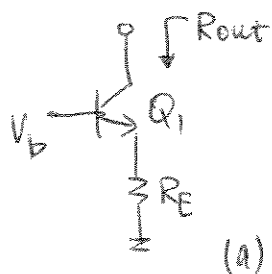

Given $I_{BIAS} = 1\text{mA}$, $V_{RE} \approx V_{CE,2} \approx 0.5\text{V}$,
design the circuit.

R_E can be readily calculated:

$$R_E = \frac{V_{RE}}{I_{BIAS}/\alpha} = \frac{0.5\text{V}}{1\text{mA}/0.909} = 505\Omega$$

$$V_{be_1} = V_T \ln\left(\frac{I_{BIAS}}{I_{S,1}}\right) = (0.026\text{V}) \ln\left(\frac{1\text{mA}}{6 \cdot 10^{-16}\text{A}}\right) \approx 0.732\text{V}$$

$$\Rightarrow V_b = V_{be_1} + V_{RE} = 0.732\text{V} + 0.5\text{V} = 1.232\text{V}$$


$$R_{out(a)} = [1 + g_{m_1}(R_E \parallel r_{\pi_1})]r_{o_1} + (R_E \parallel r_{\pi_1})$$

$$R_{out(b)} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1})]r_{o_1} + (r_{o_2} \parallel r_{\pi_1})$$

In most cases $r_o > r_{\pi} > R_E$

$\therefore R_{out(b)}$ is relatively larger than $R_{out(a)}$

55.

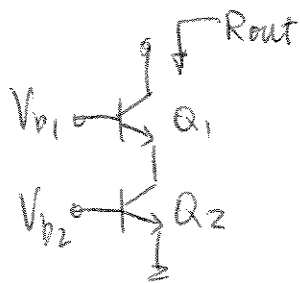

$$I_{BIAS} = 1 \text{ mA}$$

$$\beta = 100$$

Given $R_{out} = 50 \text{ k}\Omega$, $V_{BC2} = 100 \text{ mV}$,
determine V_{b1} .

$$R_{out} = [1 + g_{m1}(r_{o2} \parallel r_{\pi 1})]r_{o1} + (r_{o2} \parallel r_{\pi 1})$$

$$\approx g_{m1}(r_{o2} \parallel r_{\pi 1})r_{o1}$$

$$= \frac{\beta V_A^2}{(V_A + \beta V_T) I_{BIAS}}$$

$$\Rightarrow I_{BIAS} = \left[\frac{R_{out}(V_A + \beta V_T)}{\beta V_A^2} \right]^{-1} = \left[\frac{(50 \text{ k}\Omega)(5 \text{ V} + 100 \cdot 0.026 \text{ V})}{100(5 \text{ V})^2} \right]^{-1}$$

$$\approx 6.6 \text{ mA}$$

$$V_{b2} = V_{BE2} = V_T \ln \left(\frac{I_{BIAS}}{I_S} \right) = (0.026 \text{ V}) \ln \left(\frac{6.6 \text{ mA}}{6 \cdot 10^{-16} \text{ A}} \right)$$


$$\approx 0.78 \text{ V}$$

$$\Rightarrow V_{C2} = V_{BE2} - 100 \text{ mV} = 0.68 \text{ V}$$

$$\therefore V_{b1} = V_{C2} + V_{BE1} = V_{C2} + V_T \ln \left(\frac{I_{BIAS}}{I_S} \right)$$

$$= 0.68 \text{ V} + (0.026 \text{ V}) \ln \left(\frac{6.6 \text{ mA}}{6 \cdot 10^{-16} \text{ A}} \right) \approx 1.46 \text{ V}$$

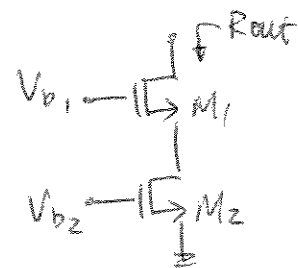5b. Given $R_{out} = 200 \text{ k}\Omega$
 $I_{BIAS} = 0.5 \text{ mA}$



(a) Determine $(W/L)_1 = (W/L)_2$ with $\lambda = 0.1 \text{ V}^{-1}$

$$R_{out} = (1 + g_{m1} r_{o2}) r_{o1} + r_{o2}$$

$$= \left[1 + \sqrt{2 I_{BIAS} \mu_n C_{ox} \left(\frac{W}{L} \right)_1} \cdot \frac{1}{\lambda I_{BIAS}} \right] \frac{1}{\lambda I_{BIAS}} + \frac{1}{\lambda I_{BIAS}}$$

$$\therefore \left(\frac{W}{L} \right)_1 \cong \frac{\left[\left(R_{out} - \frac{1}{\lambda I_{BIAS}} \right) (\lambda I_{BIAS})^2 \right]^2}{2 I_{BIAS} \mu_n C_{ox}}$$

$$= \frac{\left\{ \left[200 \text{ k}\Omega - \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} \right] (0.1 \text{ V}^{-1})^2 (0.5 \text{ mA})^2 \right\}^2}{2 (0.5 \text{ mA}) (100 \frac{\mu\text{A}}{\text{V}^2})}$$


$$\approx 2.0$$

$$(b) I_{BIAS} = 0.5 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{b2} - V_{TH,n})^2$$

$$\Rightarrow V_{b2} = \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1}} + V_{TH}$$

$$= \sqrt{\frac{2 (0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{\text{V}^2}) (2.0)}} + (0.4 \text{ V}) \approx 2.62 \text{ V}$$

57. Given $|A_v| = 500$
 $\beta = 100$

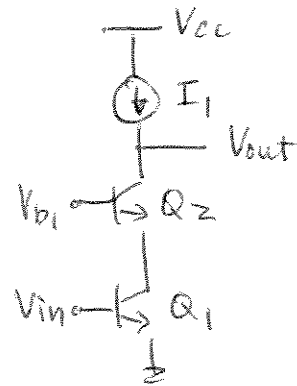

(a) $A_v = -g_{m1} r_{o1} g_{m2} (r_{o1} \parallel r_{\pi 2})$

$$= - \frac{V_A}{V_T} \times \frac{I_{C2}}{V_T} \left(\frac{V_A}{I_{C1}} \parallel \frac{\beta}{g_{m2}} \right)$$

Assume $I_{C1} \approx I_{C2}$. After expanding $(r_{o1} \parallel r_{\pi 2})$,


$$A_v \approx - \frac{V_A/V_T}{\frac{V_T}{V_A} + \frac{1}{\beta}} \Rightarrow V_A^2 + V_A \left(\frac{V_T A_v}{\beta} \right) + (A_v V_T^2) = 0$$

$$\Rightarrow V_A \approx 0.65 \text{ V}$$

(b) $V_{in} = V_T \ln\left(\frac{I_1}{I_S}\right) = (0.026 \text{ V}) \ln\left(\frac{0.5 \text{ mA}}{6 \cdot 10^{-16} \text{ A}}\right)$
 $\approx 0.71 \text{ V}$

(c) $V_{b1} = V_{BE2} + 500 \text{ mV}$
 $= V_T \ln\left(\frac{I_1}{I_S}\right) + 0.5 \text{ V}$
 $= 0.71 \text{ V} + 0.5 \text{ V} = 1.21 \text{ V}$

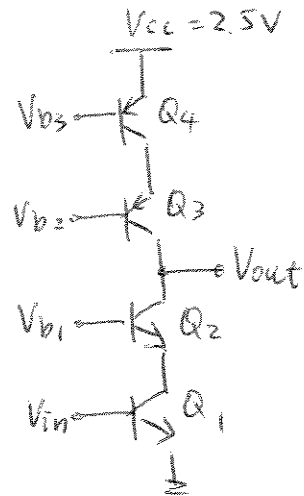58. Given power budget = 2mW
 $V_{BC1} = V_{CB4} = 200 \text{ mV}$,
 calculate voltage gain.



$$\alpha_p = \frac{50}{50+1} \approx 0.98$$

$$\alpha_n = \frac{100}{100+1} \approx 0.99$$

\therefore we assume $I_{C,p} \approx I_{E,p}$ & $I_{C,n} \approx I_{E,n}$

$$\text{This implies that } I_{BIAS} = \frac{\text{Power}}{V_{CC}} = \frac{2\text{mW}}{2.5\text{V}} \approx 0.8\text{mA}$$

$$\Rightarrow V_{BE1} = V_{in} = V_T \ln\left(\frac{I_{BIAS}}{I_{S1}}\right) = (0.026\text{V}) \cdot \ln\left(\frac{0.8\text{mA}}{6 \cdot 10^{-16}\text{A}}\right) \approx 0.726\text{V}$$

$$V_{C1} = V_{BE1} - V_{BC1} = 0.726\text{V} - 0.2\text{V} = 0.526\text{V}$$

$$\therefore V_{b1} = V_{C1} + V_{BE2} = (0.526\text{V}) + (0.026\text{V}) \ln\left(\frac{0.8\text{mA}}{6 \cdot 10^{-16}\text{A}}\right) \approx 1.252\text{V}$$

$$\Rightarrow V_{EB4} = V_{CC} - V_{b3} = V_T \ln\left(\frac{I_{BIAS}}{I_{S4}}\right) = 0.026\text{V} \cdot \ln\left(\frac{0.8\text{mA}}{6 \cdot 10^{-16}\text{A}}\right) \approx 0.726\text{V}$$

$$V_{b3} = V_{cc} - 0.726V = 1.774V$$

$$V_{c4} = V_{D3} + V_{CB4} = 1.774V + 0.2V = 1.974V$$

$$\therefore V_{D2} = V_{c4} - V_{EB3} = (1.974V) - (0.026) \ln\left(\frac{0.8mA}{6 \cdot 10^{-16}A}\right)$$

$$\approx 1.248V$$

$$A_v = -g_{m1} \{ [g_{m2} r_{D2} (r_{O1} \parallel r_{\pi2})] \parallel [g_{m3} r_{D3} (r_{O4} \parallel r_{\pi3})] \}$$

After simplifying, A_v is independent of I_{BIAS} :

$$A_v \approx \frac{V_{AN} \cdot V_{AP}}{V_T^2 \left(\frac{V_{AP}}{V_{AN}} + \frac{V_{AP}}{\beta_N V_T} + \frac{V_{AN}}{V_{AP}} + \frac{V_{AN}}{\beta_P V_T} \right)}$$


$$= \frac{5.5}{(0.026V)^2 \left(\frac{5}{5} + \frac{5}{100 \cdot 0.026} + \frac{5}{5} + \frac{5}{50 \cdot 0.026} \right)}$$

$$\approx 4760$$

59. Given $A_v = 200$
 power budget = 2mW
 all $(\frac{W}{L}) = \frac{20}{0.18}$

$$V_{b1} = V_{b2} = 0.9 \text{ V}$$

calculate V_{in} & V_{b3}

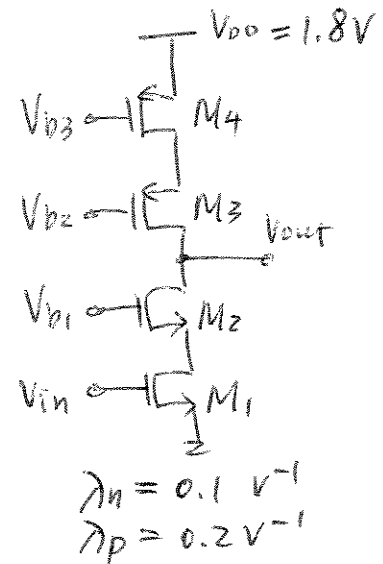

$$A_v \approx -g_{m1} (g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}) = 200$$

$$\text{power} = V_{DD} \times I_{BIAS} \Rightarrow I_{BIAS} = \frac{\text{power}}{V_{DD}} = \frac{2\text{mW}}{1.8\text{V}} \approx 1.11 \text{ mA}$$

$$\begin{aligned} g_{m2} r_{o1} r_{o2} &= \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_{BIAS}} \left(\frac{1}{\lambda_n I_{BIAS}}\right)^2 \\ &= \sqrt{2 \cdot 100 \mu\text{A} \cdot \frac{20}{0.18} \cdot 1.11 \text{ mA} \cdot \left[\frac{1}{(0.1 \text{ V}^{-1})(1.11 \text{ mA})}\right]^2} \\ &\approx 403 \text{ k}\Omega \end{aligned}$$

$$g_{m3} r_{o3} r_{o4} \approx 11 \text{ k}\Omega$$

$$\text{We know that } \frac{|A_v|}{(g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4})} = g_{m1} = \frac{2 I_D}{V_{GS1} - V_{TH}}$$

$$\therefore V_{in} = V_{GS1} = V_{TH} + \frac{2 I_D \cdot g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}}{A_v}$$

$$= (0.4 \text{ V}) + 2(1.11 \text{ mA}) \frac{(403 \text{ k}\Omega \parallel 71. \text{ k}\Omega)}{200}$$

$$\approx 1.07 \text{ V}$$


$$g_{m4} = \frac{2I_D}{V_{DD} - V_{D3} - |V_{THP}|} = \sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D}$$

$$\therefore V_{D3} = V_{DD} - |V_{THP}| - \frac{2I_D}{\sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D}}$$

$$= (1.8 \text{ V}) - (0.5 \text{ V}) - \frac{2(1.11 \text{ mA})}{\sqrt{2 \cdot (50 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right) (1.11 \text{ mA})}}$$

$$\approx 0.67 \text{ V}$$

60.

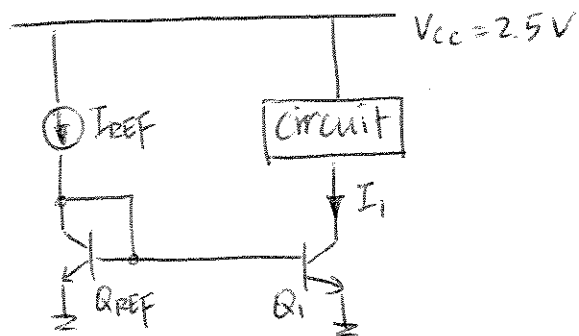

$$I_1 = 0.5 \text{ mA}$$

$$\text{power} = 2 \text{ mW}$$


$$\text{Power} = V_{CC} (I_{REF} + I_1)$$

$$\Rightarrow I_{REF} = \frac{\text{Power}}{V_{CC}} - I_1 = \frac{2 \text{ mW}}{2.5 \text{ V}} - 0.5 \text{ mA} = 0.3 \text{ mA}$$

Therefore, if Q_{REF} has area A_E , then Q_1 has area $\frac{5}{3} A_E$ for the currents specified.

$$\text{i.e. } \frac{A_{REF}}{A_1} = \frac{3}{5}$$

61.

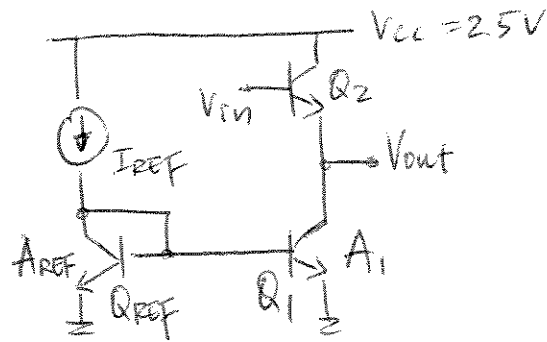

$$\text{power} = 3\text{mW}$$

$$R_{out} = 50\Omega$$

For an emitter follower, $R_{out} = r_{\pi 2} \parallel \frac{1}{g_{m2}}$

$$\Rightarrow R_{out} = 50\Omega = \frac{1}{\frac{I_{C2}}{V_T} \left(1 + \frac{1}{\beta}\right)}$$

$$\therefore I_{C2} = \frac{V_T}{R_{out}} \cdot \frac{1}{1 + 1/\beta} = \frac{0.026}{50} \cdot \frac{1}{1 + 0.01} \approx 0.51\text{mA}$$


Realize that V_{cc} is providing current through I_{REF} & I_{C2} , and we are given

$$\text{power} = V_{cc} (I_{REF} + I_{C2}) = 3\text{mW}$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{cc}} - I_{C2} = \frac{3\text{mW}}{2.5\text{V}} - 0.51\text{mA} \approx 0.69\text{mA}$$

$$\Rightarrow \frac{I_{C2}}{I_{REF}} = \frac{A_1}{A_{REF}} = \frac{0.51}{0.69} \approx \frac{5}{7}$$

62.

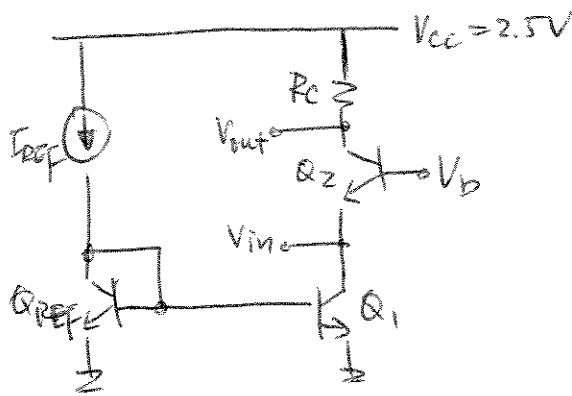

$$R_{out} = 50.5 \Omega$$

$$A_v = 20$$

$$\text{power} = 1.5 \text{ mW}$$

$$\beta \gg 1, V_A \rightarrow \infty$$

$$R_{out} = R_c \Rightarrow R_c = 50.5 \Omega$$

$$A_v = g_m R_c = 20 \Rightarrow g_m = \frac{A_v}{R_c} = \frac{I_{c2}}{V_T}$$


$$\Rightarrow I_{c2} = \frac{A_v V_T}{R_c} = \frac{20 (0.026 \text{ V})}{50.5 \Omega} \approx 10.4 \text{ mA}$$

Realize that V_{cc} is providing current through I_{REF} & I_{c2} :

$$\text{power} = V_{cc} (I_{REF} + I_{c2})$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{cc}} - I_{c2} = \frac{1.5 \text{ mW}}{2.5 \text{ V}} - 10.4 \text{ mA}$$

63.

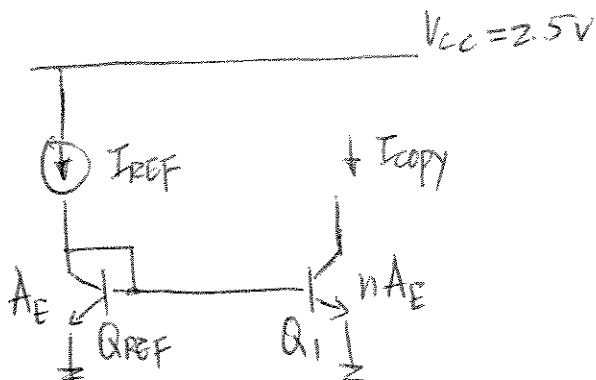Given $I_{copy} = 0.5mA$

$$\begin{aligned} \text{By KCL, } I_{REF} &= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} \\ &= \frac{I_{copy}}{n} + \frac{I_{copy}/n}{\beta} + \frac{I_{copy}}{\beta} \end{aligned}$$

$$\Rightarrow I_{copy} = I_{REF} \cdot \frac{n}{1 + \frac{1}{\beta}(n+1)} = 0.5mA$$


Within 1% implies that:

$$\Rightarrow I_{REF} \geq \frac{0.5mA}{0.99} \approx 0.505mA$$

- For given n and β , $I_{copy} \leq n I_{REF}$. Since the error term causes $I_{copy} < n I_{REF}$ (strictly less than), one needs to increase I_{REF} in order to maintain the desired I_{copy} . This, however, means an increase of power (i.e. $\Delta p = V_{CC} \cdot \Delta I_{REF}$)

\Rightarrow Trade off between accuracy & power dissipation.

64.

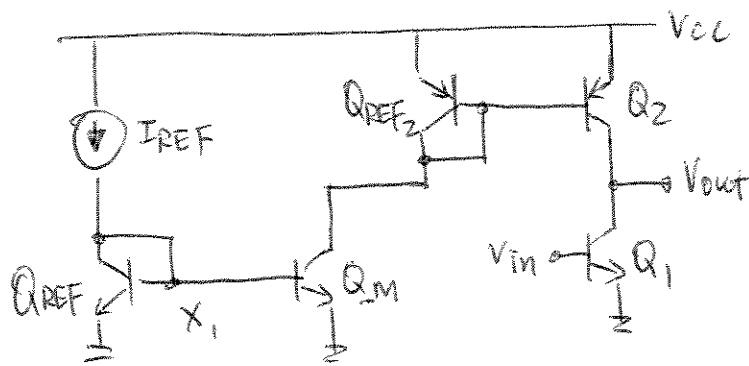

$$I_{C2} = I_{REF} \underbrace{\frac{(A_M/A_{REF})}{1 + \frac{1}{\beta_n}(A_M/A_{REF} + 1)}}_X \cdot \frac{(A_2/A_{REF2})}{1 + \frac{1}{\beta_p}(A_2/A_{REF2} + 1)}$$

Given $I_{CM} \geq 0.98 I_{REF}$ (less than 2% error)


$$I_{C2} = 1 \text{ mA} = 0.98 I_{REF} \cdot \frac{A_2/A_{REF2}}{1 + \frac{1}{50}(A_2/A_{REF2} + 1)}$$

Suppose $X = 0.98$ & $I_{REF} = 2 \text{ mA}$.

$$\Rightarrow \frac{A_2}{A_{REF2}} \approx 0.5$$

Solution is not unique because no power constraint is present (i.e. I_{REF} is arbitrary.)

65.

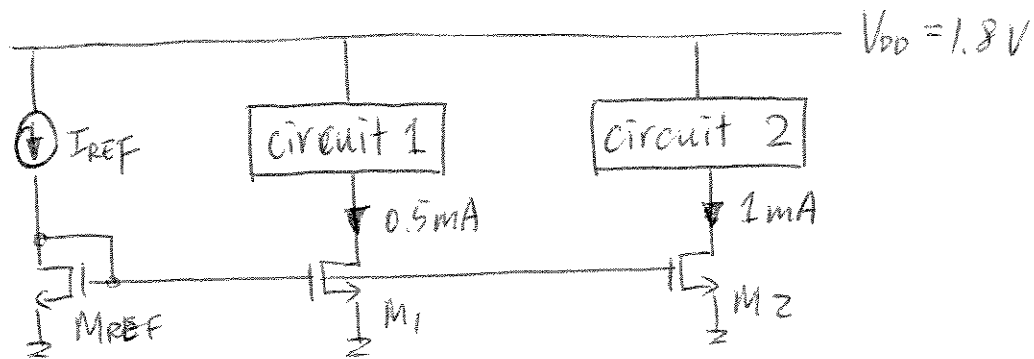

power budget = 3 mW.

$$\text{power} = V_{DD} (I_{REF} + 0.5mA + 1mA)$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{DD}} - 0.5mA - 1mA \approx 0.17mA$$


Assuming M_1 & M_2 operate in saturation,

If M_{REF} has $(\frac{W}{L})_{REF}$, then

$$\frac{(W/L)_1}{(W/L)_{REF}} = \frac{I_1}{I_{REF}} = \frac{50}{17}$$

$$\frac{(W/L)_2}{(W/L)_{REF}} = \frac{I_2}{I_{REF}} = \frac{100}{17}$$

66.

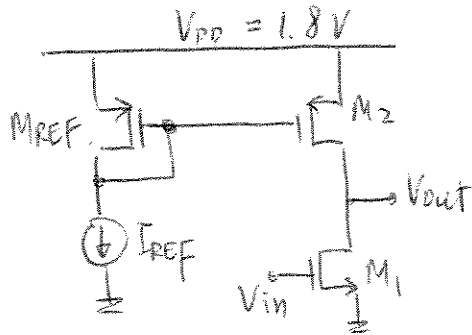

$$A_v = -20$$

$$\text{power} = 2 \text{ mW}$$

$$\left(\frac{W}{L}\right)_1 = \frac{20}{0.18}$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$\lambda_p = 0.2 \text{ V}^{-1}$$

$$R_{out} = r_{o2} \parallel r_{o1} = \frac{1}{\lambda_n I_{D1} + \lambda_p I_{D1}}$$

$$\Rightarrow A_v = -g_{m1} R_{out} = -\frac{g_{m1}}{\lambda_n I_{D1} + \lambda_p I_{D1}} = -\frac{\frac{2I_{D1}}{V_{GS1} - V_{THn}}}{I_{D1}(\lambda_n + \lambda_p)}$$

$$\Rightarrow -20 = -\frac{2}{(V_{GS1} - V_{THn})(\lambda_n + \lambda_p)}$$

$$\Rightarrow V_{GS1} = \frac{1}{10(\lambda_n + \lambda_p)} + V_{THn}$$

$$= \frac{1}{10(0.1 + 0.2) \text{ V}^{-1}} + 0.4 \text{ V} \approx 0.73 \text{ V}$$

$$\Rightarrow I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{THn})^2$$

$$= \frac{1}{2} (100 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right) (0.33 \text{ V})^2 \approx 0.61 \text{ mA}$$

$$\therefore \text{power} = V_{DD} (I_{REF} + I_{D1})$$


$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{DD}} - I_{D1} = \frac{2 \text{ mW}}{1.8 \text{ V}} - 0.61 \text{ mA}$$

$$\approx 0.5 \text{ mA}$$

\therefore if M_{REF} has $(\frac{W}{L})_{REF}$, then

$$\frac{(W/L)_2}{(W/L)_{REF}} = \frac{I_{D2}}{I_{REF}} = \frac{61}{50} \approx 1.2$$

67.

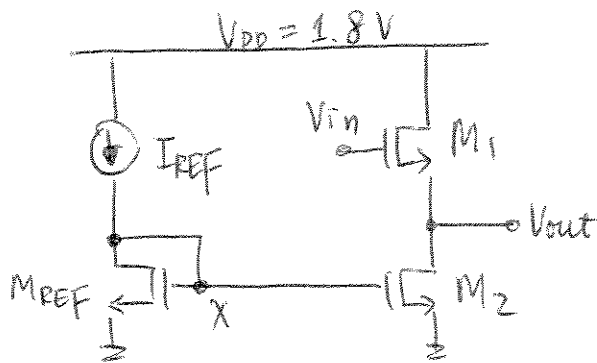

Given:

$$A_v = 0.85$$

$$R_{out} = 100 \Omega$$

$$(W/L)_2 = 10/0.18$$

$$\lambda_n = 0.1 \text{ V}^{-1}, \lambda_p = 0.2 \text{ V}^{-1}$$

$$R_{out} = r_{o2} \parallel \left(\frac{1}{g_{m1}} \parallel r_{o1} \right) = \frac{1}{g_{m1} + 1/r_{o2} + 1/r_{o1}} = 100$$

For source follower,

$$A_v = \frac{g_{m1}}{g_{m1} + 1/r_{o2} + 1/r_{o1}} = 0.85$$

$$\Rightarrow g_{m1} = \frac{0.85}{100} = 8.5 \cdot 10^{-3} \text{ S}$$

$$R_{out} = \frac{1}{g_{m1} + 2/r_o} = 100$$

$$\Rightarrow r_o = \frac{200}{1 - 100g_{m1}} = \frac{200}{1 - 100(8.5 \cdot 10^{-3})} \approx 1333 \Omega$$

$$\Rightarrow I_{D1} = \frac{1}{\lambda_n r_{o1}} = 7.5 \text{ mA}$$


Assume $V_x \approx 1 \text{ V}$

$$\left(\frac{W}{L} \right)_2 = \frac{2I_{D1}}{\mu_n C_{ox} (V_x - V_{TH})^2} \approx 416$$

Set $I_{REF} \approx 0.75 \text{ mA}$.

$$\Rightarrow \left(\frac{W}{L}\right)_{REF} = \left(\frac{W}{L}\right)_2 \frac{I_{REF}}{I_{D2}} \approx 42.$$

68.

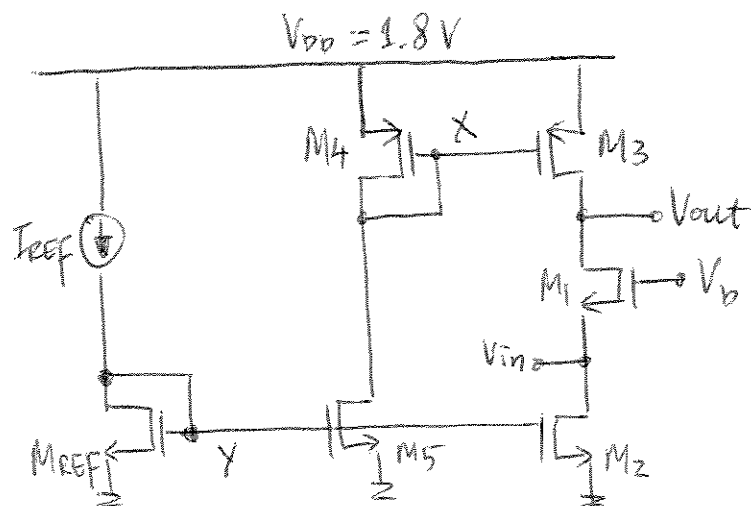

$$\left. \begin{array}{l} \left(\frac{W}{L}\right)_3 = 20/0.18 \\ \lambda_n = 0.1 \text{ V}^{-1} \\ \lambda_p = 0.2 \text{ V}^{-1} \end{array} \right\} \begin{array}{l} A_v = 20 \\ R_{in} = 50 \Omega \end{array}$$

$$R_{in} = 50 \Omega = r_{o2} \parallel \frac{1}{g_{m1}} = \frac{1}{\lambda_n I_{D1} + g_{m1}} \quad \text{--- ①}$$

$$R_{out} = r_{o3}$$

$$A_v = g_{m1} r_{o3} = \frac{g_{m1}}{\lambda_p I_{D1}} \quad \text{--- ②}$$

Solve for g_{m1} in ② and substitute it into ①:

$$50 = \frac{1}{\lambda_n I_{D1} + A_v \lambda_p I_{D1}}$$

$$\Rightarrow I_{D1} = \frac{1}{(\lambda_n + A_v \lambda_p)(50 \Omega)} = \frac{1}{(0.1 + 20(0.2))(50 \Omega)} \approx 4.88 \text{ nA}$$

$$|V_{GS3}| = \sqrt{\frac{2I_{D1}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} + |V_{THP}| \approx 1.44 \text{ V}$$

$$g_{m1} = A_v \lambda_p I_{D1} \Rightarrow \left(\frac{W}{L}\right)_1 = \left[\frac{A_v \lambda_p I_{D1}}{\sqrt{2\mu_n C_{ox} I_{D1}}} \right]^2$$

$$\approx 390.$$

Since $V_x \approx 0.4 \text{ V}$, size up other transistors to allow them to operate in saturation.

$$\text{Suppose } I_{D4} = 1.2 \text{ mA} \Rightarrow \left(\frac{W}{L}\right)_4 = \frac{2I_{D4}}{\mu_p C_{ox} (|V_{GS3}| - |V_{THP}|)^2}$$

$$\approx 10/0.18$$

$$I_{D5} = I_{D4} \Rightarrow \left(\frac{W}{L}\right)_5 = \frac{2I_{D5}}{\mu_n C_{ox} (V_y - V_{THN})^2} \approx \frac{100}{0.18}$$

(Assume $V_y = 0.6$; this is arbitrary, but must ensure M_5 in saturation.)

$$\text{Set } I_{REF} = I_{D5} \Rightarrow \left(\frac{W}{L}\right)_{REF} \approx \frac{100}{0.18}$$

$$I_{D2} \approx I_{D3} \Rightarrow \left(\frac{W}{L}\right)_2 = \frac{2I_{D2}}{\mu_n C_{ox} (V_y - V_{THN})^2} \approx \frac{45}{0.18}$$

$$\text{Total power} = V_{DD} (I_{REF} + I_{D4} + I_{D3})$$

$$= 1.8 (7.3) \text{ mW} \approx 13 \text{ mW}$$