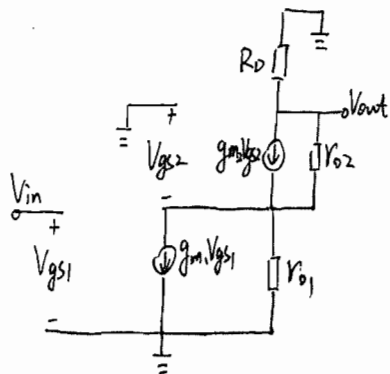



清华大学

6-38


(a)




(b)

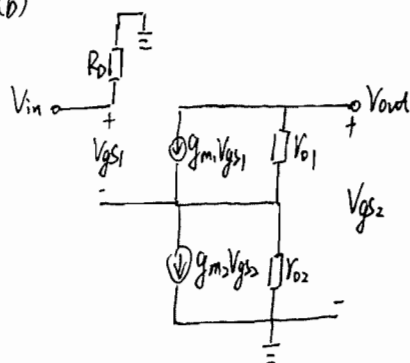


(c)

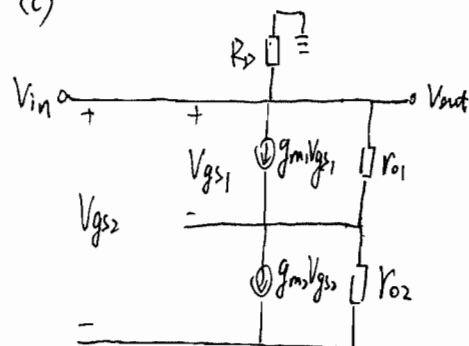

(d)

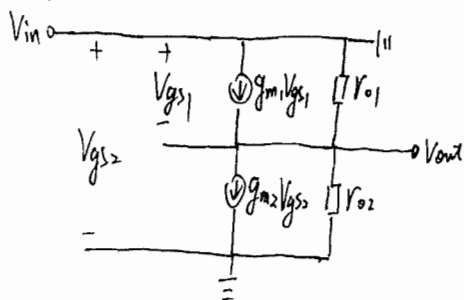


(e)

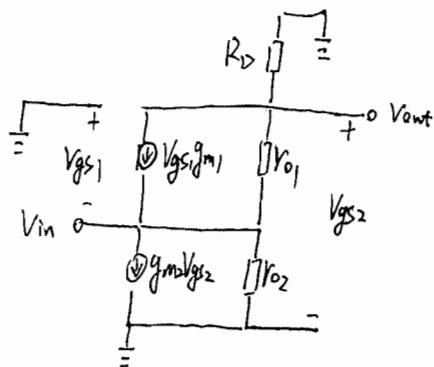

6-46

(a)

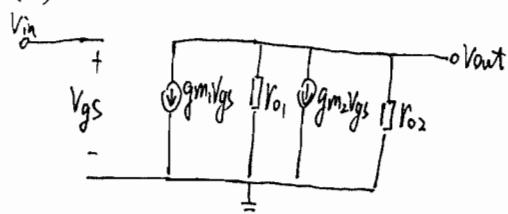


小信号等效电路中, M_1 和 M_2 的源极, 漏极和栅极分别相连
所以 M_1 和 M_2 表现为并联

$$\begin{aligned} (b) \quad V_{out} &= -(g_{m1}V_{gs} + g_{m2}V_{gs})(R_{o1} \parallel R_{o2}) \\ &= -(g_{m1} + g_{m2})(R_{o1} \parallel R_{o2})V_{gs} \\ &= -(g_{m1} + g_{m2})(R_{o1} \parallel R_{o2})V_{in} \end{aligned}$$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = -(g_{m1} + g_{m2})(R_{o1} \parallel R_{o2})$$

7-28


(a)

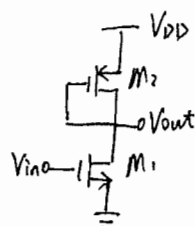

$$\begin{aligned} G_m &= -g_{m1} \\ R_L &= R_{o1} \parallel R_{o2} \parallel \frac{1}{g_{m2}} \end{aligned}$$

$$\therefore A_v = G_m R_L = -g_{m1}(R_{o1} \parallel R_{o2} \parallel \frac{1}{g_{m2}})$$


(b)

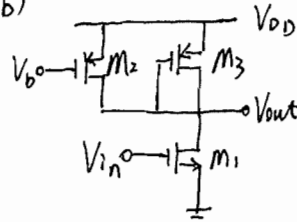

$$\begin{aligned} G_m &= -g_{m1} \\ R_L &= R_{o1} \parallel R_{o2} \parallel R_{o3} \parallel \frac{1}{g_{m2}} \end{aligned}$$

$$\therefore A_v = G_m R_L = -g_{m1}(R_{o1} \parallel R_{o2} \parallel R_{o3} \parallel \frac{1}{g_{m2}})$$


清華大學

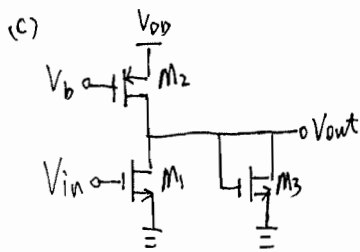

$$G_m = -g_{m1}$$

$$R_L = r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}}$$

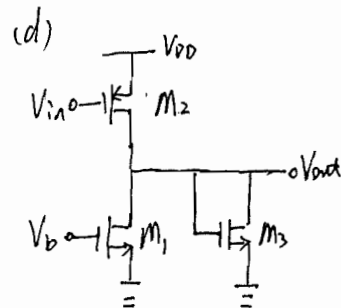
$$\therefore A_v = G_m R_L = -g_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$



$$G_m = -g_{m2}$$

$$R_L = r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}}$$

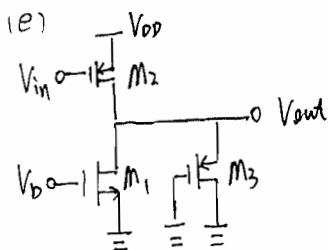
$$\therefore A_v = G_m R_L = -g_{m2} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$



$$G_m = -g_{m2}$$

$$R_L = r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}}$$

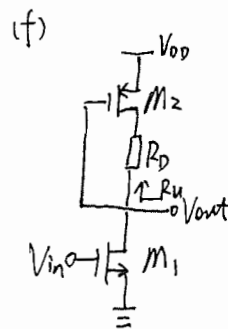
$$\therefore A_v = -g_{m2} (r_{o1} \parallel r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$



$$G_m = -g_{m1}$$

$$R_L = r_{o1} \parallel R_u$$
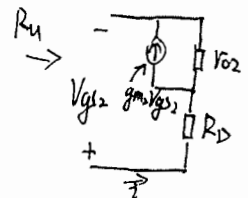
$$\therefore A_v = -g_{m1} (r_{o1} \parallel \frac{r_{o2} + R_D}{g_{m2} r_{o2} + 1})$$



$$V_{gs2} = i R_D + (i - g_{m2} V_{gs2}) r_{o2}$$

$$\Rightarrow R_u = \frac{V_{gs2}}{i} = \frac{r_{o2} + R_D}{g_{m2} r_{o2} + 1}$$

$$(46) \quad \frac{V_x}{V_{in}} = - (R_{D1} \parallel \frac{1}{g_{m2}}) g_{m1}$$


$$\frac{V_{out}}{V_x} = g_{m2} R_{D2}$$

$$\therefore \frac{V_{out}}{V_{in}} = - g_{m1} g_{m2} R_{D2} (R_{D1} \parallel \frac{1}{g_{m2}})$$

Similar to prob. (45), voltage gain approaches that of cascode stage as R_{D1} approaches infinity. The gain is $g_{m1} R_{D2}$.

(47) with $\lambda=0$, M_1 appears as a diode-connected device.

\therefore the circuit becomes :

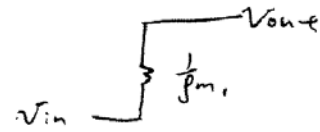


ie. $\frac{v_{out}}{v_{in}} = 1 //$

This is not a common-gate amplifier, (CG)
because the gate is not fixed. (ie. gate is not at an 'a.c. ground').

(55)

$$a) A_v = \frac{r_{o1} // (R_s + r_{o2})}{\frac{1}{\beta_{m1}} + r_{o1} // (R_s + r_{o2})}$$

$$b) A_v = \frac{r_{o1} // R_L}{\frac{1}{\beta_{m1}} + (r_{o1} // R_L)}$$

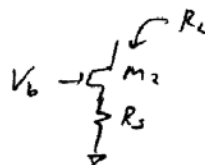
where R_L is :

$$R_L = (1 + \beta_{m2} r_{o2}) R_s + r_{o2} \quad \text{Eq. (7-110)}$$


$$\therefore A_v = \frac{r_{o1} // [(1 + \beta_{m2} r_{o2}) R_s + r_{o2}]}{\frac{1}{\beta_{m1}} + r_{o1} // [(1 + \beta_{m2} r_{o2}) R_s + r_{o2}]}$$

$$c) A_v = \frac{r_{o1} // \frac{1}{\beta_{m2}}}{\frac{1}{\beta_{m1}} + (r_{o1} // \frac{1}{\beta_{m2}})}$$

$$d) A_v = \frac{r_{o1} // R_L}{\frac{1}{\beta_{m1}} + (r_{o1} // R_L)}$$

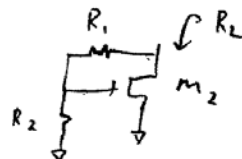where R_L is :

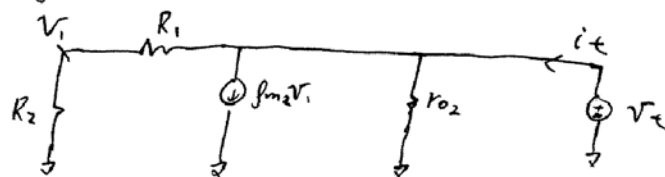(c) Finding R_L with small-signal model:
(cont'd)



$$R_L = \frac{v_e}{i_e}$$

$$\text{where } i_e = \frac{v_e}{r_{o2}} + \beta_{m2} v_i + \frac{v_e}{R_1 + R_2}$$

$$= \frac{v_e}{r_{o2}} + \frac{\beta_{m2} R_2 v_e}{R_1 + R_2} + \frac{v_e}{R_1 + R_2}$$

$$\therefore R_L = \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}$$

$$\therefore A_v = \frac{r_{o1} \parallel \frac{r_{o2} (R_1 + R_2)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}}{\frac{1}{\beta_{m1}} + r_{o1} \parallel \frac{r_{o2} (R_2 + R_1)}{R_2 + R_1 + r_{o2} + \beta_{m2} r_{o2} R_2}}$$

$$e) \quad A_v = \frac{r_{o2} \parallel (\frac{1}{\beta_{m1}} \parallel r_{o3})}{\frac{1}{\beta_{m2}} + r_{o2} \parallel (\frac{1}{\beta_{m1}} \parallel r_{o3})}$$

$$f) \quad A_v = \frac{r_{o1} \parallel [(1 + \beta_{m2} r_{o2}) r_{o3} + r_{o2}]}{\frac{1}{\beta_{m1}} + \{ r_{o1} \parallel [(1 + \beta_{m2} r_{o2}) r_{o3} + r_{o2}] \}}$$

$$(56) \quad \frac{v_x}{v_{in}} = \frac{g_{m2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$


$$\frac{v_{out}}{v_x} = g_{m2} R_D$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$b) \text{ if } g_{m1} = g_{m2},$$

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} R_D}{2}$$

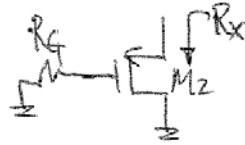19. (a) R_x is the input impedance of a common-gate configuration:



"Looking into" the source of M_2 ,




$$R_x = \frac{1}{g_{m2}} \parallel r_{o2}$$

$$\therefore R_{out} = g_{m1} r_{o1} R_x = g_{m1} r_{o1} \left(\frac{1}{g_{m2}} \parallel r_{o2} \right)$$

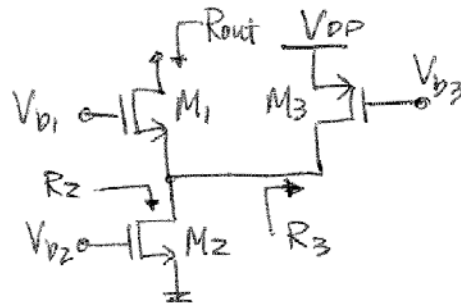(b) From observation,

$$\rightarrow R_3 = r_{o3} (\because V_{S4} = 0 \text{ in AC})$$

$$\rightarrow R_2 = r_{o2} (\because V_{S4} = 0 \text{ in AC})$$




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 \parallel R_3) = g_{m1} r_{o1} (r_{o2} \parallel r_{o3})$$

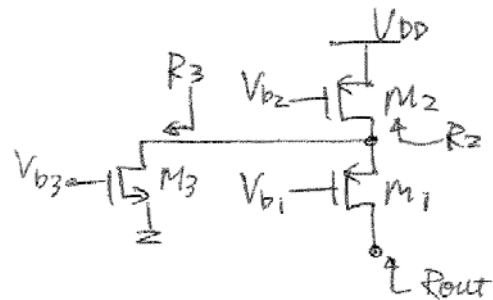(c) By observation,

$$R_2 = r_{o2} \quad (V_s = V_G = AC \text{ GND})$$

$$R_3 = r_{o3} \quad (V_s = V_G = AC \text{ GND})$$




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 \parallel R_3) = g_{m1} r_{o1} (r_{o2} \parallel r_{o3})$$


(d) $R_x = g_{m2} r_{o2} r_{o3}$

$$\Rightarrow R_{out} = g_{m1} r_{o1} R_x$$

$$= g_{m1} g_{m2} r_{o1} r_{o2} r_{o3}$$

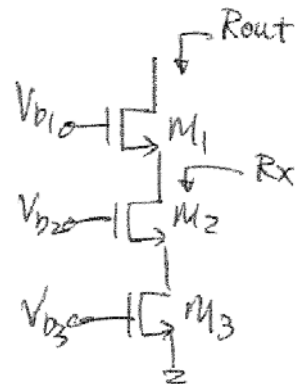

32.

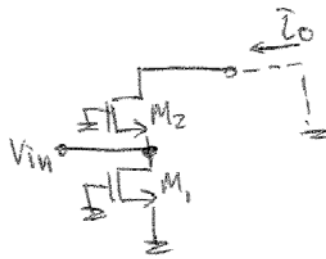


By KCL,

$$\frac{i_o}{v_{in}} = -\left(g_{m2} + \frac{1}{r_{o1} \parallel r_{o2}}\right) = G_m$$



$$R_n = r_{o2}$$

$$R_p \approx g_{m3} r_{o3} r_{o4}$$
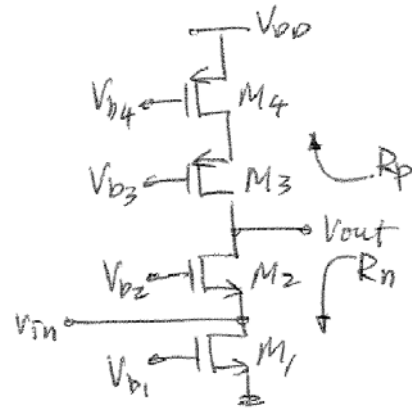
$$\therefore A_v = -G_m (R_n \parallel R_p) = \left(g_m + \frac{1}{r_{o1} \parallel r_{o2}}\right) (r_{o2} \parallel g_{m3} r_{o3} r_{o4})$$



34(a) Equivalent circuit:

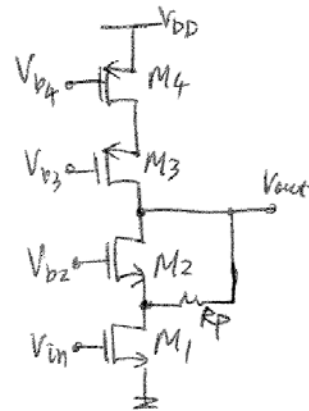
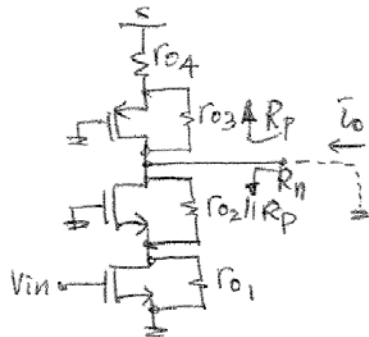


$$G_m = \frac{i_o}{V_{in}} \approx g_{m1} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} (r_{o2} \parallel R_p) r_{o1}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} (r_{o2} \parallel R_p) r_{o1}]$$

(b) Equivalent circuit

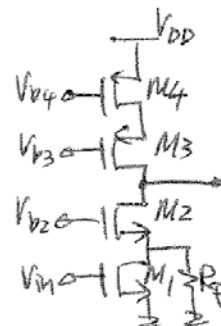
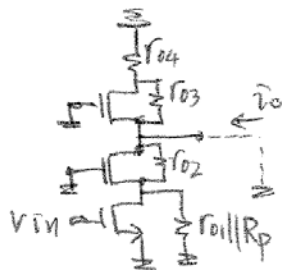


$$G_m = i_o / V_{in} \approx g_{m1} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} (r_{o1} \parallel R_p) r_{o2}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} (r_{o1} \parallel R_p) r_{o2}]$$

(c) Equivalent circuit:

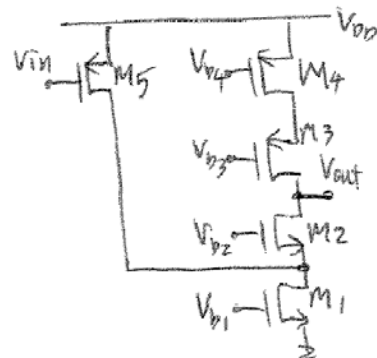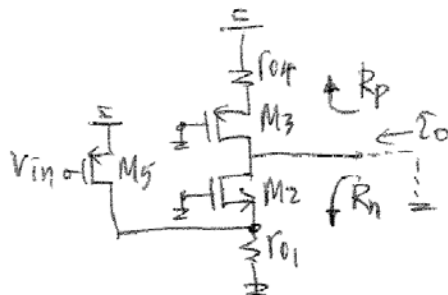



(Realize that r_{o1} & r_{o5} are in parallel.)

$$G_m = \frac{i_o}{v_{in}} \approx -g_{m5} \quad (\because g_m r_o \gg 1)$$

$$R_p = g_{m3} r_{o3} r_{o4} \quad R_n = g_{m2} r_{o2} (r_{o1} \parallel r_{o5})$$

$$\therefore A_v = -G_m R_{out} = g_{m5} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} r_{o2} (r_{o1} \parallel r_{o5})]$$

(d) Equivalent circuit:

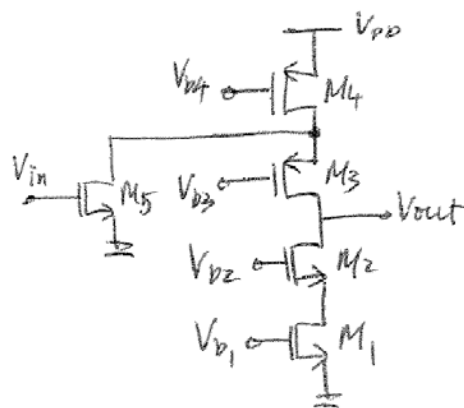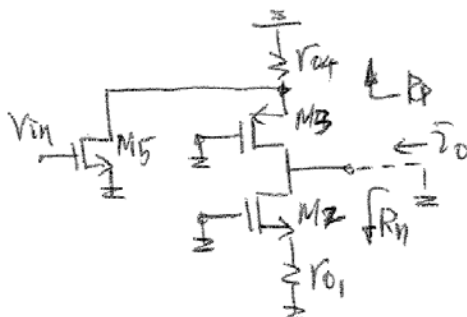


$$G_m = \frac{i_o}{v_{in}} \approx g_{m5} \quad R_p = g_{m3} r_{o3} (r_{o4} \parallel r_{o5})$$


$$R_n = g_{m2} r_{o2} r_{o1}$$

$$\therefore A_v = -G_m R_{out} = -g_{m5} [g_{m3} r_{o3} (r_{o4} \parallel r_{o5}) \parallel g_{m2} r_{o2} r_{o1}]$$


(51)

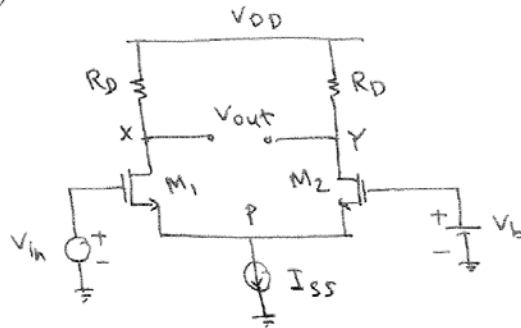

$$g_{m1} = g_{m2} = g_m$$

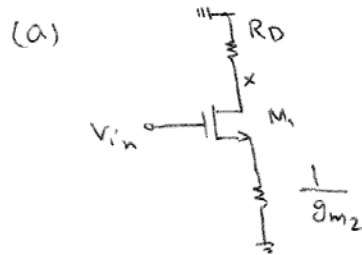
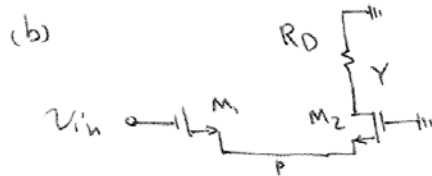
$$\begin{aligned} v_x &= -g_{m1} v_{gs1} R_D = \\ &= -g_{m1} \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in} R_D = \\ &= -\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in} = -\frac{g_m}{2} R_D v_{in} \end{aligned}$$



$$v_p = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in}$$

$$\Rightarrow v_p = \frac{g_{m1}}{g_{m1} + g_{m2}} v_{in} \Rightarrow$$


$$v_y = -g_{m2} v_{gs2} R_D = g_{m2} v_p R_D = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in}$$

$$\Rightarrow v_y = \frac{g_m}{2} R_D v_{in}$$

(c) $\frac{v_x - v_y}{v_{in}} = -g_m R_D$ This value is equal to the gain of the differential amplifier.

(70)


(a)

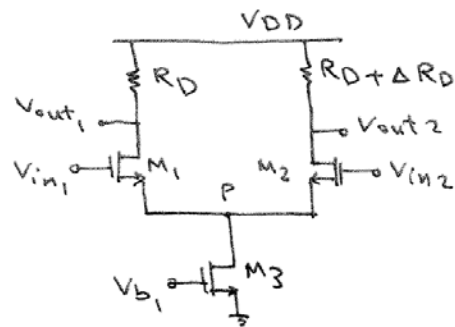

To calculate A_{DM} , using the half circuit:



To calculate A_{CM-DM} we have:

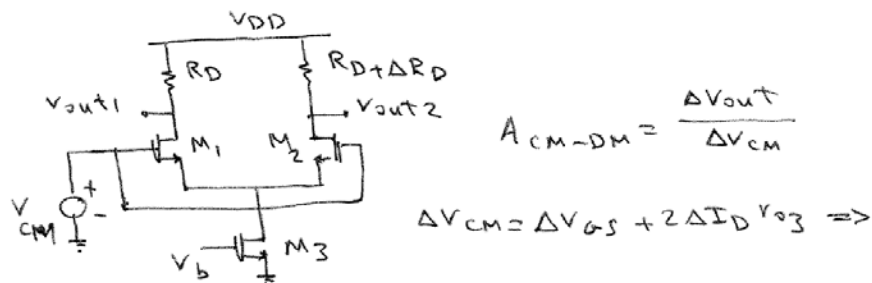

$$\Delta V_{CM} = \Delta V_{GS} + 2\Delta I_D r_{o3} \Rightarrow$$


$$\Delta V_{CM} = \Delta I_D \left(\frac{1}{g_{m1}} + 2r_{o3} \right)$$

$$\Delta V_{out} = \Delta V_{out1} - \Delta V_{out2} = -\Delta R_D \Delta I_D \Rightarrow$$

$$A_{CM-DM} = - \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}} \Rightarrow$$

$$CMMR = \frac{A_{DM}}{A_{CM-DM}} = \frac{g_{m1} R_D}{\frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}$$

(70) (b)

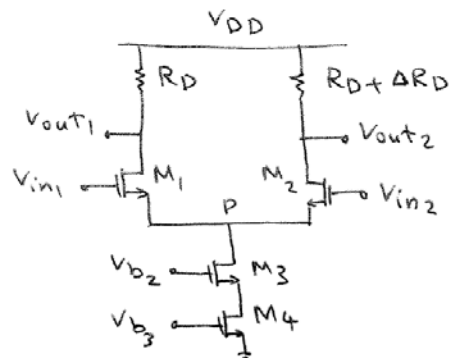

To calculate A_{DM} , using the half circuit, we have

$$A_{DM} = \frac{V_{out1}}{V_{in1}} = -g_{m1} R_D$$

Similar to part (a) we have:

$$A_{CM-DM} = - \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2 [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]}$$

$$\Rightarrow CMMR = \frac{A_{DM}}{A_{CM-DM}} = (1 + 2g_{m1} [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]) \frac{R_D}{\Delta R_D}$$

Notice that $CMMR$ of part (b) is much higher than the one for part (a).